

# CHAPTER 33

## ALTERNATING CURRENT CIRCUITS

33.1 AC SOURCES

33.2 RESISTORS IN AN AC CIRCUIT

# 33.1 AC SOURCES

- An AC circuit consists of a combination of circuit elements and a power source
- The power source provides an alternative voltage,  $\Delta v$

The output of an AC power source is sinusoidal and varies with time according to the following equation:

$$\Delta v = \Delta V_{max} \sin \omega t$$

$\Delta v$  is the **instantaneous voltage**

$\Delta V_{max}$  is the **maximum output voltage of the source**

Also called the **voltage amplitude**

$\omega$  is the **angular frequency of the AC voltage**


The **angular frequency** is

$$\omega = 2\pi f = \frac{2\pi}{T}$$

$f$  is the frequency of the source

$T$  is the period of the source

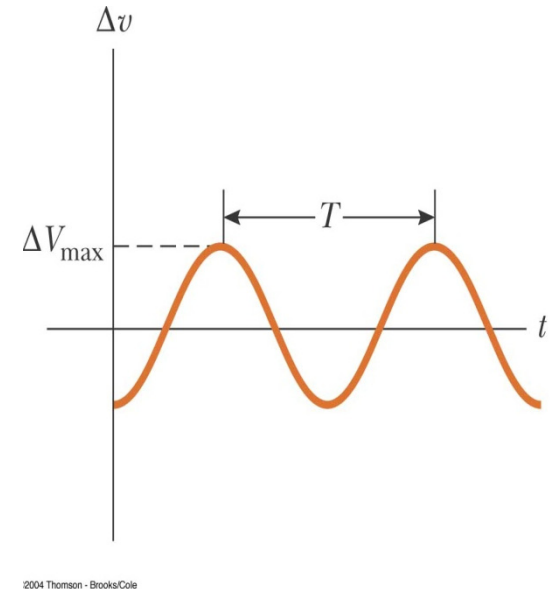The voltage is positive during one half of the cycle and negative during the other half




- The current in any circuit driven by an AC source is an alternating current that varies sinusoidally with time

Sine waves are characterized by the amplitude and period. The **amplitude** is the maximum value of a voltage or current; the **period** is the time interval for one complete cycle.


The amplitude ( $A$ ) of this sine wave is **20 V**


The period is **50.0  $\mu\text{s}$**

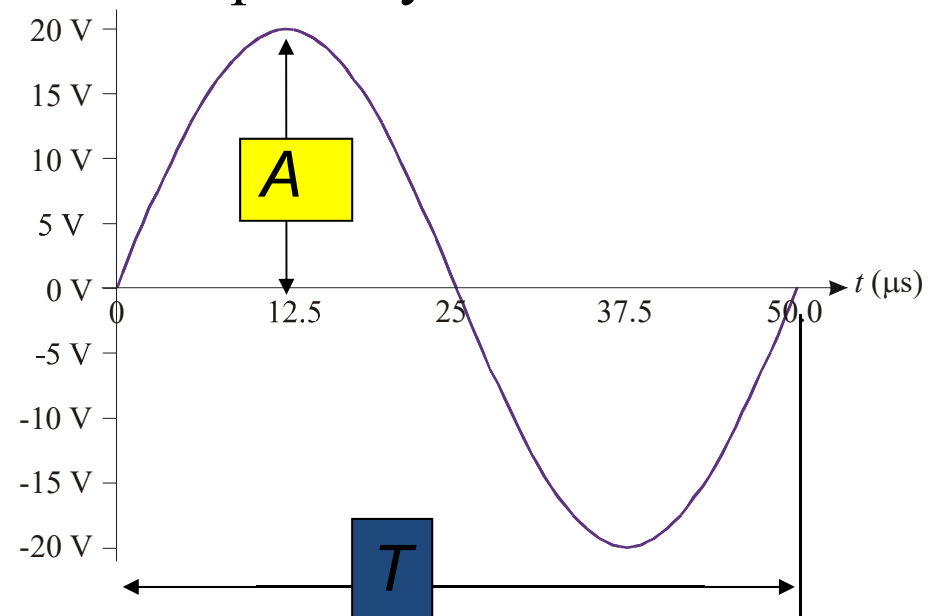

If the period is 50  $\mu\text{s}$ , the frequency is **0.02 MHz = 20 kHz.**
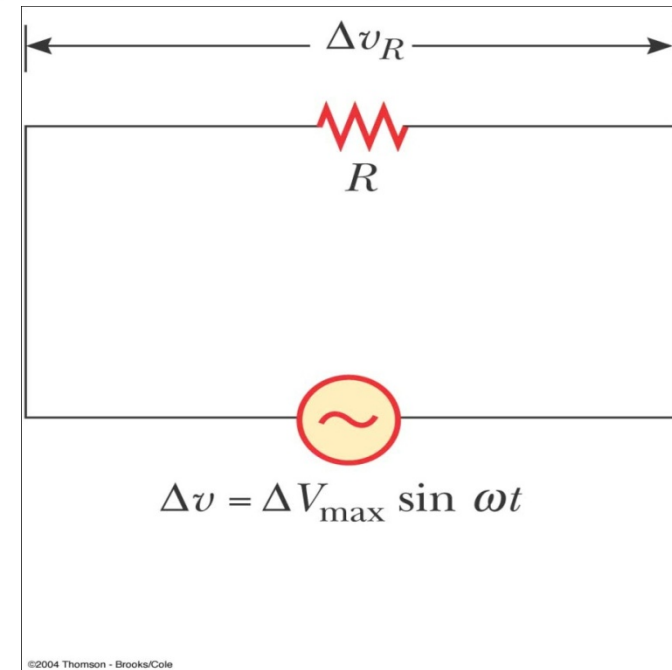
## 33.2 RESISTORS IN AN AC CIRCUIT

- Consider a circuit consisting of an AC source and a resistor
- The AC source is symbolized by 
- $\Delta v_R = \Delta v = V_{max} \sin \omega t$
- $\Delta v_R$  is the instantaneous voltage across the resistor



- The instantaneous current in the resistor is

$$i_R = \frac{\Delta v_R}{R} = \frac{\Delta V_{max}}{R} \sin \omega t = I_{max} \sin \omega t$$

- The instantaneous voltage across the resistor is also given as

$$\Delta v_R = I_{max} R \sin \omega t$$



# rms Current and Voltage

- The average current in one cycle is zero
- The rms current is the average of importance in an AC circuit
  - rms stands for root mean square

$$I_{rms} = \frac{I_{max}}{\sqrt{2}} = 0.707 I_{max}$$

- Alternating voltages can also be
- discussed in terms of rms values
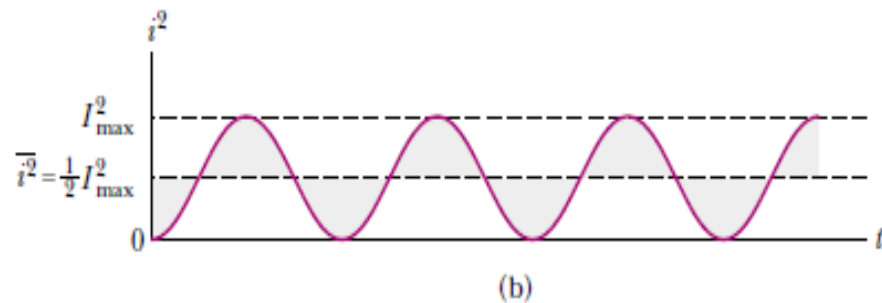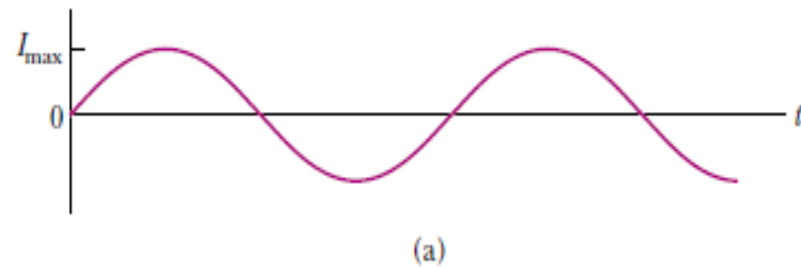
$$\Delta V_{rms} = \frac{\Delta V_{max}}{\sqrt{2}} = 0.707 \Delta V_{max}$$



## rms Current and Voltage

- The average current in one cycle is zero
- The rms current is the average of importance in an AC circuit
  - rms stands for root mean square

$$I_{rms} = \frac{I_{max}}{\sqrt{2}} = 0.707 I_{max}$$

- Alternating voltages can also be discussed in terms of rms values

$$\Delta V_{rms} = \frac{\Delta V_{max}}{\sqrt{2}} = 0.707 \Delta V_{max}$$

rms values are used when discussing alternating currents and voltages because

AC ammeters and voltmeters are designed to read rms values

Example : For a particular device, the house ac voltage is 120-V and the ac current is 10 A. What are their maximum values?

$$I_{rms} = 0.707 I_{max}$$

$$V_{rms} = 0.707 V_{max}$$

$$I_{max} = \frac{I_{rms}}{0.707} = \frac{10}{0.707} = 14.14 A$$

$$V_{max} = \frac{V_{rms}}{0.707} = \frac{120}{0.707} = 170 V$$

# Example

- A 60 W light bulb operates on a peak voltage of 156 V. Find the  $V_{\text{rms}}$ ,  $I_{\text{rms}}$ , and resistance of the light bulb.
- $V_{\text{rms}} = 110 \text{ V}$
- $I_{\text{rms}} = 0.55 \text{ A}$
- $R = 202 \Omega$

$$V_{\text{rms}} = 156 \text{ V} / \sqrt{2} = 110 \text{ V}$$

$$I_{\text{rms}}: P = IV \rightarrow 60 \text{ W} = I (110\text{V}) \rightarrow .55 \text{ A}$$

$$P=V^2/R \rightarrow 60 \text{ W} = (110 \text{ V})^2/R \quad \rightarrow \quad R = (110\text{V})^2/60\text{W} \rightarrow 202 \Omega$$



# Power

- The rate at which electrical energy is dissipated in the circuit is given by

$$- P = i^2 R$$

- $i$  is the *instantaneous current*
- The heating effect produced by an AC current with a maximum value of  $I_{\max}$  is not the same as that of a DC current of the same value
- The maximum current occurs for a small amount of time
- The average power delivered to a resistor that carries an alternating current is  $P_{av} = I_{rms}^2 R$

## Example:

Assume a sine wave with a peak value of 40 V is applied to a 100  $\Omega$  resistive load. What power is dissipated?

$$V_{rms} = 0.707 \times V_p = 0.707 \times 40 \text{ V} = 28.3 \text{ V}$$

$$P = \frac{V_{rms}^2}{R} = \frac{28.3 \text{ V}^2}{100 \Omega} = 8 \text{ W}$$

## Example 33.1 What Is the rms Current?

The voltage output of an AC source is given by the expression  $\Delta v = (200 \text{ V}) \sin \omega t$ . Find the rms current in the circuit when this source is connected to a  $100\text{-}\Omega$  resistor.

$$\Delta V_{\text{rms}} = \frac{\Delta V_{\text{max}}}{\sqrt{2}} = \frac{200 \text{ V}}{\sqrt{2}} = 141 \text{ V}$$

$$I_{\text{rms}} = \frac{\Delta V_{\text{rms}}}{R} = \frac{141 \text{ V}}{100 \text{ }\Omega} = 1.41 \text{ A}$$

1- A heater takes 10 A rms from the 230 V rms mains.  
What is its power?

A) 1,630 W

→ B) 2,300 W

C) 3,250 W

D) 4,600 W

2- The voltage output of an AC source is given by the expression :  
 $v = (200 \text{ V}) \sin \omega t$ . Find the rms current in the circuit when this source is  
connected to a 100- $\Omega$  resistor.

$$I_{rms} = \frac{V_{rms}}{R} = \frac{V_{max} / \sqrt{2}}{R} = \frac{200 / \sqrt{2}}{100}$$

$$I_{rms} = 2 \times 0.707 = 1.414 \text{ A}$$