

Question 1: (15 marks)

If the cost of electricity is defined as follow:

0.13 SR/kWh, for on-peak: 12:00 – 5:00 pm
0.05 SR/kWh, otherwise (off-peak),

what is the total cost of using the following?

1. 860 W air conditioner for 5 h on-peak
2. 4800 W clothes dryer for 30 min off-peak
3. 900 W coffee maker for 20 min on-peak
4. 110 W stereo for 3.5 h on-peak

$$\textcircled{1} \text{ Cost}_1 = (0.86 \times 5 \times 0.13) = 0.559$$

$$\textcircled{2} \text{ Cost}_2 = (4.8 \times 0.5 \times 0.05) = 0.12$$

$$\textcircled{3} \text{ Cost}_3 = (0.9 \times (\frac{20}{60}) \times 0.13) = 0.039$$

$$\textcircled{4} (0.11 \times 3.5 \times 0.13) = 0.05005$$

$$\Rightarrow \text{Total Cost} = 0.559 + 0.12 + 0.039 + 0.05005 \\ = \underline{\underline{0.76805 \text{ SR}}}$$

Question 2: (20 marks)

Find the unknown quantities for the circuits of Fig. 2 using the information provided.

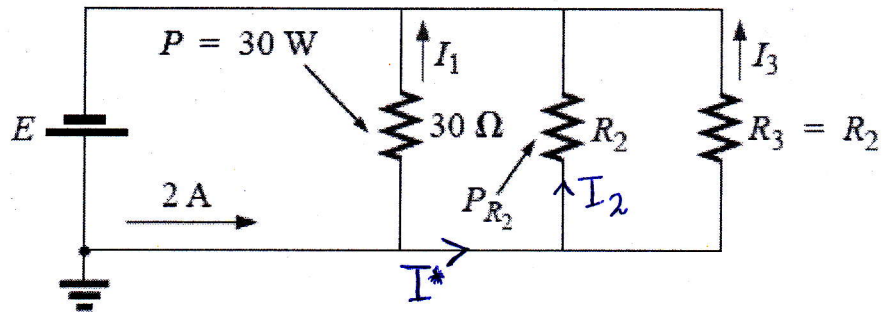


Figure 2

$$\therefore 30 = (I_1)^2 R \rightarrow I_1 = \sqrt{\frac{P}{R}} = \sqrt{\frac{30}{30}} = \underline{\underline{1A}}$$

$$\therefore V_{30\Omega} = (I_1)(R) = (1)(30) = \underline{\underline{30V}}$$

$$\therefore E = V_{R_2} = V_{R_3} = \underline{\underline{30V}} \quad (\text{parallel with } 30\Omega)$$

From KCL:-

$$2 = I_1 + I^* \rightarrow I^* = 2 - 1 = \underline{\underline{1A}}$$

$$\therefore R_2 = R_3 \Rightarrow \therefore I_2 = I_3 = \frac{I^*}{2} = \underline{\underline{0.5A}}$$

$$\therefore R_2 = R_3 = \frac{V}{I} = \frac{30}{0.5} = \underline{\underline{60\Omega}}$$

$$\Rightarrow P_{R_2} = (I_2)^2 R_2 = \frac{(V_2)^2}{R_2} = \underline{\underline{15W}}$$

Question 3: (25 marks)

For the series-parallel network of Fig. 3:

- Find the current I .
- Find the currents I_3 and I_9 .
- Find the current I_8 .
- Find the voltage V_{ab} .

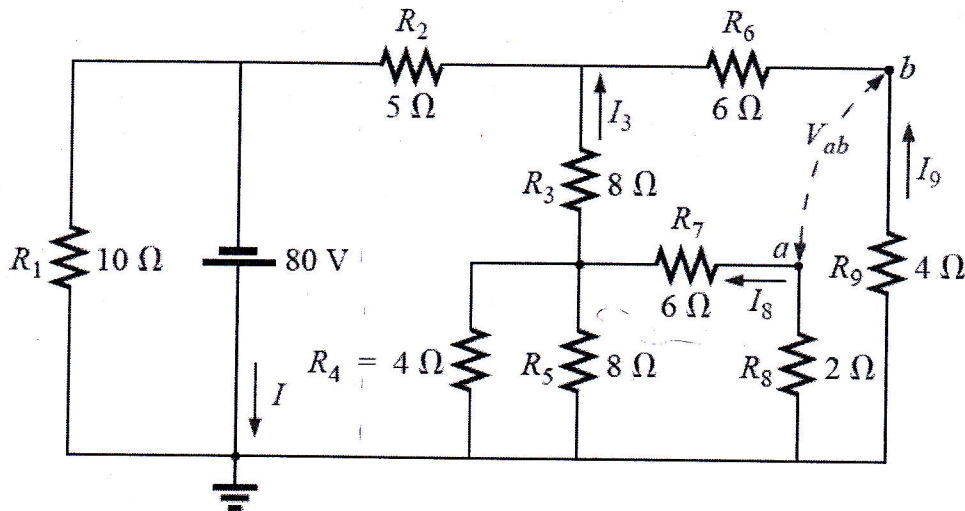


Figure 3

$$R_T = (R_1) \parallel \left(R_5 + \left(R_3 + (R_4 \parallel R_5 \parallel (R_8 + R_7)) \right) \parallel (R_6 + R_9) \right)$$

$$\Rightarrow R_T = \underline{\underline{5 \Omega}}$$

(a)

$$I = \frac{V}{R_T} = \frac{80}{5} = \underline{\underline{16 A}}$$

(b)

\therefore The equivalent Resistances are equal



$$\therefore I_3 = I_9 = \frac{8}{2} = \underline{\underline{4 A}}$$

(c)


$$R_{eq} = 2 \Omega$$

Using CDR (Current Divider Rule)
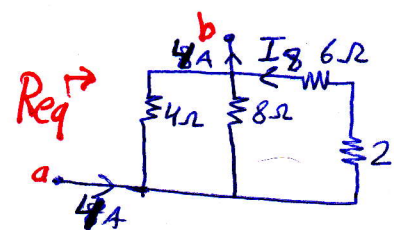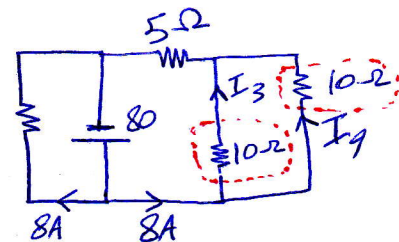
$$I_8 = \frac{I}{R_T} \frac{R_T}{R_x} = (4) \left(\frac{2}{8} \right) = \underline{\underline{1 A}}$$



(d)

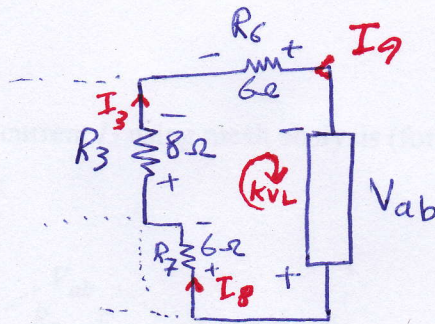

Apply KVL

$$-V_{R_3} + V_{R_6} + V_{ab} - V_{R_7} = 0$$

$$-(4 \times 8) + (4 \times 6) + V_{ab} - (I \times 6) = 0$$

$$V_{ab} = 14 \text{ V}$$

Question 4: (40 marks)

For the networks of Fig. 4, determine the current I_2 using mesh analysis (format approach), and then find the voltage V_{ab} .


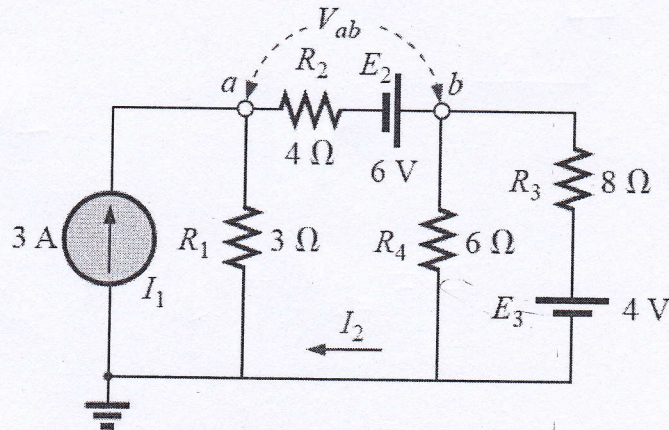


Figure 4


by transforming to voltage source

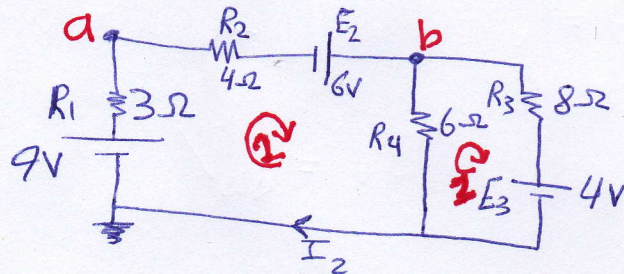

① $13I_2 - 6I_2 = 15$

② $-6I_2 + 14I_1 = -4$

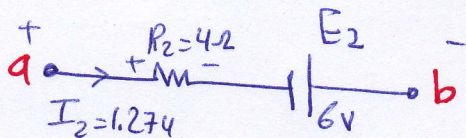Solving the equations $\Rightarrow I_2 = \underline{\underline{1.274A}}$, $I_1 = \underline{\underline{0.26A}}$



$V_{ab} = V_{R2} - 6 = -0.904V$