

King Saud University
College of Science
Physics & Astronomy Dept.

Phys 145 (General Physics)
Chapter 6: Direct Currents
Week n° 8

This presentation has been prepared by: Pr. Nabil BEN NESSIB


King Saud University, College of Science, Physics & Astronomy Dept. Phys 145(General Physics) © 2014

Chapter 6: Direct Currents

- We will learn in this chapter 6:
- Electric Current
- Resistance
- Series and Parallel Resistors; Kirchhoff's Rules
- Kirchhoff's Rules in Complex Circuits

King Saud University, College of Science, Physics & Astronomy Dept. Phys 145(General Physics) © 2014

Electric Current

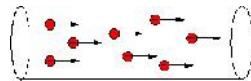

- The current is the rate at which the charge moves in the wire.
- The **average current** that passes any point in a conductor during a time Δt is defined as:

$$\bar{I} = \frac{\Delta Q}{\Delta t}$$

where ΔQ is the amount of charge crosses the shaded area in a time Δt .

- ΔQ in Coulomb (C), Δt in seconds (s) and I in Ampere (A).


$$1A = 1C/s$$

(One Ampere of current is one Coulomb per second)

- The **instantaneous current** is: $I = \frac{dQ}{dt}$

King Saud University, College of Science, Physics & Astronomy Dept. Phys 145(General Physics) © 2014

Average Drift Velocity

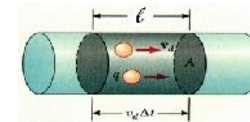

- The current is the rate at which the charge moves in the wire.
- N is the total number of charge carriers in the volume (V) of the conductor.
- n is the number of mobile charge carriers per unit volume.
- We have:

$$n = \frac{N}{V}$$

- In a time Δt , the electron moves the length ℓ with the constant velocity v_d

$$\ell = v_d \Delta t$$

- The **charges** that passes any point in the conductor during a time Δt is:


$$\Delta Q = Ne = neV = neA\ell = neAv_d\Delta t$$

where e is the charge of an electron ($e = 1.6 \times 10^{-19} \text{ C}$).

- So: $\bar{I} = \frac{\Delta Q}{\Delta t} = neAv_d$

King Saud University, College of Science, Physics & Astronomy Dept. Phys 145(General Physics) © 2014

Video 01 of week 08: Basic electricity

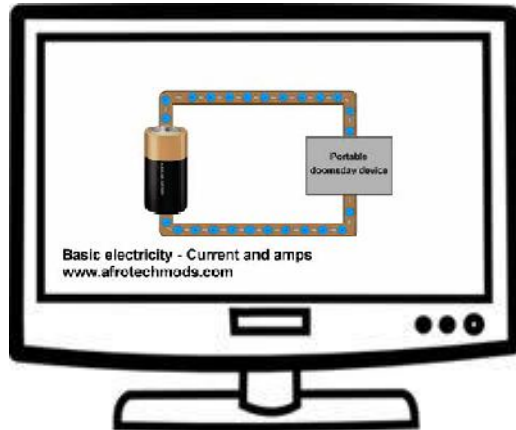

King Saud University, College of Science, Physics & Astronomy Dept. Phys 145 (General Physics) © 2014

5

Resistance

- Charges flow only if there is a potential difference. Something that provides a potential difference is known as a **voltage source**.
- The electrical resistance R of a conductor is the potential difference V between its ends divided by the current I :

$$R = \frac{V}{I}$$

- V is in volt (V), I in Ampere (A) and R in Ohm (Ω).

$$1 \Omega = \frac{1 \text{ V}}{1 \text{ A}}$$

- Materials with a constant resistance are said to obey **Ohm's law** and called **ohmic conductors**.
- Materials that do not follow Ohm's Law are called "**nonohmic**" materials.

King Saud University, College of Science, Physics & Astronomy Dept. Phys 145 (General Physics) © 2014

6

Resistance



Ohmic conductor



Nonohmic conductor

King Saud University, College of Science, Physics & Astronomy Dept. Phys 145 (General Physics) © 2014

7

Resistance

- The resistance of a conductor depends on its size, shape and composition.
- Resistance of a metal wire (R) is directly proportional to its length, (ℓ) and inversely proportional to its cross-sectional area, (A):

$$R = \rho \frac{\ell}{A}$$

- The proportionality constant ρ (rho) depends only on the properties of the material and is called the resistivity. In the S.I., ρ is in $\Omega \cdot \text{m}$.
- The conductivity σ (sigma) is the inverse of the resistivity ρ :

$$\sigma = \frac{1}{\rho}$$

It is sometimes used instead of the resistivity to characterize conductors. In the S.I., σ is in $\Omega^{-1} \cdot \text{m}^{-1}$.

King Saud University, College of Science, Physics & Astronomy Dept. Phys 145 (General Physics) © 2014

8

Resistivities in $\Omega \cdot m$ at $20^\circ C$

	substance	Resistivity ρ ($\Omega \cdot m$)
conductors	Silver	1.47×10^{-8}
	Copper	1.72×10^{-8}
	Aluminum	2.63×10^{-8}
semiconductors	Germanium	0.60
	Silicon	2300
Insulators	Glass	$10^{10} - 10^{14}$
	Sulfur	10^{15}
Ionic conductors	Body fluids	approx. 0.15

- Good conductors have **low resistivities**.
- Good insulators have **high resistivities**.

9

King Saud University, College of Science, Physics & Astronomy Dept. Phys 145 (General Physics) © 2014

Series and Parallel Resistors

- Resistors in series:

$$R_{series} = R_1 + R_2 + R_3 + \dots$$

- Resistors in parallel:

$$\frac{1}{R_{parallel}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

10

King Saud University, College of Science, Physics & Astronomy Dept. Phys 145 (General Physics) © 2014

Video 02 of week 08: Ohm's law



11

King Saud University, College of Science, Physics & Astronomy Dept. Phys 145 (General Physics) © 2014


Kirchhoff's Rules

- **Junction Rule:** $\sum I = 0$

The sum of the currents entering any point must equal the sum of the currents leaving that junction.

$$\sum I_{in} = \sum I_{out}$$

Example: $I_1 = I_2 + I_3$

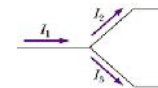

- **Loop Rule:** $\sum V = 0$



The sum of the potential changes around any closed circuit loop must be zero.

12

King Saud University, College of Science, Physics & Astronomy Dept. Phys 145 (General Physics) © 2014

Kirchhoff's Rules

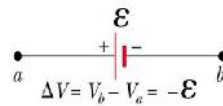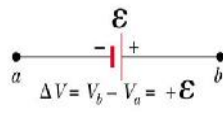The voltage across a battery is taken to be positive (a voltage rise) if traversed from $-$ to $+$ and negative if traversed in the opposite direction.




13


King Saud University, College of Science, Physics & Astronomy Dept. Phys 145(General Physics) © 2014

Kirchhoff's Rules

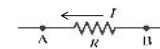- The voltage across a resistor is taken to be negative (a drop) if the loop is traversed in the direction of the assigned current and positive if traversed in the opposite direction.



$$V_{ab} = V_b - V_a = RI$$

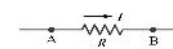

$$V_{ab} = V_b - V_a = -RI$$

14

King Saud University, College of Science, Physics & Astronomy Dept. Phys 145(General Physics) © 2014

Kirchhoff's Rules in Complex Circuits

- For any loop, we chose a direction, (in blue in the figure).
- We put $+$ the potential (V) if we enter by the positive pole and $-$ the potential ($-V$) if we enter by the negative pole.
- We put $+RI$ if we are in the same direction than the current and $-RI$ in the opposite case.
- In the left loop:

$$-2 + I_1 + 4 + 2I_2 = 0$$
- In the right loop:

$$-I_3 - 2I_2 - 4 - 3I_3 + 6 = 0$$
- The junction rule gives: $I_1 + I_3 = I_2$
- Solving the 3 equations, we obtain:


$$I_1 = -\frac{8}{7} A \approx -1.14 A; I_2 = -\frac{3}{7} A \approx -0.43 A; I_3 = \frac{5}{7} A \approx 0.71 A$$

- The negative sign means that the current is the opposite to the direction.

15

King Saud University, College of Science, Physics & Astronomy Dept. Phys 145(General Physics) © 2014

Kirchhoff's Rules in Complex Circuits

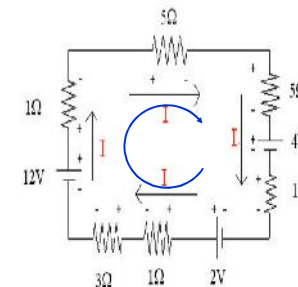

$$5I + 5I + 4 + I - 2 + I + 3I - 12 + I = 0$$

$$16I - 10 = 0$$

$$I = \frac{10}{16} = \frac{5}{8} \approx 0.625 A$$

16


King Saud University, College of Science, Physics & Astronomy Dept. Phys 145(General Physics) © 2014

Kirchhoff's Rules in Complex Circuits

$$-6 - 2I_1 + 12I_3 - 8 = 0$$

$$+8 - 12I_3 - 4I_2 = 0$$

$$I_1 + I_3 = I_2$$

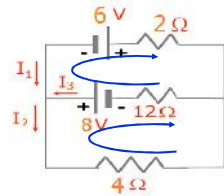


$$I_1 = -\frac{8}{5} A \approx -1.6 A; I_2 = -\frac{7}{10} A \approx -0.7 A; I_3 = \frac{9}{10} A \approx 0.9 A$$

17

King Saud University, College of Science, Physics & Astronomy Dept. Phys 145(General Physics) © 2014

Video 03 of week 08: Kirchhoff's rules

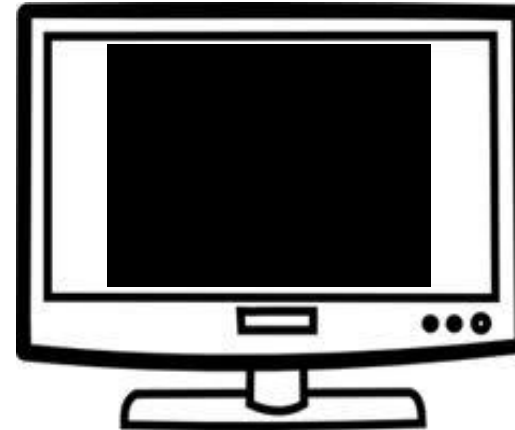

18

King Saud University, College of Science, Physics & Astronomy Dept. Phys 145(General Physics) © 2014

Summary of week 08

Average current $\bar{I} = \frac{\Delta Q}{\Delta t}$ Instantaneous current $I = \frac{dQ}{dt}$

Magnitude of the current $I_{av} = nev_d A$

Resistance of a conductor $R = \frac{V}{I}$

Resistance is determined by the geometry and by the resistivity of the material $R = \rho \frac{L}{A}$

$$R_{series} = R_1 + R_2 + R_3 + \dots + \frac{1}{R_{parallel}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$


Kirchhoff's Rules

- Junction Rule $\sum I_{in} = \sum I_{out}$
- Loop Rule $\sum V_i = 0$

19

King Saud University, College of Science, Physics & Astronomy Dept. Phys 145(General Physics) © 2014

Quiz for week 08

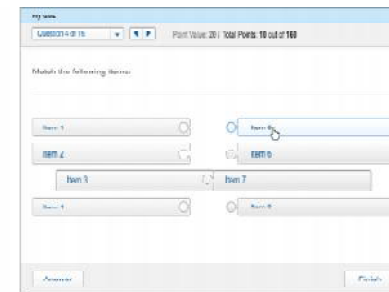

20

King Saud University, College of Science, Physics & Astronomy Dept. Phys 145(General Physics) © 2014

