



CSC 220: Computer Organization

Unit 11 Datapath Design

Prepared by:

Md Saiful Islam, PhD

Department of Computer Science
College of Computer and Information Sciences

Overview

- Guiding principles for datapath design
- Register file
- Datapath Representation
- Accessing RAM
- The Control Word

Chapter-8

M. Morris Mano, Charles R. Kime and Tom Martin, **Logic and Computer Design Fundamentals**, Global (5th) Edition, Pearson Education Limited, 2016. ISBN: 9781292096124

Datapath Design


Guiding principles for basic datapath:

- A limited set of **registers** serve as fast temporary storage
 - A set of registers with common access resources called a **register file**
- Microoperation implementation
 - **Function Unit (ALU)** - shared resource for implementing arithmetic, logic, and shift microoperations
 - **Buses** - shared transfer paths
 - For given microoperation, we need to specify;
 - Source registers
 - Destination register
 - Operation to perform
- A larger, but slower, **random-access memory** is also available.
- The datapath completes a single microoperation **each clock cycle**.




Register file

- **Register file:** A register file is an array of fast registers
- Modern processors contain a number of registers grouped together in a **register file**.
- The register file appears like a memory based on clocked flip-flops (the clock is not shown)
- Much like words stored in a RAM, individual registers are identified by an address.
- Here is a block symbol for a $2^k \times n$ register file.
 - There are 2^k registers, so register addresses are k bits long.
 - Each register holds an n -bit word, so the data inputs and outputs are n bits wide.

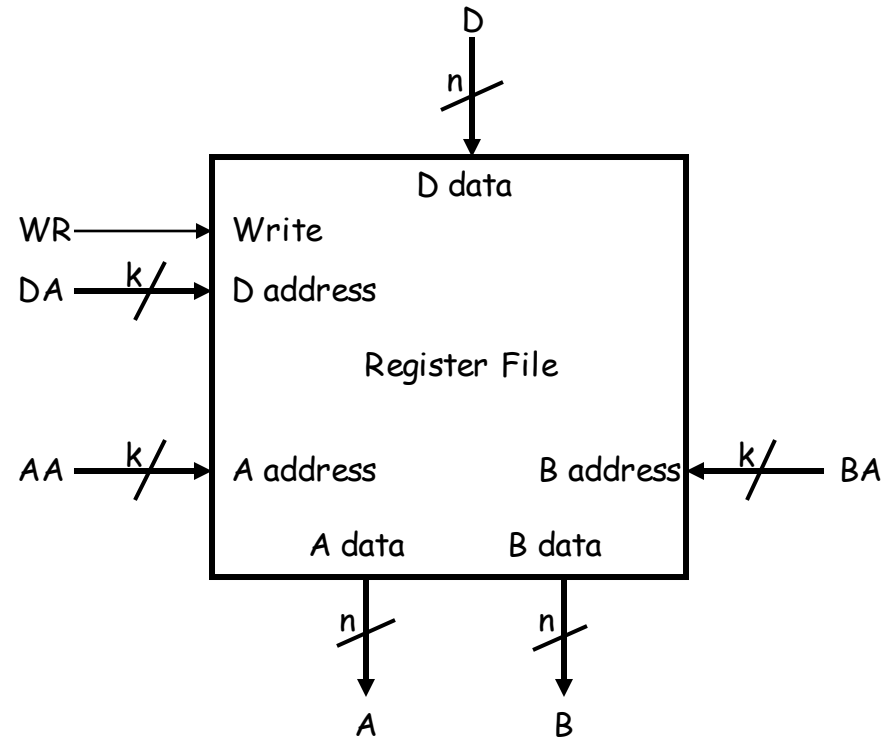


Accessing the register file ...

- You can read *two* registers at once by supplying the **AA** and **BA** inputs. The data appears on the **A** and **B** outputs.
- You can write to a register by using the **DA** and **D** inputs, and setting **WR = 1**.
- These are registers so there must be a **clock signal**, even though we usually don't show it in diagrams.
 - We can read from the register file at any time.
 - Data is written only on the positive edge of the clock.

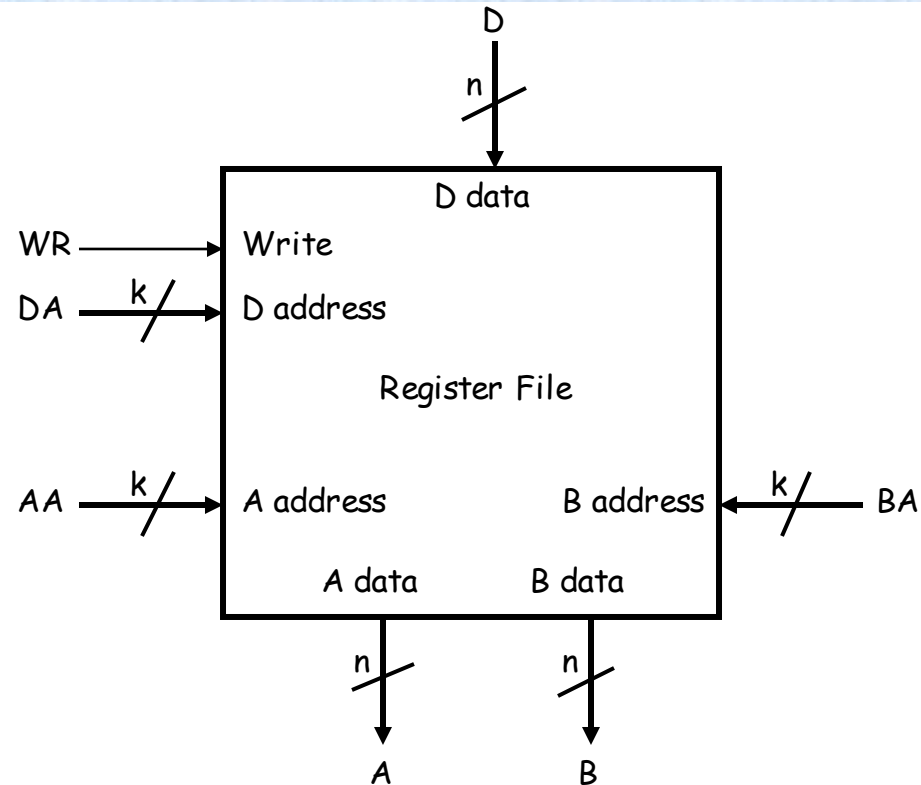

What's inside the register file ...

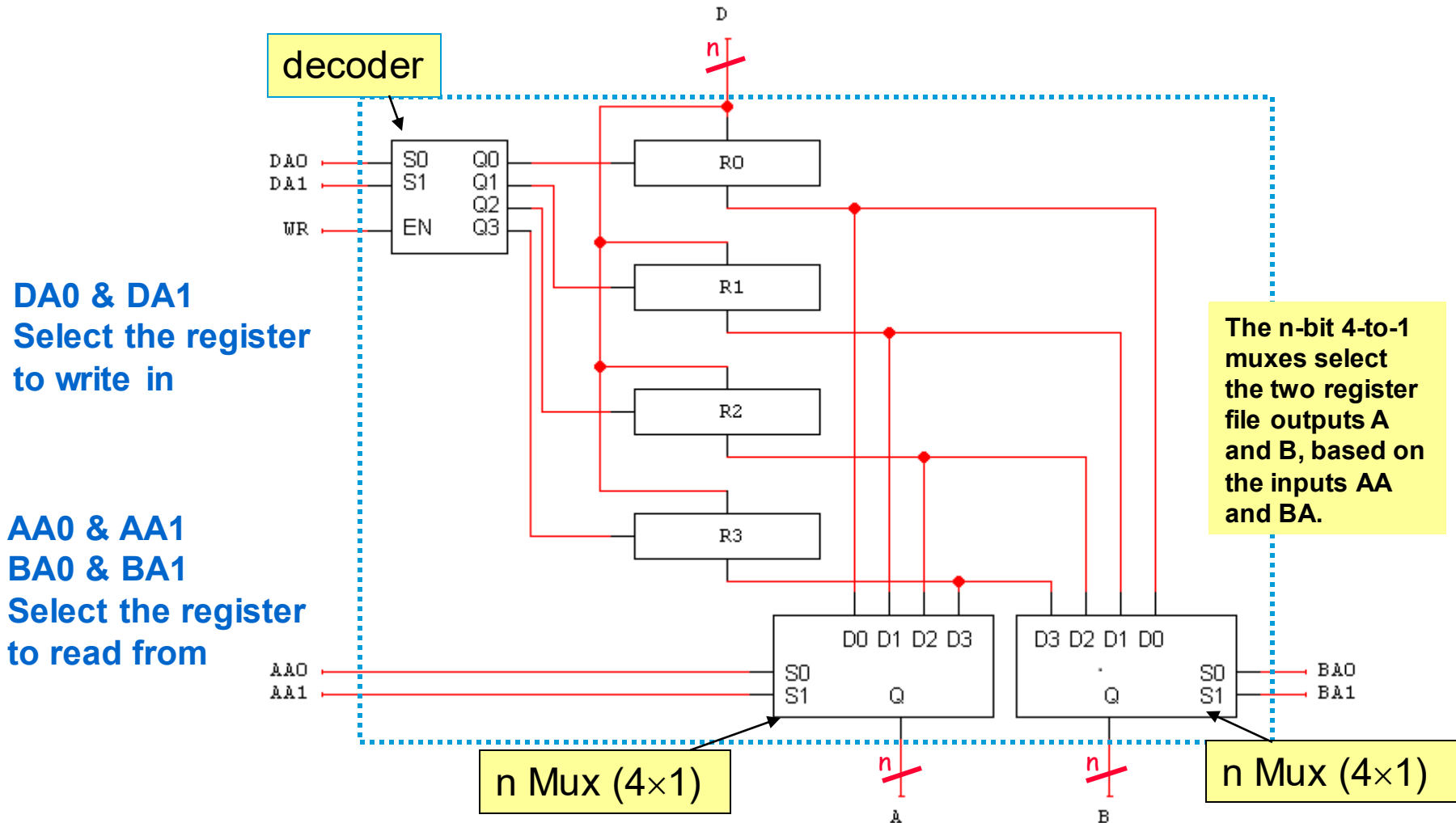- A 4 x n register file ($2^k \times n = 4 \times n$)




The Function Unit

Function Unit = ALU + Shifter


- The function select code FS is 4 bits long,
- There are only 15 different functions here.

FS	Operation
0000	$F = A$
0001	$F = A + 1$
0010	$F = A + B$
0011	$F = A + B + 1$
0100	$F = A + B'$
0101	$F = A + B' + 1$
0110	$F = A - 1$
0111	$F = A$
1000	$F = A \wedge B$ (AND)
1001	$F = A \vee B$ (OR)
1010	$F = A \oplus B$ (XOR)
1011	$F = A'$
1100	$F = B$
1101	$F = sr B$ (shift right)
1110	$F = sl B$ (shift left)

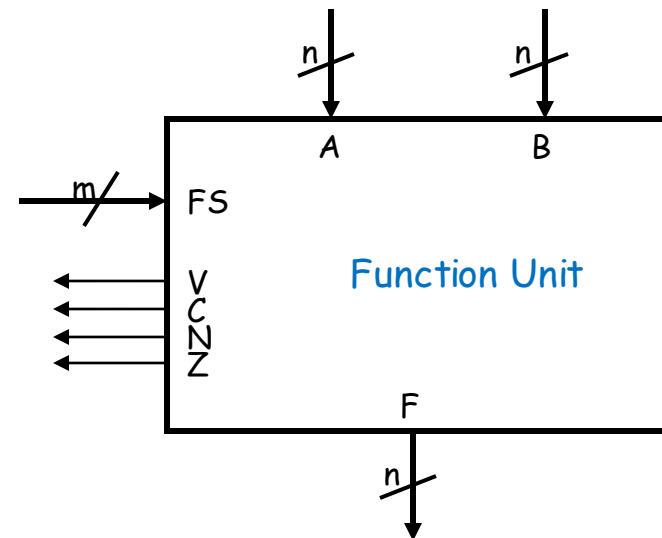


Datapath Representation

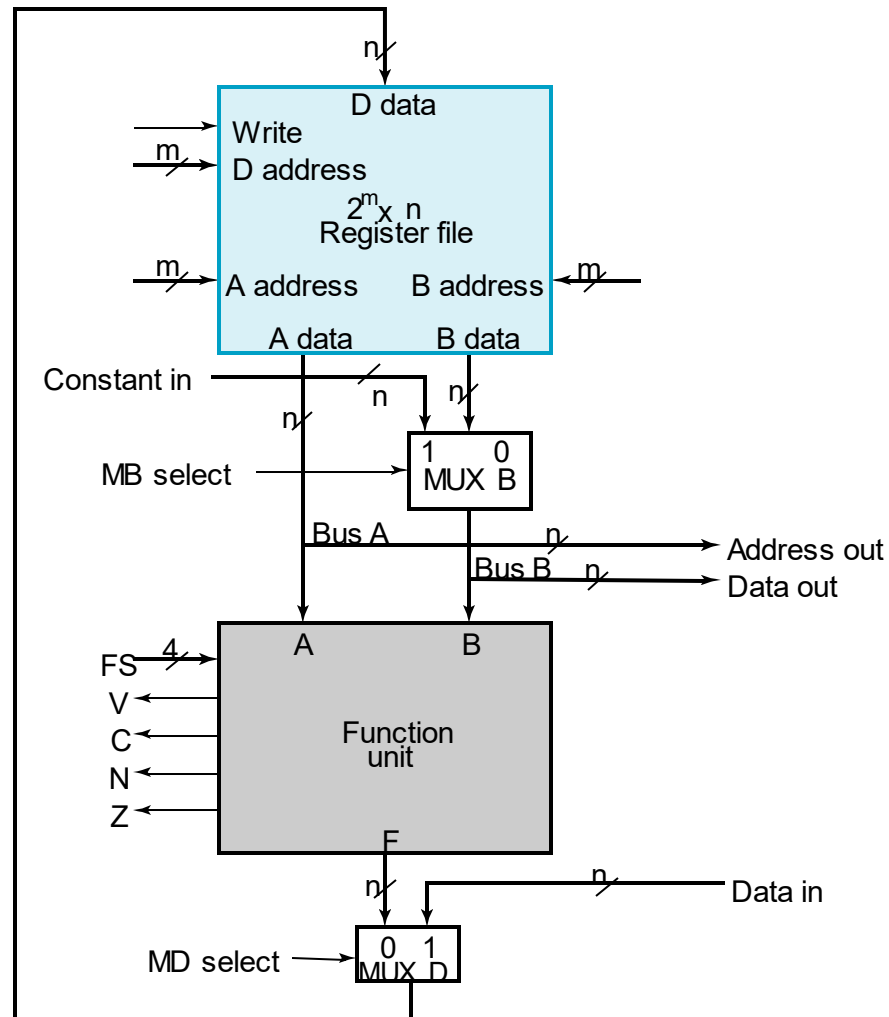- Datapath = Function unit + Register file:
- Muxes (B, D) and buses handle data transfers



Datapath Example ...

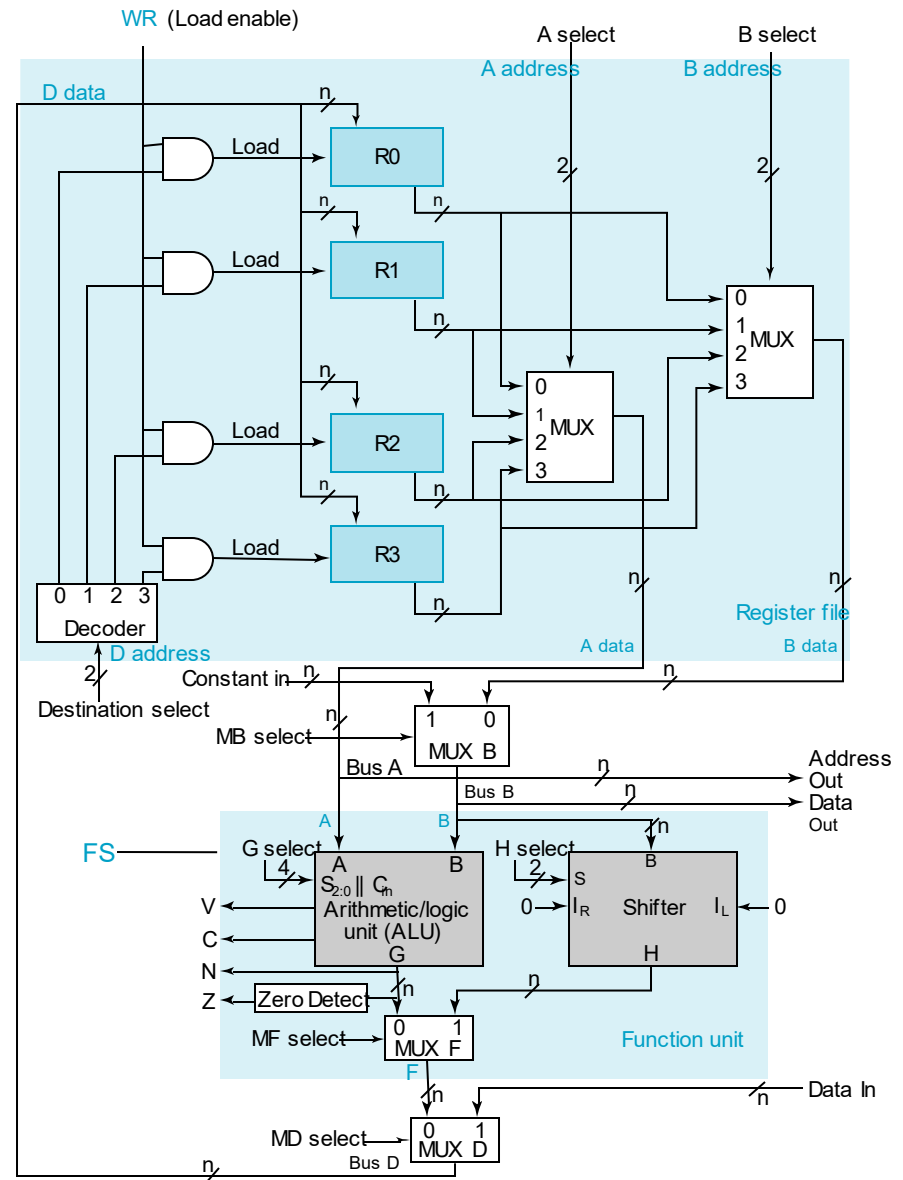
- Four parallel-load registers (R0-R3)
- Two mux-based register selectors
- Register destination decoder
- Mux B for external constant input
- Buses A and B with external address and data outputs
- Function Unit: ALU and Shifter
- Mux D for external data input



Performing a Microoperation ...


Microoperation: $R0 \leftarrow R1 + R2$

- Apply 01 to A select to place contents of R1 onto Bus A
- Apply 10 to B select to place contents of R2 onto B data
- Apply 0 to MB select to place B data on Bus B
- Apply 0010 to FS select to perform addition $G = \text{Bus A} + \text{Bus B}$
- Apply 0 to MD select to place the value of G onto BUS D
- Apply 00 to Destination select to enable the Load input to R0
- Apply 1 to Load Enable to force the Load input to R0 to 1 so that R0 is loaded on the clock pulse (not shown)
- The overall microoperation requires 1 clock cycle

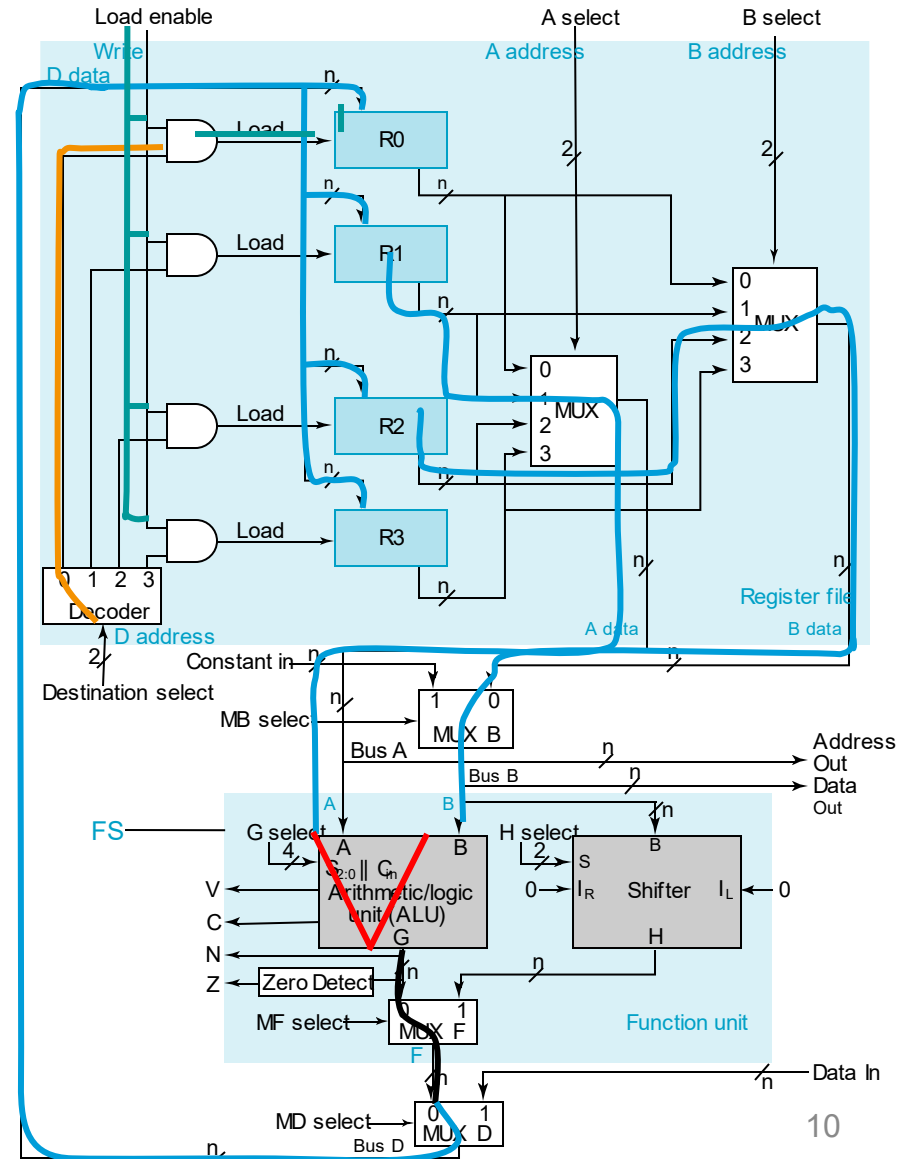


Accessing RAM

- Here's a way to connect RAM into our existing datapath.
- **Write to RAM:** we must give an address and a data value.
- These will come from the registers/Constant. We connect **A data** to the memory's **ADRS** input, and **B data** to the memory's **DATA** input.
- Set **MW = 1** to write to the RAM. (It's called MW to distinguish it from the WR write signal on the register file.)
- **WR = 0** to prevent any change to register file
- In the next clock cycle B data will be written to A data location

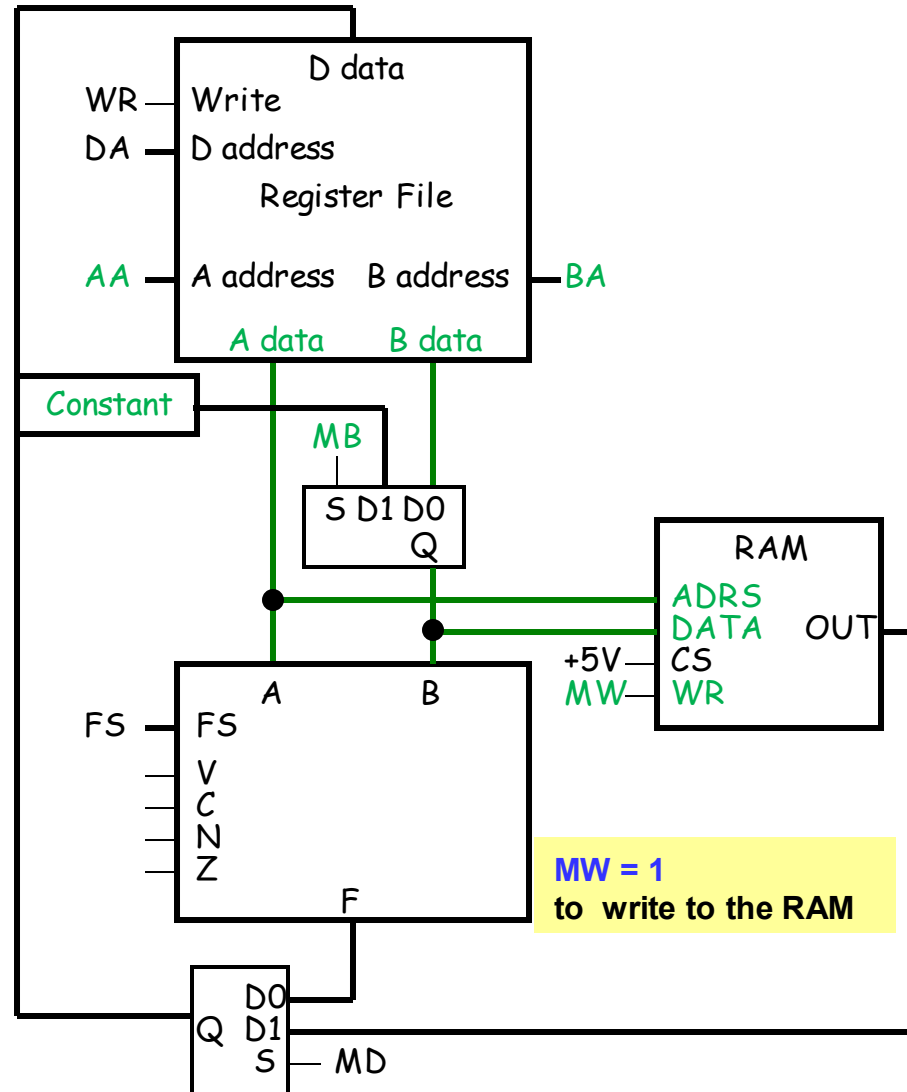


Accessing RAM...

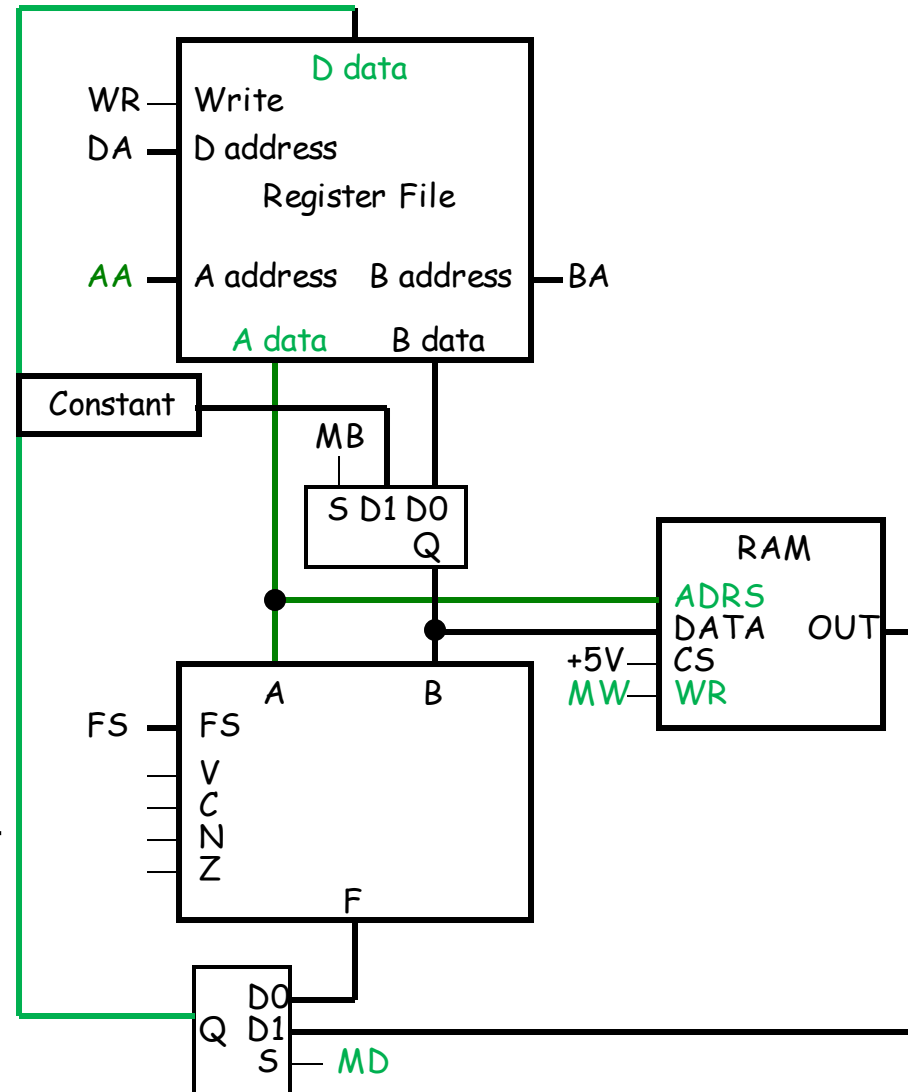- **Read from RAM:** A data must supply the address.
- Set $MW = 0$ for reading.
- The incoming data will be sent to the register file for storage.
- This means that the register file's D data input could come from either the ALU output or the RAM.
- A mux MD selects the source for the register file.
- When $MD = 1$, the RAM output is sent to the register file instead.



Notes about this setup ...

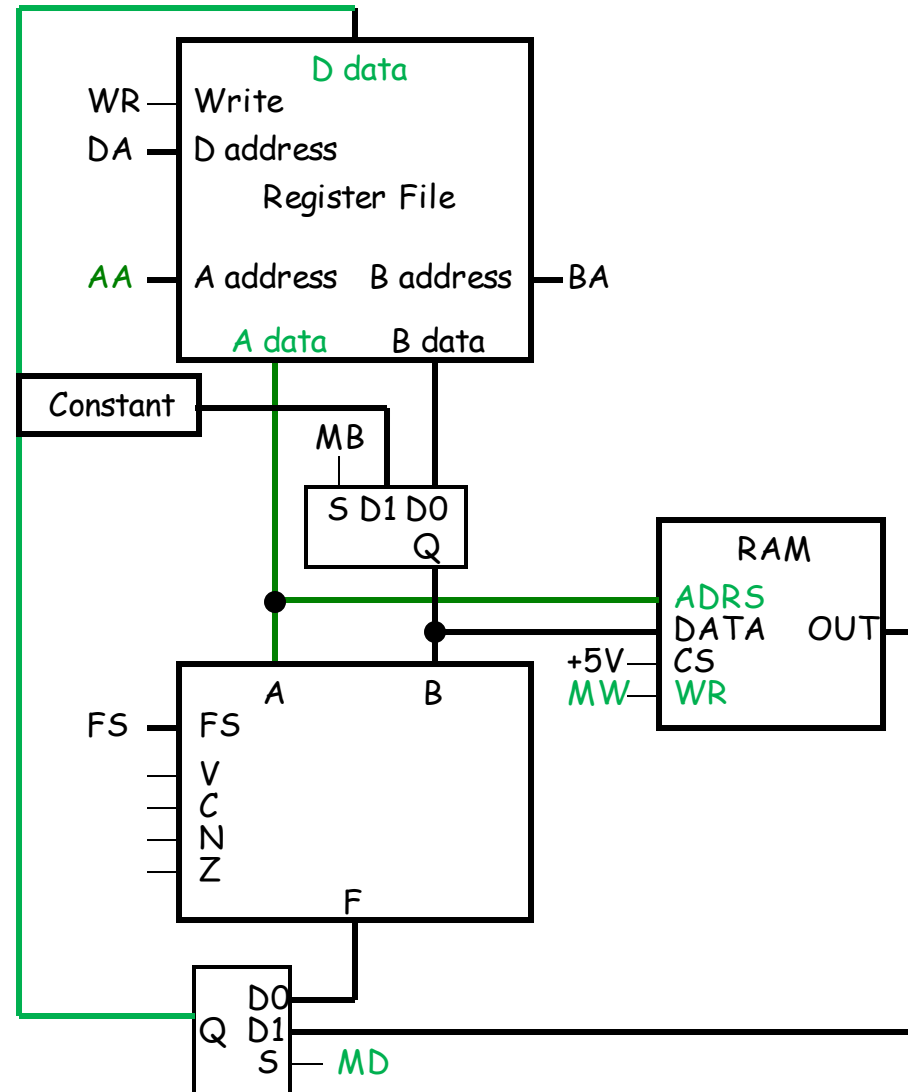
- We now have a way to copy data between our register file and the RAM.
- Notice that there's no way for the Function Unit to directly access the memory—RAM contents *must* go through the register file first.
- Here the size of the memory is limited by the size of the registers; with n -bit registers, we can only use a $2^n \times n$ RAM.



The Control Word

- The datapath has many **control inputs**
- The signals driving these inputs can be defined and **organized into a control word**
- To execute a microinstruction, we apply **control word values for a clock cycle**.
- For most microoperations, the positive edge of the **clock cycle is needed** to perform the register load
- The datapath **control word format** and the field definitions are shown on the next slide

The Control Word Fields ...

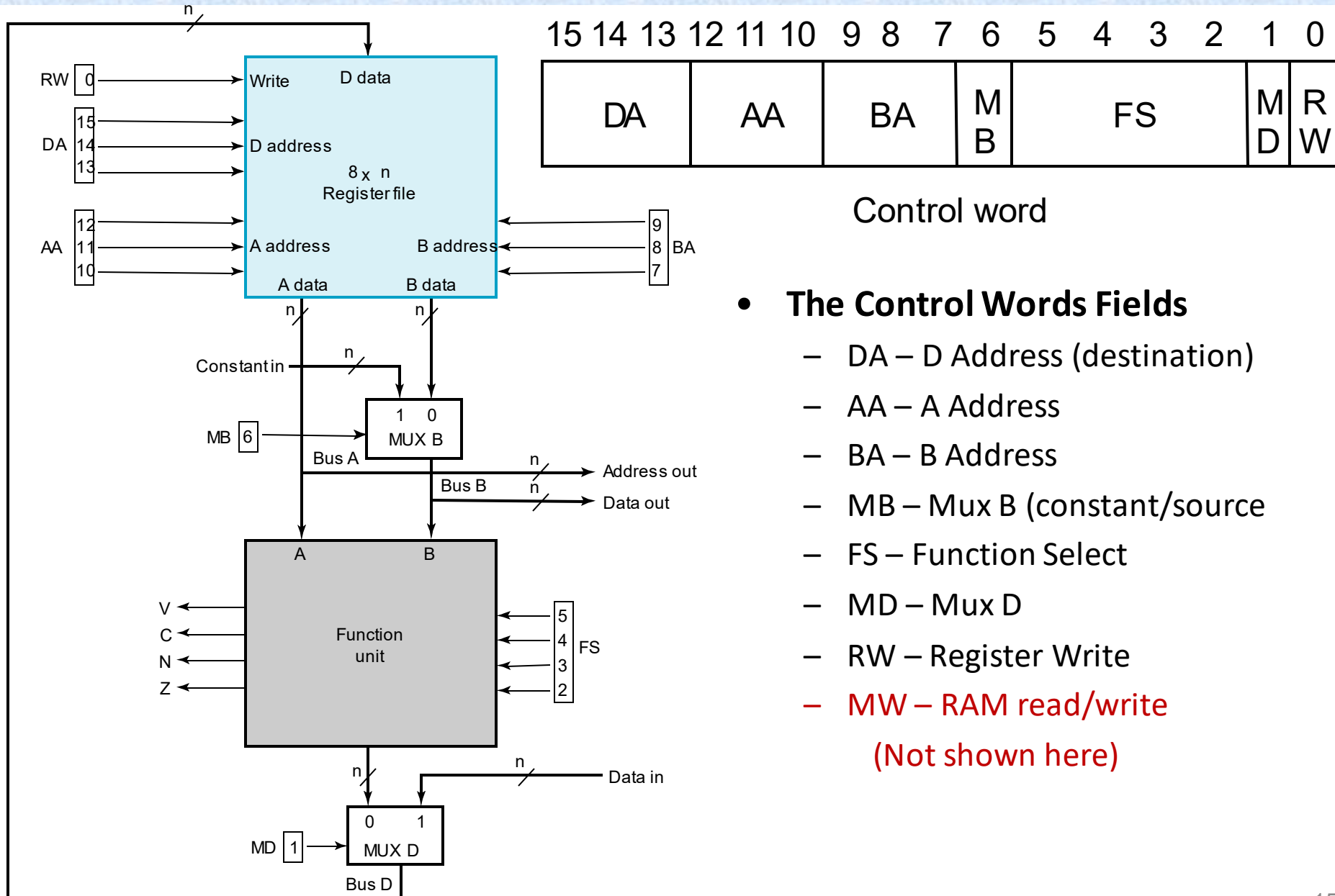

Encoding The Control Word ...

□ **TABLE 8-5**
Encoding of Control Word for the Datapath

DA, AA, BA		MB		FS		MD		RW	
Function	Code	Function	Code	Function	Code	Function	Code	Function	Code
R_0	000	Register 0	0	$F = A$	0000	Function 0	0	No Write	0
R_1	001	Constant 1	1	$F = A + 1$	0001	Data in	1	Write	1
R_2	010			$F = A + B$	0010				
R_3	011			$F = A + B + 1$	0011				
R_4	100			$F = A + \bar{B}$	0100				
R_5	101			$F = A + \bar{B} + 1$	0101				
R_6	110			$F = A - 1$	0110				
R_7	111			$F = A$	0111				
				$F = A \wedge B$	1000				
				$F = A \vee B$	1001				
				$F = A \oplus B$	1010				
				$F = \bar{A}$	1011				
				$F = B$	1100				
				$F = sr B$	1101				
				$F = sl B$	1110				

Microoperations for the Datapath...

- Symbolic Representation

□ **TABLE 8-6**

Examples of Microoperations for the Datapath, Using Symbolic Notation

Micro-operation	DA	AA	BA	MB	FS	MD	RW
$R1 \leftarrow R2 - R3$	$R1$	$R2$	$R3$	Register	$F = A + \bar{B} + I$	Function	Write
$R4 \leftarrow \text{sl } R6$	$R4$	—	$R6$	Register	$F = \text{sl } B$	Function	Write
$R7 \leftarrow R7 + 1$	$R7$	$R7$	—	—	$F = A + 1$	Function	Write
$R1 \leftarrow R0 + 2$	$R1$	$R0$	—	Constant	$F = A + B$	Function	Write
$M(R1) \leftarrow R3$	—	$R1$	$R3$	Register	—	—	No Write
$R4 \leftarrow M(R1)$	$R4$	$R1$	—	—	—	RAM	Write
$R5 \leftarrow 0$	$R5$	$R0$	$R0$	Register	$F = A \oplus B$	Function	Write

Microoperations for the Datapath ...

- Binary Representation

□ TABLE 8-7


Examples of Microoperations from Table 8-6, Using Binary Control Words

Micro-operation	DA	AA	BA	MB	FS	MD	RW
$R1 \leftarrow R2 - R3$	001	010	011	0	0101	0	1
$R4 \leftarrow sl R6$	100	XXX	110	0	1110	0	1
$R7 \leftarrow R7 + 1$	111	111	XXX	X	0001	0	1
$R1 \leftarrow R0 + 2$	001	000	XXX	1	0010	0	1
$M(R1) \leftarrow R3$	XXX	001	011	0	XXXX	X	0
$R4 \leftarrow M(R1)$	100	001	XXX	X	XXXX	1	1
$R5 \leftarrow 0$	101	000	000	0	1010	0	1

Results of simulation of the above on the next slide

Datapath Simulation ...

- Results of simulation of the above

 

Stored Program Computer

- Control words operate the datapath
- Store control words in memory
 - Sequence through them to perform a series of computational steps