



CSC 220: Computer Organization

Unit 5

COMBINATIONAL CIRCUITS-1

Prepared by:

Md Saiful Islam, PhD

Department of Computer Science

College of Computer and Information Sciences


Overview

- Introduction to Combinational Circuits
- Adder
- Ripple Carry Adder
- Subtraction
- Adder/Subtractor

Chapter-3

M. Morris Mano, Charles R. Kime and Tom Martin, **Logic and Computer Design Fundamentals**, Global (5th) Edition, Pearson Education Limited, 2016. ISBN: 9781292096124


Combinational circuits

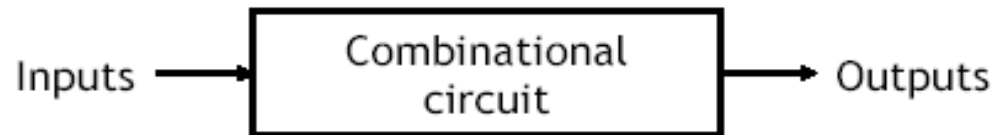

- So far we've only worked with **combinational circuits**, where applying the same inputs always produces the same outputs.
 - This corresponds to a mathematical function, where every input has a single, unique output.
 - In programming terminology, combinational circuits are similar to “functional programs” that do not contain variables and assignments.
- Such circuits are comparatively easy to design and analyze.

Binary addition by hand

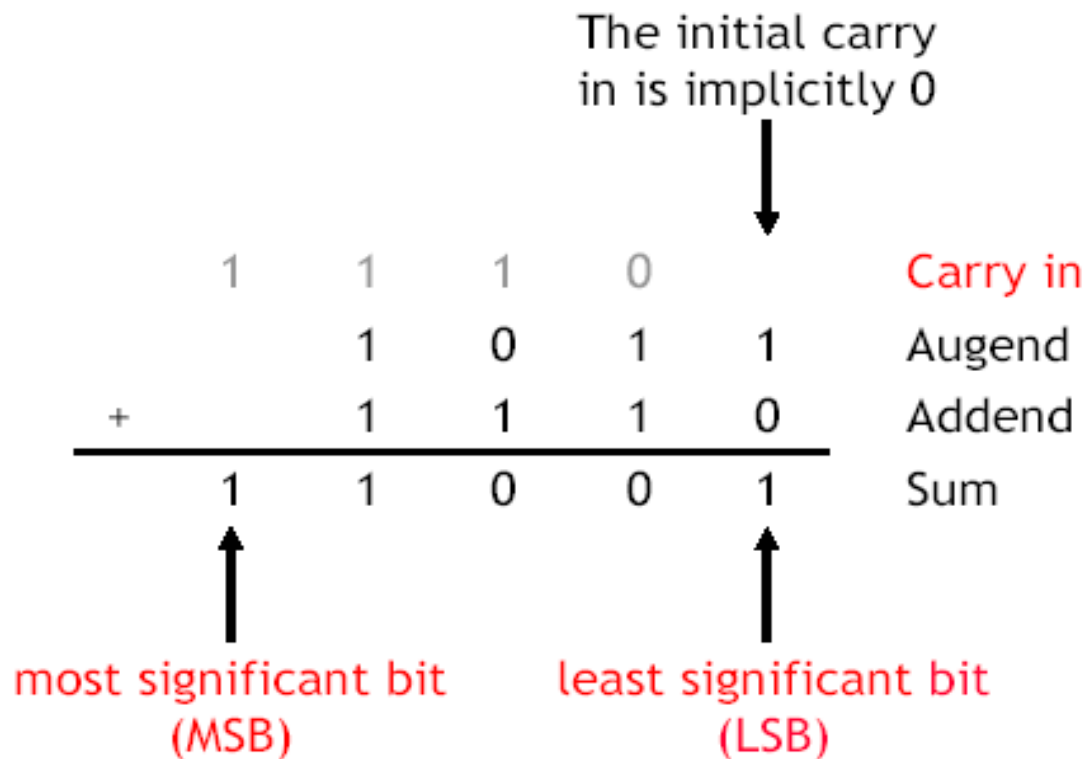- You can add two binary numbers one column at a time starting from the right, just like you add two decimal numbers.
- But remember it's binary. For example, $1 + 1 = 10$ and you have to carry!



Adder

- Design an Adder for 1-bit numbers?
- **1. Specification:**
 - 2 inputs (X,Y)
 - 2 outputs (C,S)

Adder ...

- Design an Adder for 1-bit numbers?
- **1. Specification:**
 - 2 inputs (X,Y)
 - 2 outputs (C,S)
- **2. Formulation:**

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Adder ...

- Design an Adder for 1-bit numbers?

- **1. Specification:**


2 inputs (X,Y)

2 outputs (C,S)

- **2. Formulation:**

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


- **3. Optimization/Circuit**

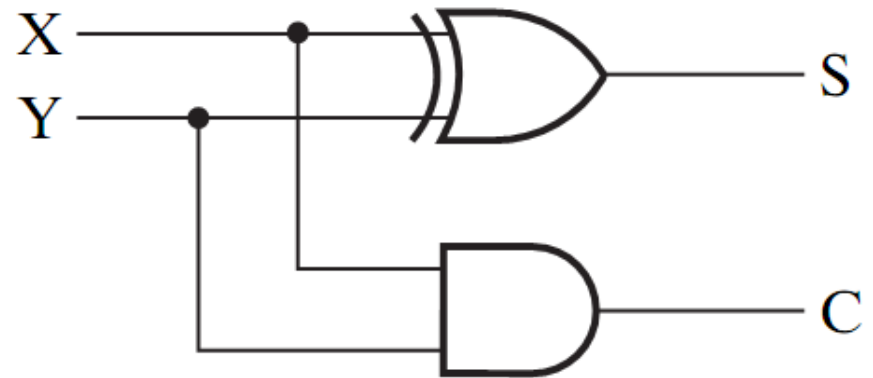

Half Adder ...

- This adder is called a Half Adder
- **Q: Why?**

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

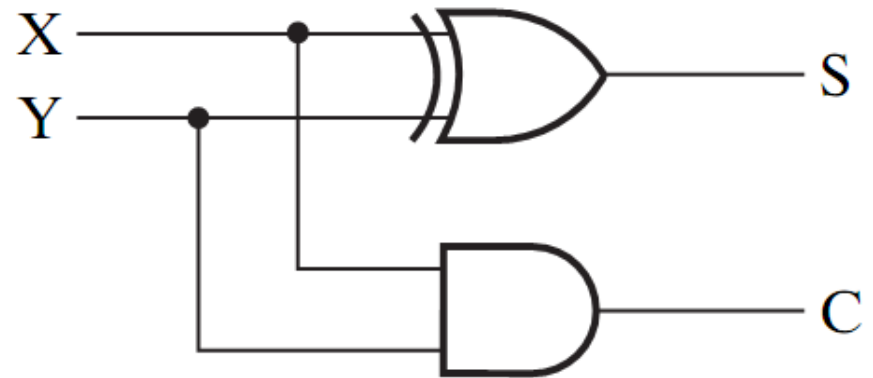

Full Adder

- A combinational circuit that adds 3 input bits to generate a Sum bit and a Carry bit
- A truth table and sum of minterm equations for C and S are shown below.

	X	Y	Z	C	S
	0	0	0	0	0
	0	0	1	0	1
	0	1	0	0	1
$0 + 1 + 1 = 10$ →	0	1	1	1	0
	1	0	0	0	1
	1	0	1	1	0
	1	1	0	1	0
$1 + 1 + 1 = 11$ →	1	1	1	1	1

$$C(X,Y,Z) = \sum m(3,5,6,7)$$

$$S(X,Y,Z) = \sum m(1,2,4,7)$$

Full Adder

- A combinational circuit that adds 3 input bits to generate a Sum bit and a Carry bit

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Sum

X \ YZ	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$\begin{aligned}
 S &= X'Y'Z + X'YZ' \\
 &+ XY'Z' + XYZ \\
 &= X \oplus Y \oplus Z
 \end{aligned}$$

Carry

X \ YZ	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$$C = XY + YZ + XZ$$

Full Adder

Full Adder = 2 Half Adders

Manipulating the Equations:

$$S = (X \oplus Y) \oplus Z$$

$$C = XY + XZ + YZ$$

$$= XY + XZ(Y + Y') + YZ(X + X')$$

$$= XY + XYZ + XY'Z + X'YZ + \cancel{XYZ}$$

$$= XY(1 + Z) + Z(XY' + X'Y)$$

$$= XY + Z(X \oplus Y)$$


Full Adder

Full Adder = 2 Half Adders

Manipulating the Equations:

$$S = (X \oplus Y) \oplus Z$$
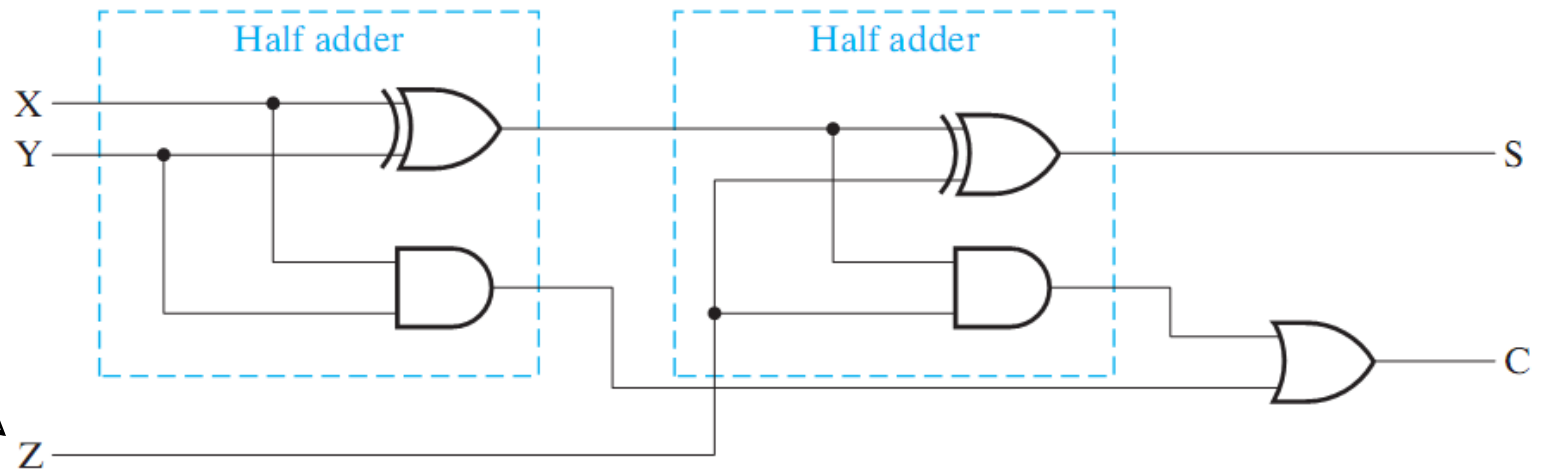
$$C = XY + XZ + YZ = XY + Z(X \oplus Y)$$



Think of
Z as a
carry in

Src: Mano's Book

n-bit Adder

- How to build an adder for n-bit numbers?
 - Example: 4-Bit Adder
 - Inputs ?
 - Outputs ?
 - What is the size of the truth table?
 - How many functions to optimize?

n-bit Adder ...

- How to build an adder for n-bit numbers?
 - Example: 4-Bit Adder
 - Inputs ? **9 inputs**
 - Outputs ? **5 outputs**
 - What is the size of the truth table? **512 rows!**
 - How many functions to optimize? **5 functions**


Binary Parallel Adder

- To add n-bit numbers:
- Use n Full-Adders in parallel
- The carries propagates as in addition by hand
- Use Z in the circuit as a C_{in}

- $$\begin{array}{r} 1\ 0\ 0\ 0 \\ 0\ 1\ 0\ 1 \\ 0\ 1\ 1\ 0 \\ \hline 1\ 0\ 1\ 1 \end{array}$$

Binary Parallel Adder ..

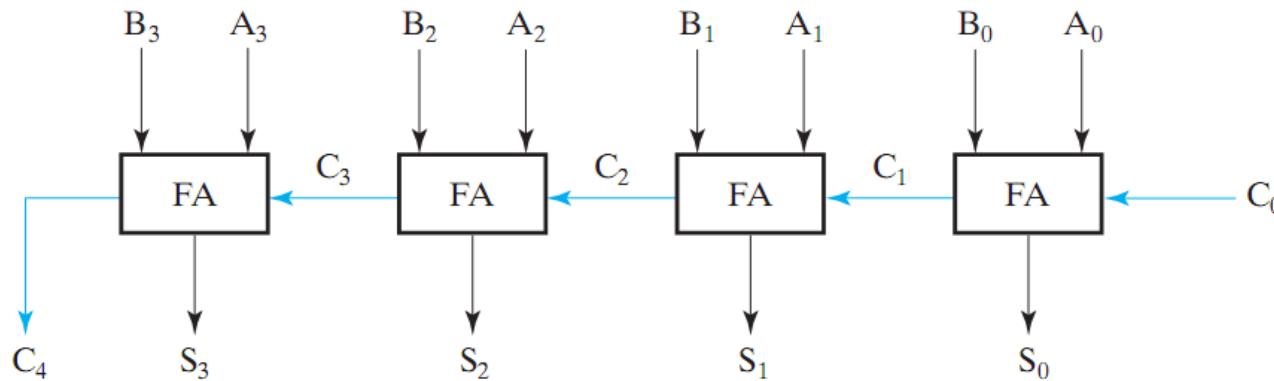- To add n-bit numbers:
- Use n Full-Adders in parallel
- The carries propagates as in addition by hand




This adder is called *ripple carry adder*

Src: Mano's Book

Subtraction (2's Complement)

- How to build a subtractor using 2's complement?


$$S = A - B$$
$$= A + (-B)$$

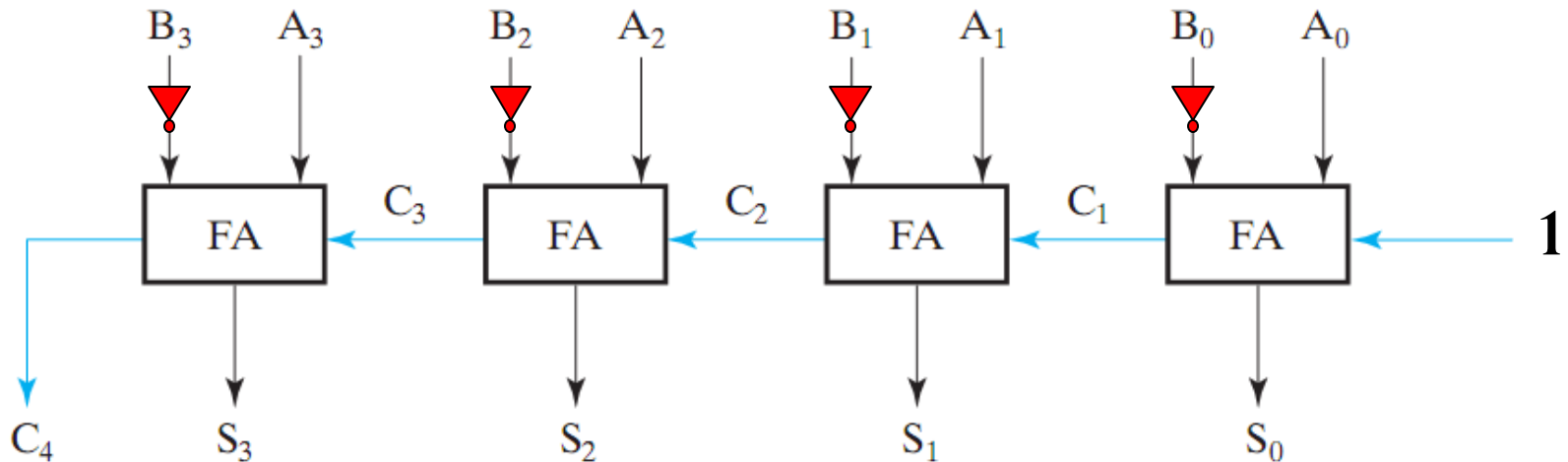

Src: Mano's Book

Adder-Subtractor

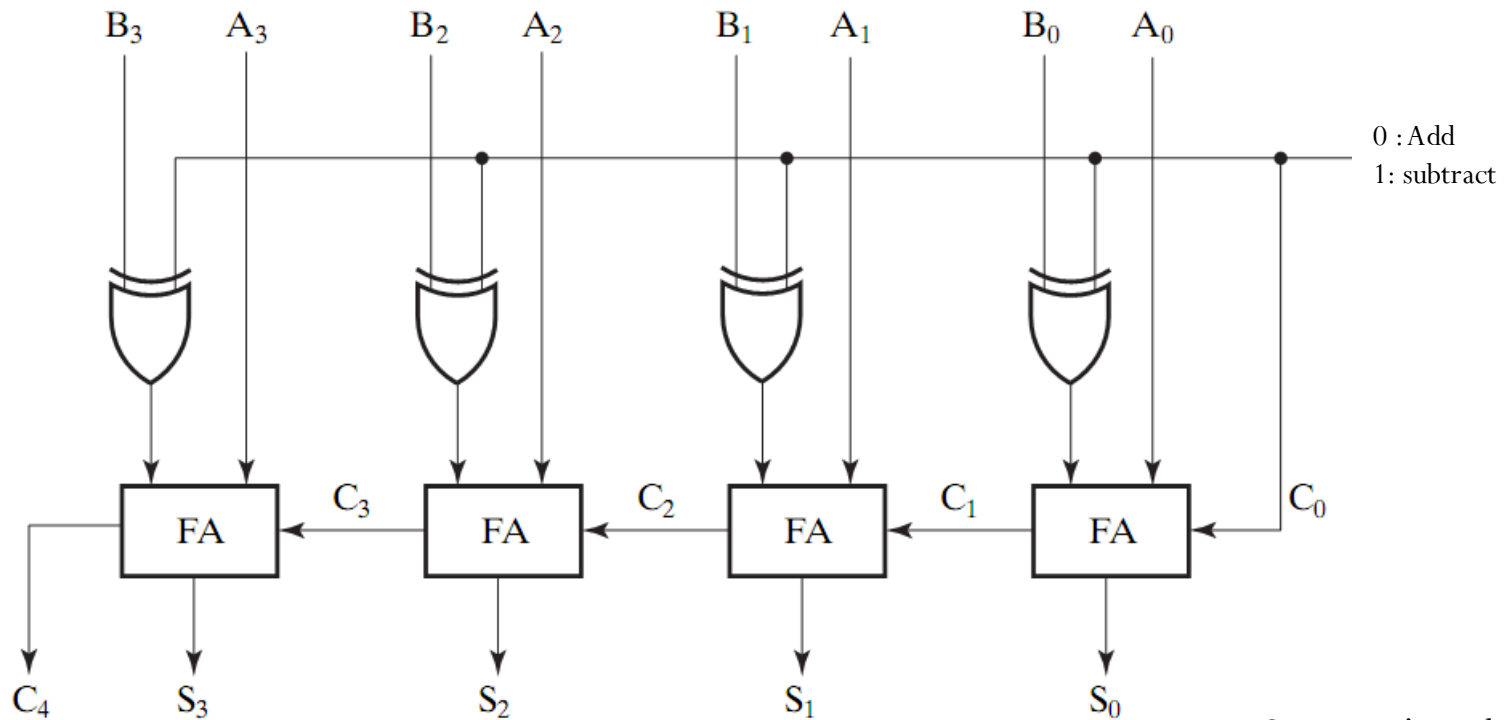
- How to build a circuit that performs both addition and subtraction?




Src: Mano's Book

Using full adders and XOR we can build an Adder/Subtractor!

Carry Look Ahead Adder

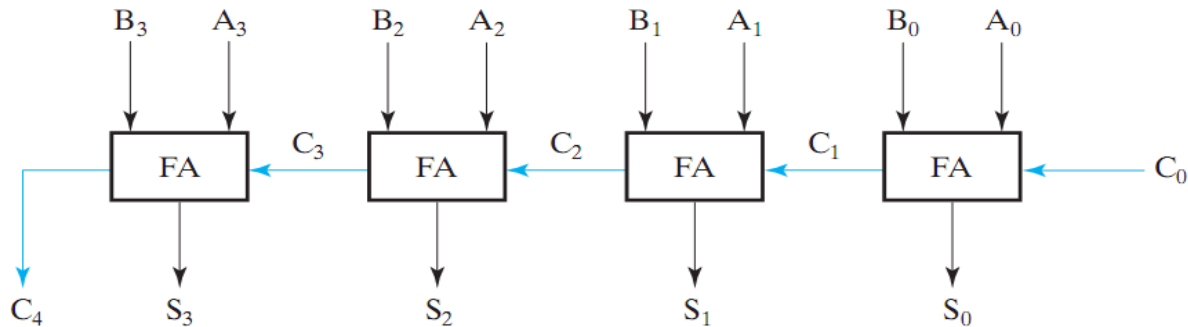

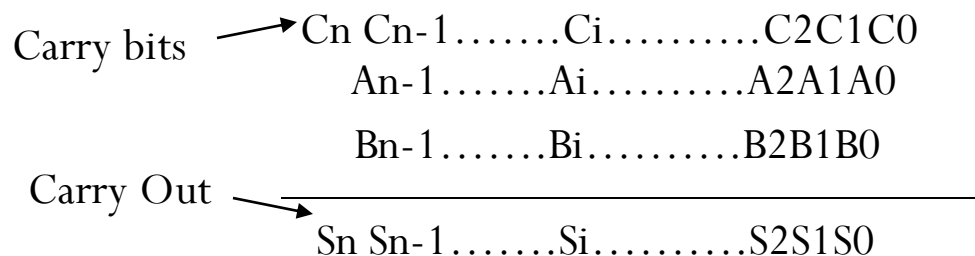- How to reduce propagation delay of ripple carry adders?
- **Carry look ahead adder:** All carries are computed as a function of C_0 (independent of n !)
- It works on the following standard principles:
 - A carry bit is generated when both input bits A_i and B_i are 1, or
 - When one of input bits is 1, and a carry in bit exists



Detecting signed overflow

- The easiest way to detect signed overflow is to look at all the sign bits.

$$\begin{array}{r} \begin{array}{r} 0100 \quad (+4) \\ + 0101 \quad (+5) \\ \hline 01001 \quad (-7) \end{array} \qquad \begin{array}{r} 1100 \quad (-4) \\ + 1011 \quad (-5) \\ \hline 10111 \quad (+7) \end{array} \end{array}$$

- Overflow occurs only in the two situations above.
 - If you add two *positive* numbers and get a *negative* result.
 - If you add two *negative* numbers and get a *positive* result.
- Overflow can never occur when you add a positive number to a negative number. (Do you see why?)



Detecting Sign Overflow ...

