



Chapter 28

Direct Current Circuits



Direct Current

- When the current in a circuit has a constant magnitude and direction, the current is called ***direct current***
- Because the potential difference between the terminals of a battery is constant, the battery produces direct current
- The battery is known as a source of emf




Electromotive Force

- The electromotive force (emf), ε , of a battery is the maximum possible voltage that the battery can provide between its terminals
 - The emf supplies energy, it does not apply a force
- The battery will normally be the source of energy in the circuit


Sample Circuit

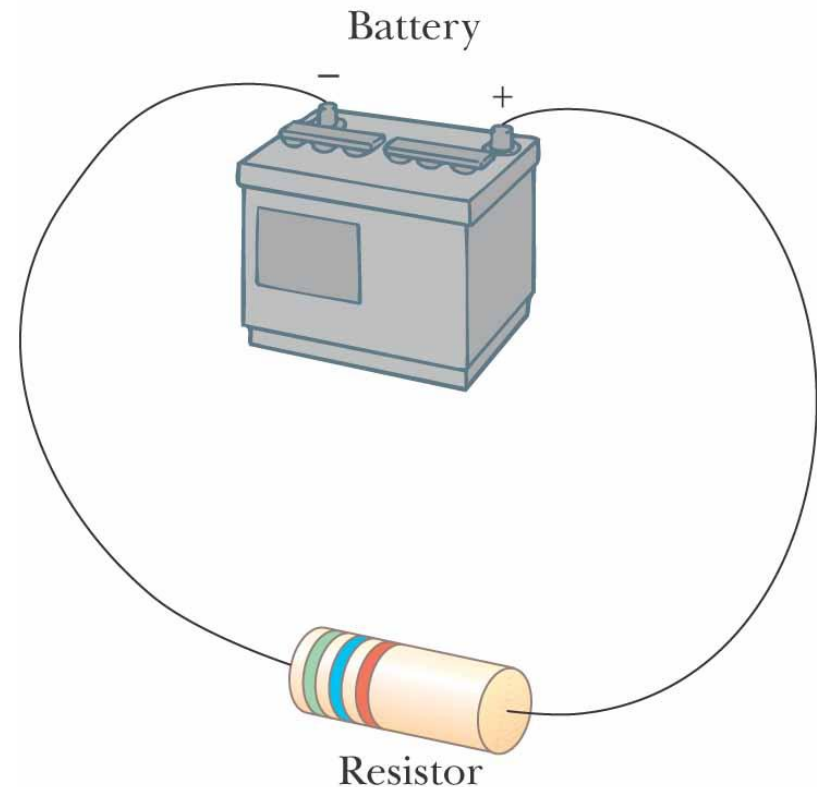- We consider the wires to have no resistance
- The positive terminal of the battery is at a higher potential than the negative terminal
- There is also an internal resistance in the battery



Internal Battery Resistance

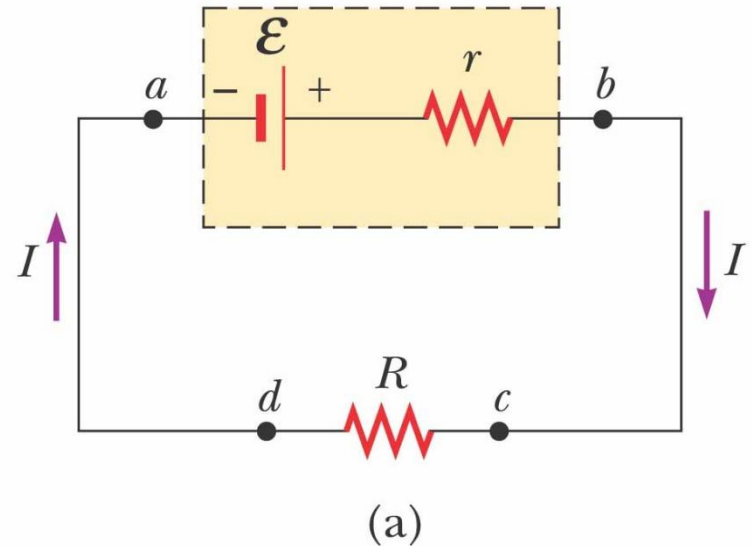- If the internal resistance is zero, the terminal voltage equals the emf
- In a real battery, there is internal resistance, r
- The terminal voltage, $\Delta V = \varepsilon - Ir$





EMF, cont

- The emf is equivalent to the *open-circuit* voltage
 - This is the terminal voltage when no current is in the circuit
 - This is the voltage labeled on the battery
- The actual potential difference between the terminals of the battery depends on the current in the circuit



Load Resistance

- The terminal voltage also equals the voltage across the external resistance
 - This external resistor is called the *load resistance*
 - In the previous circuit, the load resistance is the external resistor
 - In general, the load resistance could be any electrical device



Power

- The total power output of the battery is
 $P = I\Delta V = I\mathcal{E}$
- This power is delivered to the external resistor ($I^2 R$) and to the internal resistor ($I^2 r$)
- $P = I\mathcal{E} = I^2 R + I^2 r$




Resistors in Series

- When two or more resistors are connected end-to-end, they are said to be in *series*
- For a series combination of resistors, the currents are the same in all the resistors because the amount of charge that passes through one resistor must also pass through the other resistors in the same time interval
- The potential difference will divide among the resistors such that the sum of the potential differences across the resistors is equal to the total potential difference across the combination

Resistors in Series, cont

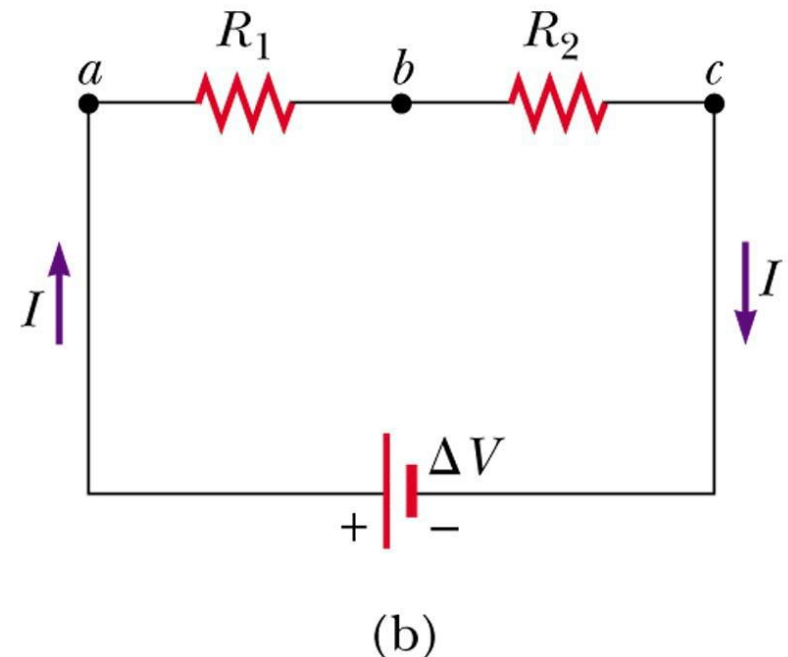- Potentials add
 - $\Delta V = IR_1 + IR_2$
 $= I(R_1 + R_2)$
 - Consequence of Conservation of Energy
- The equivalent resistance has the same effect on the circuit as the original combination of resistors






Equivalent Resistance – Series

- $R_{eq} = R_1 + R_2 + R_3 + \dots$
- The equivalent resistance of a series combination of resistors is the algebraic sum of the individual resistances and is always greater than any individual resistance
- If one device in the series circuit creates an open circuit, all devices are inoperative

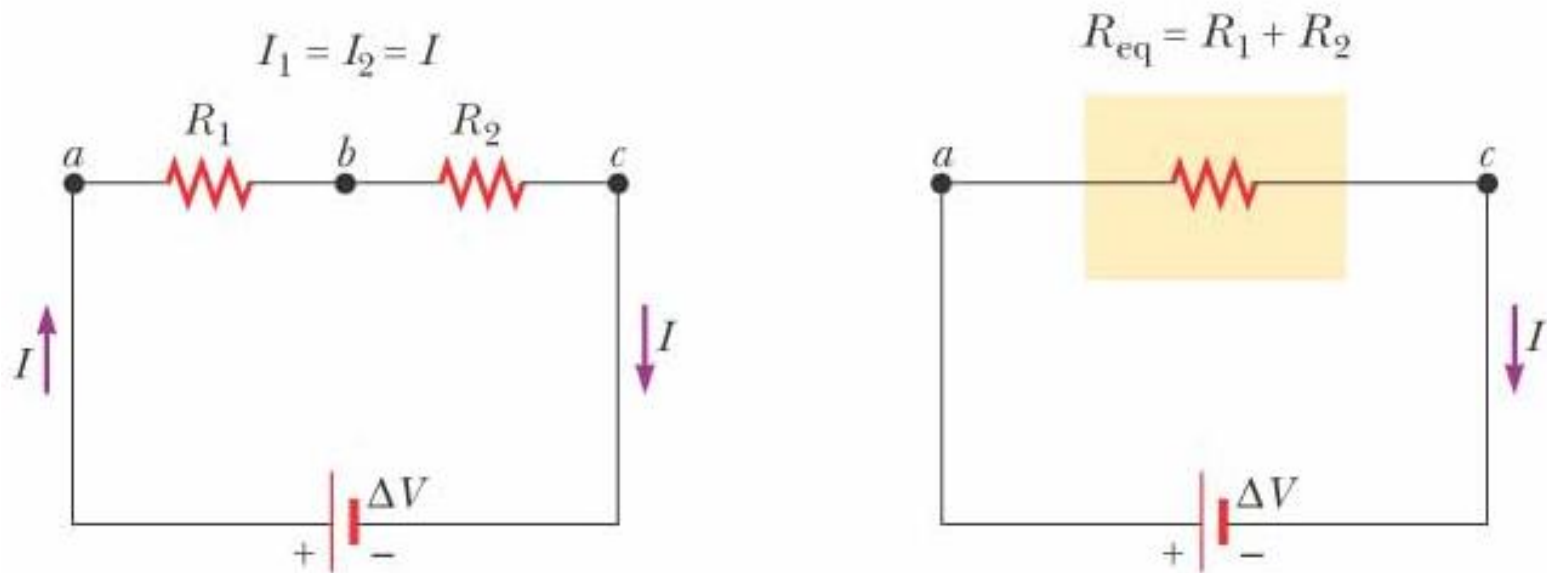Equivalent Resistance – Series – An Example




- Two resistors are replaced with their equivalent resistance



Resistors in Parallel

- The potential difference across each resistor is the same because each is connected directly across the battery terminals
- The current, I , that enters a point must be equal to the total current leaving that point
 - $I = I_1 + I_2$
 - The currents are generally not the same
 - Consequence of Conservation of Charge

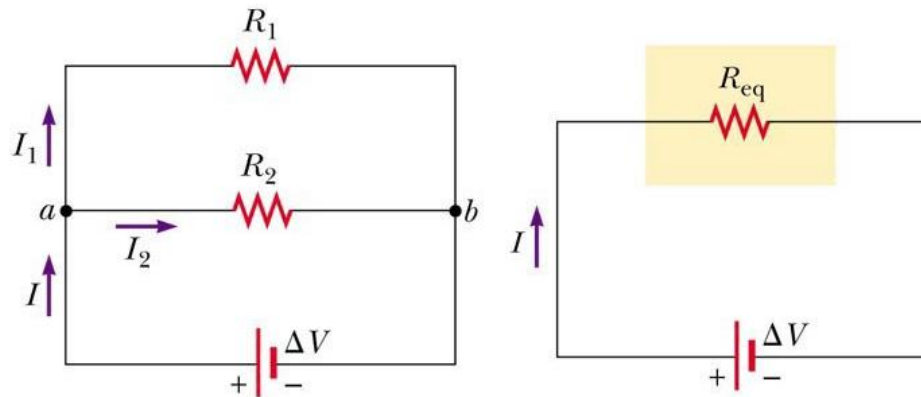Equivalent Resistance – Parallel, Examples




- Equivalent resistance replaces the two original resistances
- *Household circuits* are wired so that electrical devices are connected in parallel
 - Circuit breakers may be used in series with other circuit elements for safety purposes

Equivalent Resistance – Parallel

- Equivalent Resistance

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

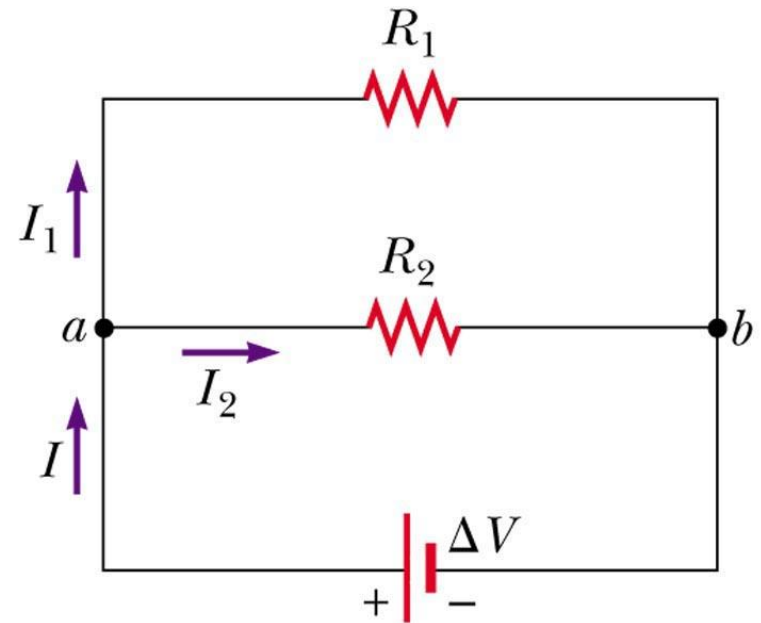- The inverse of the equivalent resistance of two or more resistors connected in parallel is the algebraic sum of the inverses of the individual resistance
 - The equivalent is always less than the smallest resistor in the group



(b)




Resistors in Parallel, Final

- In parallel, each device operates independently of the others so that if one is switched off, the others remain on
- In parallel, all of the devices operate on the same voltage
- The current takes all the paths
 - The lower resistance will have higher currents
 - Even very high resistances will have some currents


Combinations of Resistors

- The $8.0\text{-}\Omega$ and $4.0\text{-}\Omega$ resistors are in series and can be replaced with their equivalent, $12.0\ \Omega$
- The $6.0\text{-}\Omega$ and $3.0\text{-}\Omega$ resistors are in parallel and can be replaced with their equivalent, $2.0\ \Omega$
- These equivalent resistances are in series and can be replaced with their equivalent resistance, $14.0\ \Omega$

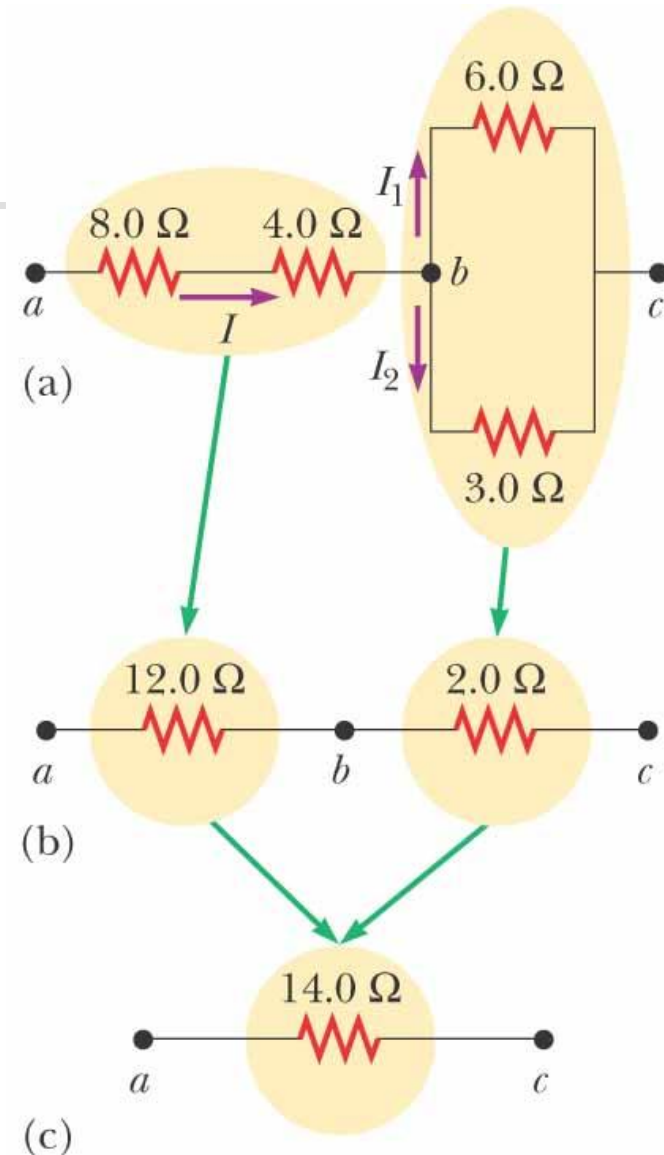


Question 1

What is the current passing through each resistor?
Determine the voltage for each resistor?

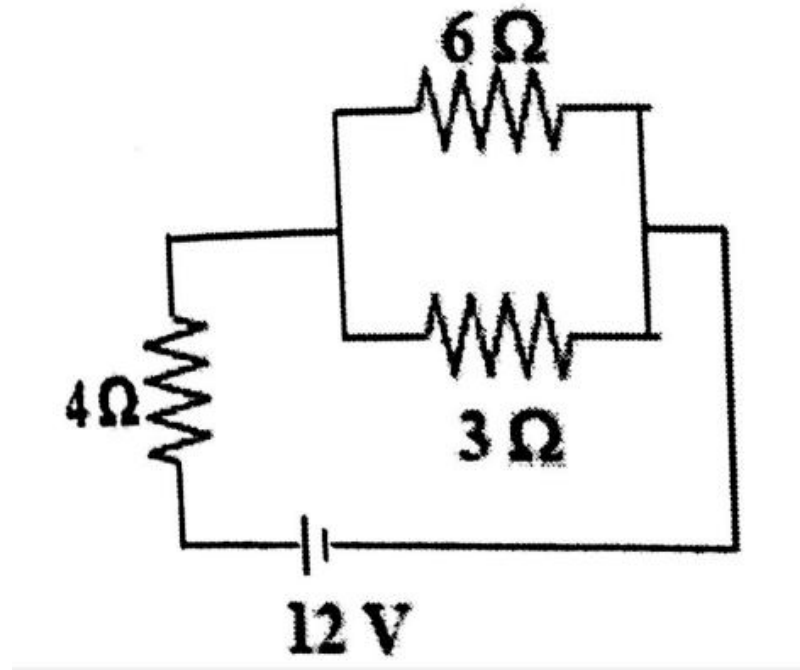

Question 2


Find the equivalent resistance if each resistor is $1\ \Omega$?

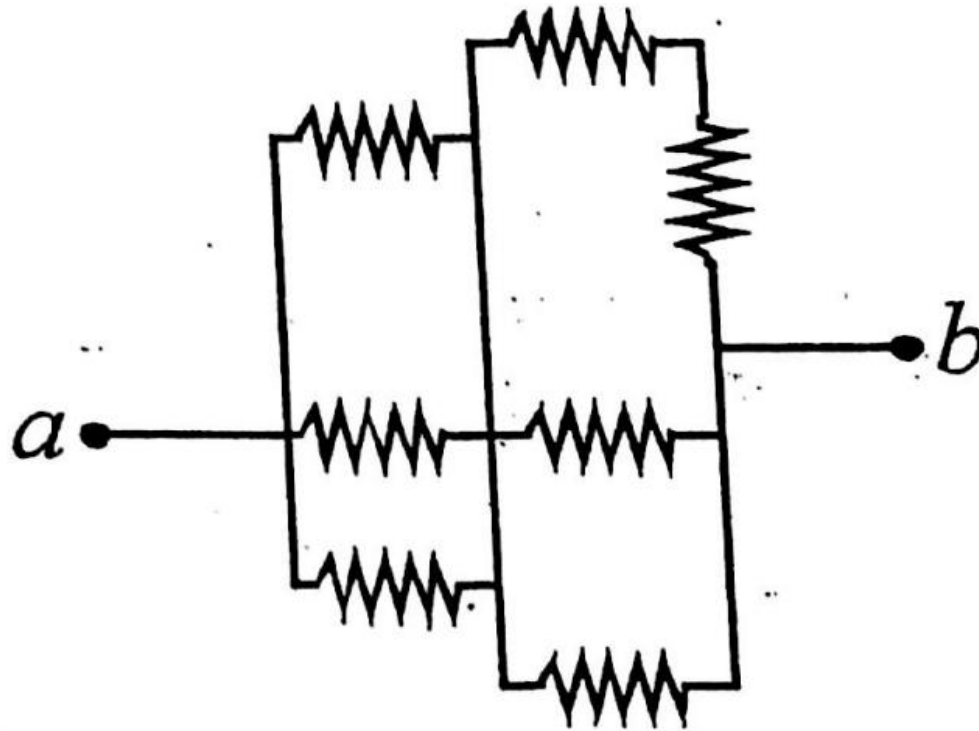




Question 3

What is the equivalent resistance?

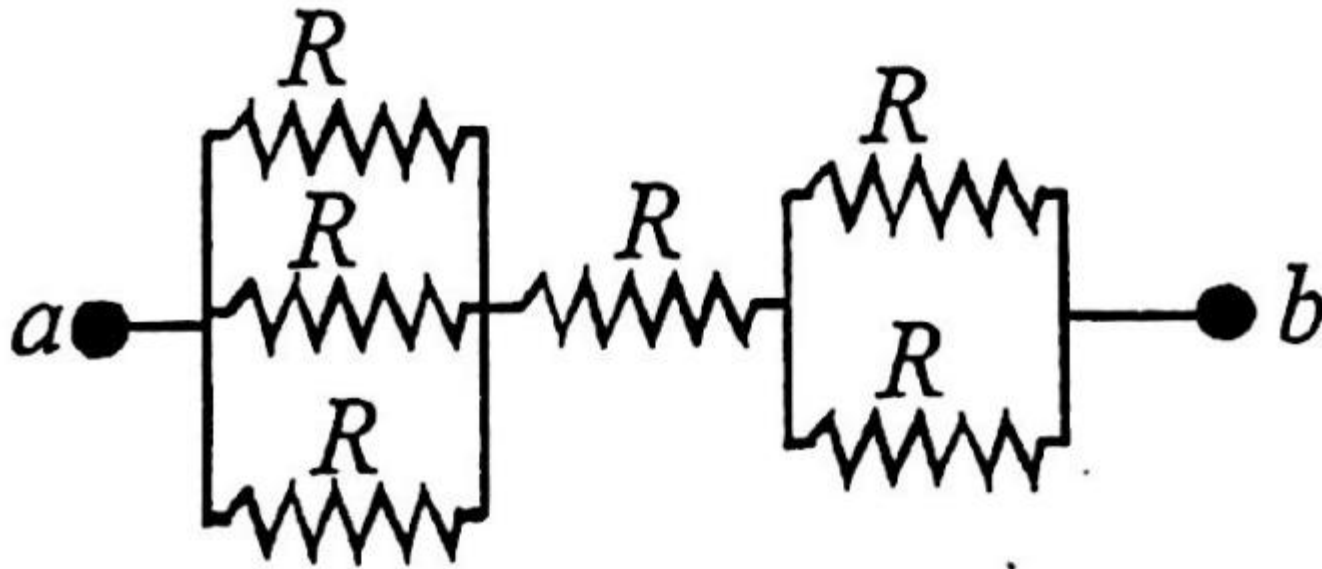

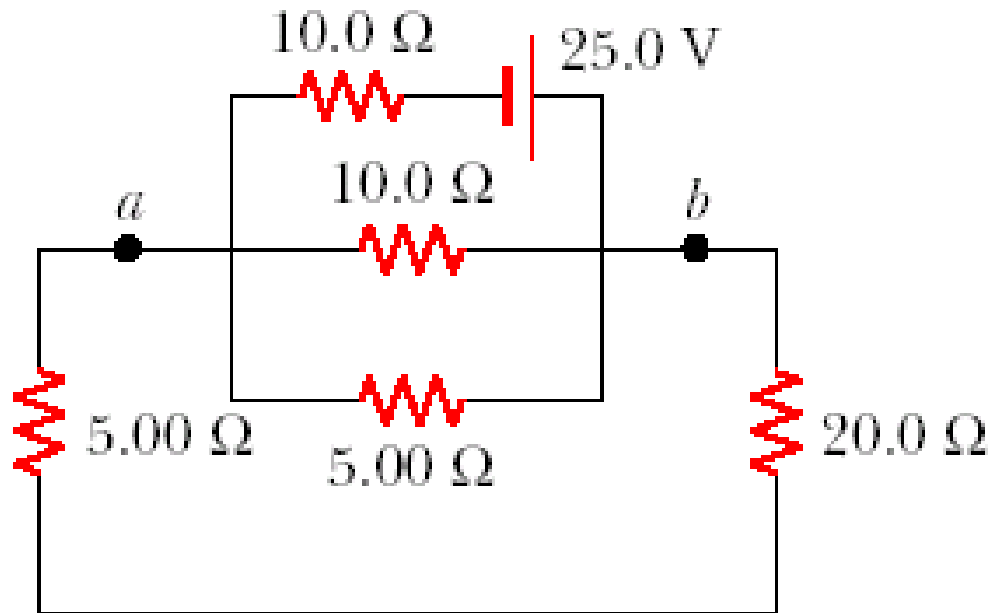Question 4

Consider the circuit shown in Figure P28.9. Find (a) the current in the $20.0\text{-}\Omega$ resistor and (b) the potential difference between points a and b .





Kirchhoff's Rules

- There are ways in which resistors can be connected so that the circuits formed cannot be reduced to a single equivalent resistor
- Two rules, called **Kirchhoff's rules**, can be used instead



Statement of Kirchhoff's Rules

- Junction Rule

- The sum of the currents entering any junction must equal the sum of the currents leaving that junction
 - A statement of Conservation of Charge

- Loop Rule

- The sum of the potential differences across all the elements around any closed circuit loop must be zero
 - A statement of Conservation of Energy



Mathematical Statement of Kirchhoff's Rules

- Junction Rule:



$$\Sigma I_{\text{in}} = \Sigma I_{\text{out}}$$

- Loop Rule:

$$\sum_{\text{closed loop}} \Delta V = 0$$



More about the Junction Rule

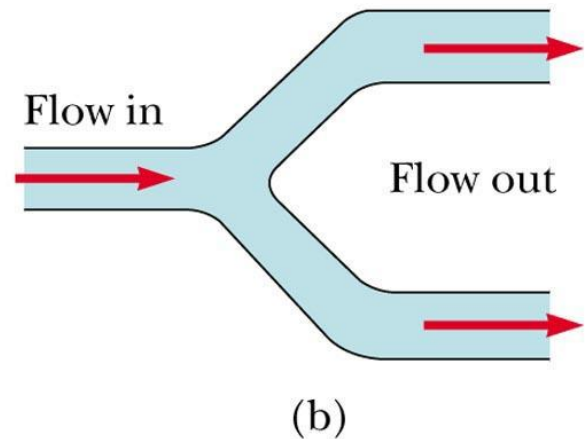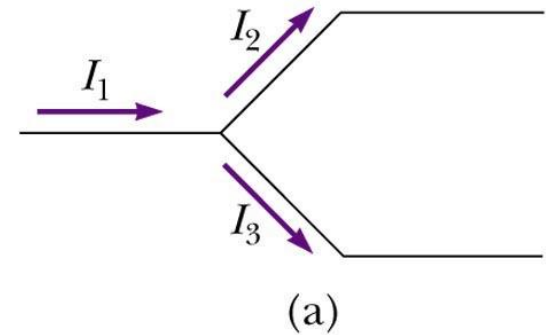- $I_1 = I_2 + I_3$
- From Conservation of Charge
- Diagram (b) shows a mechanical analog




More about the Loop Rule

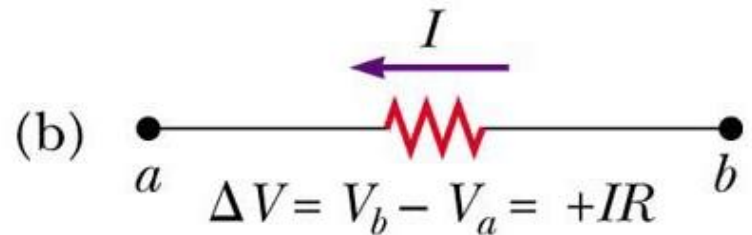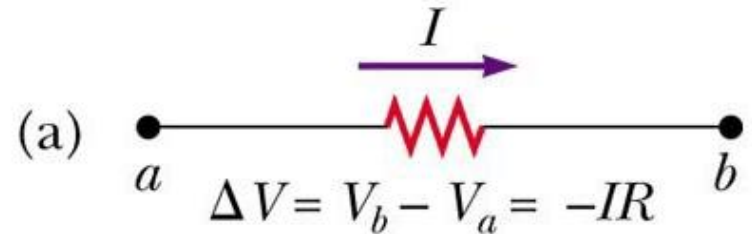- Traveling around the loop from a to b
- In (a), the resistor is traversed in the direction of the current, the potential across the resistor is $-IR$
- In (b), the resistor is traversed in the direction opposite of the current, the potential across the resistor is $+IR$




Loop Rule, final


- In (c), the source of emf is traversed in the direction of the emf (from $-$ to $+$), and the change in the electric potential is $+\mathcal{E}$
- In (d), the source of emf is traversed in the direction opposite of the emf (from $+$ to $-$), and the change in the electric potential is $-\mathcal{E}$

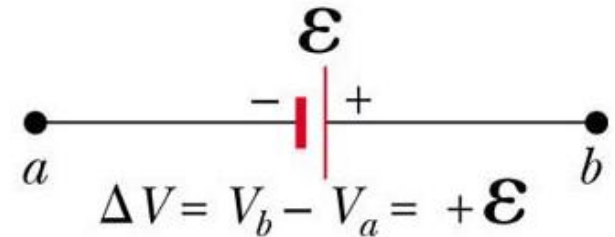(c) 

$$\Delta V = V_b - V_a = +\mathcal{E}$$

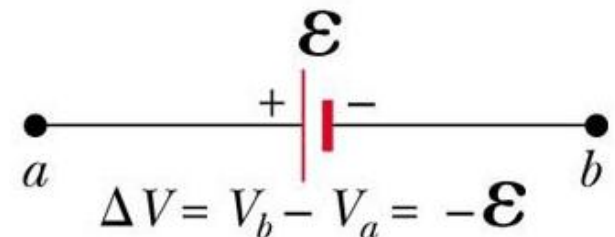(d) 

$$\Delta V = V_b - V_a = -\mathcal{E}$$

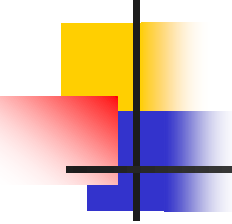

Junction Equations from Kirchhoff's Rules

- Use the junction rule as often as needed, so long as each time you write an equation, you include in it a current that has not been used in a previous junction rule equation
 - In general, the number of times the junction rule can be used is one fewer than the number of junction points in the circuit



Loop Equations from Kirchhoff's Rules

- The loop rule can be used as often as needed so long as a new circuit element (resistor or battery) or a new current appears in each new equation
- You need as many independent equations as you have unknowns



Kirchhoff's Rules Equations, final

- In order to solve a particular circuit problem, the number of independent equations you need to obtain from the two rules equals the number of unknown currents
- Any capacitor acts as an open branch in a circuit
 - The current in the branch containing the capacitor is zero under steady-state conditions



Problem-Solving Hints – Kirchhoff's Rules

- Draw the circuit diagram and assign labels and symbols to all known and unknown quantities. Assign directions to the currents.
 - The direction is arbitrary, but you must adhere to the assigned directions when applying Kirchhoff's rules
- Apply the junction rule to any junction in the circuit that provides new relationships among the various currents




Problem-Solving Hints, cont

- Apply the loop rule to as many loops as are needed to solve for the unknowns
 - To apply the loop rule, you must correctly identify the potential difference as you cross various elements
- Solve the equations simultaneously for the unknown quantities
 - If a current turns out to be negative, the magnitude will be correct and the direction is opposite to that which you assigned

Example 28.7

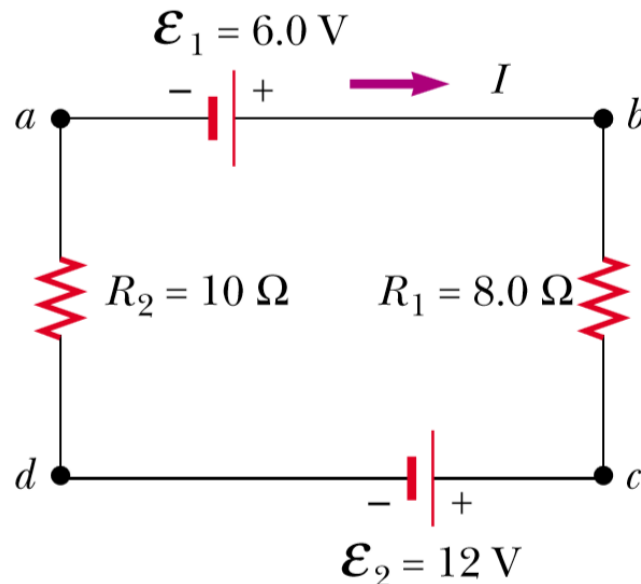
EXAMPLE 28.7 A Single-Loop Circuit

A single-loop circuit contains two resistors and two batteries, as shown in Figure 28.13. (Neglect the internal resistances of the batteries.) (a) Find the current in the circuit.




Exercise

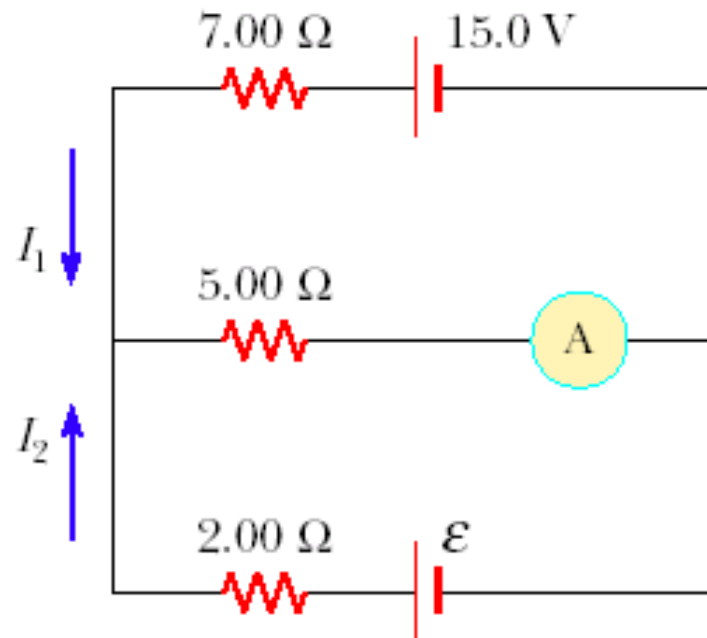Q28.20. The ammeter shown in the figure reads 2.00 A. Find I_1 , I_2 , and \mathcal{E} .




Exercise

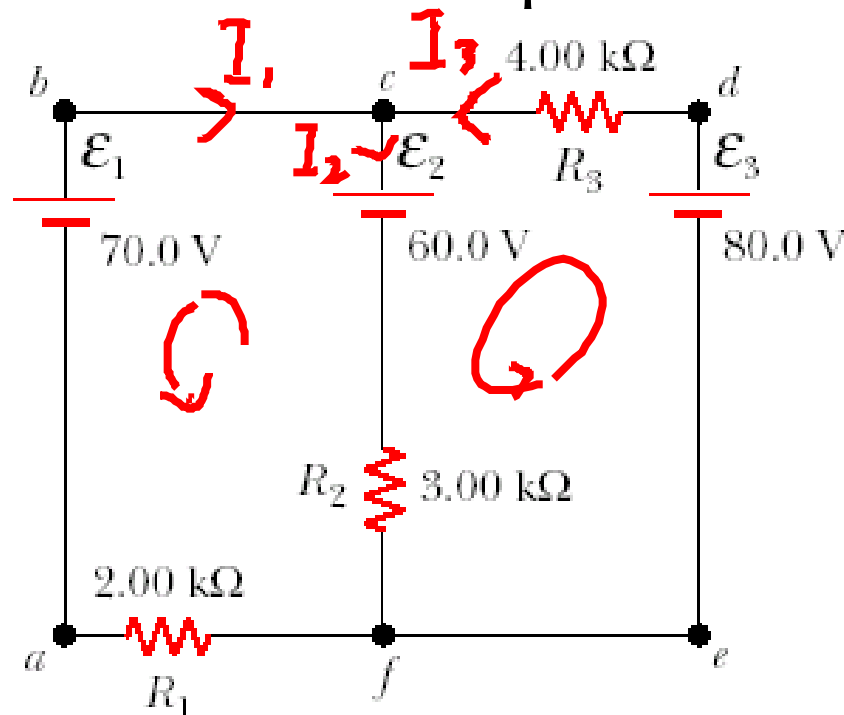Q28.24. Using Kirchhoff's rules, (a) find the current in each resistor in Figure. (b) Find the potential difference between points c and f . Which poi



Exercise

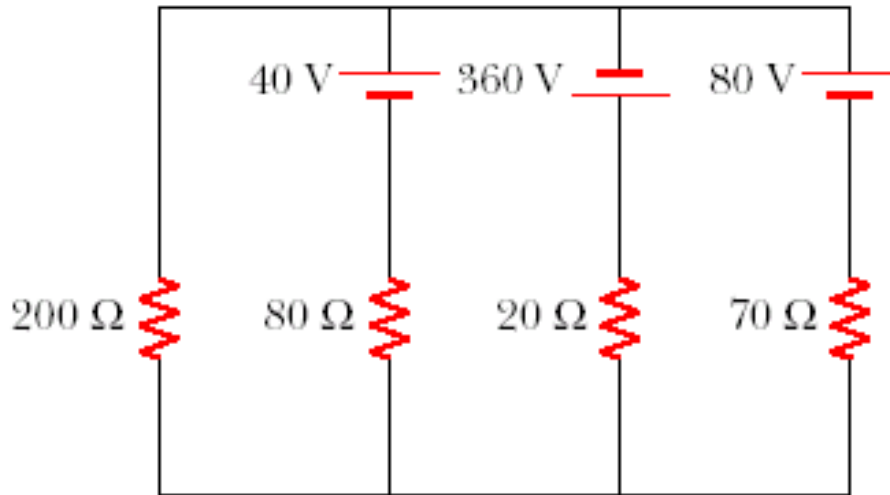26. In the circuit of Figure P28.26, determine the current in each resistor and the voltage across the 200- Ω resistor.



Exercise

30. Calculate the power delivered to each resistor shown in Figure P28.30.


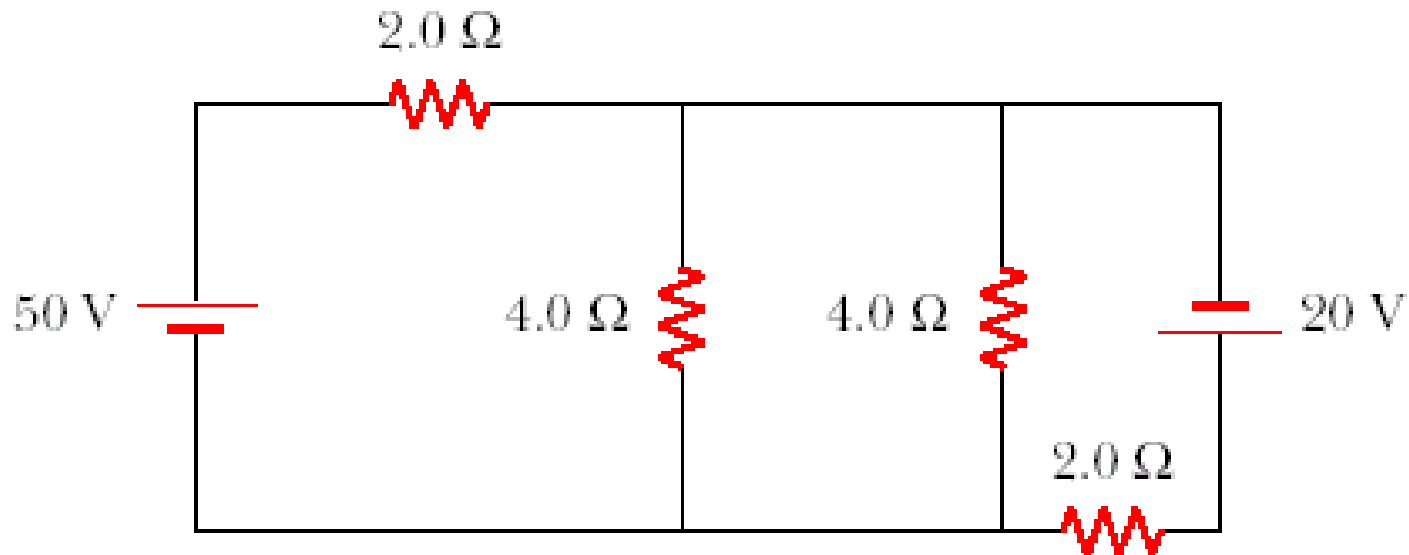


Figure P28.30

Exercise

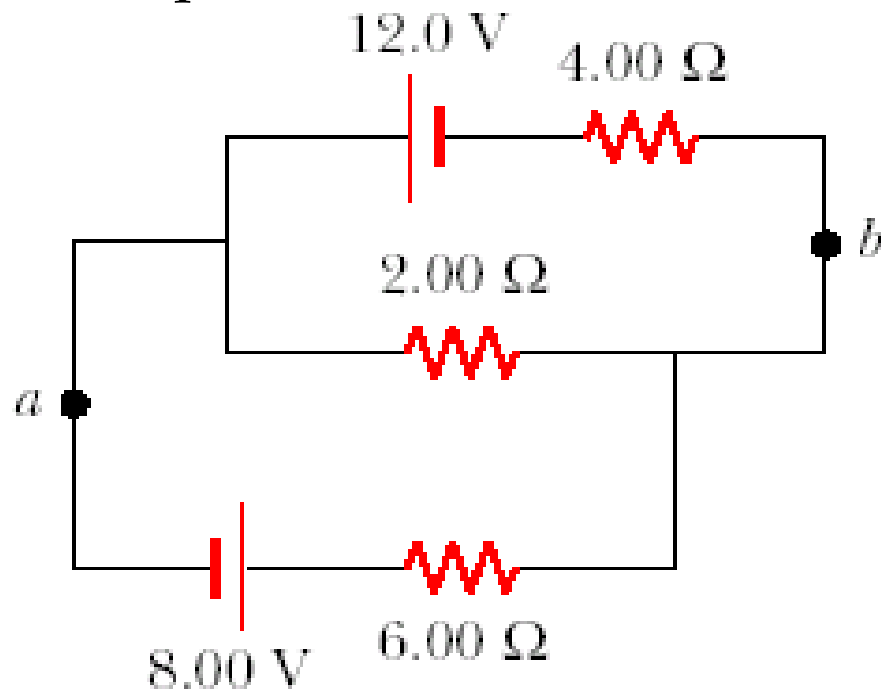29. For the circuit shown in Figure P28.29, calculate (a) the current in the $2.00\text{-}\Omega$ resistor and (b) the potential difference between points a and b .





RC Circuits

- A direct current circuit may contain capacitors and resistors, the current will vary with time
- When the circuit is completed, the capacitor starts to charge
- The capacitor continues to charge until it reaches its maximum charge ($Q = C\varepsilon$)
- Once the capacitor is fully charged, the current in the circuit is zero




Charging an RC Circuit

- As the plates are being charged, the potential difference across the capacitor increases
- At the instant the switch is closed, the charge on the capacitor is zero
- Once the maximum charge is reached, the current in the circuit is zero
 - The potential difference across the capacitor matches that supplied by the battery

Charging a Capacitor in an RC Circuit

- The charge on the capacitor varies with time
 - $q = C\varepsilon(1 - e^{-t/RC}) = Q(1 - e^{-t/RC})$
 - τ is the *time constant*
 - $\tau = RC$
- The current can be found
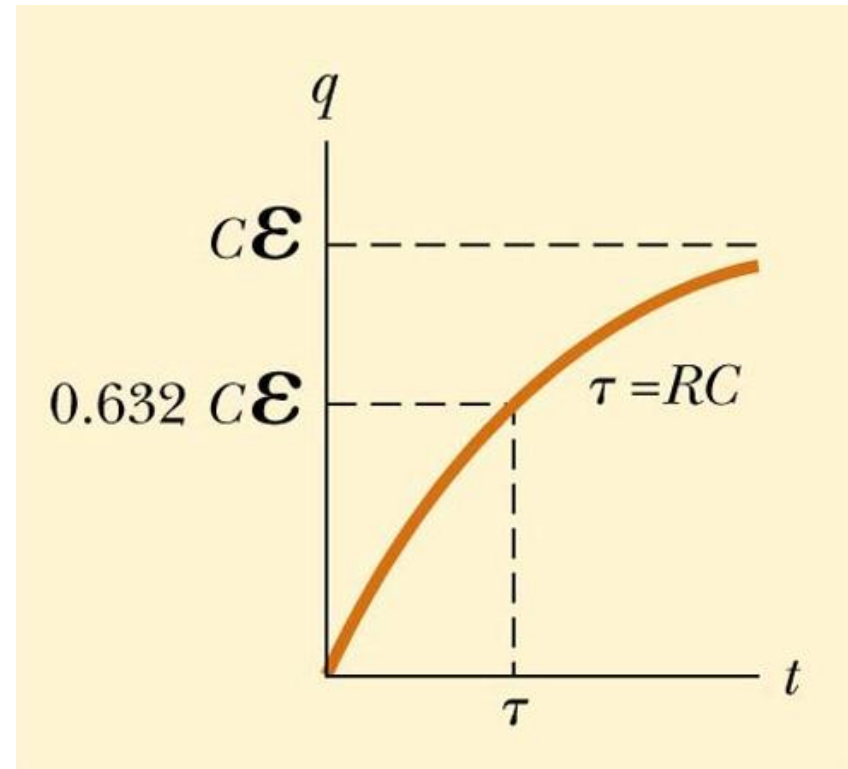
$$I(t) = \frac{\varepsilon}{R} e^{-t/RC}$$






Time Constant, Charging

- The time constant represents the time required for the charge to increase from zero to 63.2% of its maximum
- τ has units of time
- The energy stored in the charged capacitor is $\frac{1}{2} Q\varepsilon = \frac{1}{2} C\varepsilon^2$

Discharging a Capacitor in an RC Circuit

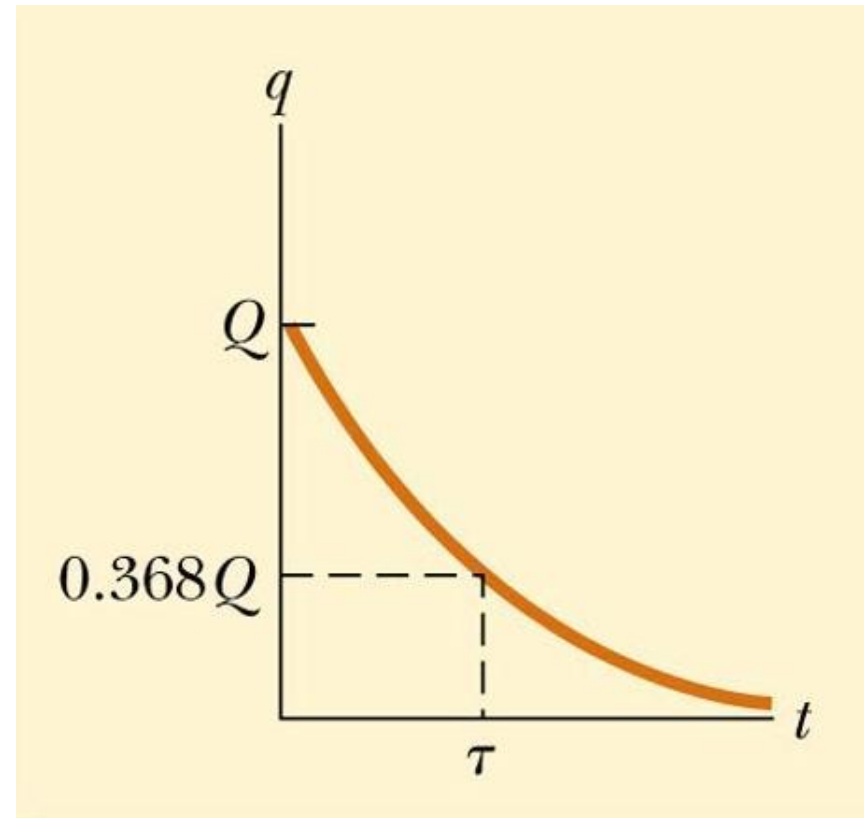- When a charged capacitor is placed in the circuit, it can be discharged
 - $q = Qe^{-t/RC}$
- The charge decreases exponentially





Discharging Capacitor

- At $t = \tau = RC$, the charge decreases to $0.368 Q_{\max}$
 - In other words, in one time constant, the capacitor loses 63.2% of its initial charge


- The current can be found

$$I(t) = \frac{dq}{dt} = -\frac{Q}{RC} e^{-t/RC}$$

- Both charge and current decay exponentially at a rate characterized by $\tau = RC$

Galvanometer

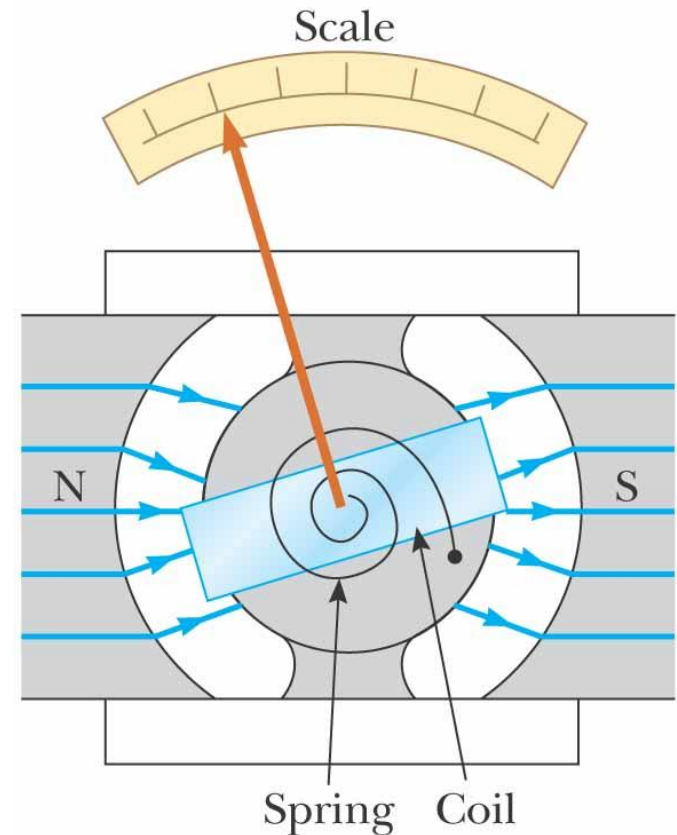- A galvanometer is the main component in analog meters for measuring current and voltage
- Digital meters are in common use
 - Digital meters operate under different principles





Galvanometer, cont

- A galvanometer consists of a coil of wire mounted so that it is free to rotate on a pivot in a magnetic field
- The field is provided by permanent magnets
- A torque acts on a current in the presence of a magnetic field



Galvanometer, final

- The torque is proportional to the current
 - The larger the current, the greater the torque
 - The greater the torque, the larger the rotation of the coil before the spring resists enough to stop the rotation
- The deflection of a needle attached to the coil is proportional to the current
- Once calibrated, it can be used to measure currents or voltages




Ammeter

- An **ammeter** is a device that measures current
- The ammeter must be connected in series with the elements being measured
 - The current must pass directly through the ammeter


Ammeter in a Circuit

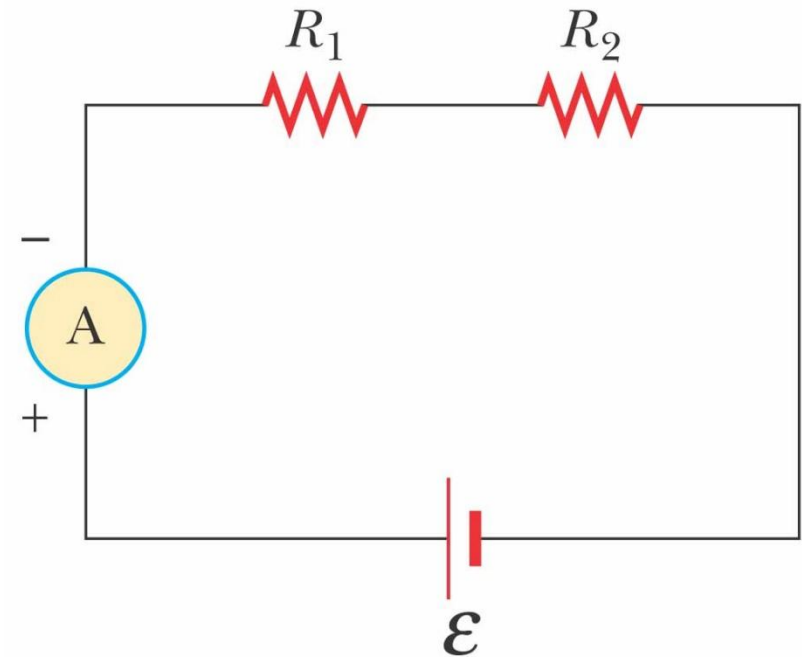- The ammeter is connected in series with the elements in which the current is to be measured
- Ideally, the ammeter should have zero resistance so the current being measured is not altered



Ammeter from Galvanometer

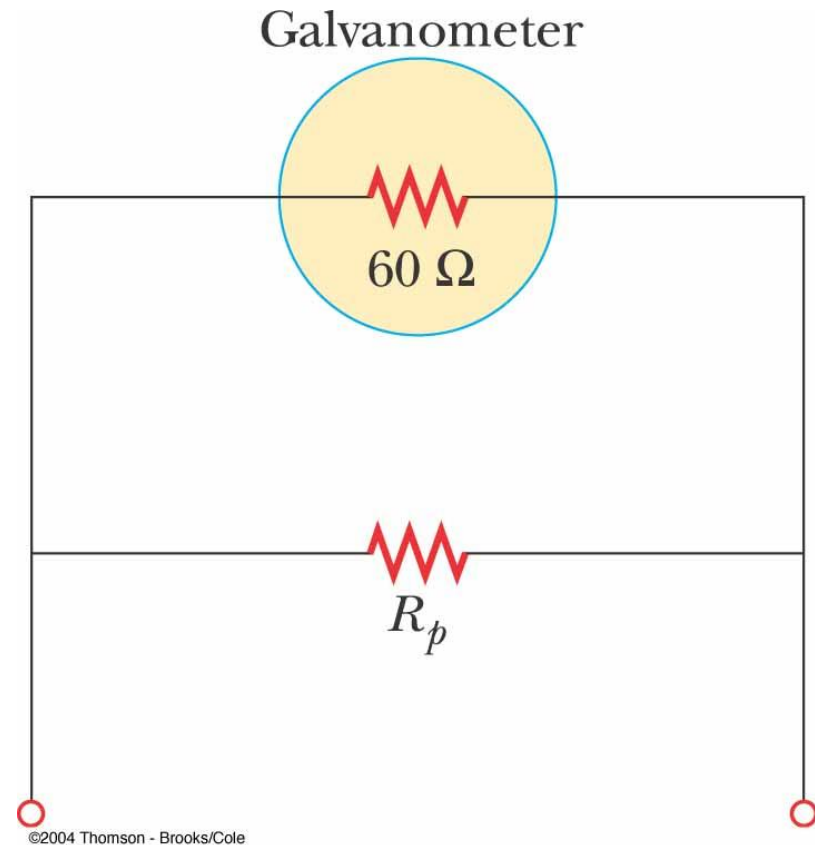- The galvanometer typically has a resistance of $60\ \Omega$
- To minimize the resistance, a *shunt resistance*, R_p , is placed in parallel with the galvanometer





Ammeter, final

- The value of the shunt resistor must be much less than the resistance of the galvanometer
 - Remember, the equivalent resistance of resistors in parallel will be less than the smallest resistance
- Most of the current will go through the shunt resistance, this is necessary since the full scale deflection of the galvanometer is on the order of 1 mA




Voltmeter

- A **voltmeter** is a device that measures potential difference
- The voltmeter must be connected in parallel with the elements being measured
 - The voltage is the same in parallel


Voltmeter in a Circuit

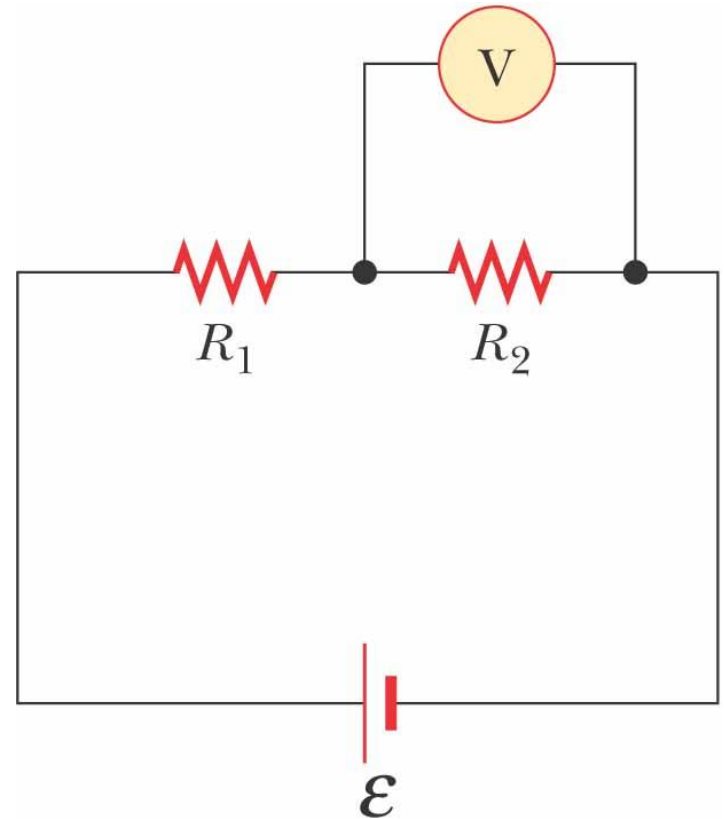- The voltmeter is connected in parallel with the element in which the potential difference is to be measured
 - Polarity must be observed
- Ideally, the voltmeter should have infinite resistance so that no current would pass through it



Voltmeter from Galvanometer

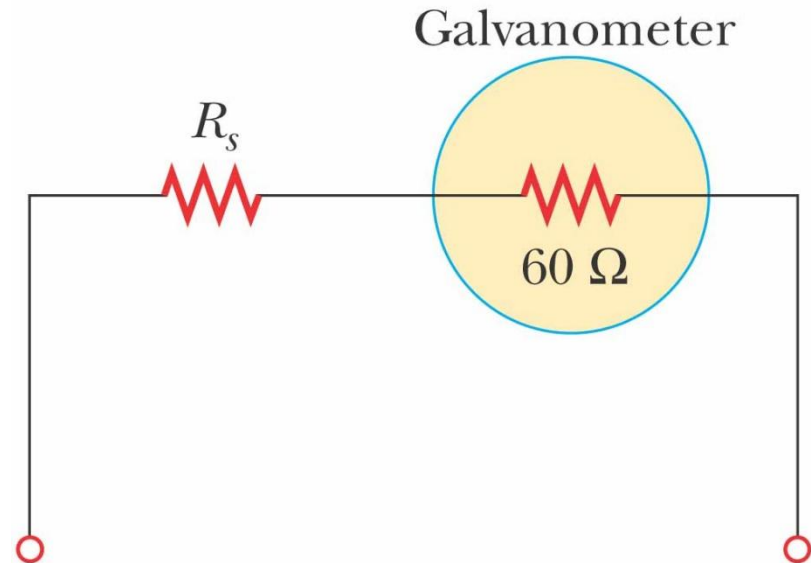- The galvanometer typically has a resistance of $60\ \Omega$
- To maximize the resistance, another resistor, R_s , is placed in series with the galvanometer





Voltmeter, final

- The value of the added resistor must be much greater than the resistance of the galvanometer
 - Remember, the equivalent resistance of resistors in series will be greater than the largest resistance
- Most of the current will go through the element being measured, and the galvanometer will not alter the voltage being measured




Household Wiring

- The utility company distributes electric power to individual homes by a pair of wires
- Each house is connected in parallel with these wires
- One wire is the “live wire” and the other wire is the neutral wire connected to ground

Household Wiring, cont

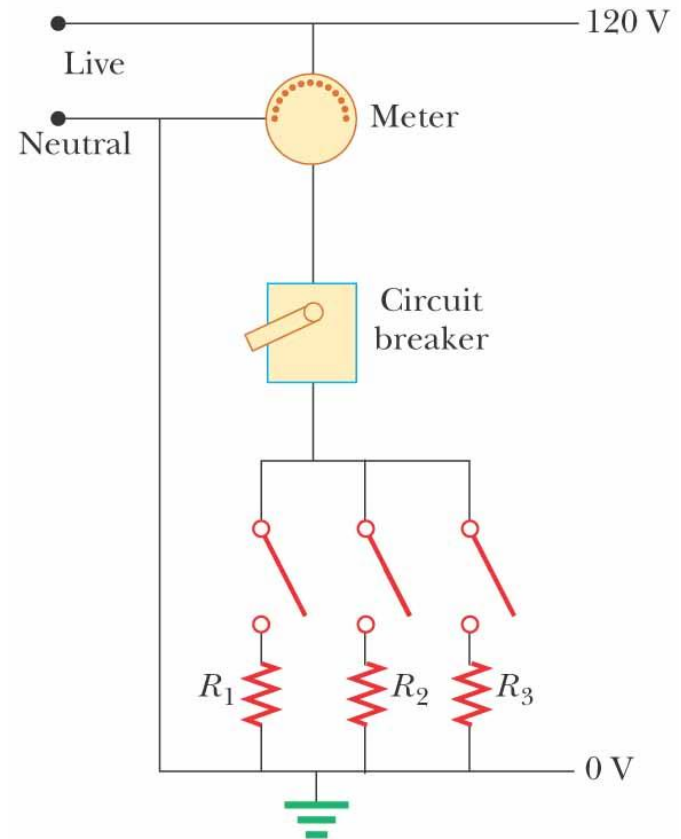- The potential of the neutral wire is taken to be zero
 - Actually, the current and voltage are alternating
- The potential difference between the live and neutral wires is about 120 V





Household Wiring, final

- A meter is connected in series with the live wire entering the house
 - This records the household's consumption of electricity
- After the meter, the wire splits so that multiple parallel circuits can be distributed throughout the house
- Each circuit has its own circuit breaker
- For those applications requiring 240 V, there is a third wire maintained at 120 V below the neutral wire



Short Circuit

- A *short circuit* occurs when almost zero resistance exists between two points at different potentials
- This results in a very large current
- In a household circuit, a circuit breaker will open the circuit in the case of an accidental short circuit
 - This prevents any damage
- A person in contact with ground can be electrocuted by touching the live wire



Electrical Safety

- Electric shock can result in fatal burns
- Electric shock can cause the muscles of vital organs (such as the heart) to malfunction
- The degree of damage depends on:
 - the magnitude of the current
 - the length of time it acts
 - the part of the body touching the live wire
 - the part of the body in which the current exists



Effects of Various Currents

- 5 mA or less
 - can cause a sensation of shock
 - generally little or no damage
- 10 mA
 - muscles contract
 - may be unable to let go of a live wire
- 100 mA
 - if passing through the body for 1 second or less, can be fatal
 - paralyzes the respiratory muscles




More Effects


- In some cases, currents of 1 A can produce serious burns
 - Sometimes these can be fatal burns
- No contact with live wires is considered safe whenever the voltage is greater than 24 V

Ground Wire

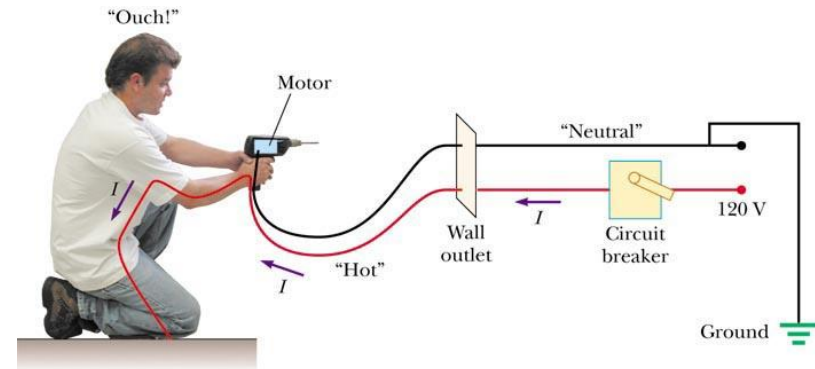- Electrical equipment manufacturers use electrical cords that have a third wire, called a ground
- This safety ground normally carries no current and is both grounded and connected to the appliance



(a)

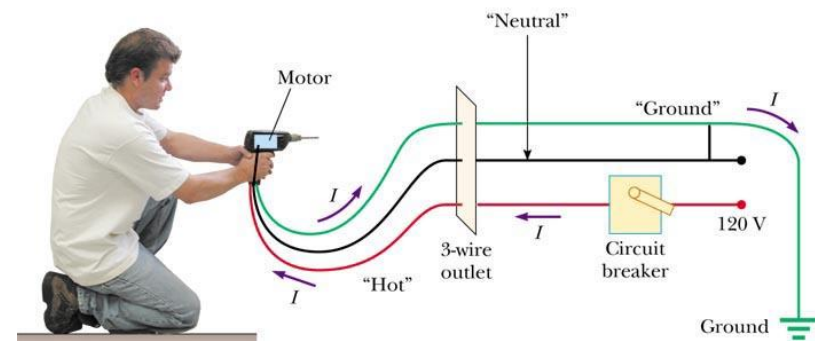

(b)



Ground Wire, cont

- If the live wire is accidentally shorted to the casing, most of the current takes the low-resistance path through the appliance to the ground
- If it was not properly grounded, anyone in contact with the appliance could be shocked because the body produces a low-resistance path to ground



Ground-Fault Interrupters (GFI)

- Special power outlets
- Used in hazardous areas
- Designed to protect people from electrical shock
- Senses currents (of about 5 mA or greater) leaking to ground
- Shuts off the current when above this level