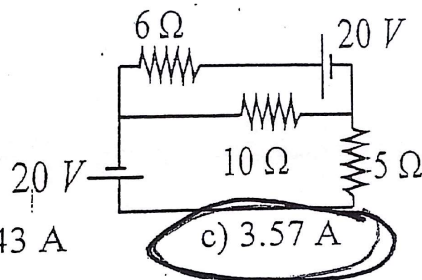


Q15. The electric current passing through $R = 6 \Omega$ equals:



a) 0.357 A

b) 0.143 A

c) 3.57 A


d) 1.43 A

e) 4.37 A

Q16. If the length of a conductor is doubled, then the resistivity is:

- a) Doubled b) Reduced to half c) Tripled **d) Does not change** e) All wrong

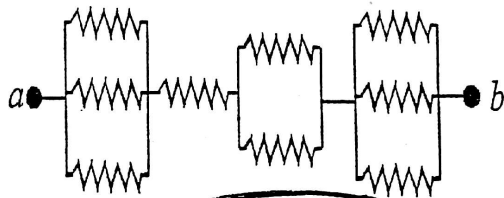Q17. If each resistor is $3\ \Omega$, the equivalent resistance between a and b is:



- a) $81\ \Omega$ b) $19.5\ \Omega$ **c) $6.5\ \Omega$** d) $27\ \Omega$ e) $65\ \Omega$

Q8. A cylindrical wire of length L and diameter D has a resistance of 8 ohms. A second wire made of the same material has length $2L$ and diameter $D/2$. The resistance of the second wire is:


- a) 1 ohm b) 2 ohms c) 8 ohms d) 32 ohms e) 64 ohms

Q9. A 0.900-V potential difference is maintained across a 1.50-m length of tungsten wire that has a radius of 4.37mm. If the resistivity of tungsten is $5.60 \times 10^{-8} \Omega \cdot m$ at $20^\circ C$. The current in the wire is:

- a) 6.43 A b) 7.52 A c) 2.33 A d) 1.42 A e) 7.95 A

Q10. Calculate the current in the following circuit

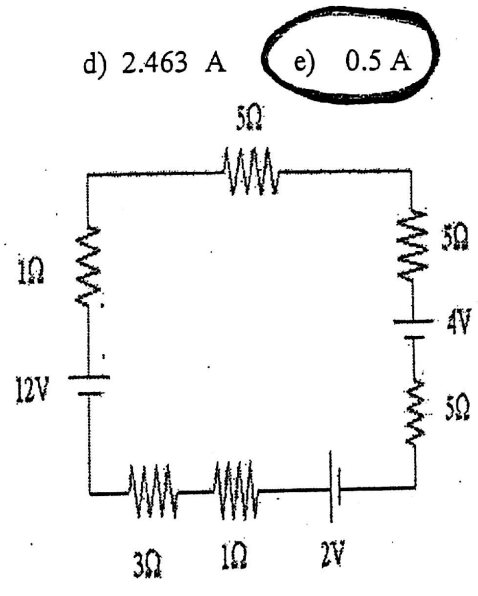- a) 0.436 A b) 0.625 A c) 1.125 A d) 2.463 A e) 0.5 A



Q13. The number of electrons flow through a battery that delivers a current of 3.0 A for 12s is

a) 4×10^{21}

b) 2.2×10^{20}

c) 4.8×10^{15}

d) 36×10^{21}

e) 9.4×10^{15}

Q14. In the circuit shown, the current I is


a) 0.2 A

b) 0.06 A

c) 0.1 A

d) 0.02 A.

e) 0.15 A

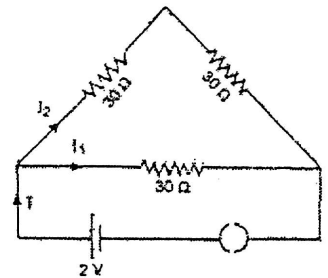

Q6. Determine the equivalent resistance for this circuit.


a) 50Ω

b) 12Ω

c) 29Ω

d) 120Ω

e) 5Ω

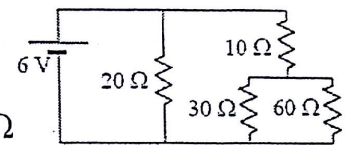

Q7. Determine the length of a copper wire that has a resistance of 0.172Ω and cross-sectional area of $1 \times 10^{-4} \text{ m}^2$. The resistivity of copper is $1.72 \times 10^{-8} \Omega \cdot \text{m}$.

a) 1000 m

b) 100 m

c) 10 000 m

d) 10 m

e) 0.1 m

Q8. Four $20\text{-}\Omega$ resistors are connected in series and the combination is connected to a 20-V emf device. The current in any one of the resistors is:

a) 100A






b) 1.0A

c) 4.0A

d) 5.0A

e) 0.25A

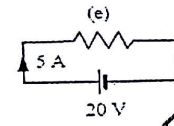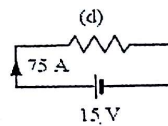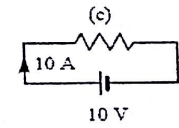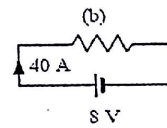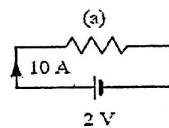Q9. Which one of the following circuits has the largest resistance



a) a

b) b

c) c

d) d

e) e

- Q12 A 4.0Ω resistor has a current of 3.0 A in it for 5.0 min . How many electrons pass through the resistor during this time interval?
- a) 7.5×10^{21} **b) 5.6×10^{21}** c) 6.6×10^{21} d) 8.4×10^{21} e) 2.1×10^{21}

- Q13 What is the magnitude of the potential difference across the 20Ω resistor?


a) 3.2 V

b) 7.8 V


c) 11 V

d) 5.0 V

e) 8.6

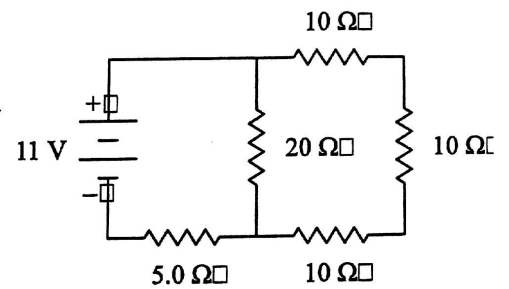

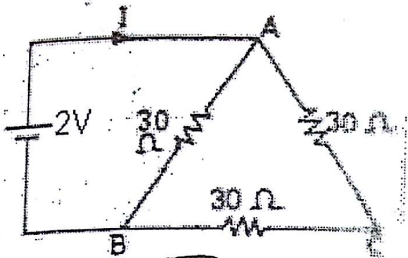Q14. In the circuit shown, the value of current I in (Amps) is:



a) 0.1

b) 0.2

c) 0.3

d) 1

e) 3

Q15. In the circuit shown, if $I_1 = 2.0$ A, $I_3 = 1.0$ A, the potential difference across the 4.0Ω resistor (V_{be}) in Volts is:

a) 6

b) 2

c) 14

d) 12

e) -2

Q16. A cylindrical wire has a radius r and length ℓ . If both r and ℓ are doubled, the resistance of the wire (R) will be:


a) $4R$

b) $R/2$

c) R

d) $2R$

e) $R/4$

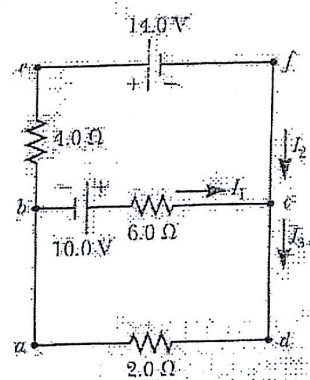

Q4. A copper wire has a resistance of $10\ \Omega$. A second copper wire is twice as long and has half the diameter. Its resistance is :

a) $80\ \Omega$

b) $8\ \Omega$

c) $32\ \Omega$

d) $1\ \Omega$

e) $15\ \Omega$

Q5. The current through the $4\ \Omega$ resistor of the adjacent circuit is:


a) $0.92\ \text{A}$

b) $3\ \text{A}$

c) $2\ \text{A}$

d) $6\ \text{A}$

e) $8\ \text{A}$

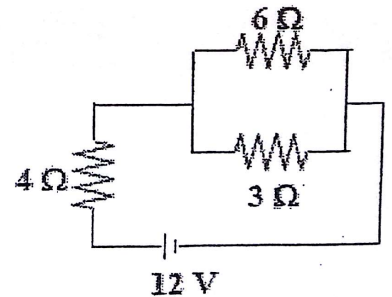

Q6. The equivalent resistance between points *a* and *b* in the figure is:

a) $18\ \Omega$

b) $15\ \Omega$

c) $19\ \Omega$

d) $7.6\ \Omega$

e) $13\ \Omega$

