

Tutorial EE201: Fundamentals Of Electric Circuits

Email: Yaltheyabi@ksu.edu.sa

Office number: ١/٢٠ ج٢

Tutorial 1: Voltage, Current, Resistance, Power and Energy





(a) $V = \frac{W}{Q}$

(b) $I = \frac{Q}{t}$

(c) $P = \frac{w}{t}$

(d) $R = \frac{V}{I}$

(e) $Life(h) = \frac{Ah}{A}$

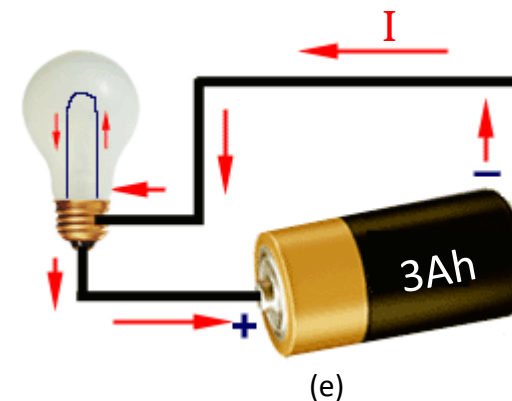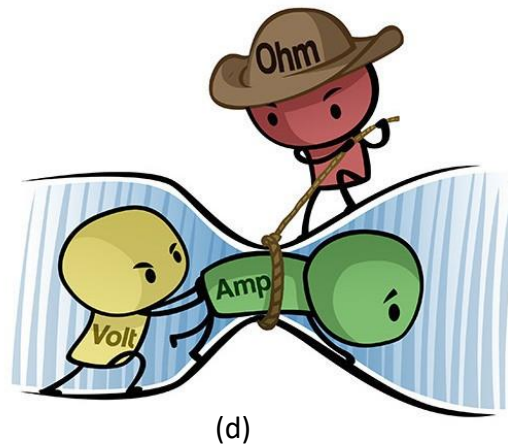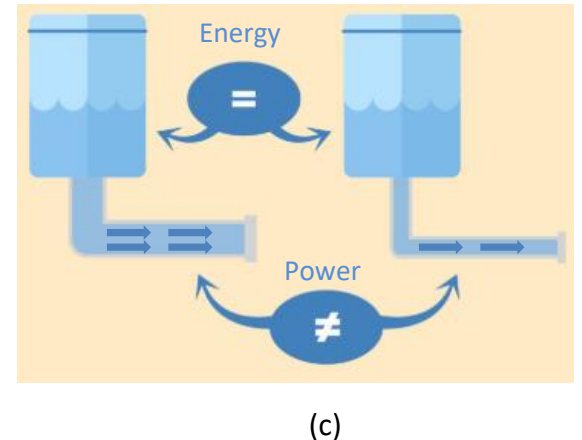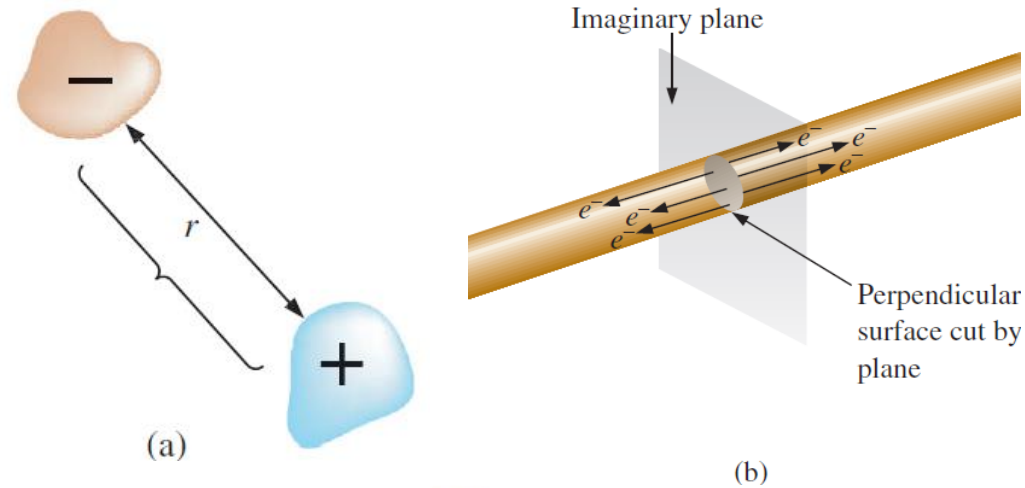

Problem 8, page 61

What is the voltage between two points if 1.2 J of energy are required to move 20 μC between the two points?

$$V = \frac{W}{Q} = \frac{1.2\text{J}}{20\mu\text{C}} = 60 \text{ kV}$$




60 kV, Set San Luis - Set Central - Set San Isidro Peru

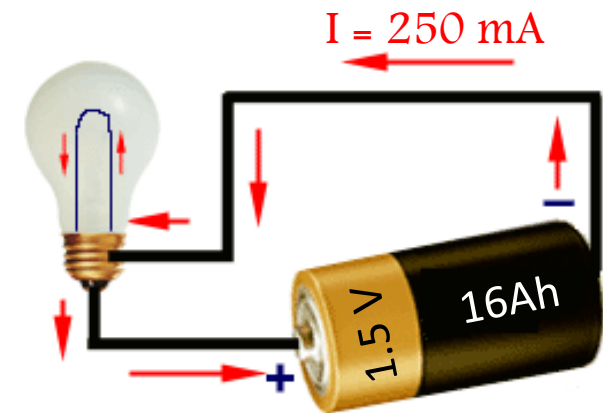Example 6, page 51

How long can a 1.5 V flashlight battery provide a current of 250 mA to light the bulb if the ampere-hour rating is 16 Ah?


$$Life(h) = \frac{Ah}{A} = \frac{16 Ah}{250 mA} = 64 \text{ hours}$$



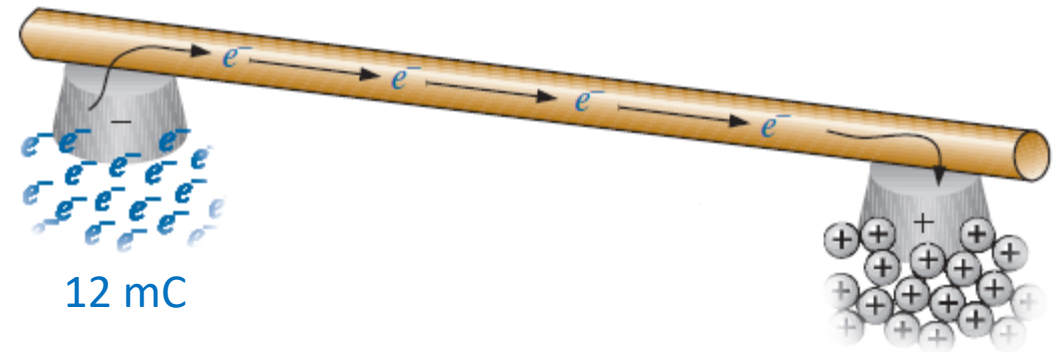Problem 13, page 61

Find the current in amperes if 12 mC of charge pass through a wire in 2.8 s.

$$I = \frac{Q}{t} = \frac{12 \text{ mC}}{2.8 \text{ s}} = 4.286 \text{ mA}$$



*Problem 14, page 61

if 312 C in 2 minutes ?


$$I = \frac{Q}{t} = \frac{312 \text{ C}}{2 \times 60 \text{ s}} = 2.6 \text{ A}$$

Problem 23, page 61

If a conductor with a current of 200 mA passing through it converts 40 J of electrical energy into heat in 30 s, what is the potential drop across the conductor?

$$V = \frac{W}{Q} \quad \Rightarrow \quad Q = I * t = 200 \text{ mA} * 30 \text{ s} = 6 \text{ C}$$
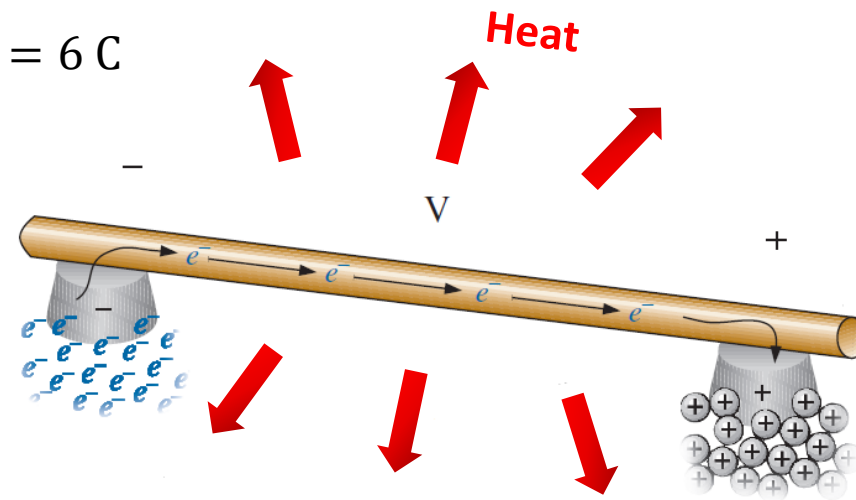
$$V = \frac{W}{Q} = \frac{40 \text{ J}}{6 \text{ C}} = 6.667 \text{ V}$$



Made up Problem


Find the current, power, energy observed over 6s, and battery rating to supply the load for 2h?

$$I = \frac{V}{R} = \frac{6-5}{2} = 0.5 \text{ A}$$

$$P = V * I = (6 - 5) * 0.5 = 0.5 \text{ Watt}$$

$$\text{Energy} = P * t = 0.5 * 6 = 3 \text{ J}$$

$$\text{Capacity} = \text{current} * \text{time} = 0.5 * 2 = 1 \text{ Ah}$$




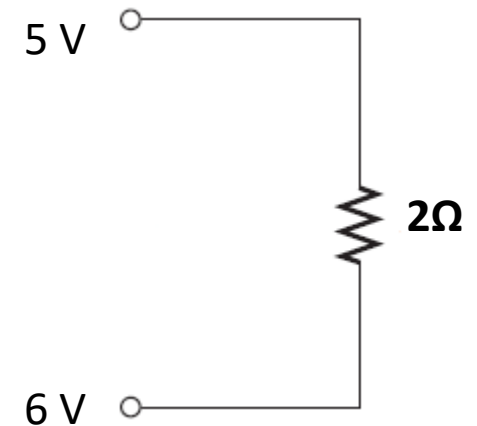


Tutorial 2: Series dc Circuits

(a) $R_T = \sum_1^{\infty} R_n$ series

(b) $\sum_{close-loop} V_{rises} = \sum_{close-loop} V_{drop}$


(c) $V_x = R_x \frac{E}{R_T}$

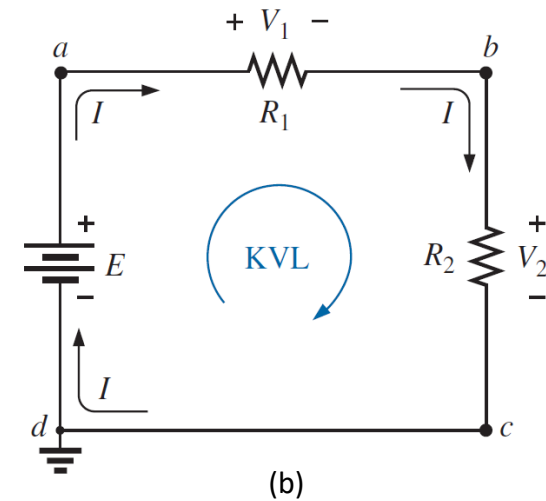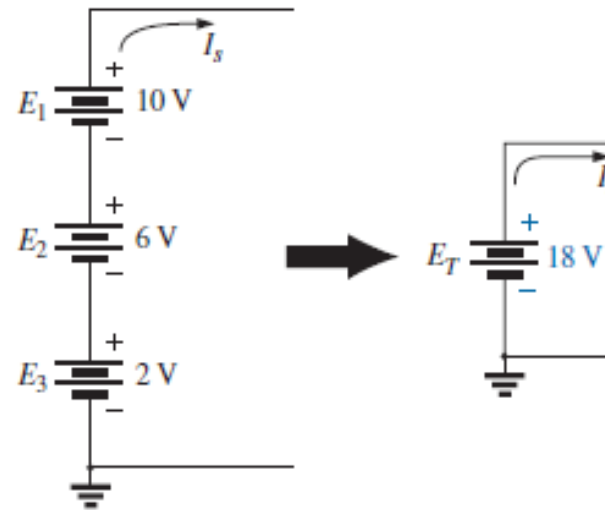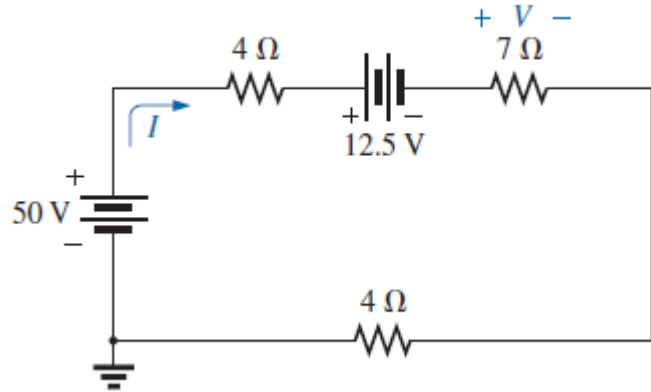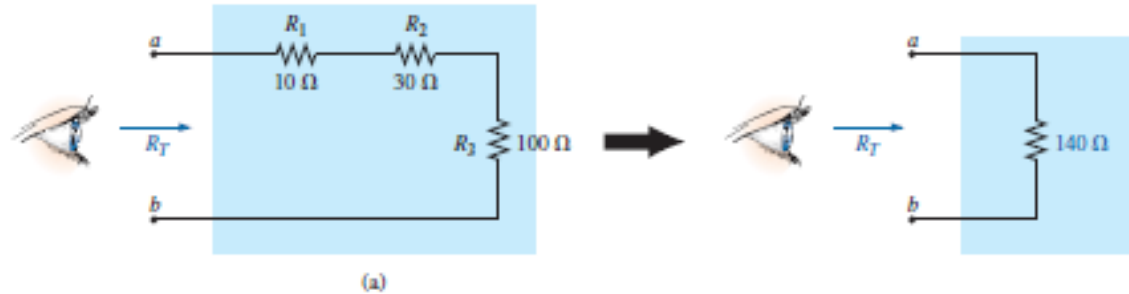

Example 12, page 152

Determine the voltage V_x for the circuit in shown. Note that the polarity of V_x was not provided.

$$\begin{aligned} -6\text{ V} - 14\text{ V} - V_x + 2\text{ V} &= 0 && \text{Assuming } a \text{ is positive} \\ V_x &= -18\text{ V} \end{aligned}$$

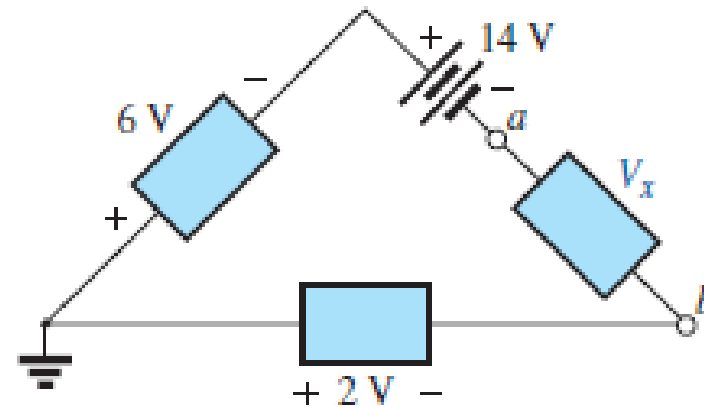

Example 3.5, page 141


Determine the total resistance, the source current, and all the voltage drops.

KVL

$$\begin{aligned} E - R_1 I - R_2 I - R_3 I &= 0 \\ 8.4 - 10xI - 30xI - 100xI &= 0 \\ I &= 60 \text{ mA} \end{aligned}$$

VDL
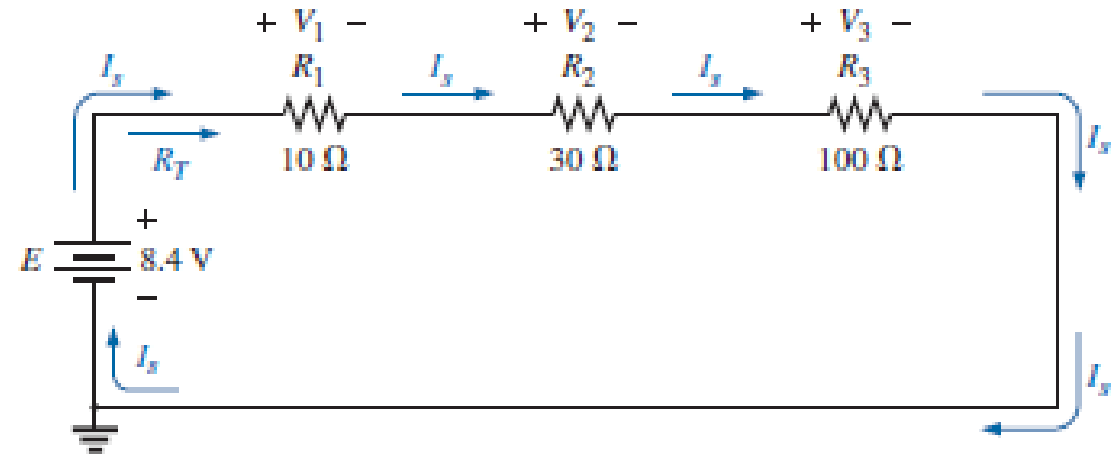
$$\begin{aligned} V_1 &= R_1 \frac{E}{R_T} = 10 * \frac{8.4}{10 + 30 + 100} = 0.6 \text{ V} \\ V_2 &= R_2 \frac{E}{R_T} = 30 * \frac{8.4}{10 + 30 + 100} = 1.8 \text{ V} \\ V_3 &= R_3 \frac{E}{R_T} = 100 * \frac{8.4}{10 + 30 + 100} = 6 \text{ V} \end{aligned}$$




$$E = V_1 + V_2 + V_3$$

$$E = 0.6 + 1.8 + 6 = 8.4$$

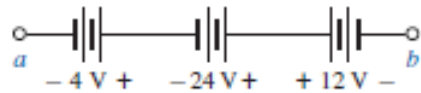
Example 18, page 182

Combine the series voltage sources into a single voltage source between points a and b find V_{ab} .




(a)

$$V_{ab} = -16\text{ V}$$

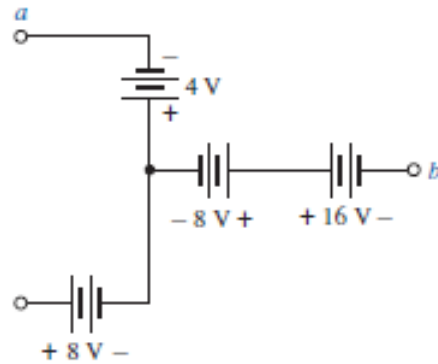

(b)

$$V_{ab} = 4\text{ V}$$

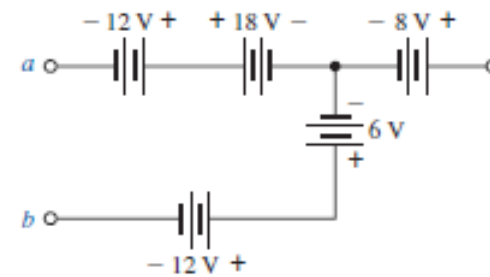

(c)

$$V_{ab} = 12\text{ V}$$




Tutorial 2: parallel dc Circuits

$$\frac{1}{R_T} = \sum_{n=1}^{\infty} \frac{1}{R_n} \quad \text{parallel}$$

$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

$$\sum I_{in} = \sum I_{out}$$

$$I_x = I_T \frac{R_T}{R_x}$$

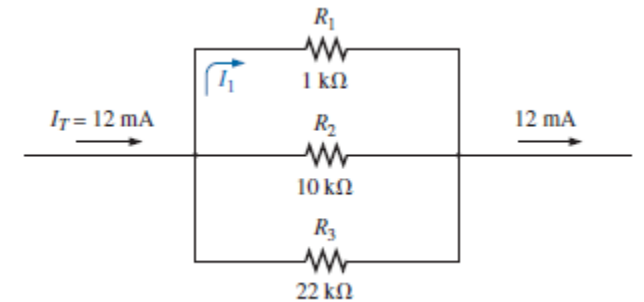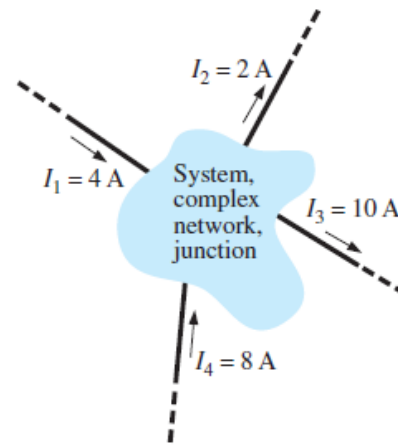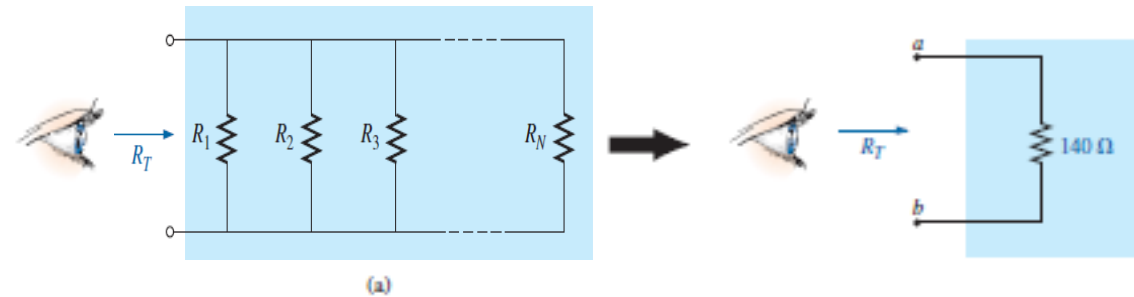

(b)

Example 15, page 207

For the parallel network, Determine the total resistance R_T , Find the source current and the current through each resistor, Calculate the power delivered by the source , and Determine the power absorbed by each parallel resistor.

$$\frac{1}{R_T} = \frac{1}{1.6k} + \frac{1}{20k} + \frac{1}{56k} \quad R_T = 1.4433 \text{ k}\Omega$$

$$I_s = \frac{E}{R_T} = \frac{28}{1.4433k} = 19.4 \text{ mA}$$


$$I_1 = (19.4 \text{ mA}) \frac{1.4433 \text{ k}}{1.6 \text{ k}} = 17.5 \text{ mA}$$

$$I_2 = 1.4 \text{ mA} \quad I_3 = 0.5 \text{ mA}$$

$$P_T = V * I_s = 28 * 19.4m = 543.2 \text{ mW}$$

$$P_1 = R_1 * I_1^2 = 1.6k * (17.4m)^2 = 490 \text{ mW}$$
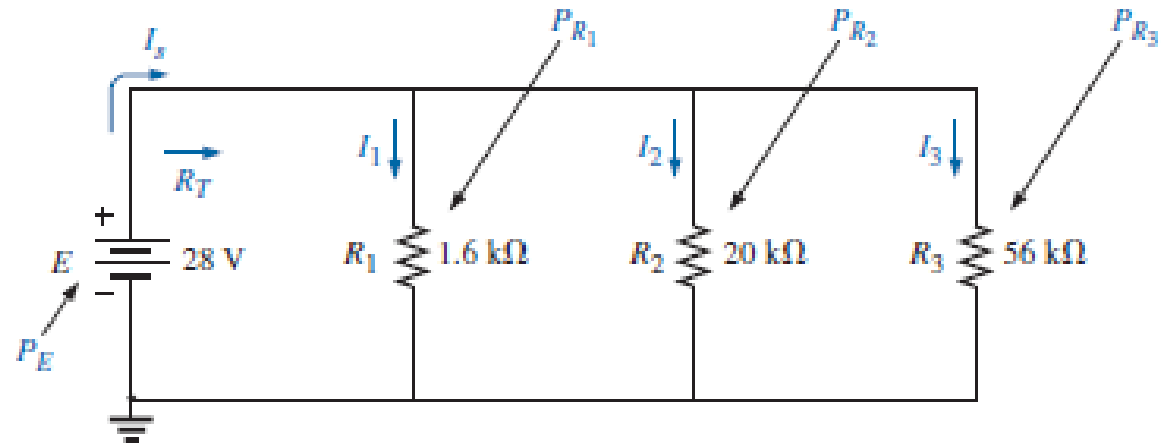
$$P_2 = 39.2 \text{ mW} \quad P_3 = 14 \text{ mW}$$



Example 18, page 216


Determine currents I_3 and I_5 through applications of Kirchhoff's current law.

$$I_1 + I_3 = I_3$$

$$I_3 = 4 + 3 = 7 \text{ A}$$

$$I_3 = I_4 + I_5$$
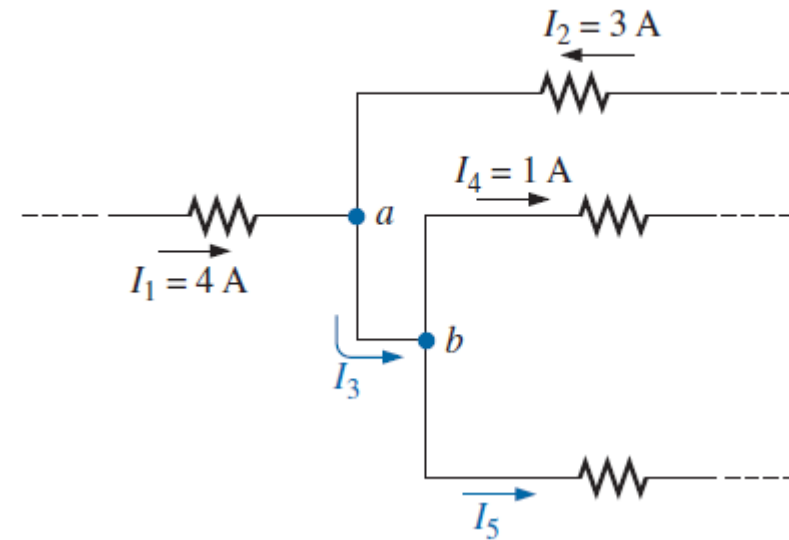
$$I_5 = I_3 - I_4 = 7 - 1 = 6 \text{ A}$$



Example 18, page 252


Determine All unknowns

$$\frac{1}{R'} = \frac{1}{18k} + \frac{1}{2k} \quad R' = 1.8 \text{ k}\Omega$$

$$I_s = \frac{12}{6.8k + 1.8k} + \frac{12}{8.2k} = 2.859 \text{ mA}$$

$$I_4 = \frac{12}{8.2k} = 1.463 \text{ mA}$$
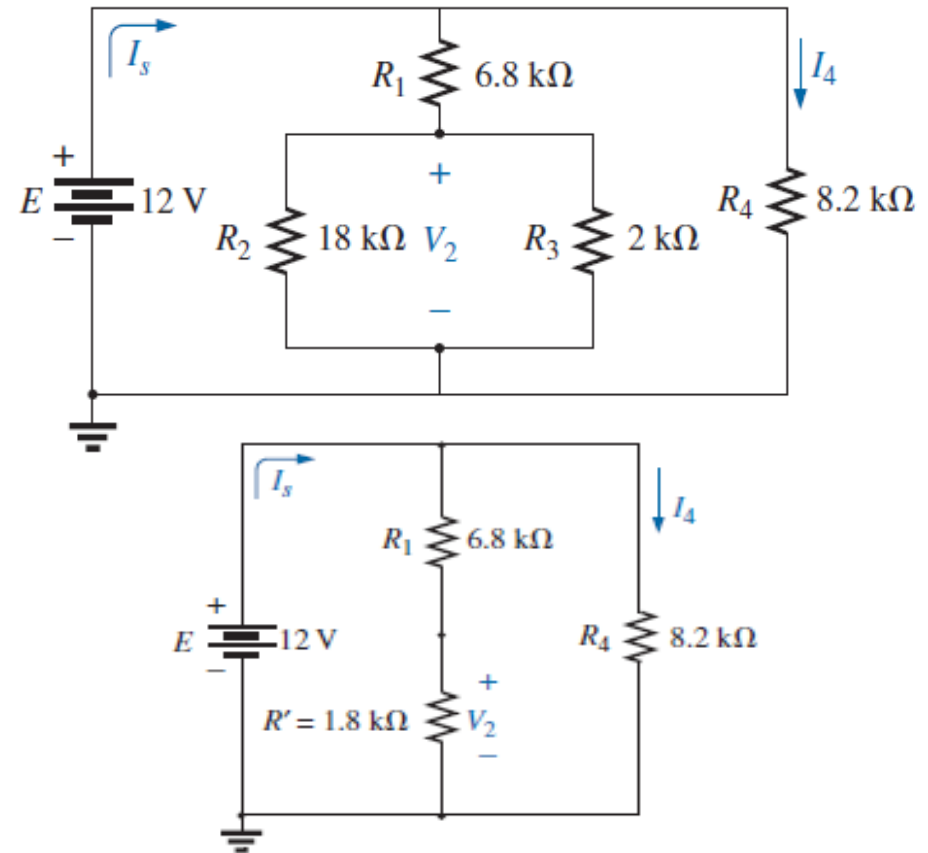
$$V_2 = \left(\frac{12}{6.8k + 1.8k} \right) * (1.8k) = 2.511 \text{ V}$$



Example 10, page 261

Calculate the indicated currents and voltage

$$R' = ((R_8 + R_9) || R_7) + R_6$$

$$R' = ((3k+6k) || 9k) + 12k = 16.5 \text{ k}\Omega$$

$$I' = \frac{E}{R'} = \frac{72}{16.5k} = 4.364 \text{ mA}$$

$$R'' = ((R_1 + R_2 + R_3) || R_4) + R_5$$



$$R'' = ((4k + 8k + 12k) || 24k) + 12k = 24k\Omega$$

$$I'' = \frac{E}{R''} = \frac{72}{24k} = 3 \text{ mA}$$

$$I_5 = I' + I'' \quad I_5 = 4.364 + 3 = 7.364 \text{ mA}$$

$$R_x = (R_8 + R_9) || R_7 = (3k+6k) || 9k = 4.5k \Omega$$
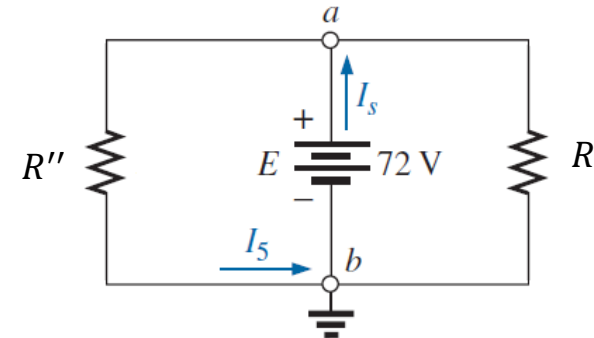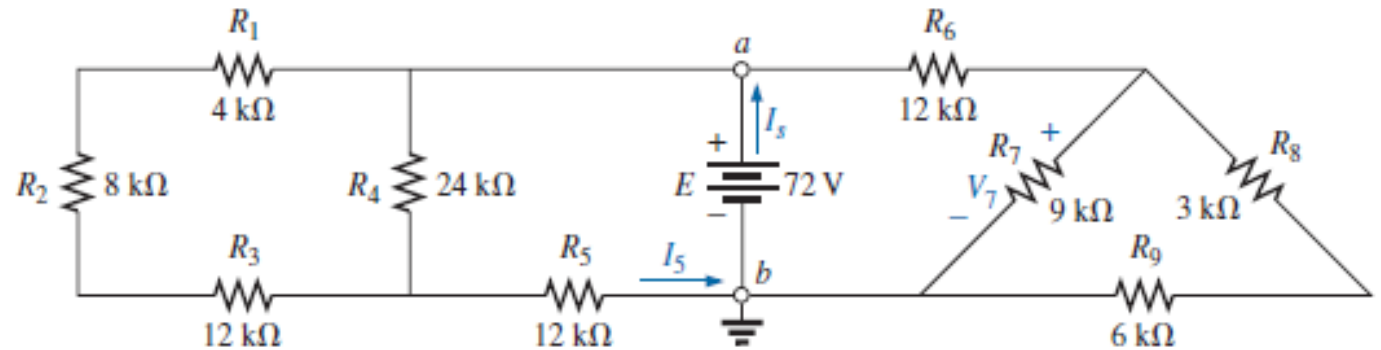
$$V_7 = R_x \times I' = 4.5k \times 4.364 \text{ mA} = 19.638 \text{ V}$$



$$I_5 = I''$$

Example 11, page 262

Determine all unknowns including V_{ac} , and V_{bc} .

$$V_a = E_1 = 20 \text{ V} \quad V_c = E_3 = 8 \text{ V}$$

$$V_b = E_1 - E_2 = 20 - 5 = 15 \text{ V}$$

$$V_{ac} = V_a - V_c = 20 - 8 = 12 \text{ V}$$

$$V_{bc} = V_b - V_c = 15 - 8 = 7 \text{ V}$$

$$I_2 = \frac{V_{bc}}{R_2} = \frac{7}{4} \text{ A} = 1.75 \text{ A}$$

$$I_{ac} = \frac{V_{ac}}{R_1} = \frac{12}{10} \text{ A} = 1.2 \text{ A}$$

$$I_2 + I_{ac} + I_{s3} = 0$$

$$1.75 + 1.2 + I_{s3} = 0 \quad I_{s3} = -2.95 \text{ A}$$

