

EE310

Solved Problems on BJT


Sedra/Smith 5th/6th ed.

By Turki Almadhi,

EE Dept., KSU,

Riyadh, Saudi Arabia

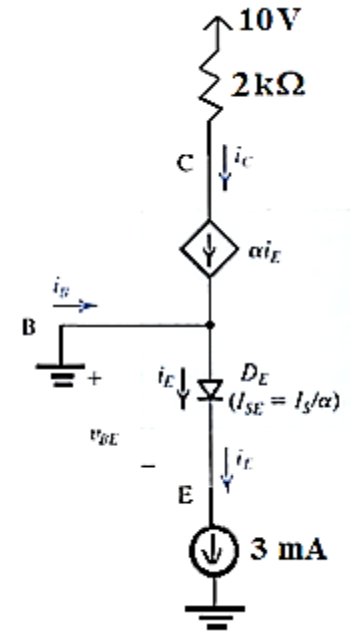5.12 Using the *npn* transistor model of Fig. 5.5(b), consider the case of a transistor for which the base is connected to ground, the collector is connected to a 10-V dc source through a 2-k Ω resistor, and a 3-mA current source is connected to the emitter with the polarity so that current is drawn out of the emitter terminal. If $\beta = 100$ and $I_S = 10^{-15}$ A, find the voltages at the emitter and the collector and calculate the base current.



$$I_E = 3 \text{ mA}; I_{SE} = \frac{1}{\alpha} I_S = \frac{\beta+1}{\beta} I_S = 1.01 I_S$$

$$I_E = I_{SE} e^{\frac{V_{BE}}{V_T}} \rightarrow V_{BE} = V_T \times \ln\left(\frac{I_E}{I_{SE}}\right) = 0.747 \text{ V}$$


$$\therefore V_{BE} = V_B - V_E \rightarrow 0.747 = 0 - V_E \rightarrow V_E = -0.747 \text{ V}$$

$$I_C = \alpha I_E = \frac{\beta}{\beta+1} I_E = 0.9901 \times 3 = 2.9703 \text{ mA}$$

$$V_C = 10 - 2.9703 \times 2 = 4.0594 \text{ V (which verifies active mode)}$$

$$I_B = I_E - I_C = 3 - 2.9703 = 29.7 \times 10^{-3} \text{ mA} = 29.7 \mu\text{A}$$

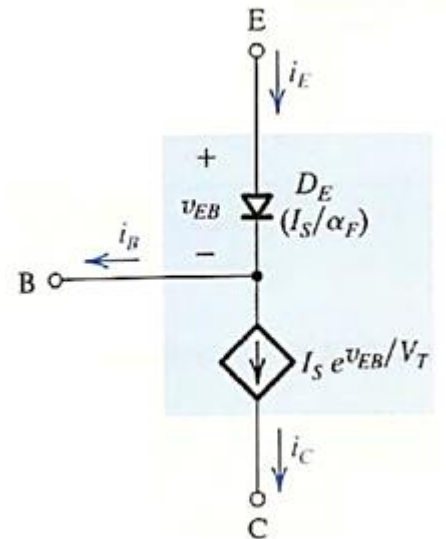5.19 A *pnp* power transistor operates with an emitter-to-collector voltage of 5 V, an emitter current of 10 A, and $V_{EB} = 0.85$ V. For $\beta = 15$, what base current is required? What is I_S for this transistor? Compare the emitter-base junction area of this transistor with that of a small-signal transistor that conducts $i_C = 1$ mA with $v_{EB} = 0.70$ V. How much larger is it?



$\therefore V_{EC} = 5$, that means the pnp transistor is operating in the active mode.

$$\text{Given that } I_{E1} = 10 \text{ A} \rightarrow I_{B1} = \frac{10}{\beta+1} = \frac{10}{16} = 0.625 \text{ A}$$

$$I_{C1} = \beta I_{B1} = 15 \times \frac{10}{16} = 9.375 \text{ A};$$

$$I_{C1} = I_{S1} e^{\frac{V_{BE}}{V_T}} \rightarrow I_{S1} = I_{C1} e^{\frac{-V_{BE}}{V_T}} \rightarrow I_{S1} = 9.375 \times e^{\frac{-0.85}{26 \times 10^{-3}}} = 59.4 \times 10^{-15} \text{ A}$$

$$\frac{A_{EBJ1}}{A_{EBJ2}} = \frac{59.4 \times 10^{-15} \text{ A}}{I_{S2} = I_{C2} e^{\frac{-V_{BE}}{V_T}}} = \frac{59.4 \times 10^{-15}}{2.03 \times 10^{-15}} = 29.3$$

The power BJT has an emitter-base junction area 29.3 times larger than the small signal BJT.

6.28 For the circuits in Fig. P6.28, assume that the transistors have very large β . Some measurements have been made on these circuits, with the results indicated in the figure. Find the values of the other labeled voltages and currents.


a)

$$I_1 = I_E = \frac{10.7 - 0.7}{10} = 1 \text{ mA}$$

$\therefore \beta$ is very large, we can assume I_B is 0 \rightarrow

$$I_C = I_E = 1 \text{ mA}$$
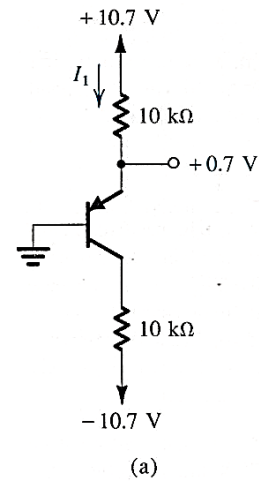
$$V_2 = 10 \times 1 + (-10.7) = -0.7 \text{ V}.$$



d)


Equating the collector and emitter currents:

$$I_C = I_E$$

$$\frac{10 - V_6}{15} = \frac{(V_6 - 0.7) - (-10)}{5} \rightarrow 10 - V_6 = 3V_6 + 27.9 \rightarrow$$

$$4V_6 = -17.9 \rightarrow V_6 = -4.475 \text{ V}.$$
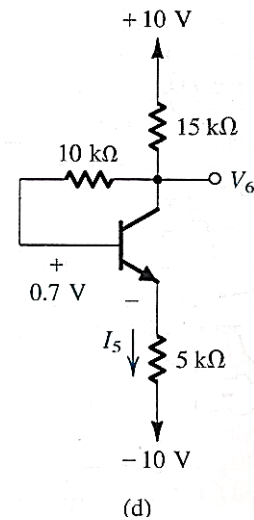
$$I_C = \frac{10 - (-4.475)}{15} = 0.965 \text{ mA} = I_E = I_5$$



6.29 Measurements on the circuits of Fig. P6.29 produce labeled voltages as indicated. Find the value of β for each transistor.

To be able to find β , we must find two of the three currents:

I_B , I_C , and I_E .


$$I_E = \frac{10 - 7}{1} = 3 \text{ mA}.$$

The current flowing into the lower 1-k Ω resistor is exactly equal to I_E ; why?


$$V_C = 3 \times 1 = 3 \text{ V} \rightarrow I_B = \frac{6.3 - 3}{100} = 0.033 \text{ mA}$$

(I_B is flowing out of the base for a pnp transistor.)
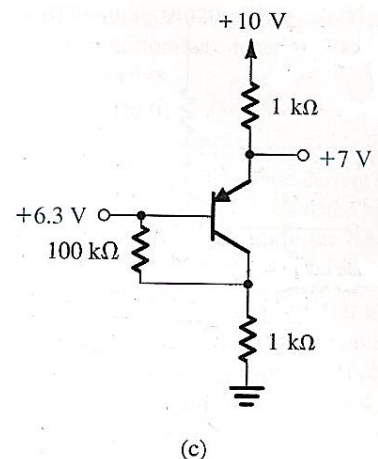
$$I_E = (\beta + 1)I_B \rightarrow \beta = \frac{I_E}{I_B} - 1 \approx 90.$$



6.35 For each of the circuits shown in Fig. P6.35, find the emitter, base, and collector voltages and currents. Use $\beta = 50$, but assume $|V_{BE}| = 0.8 \text{ V}$ independent of current level.

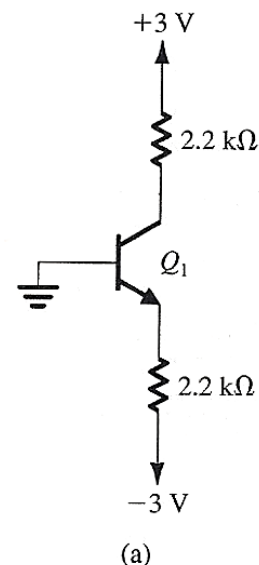

Assuming the transistor is in active mode:

$$V_E = -0.8 \rightarrow I_E = \frac{-0.8 - (-3)}{2.2} = \frac{2.2}{2.2} = 1 \text{ mA}$$

$$I_B = \frac{I_E}{\beta + 1} = \frac{1}{51} = 19.61 \times 10^{-3} \text{ mA}$$

$$I_C = \beta I_B = 50 \times 19.61 \times 10^{-3} = 0.980 \text{ mA}$$

$$V_B = 0$$

$$V_C = 3 - 2.2 \times 0.980 = 0.844 \text{ V.}$$

$$V_{BC} = 0 - (0.844) = -0.844 \leq 0.4 \rightarrow \text{the CBJ is}$$

reverse-biased \rightarrow the transistor is in active mode as assumed!

5.26 For the circuit shown in Fig. P5.26, measurement indicates that $V_B = -1.5 \text{ V}$. Assuming $V_{BE} = 0.7 \text{ V}$, calculate V_E , α , β , and V_C . If a transistor with $\beta = \infty$ is used, what values of V_B , V_E , and V_C result?

(i) Note: the negative value of V_B indicates that the base current is going (into) the base which is the right direction for an npn BJT.

$$I_B = \frac{0 - (-1.5)}{10} = 0.15 \text{ mA}$$

(current is in mA because the resistance is in kΩ.)

$$V_E = V_B - 0.7 = -1.5 - 0.7 = -2.2 \text{ V}$$

$$I_E = \frac{V_E - (-9)}{10} = \frac{-2.2 + 9}{10} = \frac{6.8}{10} = 0.68 \text{ mA}$$


$$I_C = I_E - I_B = 0.68 - 0.15 = 0.53 \text{ mA}$$

$$V_C = 9 - 0.53 \times 10 = 3.7 \text{ V} \rightarrow V_{BC} = -1.5 - 3.7 = -5.2 \text{ V} \leq 0.4 \text{ V,}$$

which means the transistor is operating in the active mode.

$$\beta = \frac{I_C}{I_B} = \frac{0.53}{0.15} = 3.5333 \rightarrow \alpha = \frac{\beta}{\beta + 1} = \frac{3.5333}{4.5333} = 0.7794 = \frac{I_C}{I_E}$$
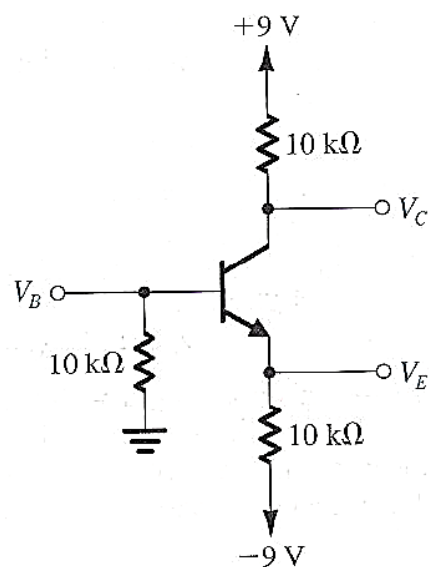
$$(ii) I_B = 0 \rightarrow V_B = 0 \rightarrow V_E = -0.7 \text{ V} \rightarrow V_C = 0.7 \text{ V}$$



5.78 For the circuit in Fig. P5.78, find V_B , V_E , and V_C for $R_B = 100\text{ k}\Omega$, $10\text{ k}\Omega$, and $1\text{ k}\Omega$. Let $\beta = 100$.

(i) $R_B = 100\text{ k}\Omega$

Assuming the transistor is in active mode:

$$(\beta + 1)I_B = I_E$$

$$101 \times \frac{5 - (0.7 + V_E)}{100} = \frac{V_E}{1} \rightarrow 4.3 - V_E = \frac{100}{101} V_E$$

$$\rightarrow V_E = 2.16\text{ V} \rightarrow I_E = \frac{2.16}{1} = 2.16\text{ mA}$$

$$V_B = V_E + 0.7 = 2.16 + 0.7 = 2.86\text{ V}$$

$$V_C = 5 - 1 \times I_C = 5 - \left(\frac{100}{101}\right) \times I_E = 2.86\text{ V}$$

$$V_{BC} = V_B - V_C = 0 \leq 0.4\text{ V} \rightarrow \text{the BJT is in active mode as assumed.}$$

(ii) $R_B = 10\text{ k}\Omega$

Assuming the transistor is in active mode:

$$(\beta + 1)I_B = I_E$$

$$101 \times \frac{5 - (0.7 + V_E)}{10} = \frac{V_E}{1} \rightarrow 4.3 - V_E = \frac{10}{101} V_E$$

$$\rightarrow V_E = 3.91\text{ V} \rightarrow I_E = \frac{3.91}{1} = 3.91\text{ mA}$$

$$V_B = V_E + 0.7 = 3.91 + 0.7 = 4.61\text{ V}$$

$$V_C = 5 - 1 \times I_C = 5 - \left(\frac{100}{101}\right) \times I_E = 1.13\text{ V}$$

$$V_{BC} = V_B - V_C = 3.48\text{ V} > 0.4\text{ V} \rightarrow \text{the BJT is saturated.}$$

Restarting, and considering $V_{CE(sat)} = 0.2\text{ V}$:


$$I_E = I_C + I_B$$

$$\frac{V_E}{1} = \frac{5 - V_C}{1} + \frac{5 - V_B}{10}$$

$$\frac{V_E}{1} = \frac{5 - (0.2 + V_E)}{1} + \frac{5 - (0.7 + V_E)}{10}$$

$$V_E = 4.8 - V_E + 0.43 - 0.1V_E \rightarrow 2.1V_E = 5.23 \rightarrow V_E = 2.49\text{ V.}$$
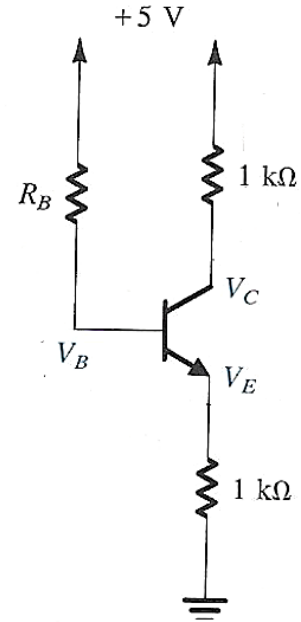
$$V_C = 0.2 + V_E = 2.69\text{ V}; \quad V_B = 0.7 + V_E = 3.19\text{ V.}$$



D5.65 For the circuit in Fig. P5.65 select a value for R_B so that the transistor saturates with an overdrive factor of 10. The BJT is specified to have a minimum β of 20 and $V_{CEsat} = 0.2$ V. What is the value of forced β achieved?

Useful relationships:

$$I_{B(\text{EdgeOfSaturation})} = I_{B(\text{EOS})} = \frac{I_{C(\text{sat})}}{\beta_{\min}}; \beta_{\text{forced}} = \frac{I_{C(\text{sat})}}{I_B};$$

$$\text{Over Drive Factor (ODF)} \triangleq \frac{I_B}{I_{B(\text{EOS})}}$$

$$I_{C(\text{sat})} = \frac{5 - 0.2}{1} = 4.8 \text{ mA}$$

$$I_{B(\text{EOS})} = \frac{I_{C(\text{sat})}}{\beta_{\min}} = \frac{4.8}{20} = 0.24 \text{ mA} \rightarrow I_B = I_{B(\text{EOS})} \times \text{ODF} = 2.4 \text{ mA}$$

$$I_B = \frac{5 - 0.7}{R_B} \rightarrow R_B = \frac{4.3}{2.4} = 1.792 \text{ k}\Omega$$

$$\beta_{\text{forced}} = \frac{I_{C(\text{sat})}}{I_B} = \frac{4.8 \text{ mA}}{2.4 \text{ mA}} = 2;$$

Note that β_{forced} is only defined in saturation and it changes with I_B and always is less than β_{\min} .

5.130 For the common-emitter amplifier shown in Fig. P5.130, let $V_{CC} = 9$ V, $R_1 = 27$ k Ω , $R_2 = 15$ k Ω , $R_E = 1.2$ k Ω , and $R_C = 2.2$ k Ω . The transistor has $\beta = 100$ and $V_A = 100$ V.

Calculate the dc bias current I_E . If the amplifier operates between a source for which $R_{\text{sig}} = 10$ k Ω and a load of 2 k Ω , replace the transistor with its hybrid- π model, and find the values of R_{in} , the voltage gain v_o/v_{sig} , and the current gain i_o/i_i .

We first draw the DC equivalent circuit (all caps are open-circuited), then we find Thevenin's equivalent looking out of the base.




$$R_{th} = R_1 \parallel R_2 = 27 \text{ k}\Omega \parallel 15 \text{ k}\Omega = \frac{27 \times 15}{27 + 15} = 9.64 \text{ k}\Omega$$

$$V_{th} = \frac{R_2}{R_1 + R_2} \times V_{CC} = \frac{15}{27 + 15} \times 9 = 3.21 \text{ V}$$

Assuming the transistor is in active mode:

$$(\beta + 1)I_B = I_E$$
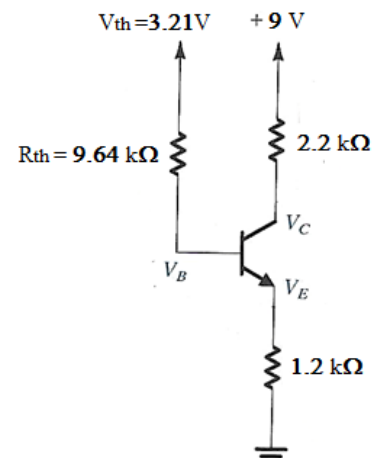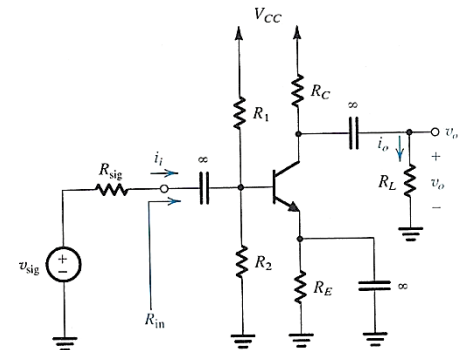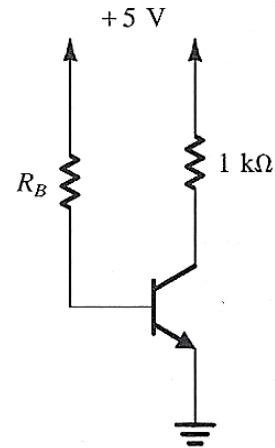
$$101 \times \frac{3.21 - (0.7 + V_E)}{9.64} = \frac{V_E}{1.2} \rightarrow 2.51 - V_E = 0.0796 V_E$$



DC equivalent circuit

$$\rightarrow V_E = 2.325 \text{ V} \rightarrow I_E = \frac{2.325}{1.2} = 1.9375 \text{ mA};$$

$$I_C = \left(\frac{100}{101}\right) \times I_E = 1.918 \text{ mA}$$

$$V_B = V_E + 0.7 = 2.325 + 0.7 = 3.025 \text{ V}$$

$$V_C = 9 - 2.2 \times I_C; = 9 - 2.2 \times 1.918 = 4.78 \text{ V}$$

$$V_{BC} = V_B - V_C = 3.025 - 4.78 = -1.755 \text{ V} \leq 0.4 \text{ V}$$

→ the BJT is in active mode as assumed.

$$g_m = \frac{I_C}{V_T} = \frac{1.918}{26} = 73.8 \text{ mS};$$

$$r_\pi = \frac{V_T}{I_B} = \beta \frac{V_T}{I_C} = \frac{\beta}{g_m} = \frac{100}{73.8} \times 10^3 = 1.355 \text{ k}\Omega$$


$$R_{in} = R_1 \parallel R_2 \parallel r_\pi = R_{th} \parallel r_\pi = 9.64 \parallel 1.355 = 1.18 \text{ k}\Omega$$

$$\frac{v_{be}}{v_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}} = \frac{1.19}{1.19 + 10} = 0.106$$

$$v_o = -g_m v_{be} \times (R_C \parallel R_L) = -77.3 v_{be} \rightarrow \frac{v_o}{v_{be}} = -77.3$$

$$A_v = \frac{v_o}{v_{sig}} = \frac{v_o}{v_{be}} \times \frac{v_{be}}{v_{sig}} = 0.106 \times (-77.3) = -8.2 \text{ V/V}$$
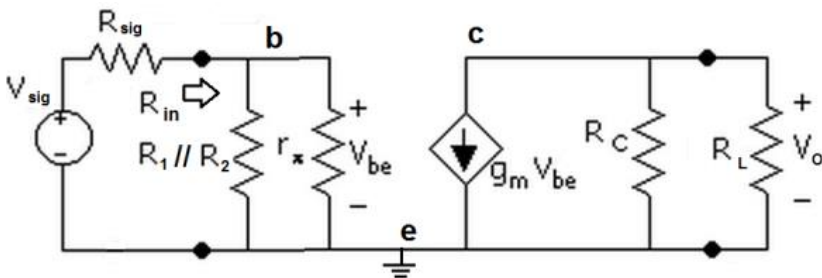
$$\frac{v_o}{v_{be}} = \frac{i_o \times R_L}{i_i \times R_{in}} = -77.3 \rightarrow \frac{i_o}{i_i} = \frac{R_{in}}{R_L} \times \frac{v_o}{v_{be}} = -45.6 \text{ A/A}$$



Small signal equivalent circuit