

## EE 310

### Practice Problem 2

A diode  $D$  with  $n = 1$  and  $I_s = 1 \times 10^{-15} \text{ A}$  at room temperature ( $T = 300 \text{ K}$ ) is connected in series with a dc voltage source  $V_{DD}$  and a resistance  $R = 1 \text{ k}\Omega$  in such a way to make  $D$  forward biased. Using the iterative method, estimate  $V_D$  down to the mV as well as  $I_D$  if :

- 1)  $V_{DD} = 1.5 \text{ V}$       (Ans.:  $V_D = 0.712 \text{ V}$ ,  $I_D = 0.788 \text{ mA}$ )
- 2)  $V_{DD} = 3 \text{ V}$       (Ans.:  $V_D = 0.740 \text{ V}$ ,  $I_D = 2.26 \text{ mA}$ )
- 3)  $V_{DD} = 0.75 \text{ V}$       (Ans.:  $V_D = 0.657 \text{ V}$ ,  $I_D = 0.093 \text{ mA}$ )