

**Mobile Phones and Programmable Calculators Are Not Allowed**


الرقم:

الاسم:

**Question 1 A:**

For the circuit shown in **Fig.1**,


- (a) Find the open-circuit voltage  $V_{ab}$
- (b) The Thevenin resistance ( $R_{TH}$ ) between terminals  $a$  and  $b$

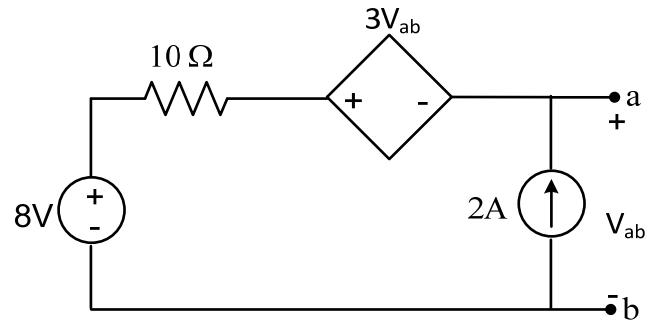

**Fig.1**

**Question 1 B:**


In the circuit shown in **Fig.2**, find  $V_1$  and  $V_2$ .

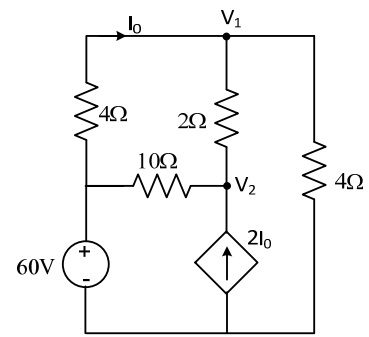

**Fig.2**

**Question 2 A:**

For the ideal op-amp circuit shown in **Fig.3**, find  $V_0$  and  $i_0$

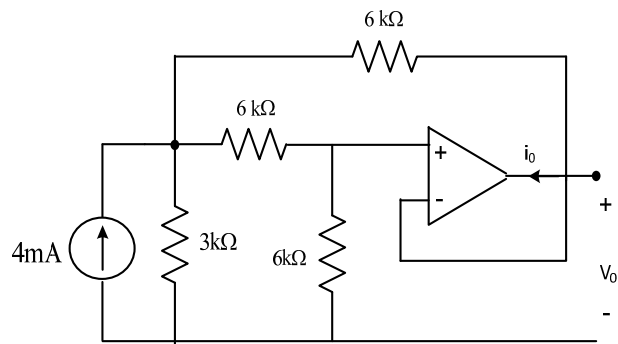


**Fig.3**

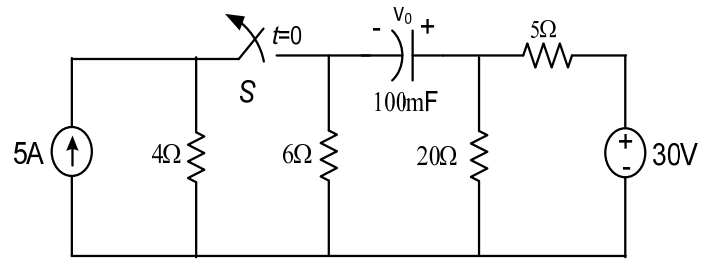**Question 2 B:**

In the circuit shown in **Fig. 4**, the switch  $S$  has been closed for a long time. It is opened at time  $t = 0$ . Determine

- a)  $V_o(0^+)$
- b)  $V_o(\infty)$
- c) Expression for  $V_o(t)$  for  $t > 0$ .
- d) Sketch  $V_o(t)$  for  $t > 0$ .




**Question 3 A:**

In the circuit shown in **Fig. 5**, the Switch has been in position “a” for a long time. It is moved to position “b” at time  $t = 0$ .

Determine


- a)  $V_C(0^+)$
- b)  $I(0^+)$
- c)  $V_L(0^+)$
- d) Expression for  $i(t)$  for  $t > 0$ .

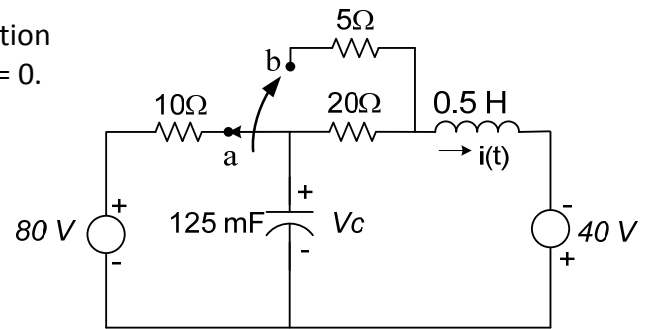

**Fig. 5**

**Question 3 B:**

For the circuit shown in **Fig. 6**, find the h-parameters such that  $V_1 = h_{11}I_1 + h_{12}V_2$  &  $I_2 = h_{21}I_1 + h_{22}V_2$ .

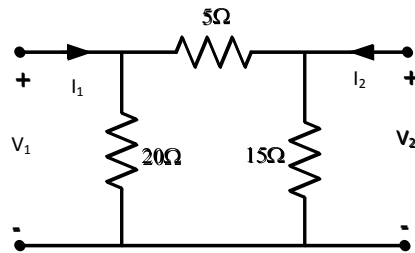


**Fig. 6**

**Question 4 A:**

The Y-parameters of a 2-port circuit are given in **Fig. 7**.

Find  $V_1$  and  $V_2$

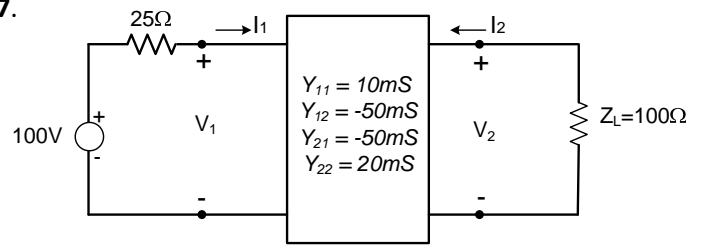


**Fig. 7**

**Question 4B:**

In the circuit shown in **Fig. 8**,

- (a) Find the coefficient of coupling.
- (b) Find  $I_1$  and  $I_2$

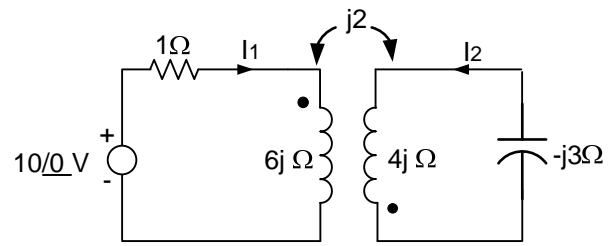


**Fig. 8**



**Question 5A:**

For the circuit shown in **Fig. 9** the input is current source  $I_0$  and the output is the voltage across the 2- $\Omega$  resistor.

- (a) Find the transfer function  $H(s) = \frac{V_0(s)}{I_0(s)}$
- (b) Find the poles and zeroes of  $H(s)$

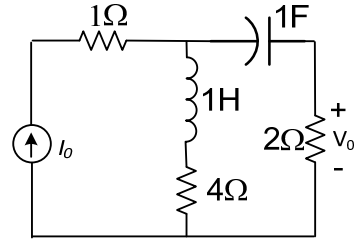

**Fig. 9**

**Question 5 B:**

For the circuit shown in **Fig. 10**, show that, for certain values of  $R$ ,  $L$ , and  $C$ , the transfer

function can be written as  $H(s) = \frac{V_2(s)}{V_1(s)} = \frac{2s}{s^2 + 2s + 1600}$

- a) If  $R = 1 \text{ k}\Omega$ , find  $L$  and  $C$ .
- b) What is the resonant frequency ( $\omega_0$ ) of the circuit?
- c) What type of filter does this circuit represent?
- d) What is the bandwidth of this filter?

