

2nd Semester 1436/1437 (2015/2016)
Date of Exam: 24th May, 2016



Department of Electrical Engg.
College of Engineering
King Saud University

EE 212: Electric Circuits Analysis

Final Examination

Time allowed: 3 Hours

Instructors: Prof. Nazar H. Malik, Prof. Saad M. Alghuwainum. & Dr. Yasin Khan

Student Name:

Student No.:

Section No.:

Final Exam. Mark (40):

Term Work Mark (60):

Total (100):

Grade:

Course Learning Objectives:

CLO-A: An ability to apply knowledge of mathematics, science, and engineering [5]

[CLO-A = 40% each question]

CLO-C: Ability to design a system, component, or process to meet desired needs within realistic constraints such as economic, environmental, social, political, ethical, health and safety, manufacturability, and sustainability [2] **[CLO-C = 20% each question]**

CLO-E: Ability to identify, formulate, and solve engineering problems [5] **[CLO-E = 40% each]**

Questions	Full Mark	Marks obtained
1	20	
2	20	
3	20	
4	20	
5	20	
Total	100	

Answer all questions

Question #1 (a)

Use nodal analysis to determine V_1 and power being supplied by the dependent current source in the circuit shown in **Fig. 1(a)**.

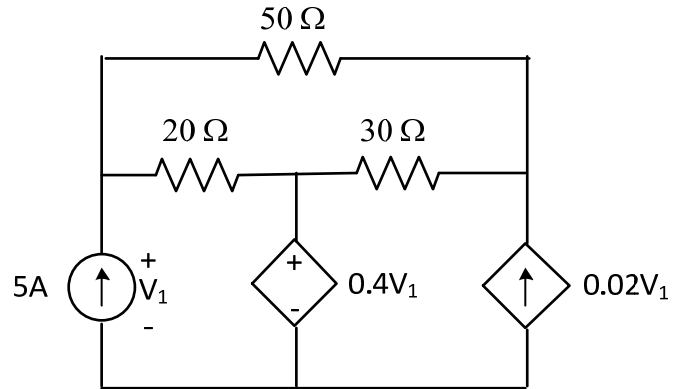


Fig.1(a)

Question #1 (b)

For the circuit shown in **Fig.1(b)**, the switch S is closed for a long time. It is opened at $t=0$. Find $i(t)$ for $t \geq 0$.


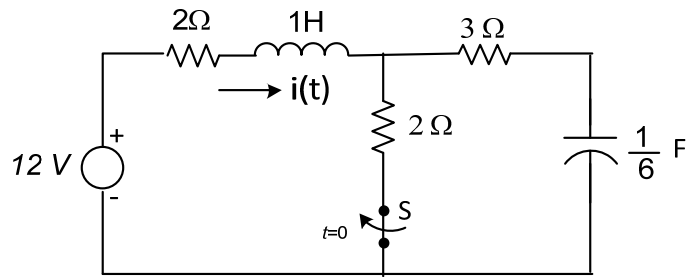


Fig.1(b)

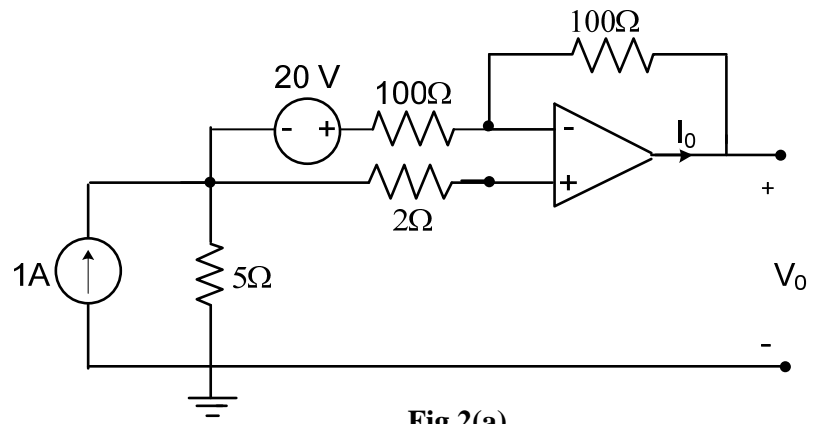Question #2 (a)

For the circuit shown in **Fig. 2 (a)**, find V_o and I_o .



Question #2 (b)

For the circuit shown in **Fig. 2 (b)**, find V_o and I_o

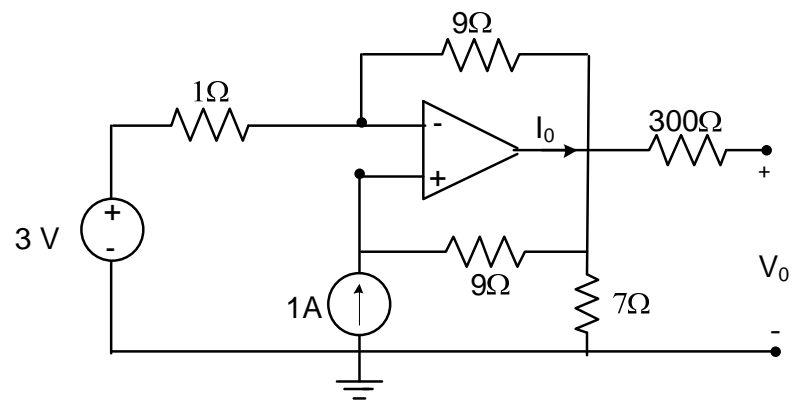


Fig.2(b)

Question #3 (a)

For the circuit shown in **Fig. 3(a)**, the switch S has been opened for very long time. It is closed at time $t=0$. Find $i(t)$ for $t \geq 0$ and sketch $i(t)$ versus t .

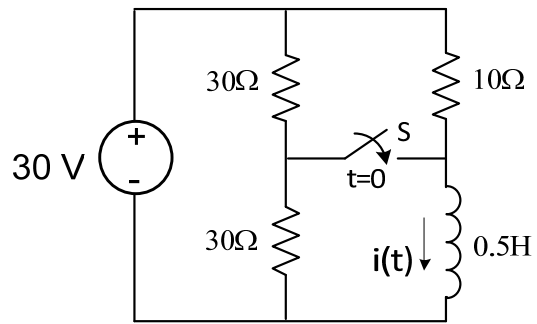


Fig.3(a)

Question #3(b)

For the circuit shown in **Fig. 3(b)**, the switch S has been opened for very long time. It is closed at time $t=0$. Find $v(t)$ for $t \geq 0$

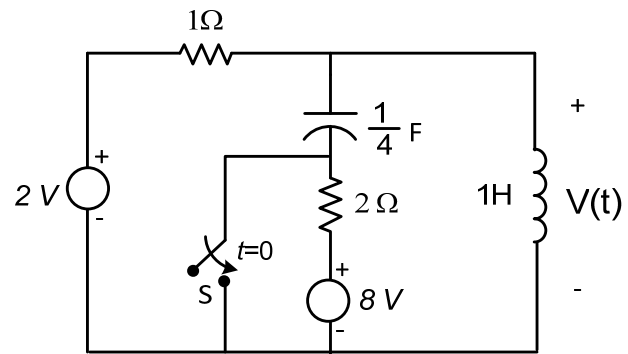


Fig.3(b)

Question #4 (a)

For the circuit shown in **Fig. 4(a)**, calculate the following:

- (i) $V_1(t)$ (ii) $V_2(t)$

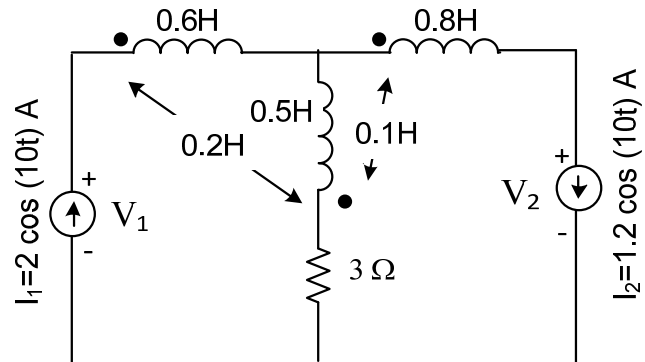


Fig.4(a)

Question #4(b)


(a) For the circuit shown in **Fig. 4(b)**, the quality factor $Q=3$, calculate

(i) L (ii) ω_0 (iii) β

(iv) ω_1 and ω_2

(b) What type of filter is this, if output is taken:

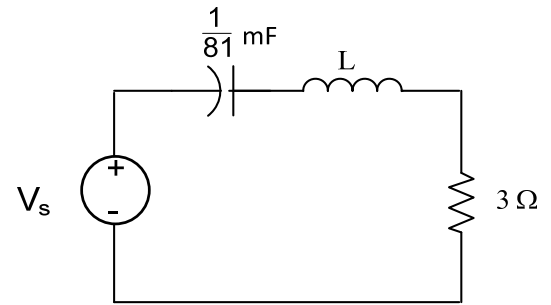(v) across R , (vi) across L , (vii) across C



$Q=3$

Fig.4(b)

Question #5(a)

For the circuit shown in **Fig. 5(a)**, calculate the following:

- (i) Transfer function $H(s) = \frac{I_o(s)}{I_s(s)}$
- (ii) Poles and zeros of $H(s)$
- (iii) What type of filter does this circuit represent?
- (iv) If $H(j\omega)$ is written as: $H(j\omega) = \frac{k}{(1 + j\frac{\omega}{a})(1 + j\frac{\omega}{b})}$ find k , a and b .

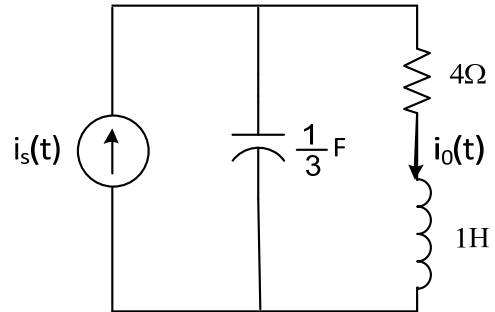


Fig.5(a)

Question #5(b)

- (a) For the circuit shown in **Fig. 5(b)**, use the given Z-parameters to determine V_2 .
(b) Find an equivalent T-circuit for the two-port network which will have the given Z-parameters.

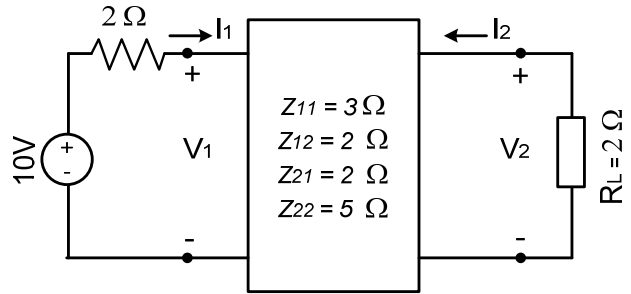


Fig.5(b)