

Student Name:

ID #

Question 1A:

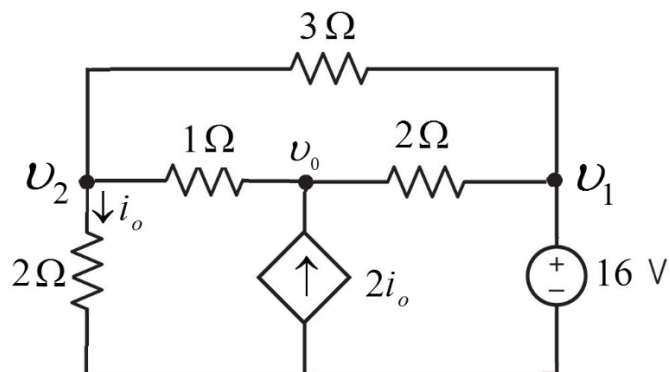


Fig. 1

Find v_0 and i_o in the circuit of Fig. 1, using node method.

Question 1B:

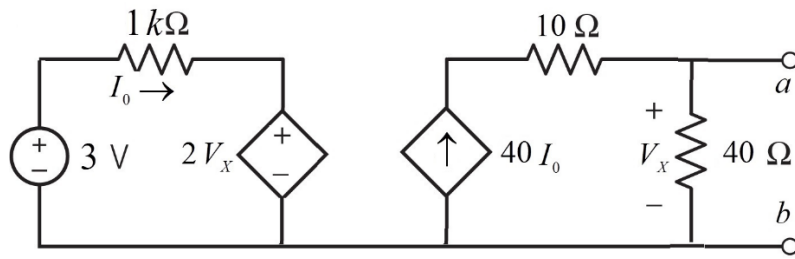


Fig. 2

Find the Thevenin equivalent circuit between terminals a-b of the circuit of Fig. 2.

Question 2A:

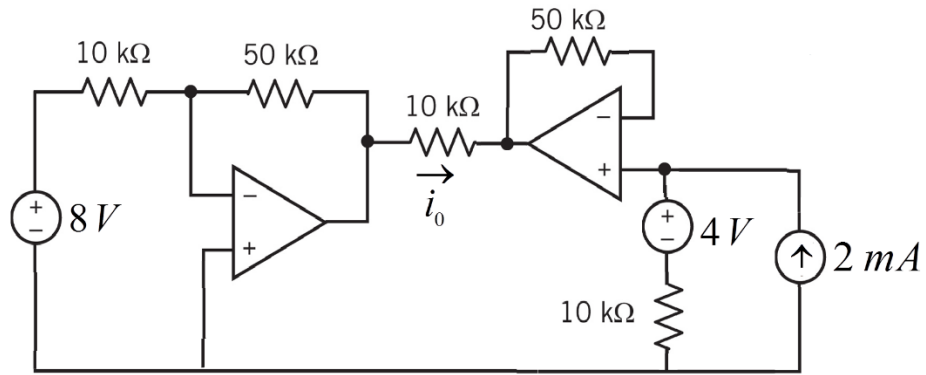


Fig.3

Find i_0 in the op amp circuit of Fig. 3.

Question 2B:

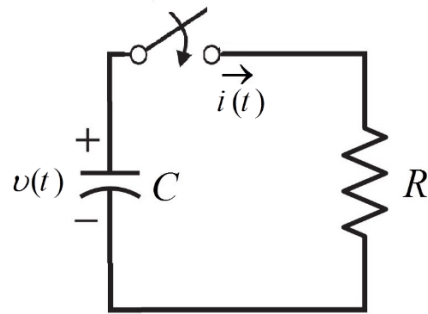


Fig.4

For the circuit of Fig. 4, if

$$v(t) = 10 e^{-4t} \text{ V} \quad \text{and} \quad i(t) = 0.2 e^{-4t} \text{ A} \quad t > 0$$

- i) Find R and C .
- ii) Calculate the initial energy in the capacitor.

Question 3A:

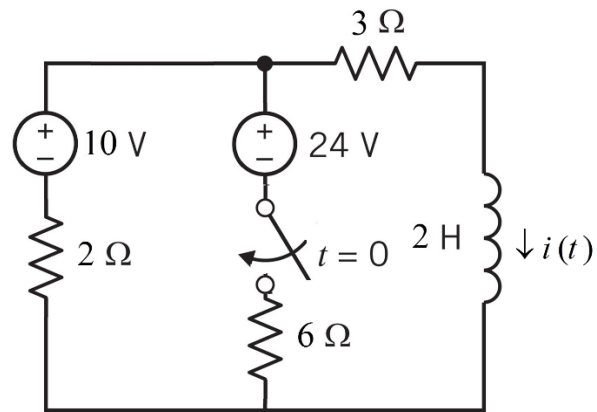


Fig. 5

In the circuit of Fig. 5

- i) Find the inductor current $i(t)$ for $t > 0$.
- ii) Sketch $i(t)$.

Question 3B:

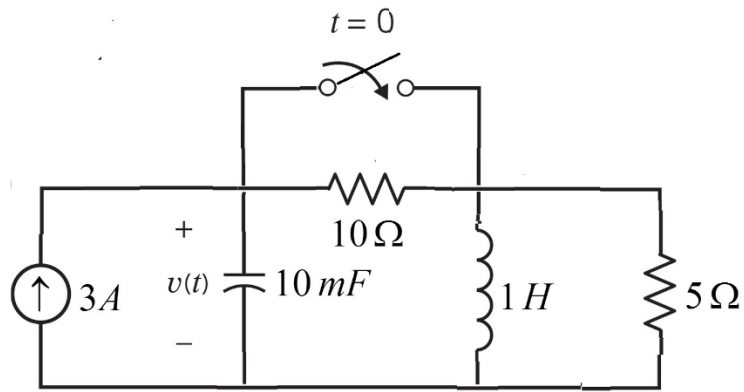


Fig. 6

Find the voltage across the capacitor $v(t)$ for $t > 0$ in the circuit of Fig. 6.

Question 4A:

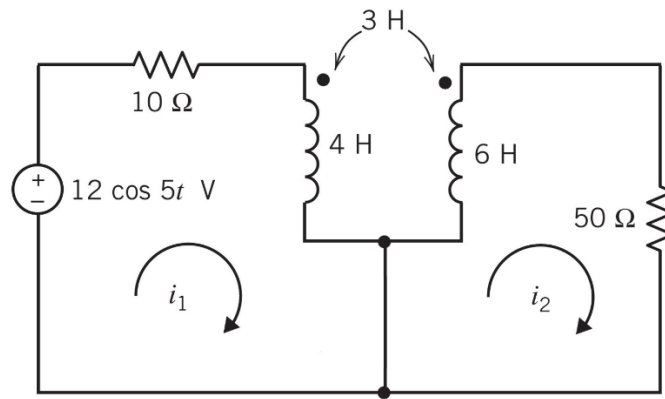


Fig.7

Find i_1 and i_2 in the circuit of Fig. 7.

Question 4B:

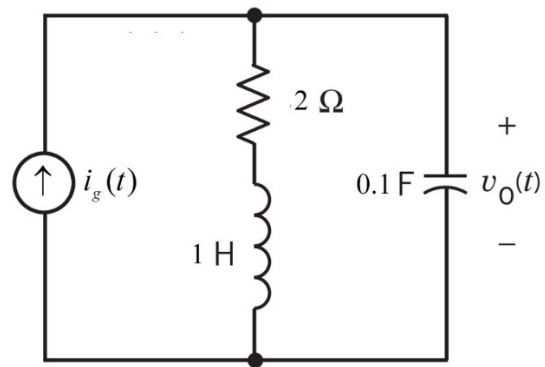


Fig. 8

For the circuit in Fig. 8,

- i) Find the transfer function $H(s) = \frac{V_o(s)}{I_g(s)}$
- ii) Determine poles and zeros of $H(s)$

Question 5A:

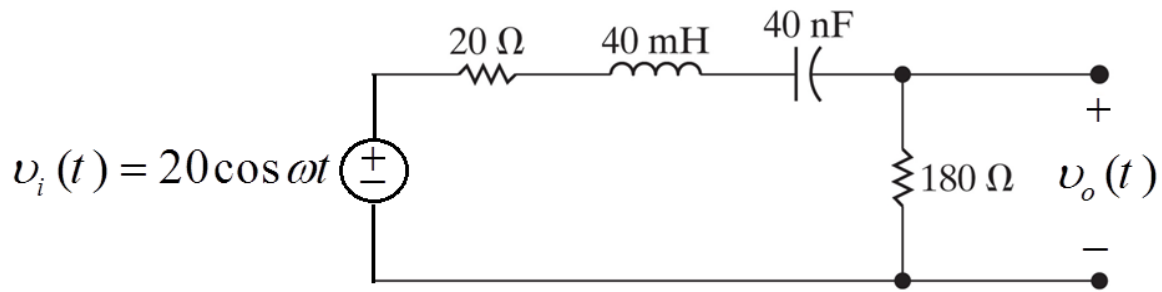


Fig. 9

For the resonant circuit in Fig. 9,

- Calculate ω_0 , Q , ω_{c1} , ω_{c2} , and β .
- If ω of the source is equal to ω_0 of the circuit, determine $v_o(t)$.
- If ω of the source is equal to ω_{c1} of the circuit, determine $v_o(t)$.
- If ω of the source is equal to ω_{c2} of the circuit, determine $v_o(t)$.

Question 5B:

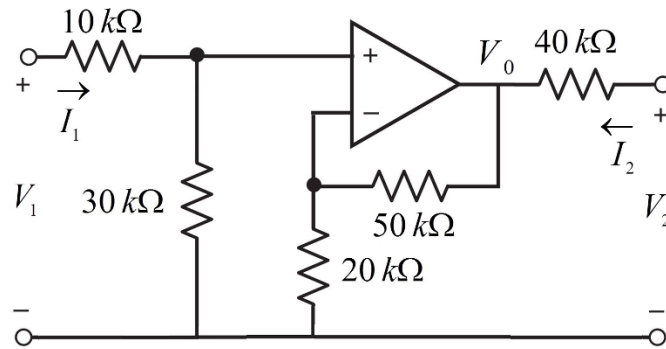


Fig. 10

For the op amp circuit in Fig.,

- i) Find V_0 in terms of I_1
- ii) If $V_1 = Z_{11}I_1 + Z_{12}I_2$ and $V_2 = Z_{21}I_1 + Z_{22}I_2$
Determine the Z parameters Z_{11}, Z_{12}, Z_{21} , and Z_{22} .