
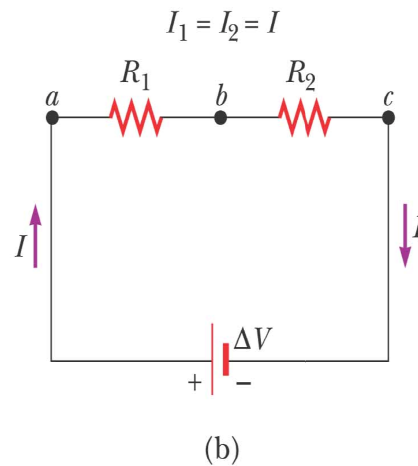


28.2 resistors in series and parallel:

▪ Combining resistors in series:

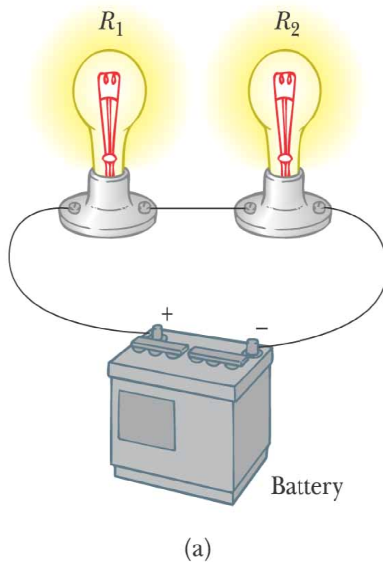

©2004 Thomson - Brooks/Cole

©2004 Thomson - Brooks/Cole

When two or more resistors are connected together as are the light- bulbs in the figure, they are said to be in *series*.

In a series connection, all the charges moving through one resistor must also pass through the second resistor.

For a series combination of resistors, the current in the two resistors are the same because any charge passes through R_1 must also pass through R_2 . As a result,

$$I=I_1=I_2 \quad (28.4)$$

However, the voltage differences at each resistor is different,

$$\nabla V = \nabla V_1 + \nabla V_2 \quad (28.5)$$

To find the equivalent resistance, one can do the following:


$$\nabla V = \nabla V_1 + \nabla V_2 = I_1 R_1 + I_2 R_2 \quad (28.6)$$

However,

$$I=I_1=I_2$$

So, $\nabla V = I(R_1 + R_2)$

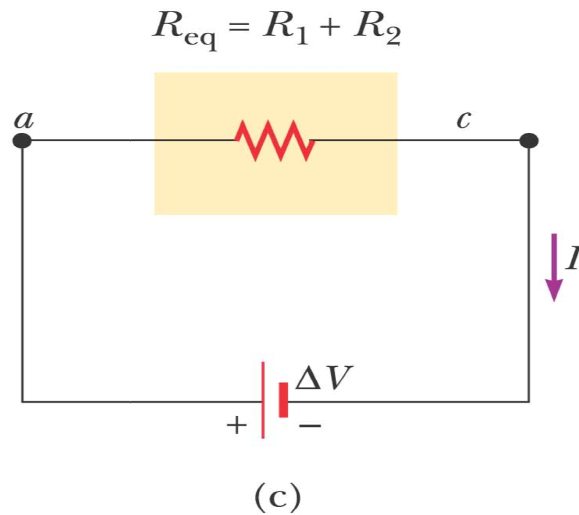Then, $IR_{eq} = I(R_1 + R_2)$
 $R_{eq} = R_1 + R_2$ (28.7)




©2004 Thomson - Brooks/Cole


This relationship indicates that the equivalent resistance of a series connection of resistors is always greater than any individual resistance.

- **Combining resistors in parallel:**

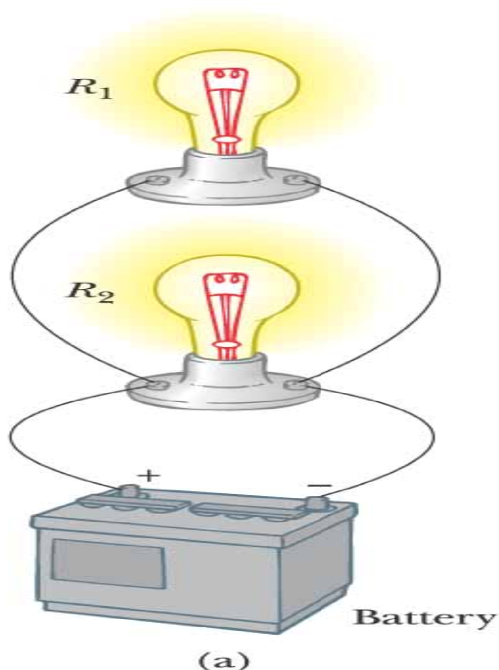On the otherwise, one can combine the resistors in parallel as shown in the figure below.



©2004 Thomson - Brooks/Cole

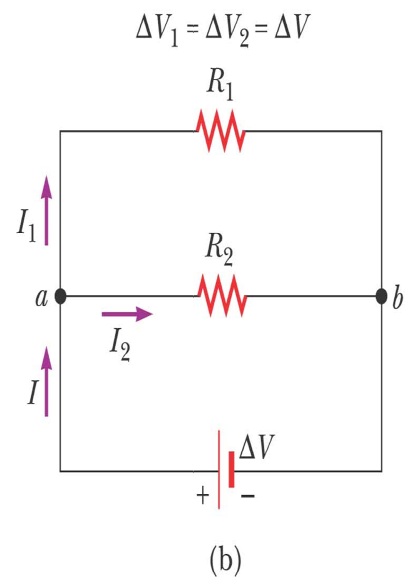

©2004 Thomson - Brooks/Cole

In this figure, When the current I reaches point a , called a *junction*, it splits into two parts, with I_1 going through R_1 and I_2 going through R_2 . A *junction* is any point in a circuit where a current can split,

$$I = I_1 + I_2 \quad (28.8)$$


When the resistors are connected in parallel, the potential difference is the same.

$$\nabla V = \nabla V_1 = \nabla V_2 \quad (28.9)$$

From eq. (28.2),

$$\begin{aligned} \frac{\nabla V}{R_{eq}} &= \frac{\nabla V_1}{R_1} + \frac{\nabla V_2}{R_2} = \nabla V \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \\ \frac{1}{R_{eq}} &= \frac{1}{R_1} + \frac{1}{R_2} \end{aligned} \quad (28.10)$$

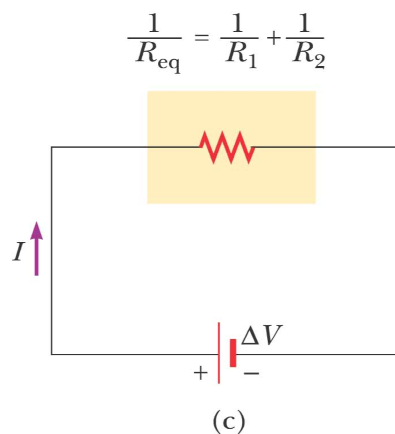So, one can say that the equivalent resistance of two or more resistors connected in parallel is always less than the least resistance in the group.



©2004 Thomson - Brooks/Cole

Please note that:



Household circuits are always wired such that the appliances are connected in parallel. Each device operates independently of the others so that if one is switched off, the others remain on. In

addition, the devices operate on the same voltage.

Examples (28.3) (28.4) (28.5)

a- Find the equivalent resistance between points *a* and *c*.

b- What is the current in each resistor if a potential differences of 42 V is maintained between *a* and *c*?

(A) Find the equivalent resistance between points *a* and *c*.


Solution The combination of resistors can be reduced in steps, as shown in Figure 28.9. The 8.0-Ω and 4.0-Ω resistors are in series; thus, the equivalent resistance between *a* and *b* is 12.0 Ω (see Eq. 28.5). The 6.0-Ω and 3.0-Ω resistors are in parallel, so from Equation 28.7 we find that the equivalent resistance from *b* to *c* is 2.0 Ω. Hence, the equivalent resistance from *a* to *c* is 14.0 Ω.

(B) What is the current in each resistor if a potential difference of 42 V is maintained between *a* and *c*?

Solution The currents in the 8.0-Ω and 4.0-Ω resistors are the same because they are in series. In addition, this is the same as the current that would exist in the 14.0-Ω equivalent resistor subject to the 42-V potential difference. Therefore, using Equation 27.8 ($R = \Delta V/I$) and the result from part (A), we obtain

$$I = \frac{\Delta V_{ac}}{R_{eq}} = \frac{42 \text{ V}}{14.0 \Omega} = 3.0 \text{ A}$$

This is the current in the 8.0-Ω and 4.0-Ω resistors. When this 3.0-A current enters the junction at *b*, however, it splits with part passing through the 6.0-Ω resistor (I_1) and part through the 3.0-Ω resistor (I_2). Because the potential difference is ΔV_{bc} across each of these parallel resistors, we see that $(6.0 \Omega)I_1 = (3.0 \Omega)I_2$, or $I_2 = 2I_1$. Using this result and the fact that $I_1 + I_2 = 3.0 \text{ A}$, we find that $I_1 = 1.0 \text{ A}$ and

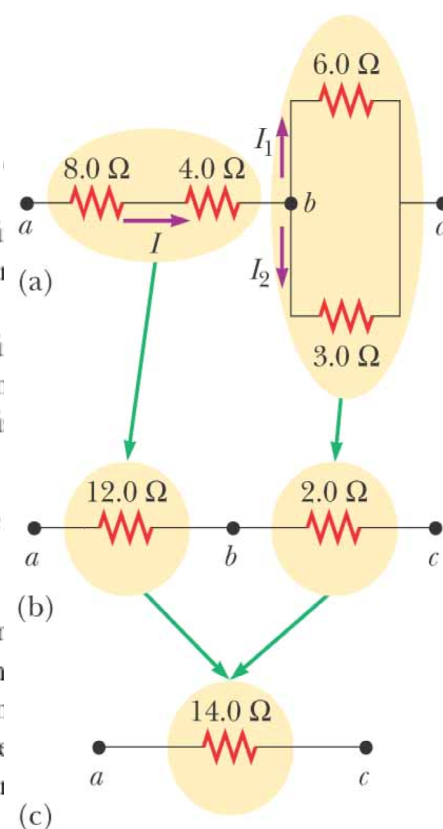

©2004 Thomson - Brooks/Cole

$I_2 = 2.0$ A. We could have guessed this at the start by noting that the current in the $3.0\text{-}\Omega$ resistor has to be twice that in the $6.0\text{-}\Omega$ resistor, in view of their relative resistances and the fact that the same voltage is applied to each of them.

As a final check of our results, note that $\Delta V_{bc} = (6.0\text{ }\Omega)I_1 = (3.0\text{ }\Omega)I_2 = 6.0$ V and $\Delta V_{ab} = (12.0\text{ }\Omega)I = 36$ V; therefore, $\Delta V_{ac} = \Delta V_{ab} + \Delta V_{bc} = 42$ V, as it must.

