

Student Name: _____

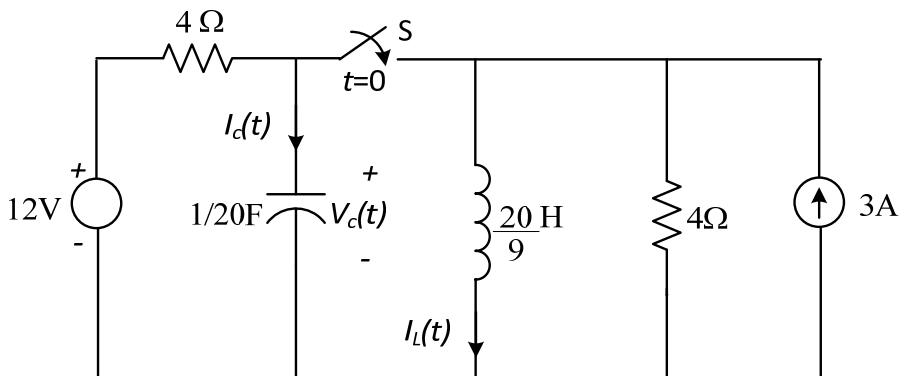
ID # _____

Question 1:

For the circuit shown in **Fig.1**, the switch has been open for a long time. It is closed at $t = 0$.

Find:

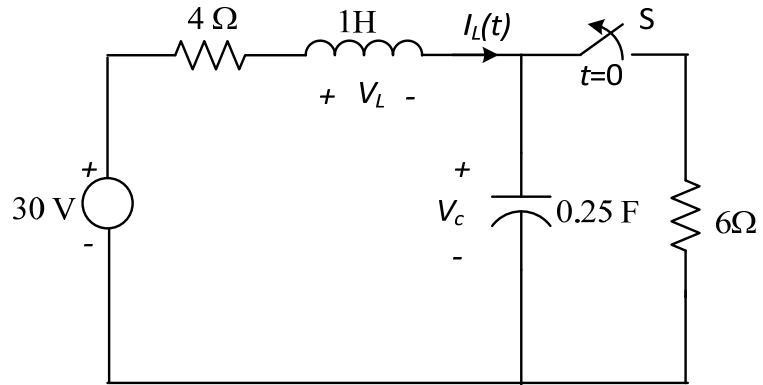
- (a) $V_C(0^+)$
- (b) $I_L(0^+)$
- (c) $I_C(0^+)$
- (d) $V_C(t)$ for $t > 0$

**Fig. 1**

Question 2:

In the circuit shown in **Fig. 2**, the switch has been closed for a long time. It is opened at time $t=0$. Find:

- (a) $V_C(0^+)$
- (b) $I_L(0^+)$
- (c) $V_L(0^+)$
- (d) $I_L(t)$ for $t > 0$

**Fig. 2**

Question 3:

For the circuit shown in **Fig. 3**, find

- (a) The open circuit voltage V_{ab}
- (b) Short circuit current I_{ab}
- (c) Thevenin's impedance Z_{th}
at terminals a, b

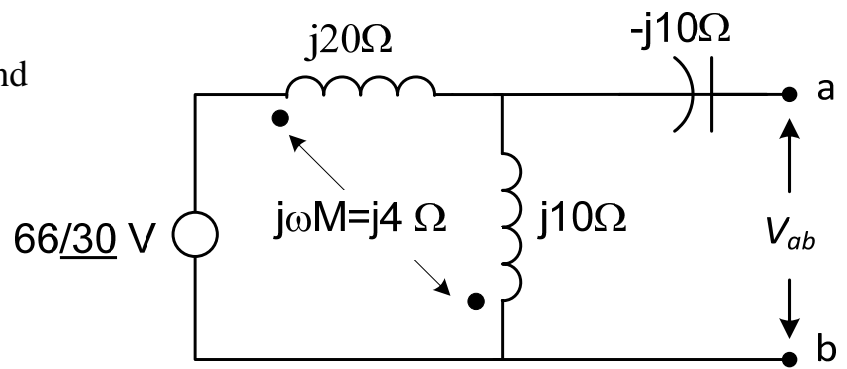


Fig. 3

Question 4:

The series RLC circuit shown in **Fig. 4** is used as a band-pass filter, if the upper cut-off frequency $\omega_2 = 1000$ rad/s, find

- a) Inductance L
- b) Resonance frequency ω_0
- c) Lower cut-off frequency ω_1
- d) Bandwidth β
- e) Quality factor Q

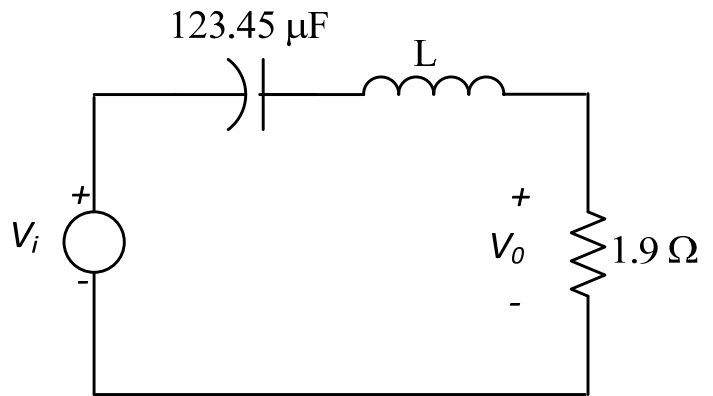


Fig. 4

Question 5:

For each circuit shown in **Fig. 5a** and **Fig. 5b**.

(a) Find the transfer function $H(\omega) = \frac{V_o}{V_s}$

(b) Name the type of filter which each circuit represents.

(c) Find the cut-off frequency in each case.

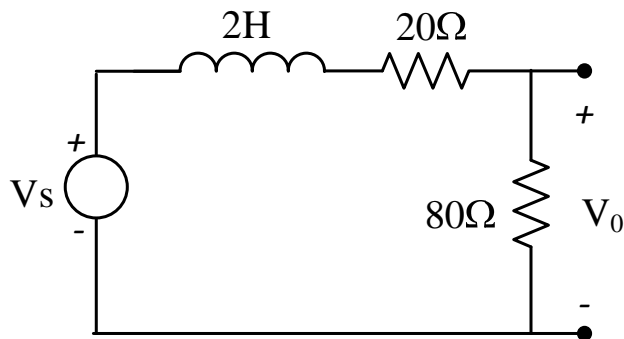


Fig 5(a)

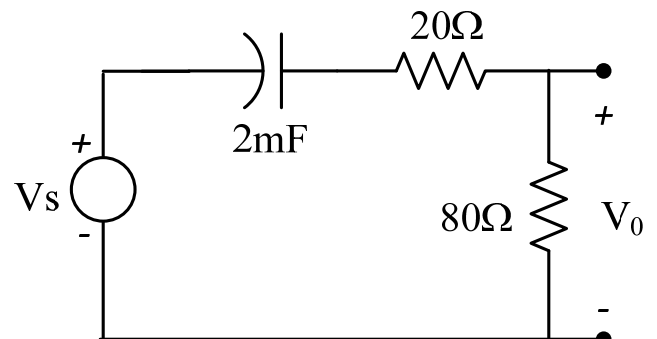


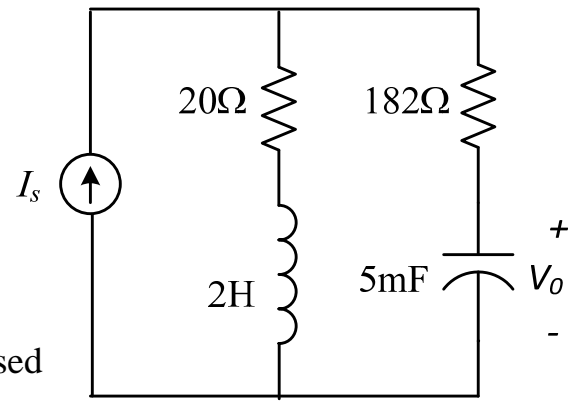
Fig 5(b)

Question 6:

In the circuit shown in **Fig. 6**,

- (i) Find the transfer function $H(s) = \frac{V_o}{I_s}$
- (ii) Find the numerical values of poles and zeros of $H(s)$.
- (iii) Find the values of a, b, c and K , if $H(\omega)$ is expressed as

$$H(\omega) = \frac{K (1 + \frac{j\omega}{a})}{(1 + \frac{j\omega}{b})(1 + \frac{j\omega}{c})}$$

**Fig. 6**