

Question1

A) (14 points).

In the circuit shown in Figure 1, determine the value of current I_x .

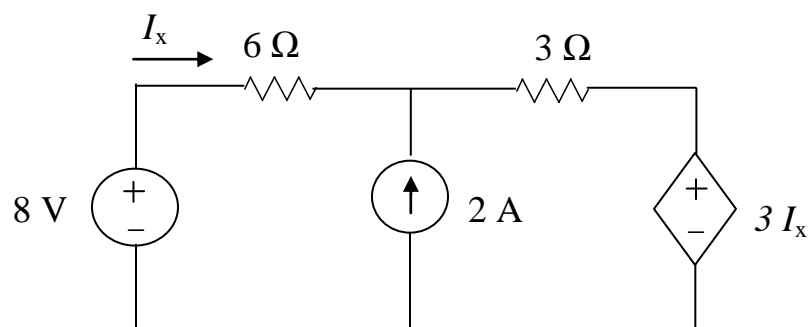


Fig. 1

B) (14 points)

In the circuit shown in Figure 2, determine the power supplied by the 12-V voltage source.

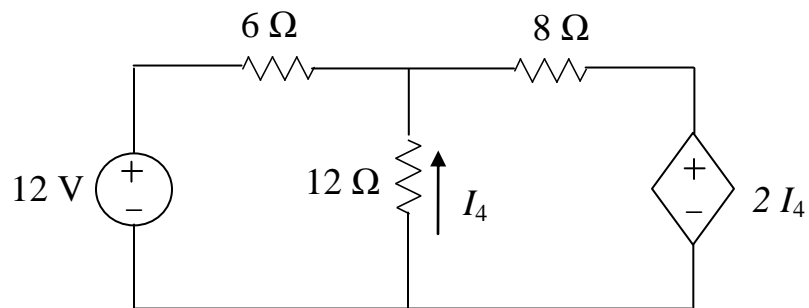


Fig. 2

C) (14 points).

In the circuit shown in Figure 3, the 20-V voltage source supplies 2 W of power. The value of the voltage v_2 across the $25\text{-}\Omega$ resistor is $v_2 = 4\text{ V}$. Determine the value of the resistance R_1 and of the value of G .

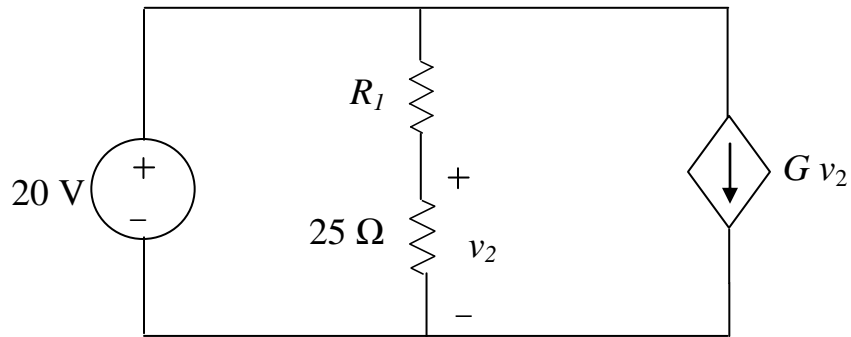


Fig. 3

Question2

A)(14 points).

In the circuit shown in Figure 4, determine the value of V_0 and I_0 . Assume ideal amplifier.

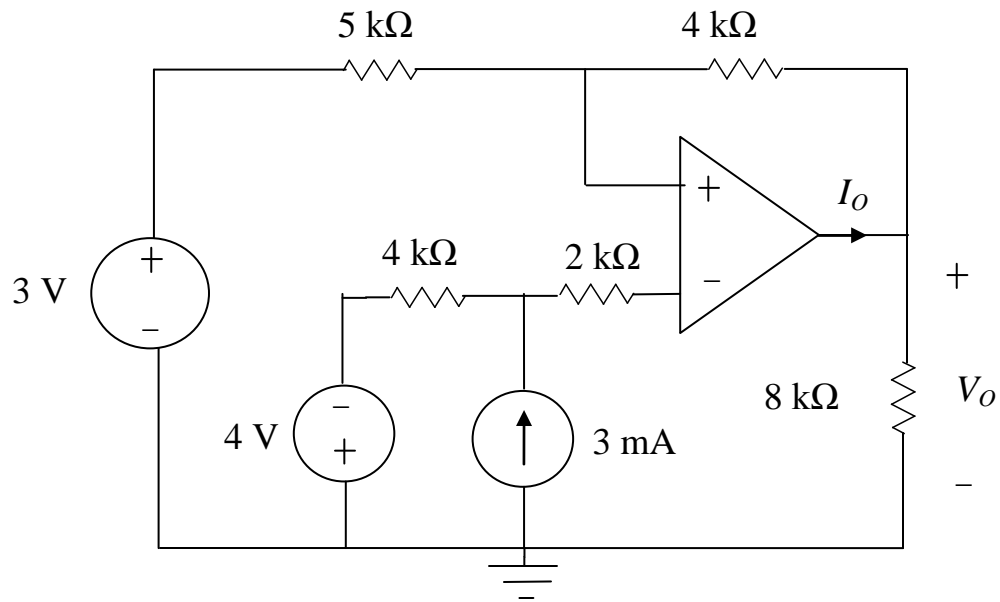


Fig. 4

B) (14 points).

In the circuit shown in Figure 5, determine the value of voltages at nodes a , b , c , and d . Assume ideal amplifier.

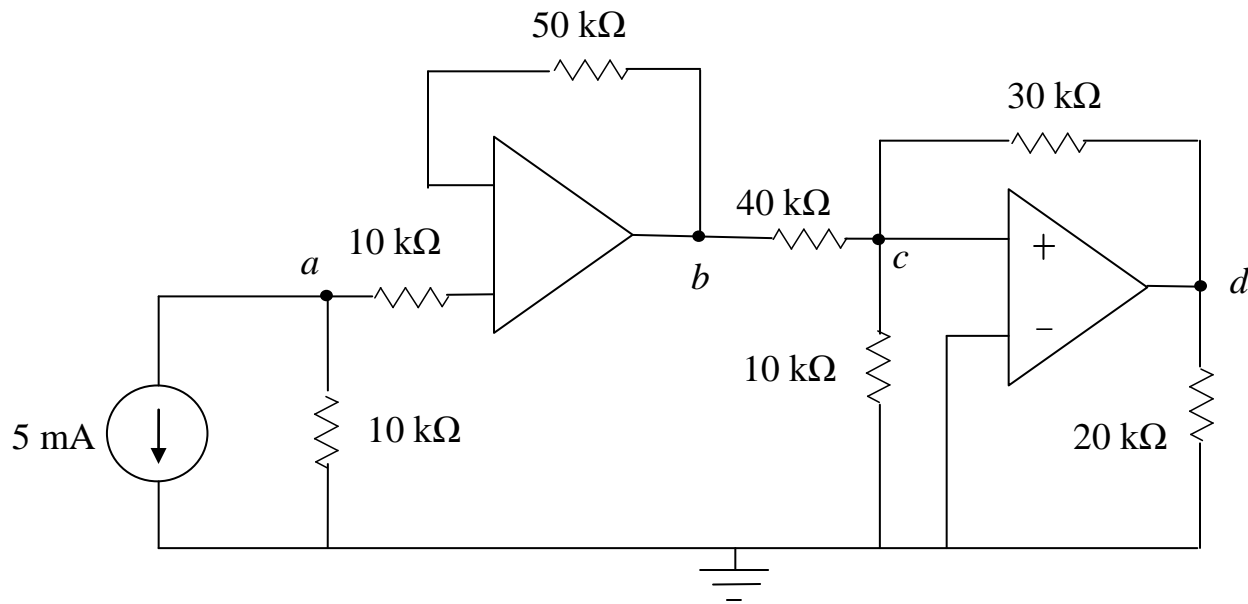


Fig. 5

C) (15 points).

In the circuit shown in Figure 6, determine the value of V_o . Assume ideal amplifier.

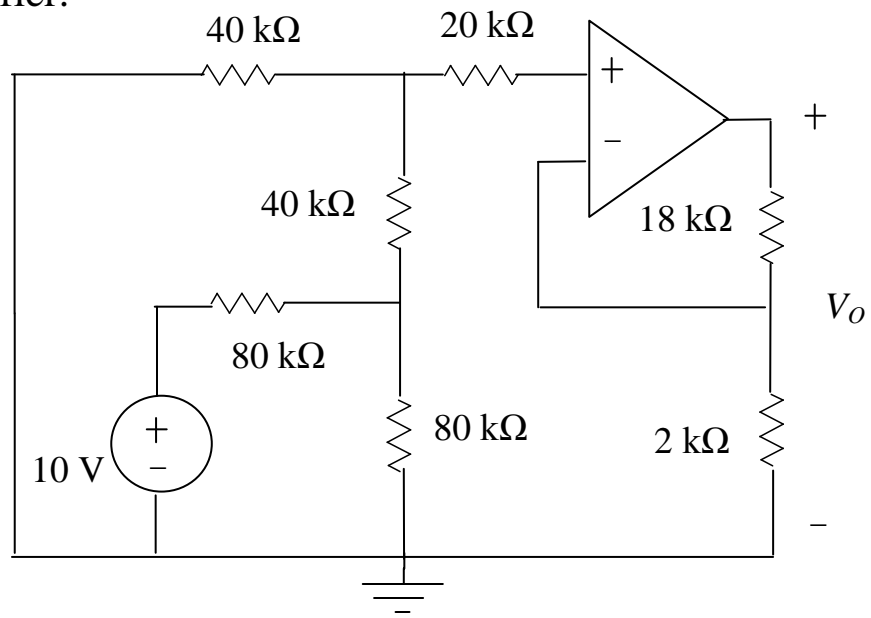


Fig. 6

Question3 (16 points)

In the circuit shown in Figure 7, the switch S has been closed for a long time.

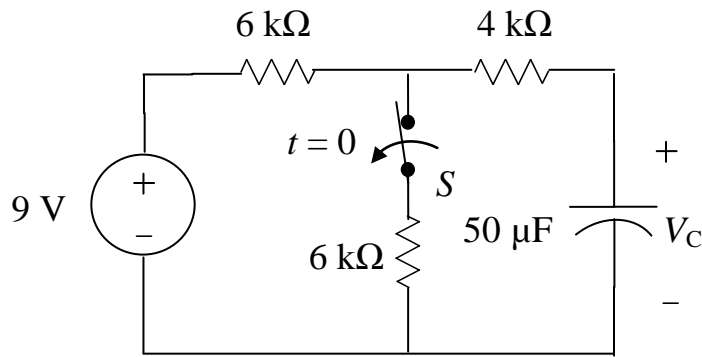


Fig. 7

- With switch S closed, determine the voltage across the capacitor V_C .
- If the switch S is opened at $t = 0$, and left open for a long time, determine the final value of the capacitor voltage $V_C(\infty)$.
- Write the mathematical expression for V_C as a function of time $V_C(t)$ for $t > 0$.
- Sketch variation of $V_C(t)$ with time .