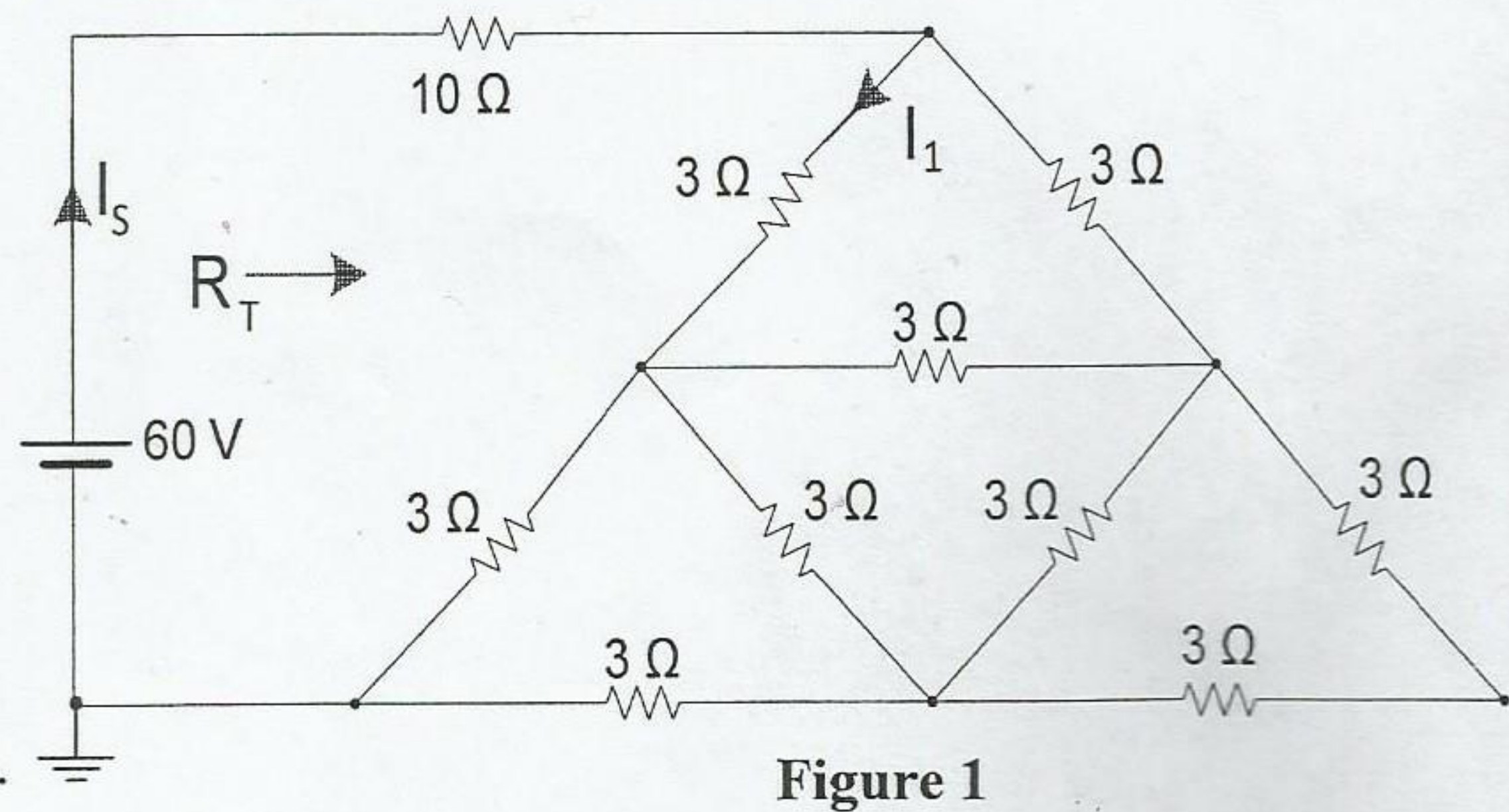


Question 1:

For the circuit shown in figure 1, find:


- The total input resistance ' R_T '.
- The total source current ' I_S '.
- The current ' I_1 '.
- The total power dissipated by all resistors.



Question 2:

For the circuit shown in figure 2:

- Write down the Mesh equations for the circuit.
- Write down the Nodal equations for the circuit.
- Find the voltage ' V_a '.

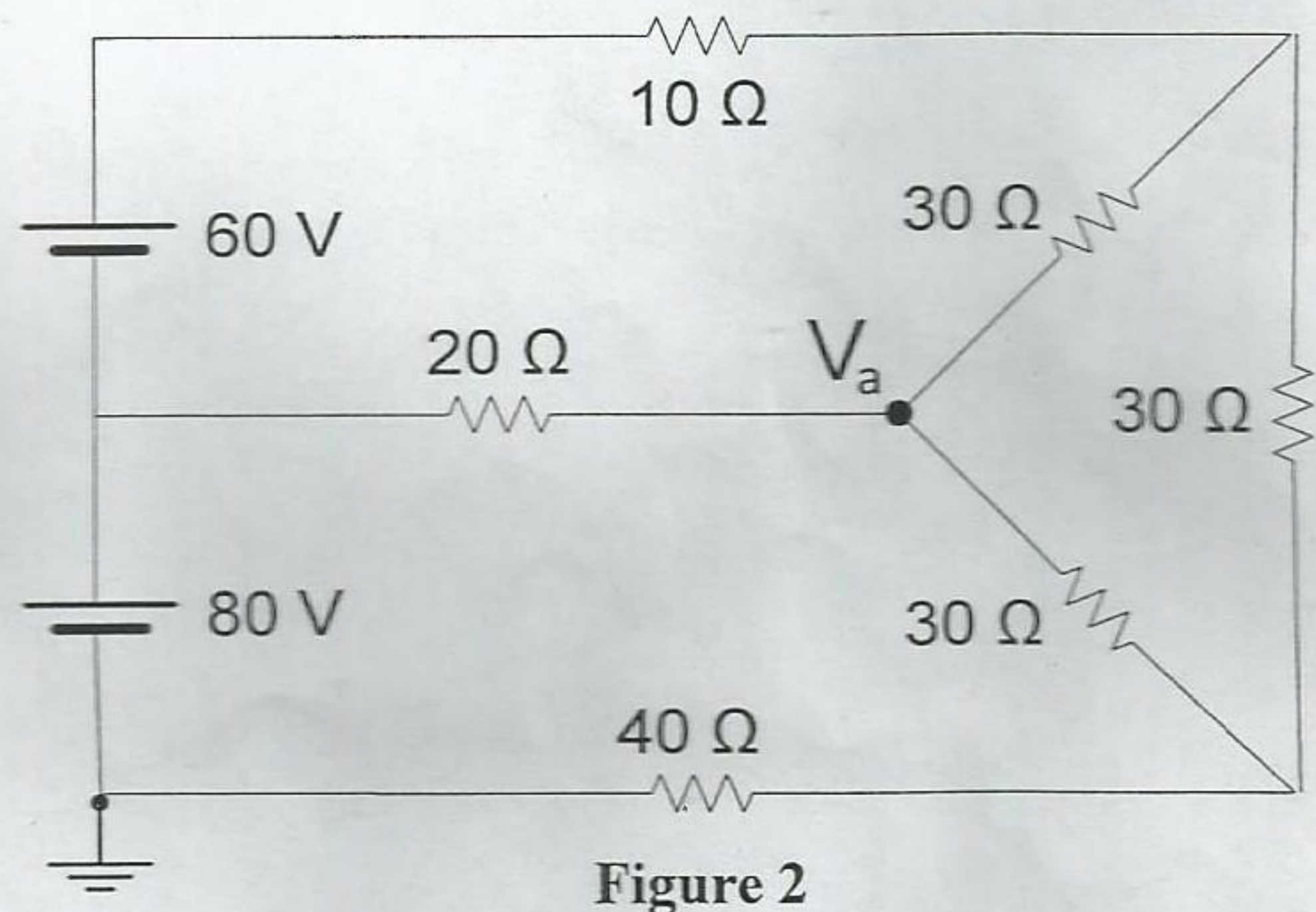

Question 3:

For the circuit shown in figure 3:

- Find the voltage ' V_{ab} ' using **Superposition theorem**.
- Find the Norton equivalent circuit between nodes 'a' and 'b'.
- If ' R_L ' is connected between nodes 'a' and 'b', find the maximum power transfer to ' R_L '.

