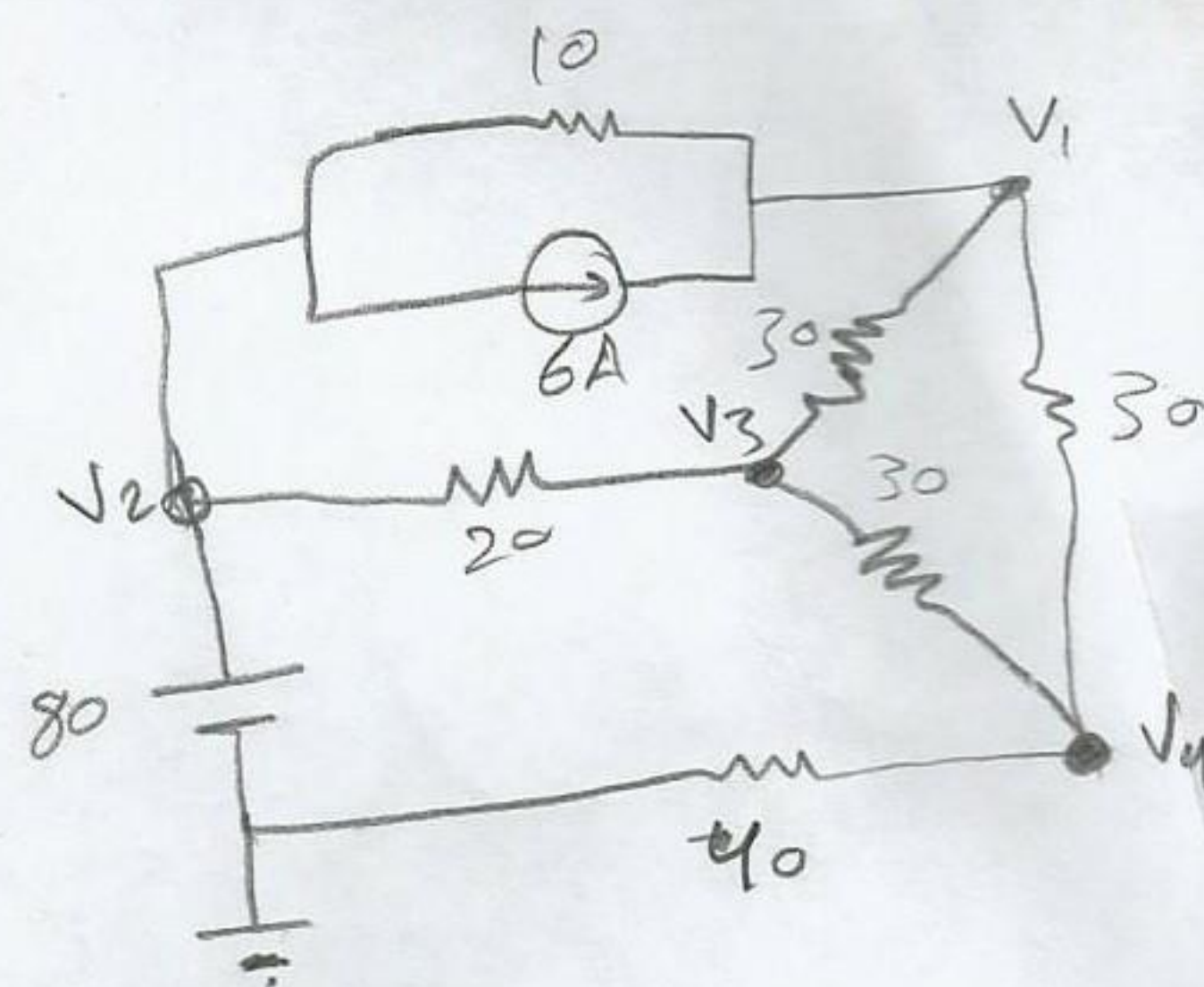


(a)



(b)

- write down the mesh eqs?

- Find V_a

$$\textcircled{I} I_1(10+20+30) - I_2(30) - I_3(20) = 60$$

$$\textcircled{II} 60I_1 - 30I_2 - 20I_3 = 60$$

$$-I_1(30) + I_2(30+30+30) - I_3(30) = 0$$

$$\textcircled{III} -30I_1 + 90I_2 - 30I_3 = 0$$

$$-I_1(20) - I_2(30) + I_3(20+30+40) = 80$$

$$\textcircled{IV} -20I_1 - 30I_2 + 90I_3 = 80$$

$$I_1 = 2.32 \text{ A}$$

$$I_2 = 1.4 \text{ A}$$

$$I_3 = 1.87 \text{ A}$$

$$V_a = 80 + (20)[I_3 - I_1] = 80 - [20](1.87 - 2.32) = 89.03 \text{ V}$$

- write down the Nodal eqs?!

- find V_a

$$\textcircled{1} V_1\left(\frac{1}{10} + \frac{1}{30} + \frac{1}{30}\right) - \frac{V_2}{10} - \frac{V_3}{30} - \frac{V_4}{30} = 6$$

$$\textcircled{2} V_2 = 80$$

$$\textcircled{3} -\frac{V_1}{30} - \frac{V_2}{20} + V_3\left(\frac{1}{20} + \frac{1}{30} + \frac{1}{30}\right) - \frac{V_4}{30} = 0$$

$$\textcircled{4} -\frac{V_1}{30} - \frac{V_3}{30} + V_4\left(\frac{1}{30} + \frac{1}{40} + \frac{1}{30}\right) = 0$$

by calc

$$\begin{aligned} V_1 &= 116.78 \text{ V} \\ V_3 &= 89.03 \text{ V} \\ V_4 &= 79.89 \text{ V} \end{aligned}$$