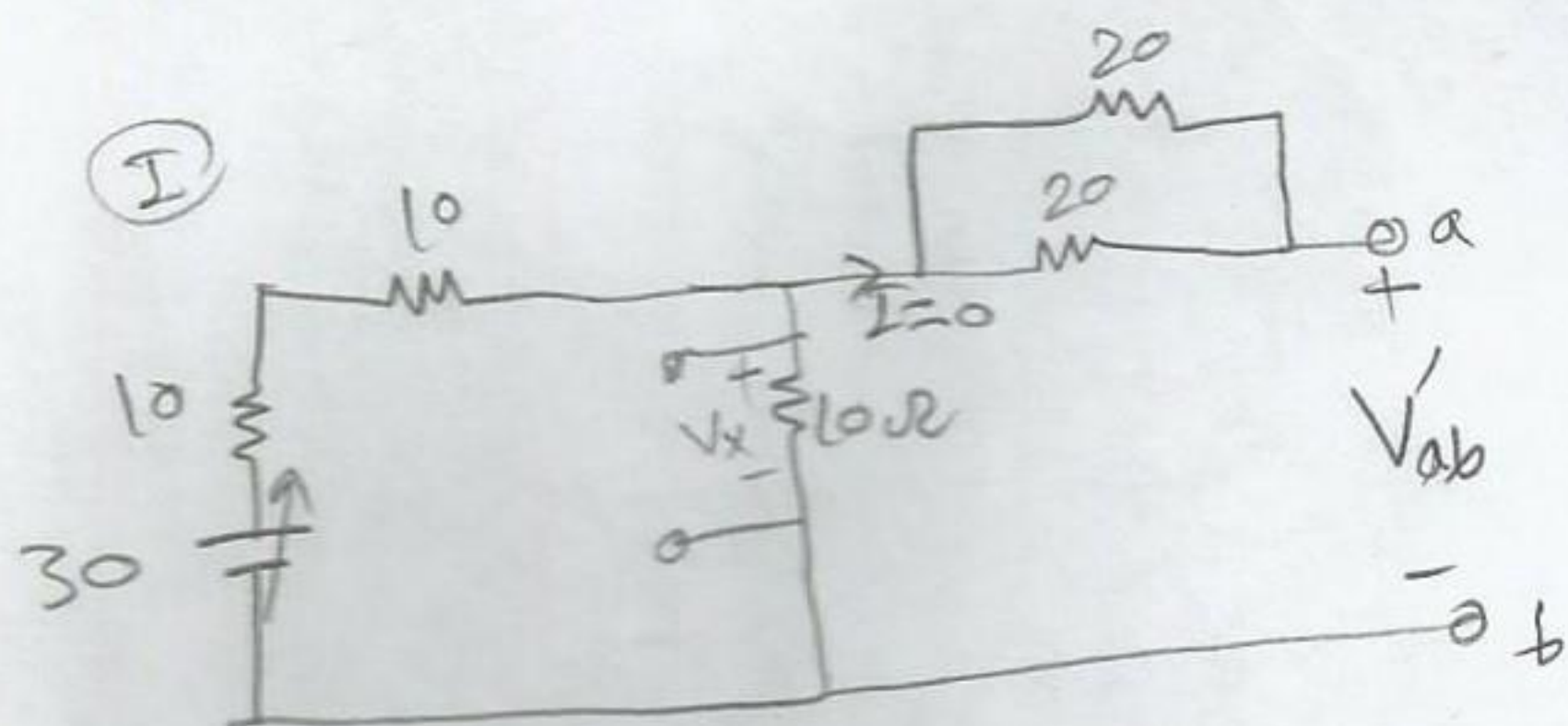



Q-3

(a)



$$\therefore V_{ab} = V_x = 30 \times \frac{10}{10+10+0} = 10V$$


(II)

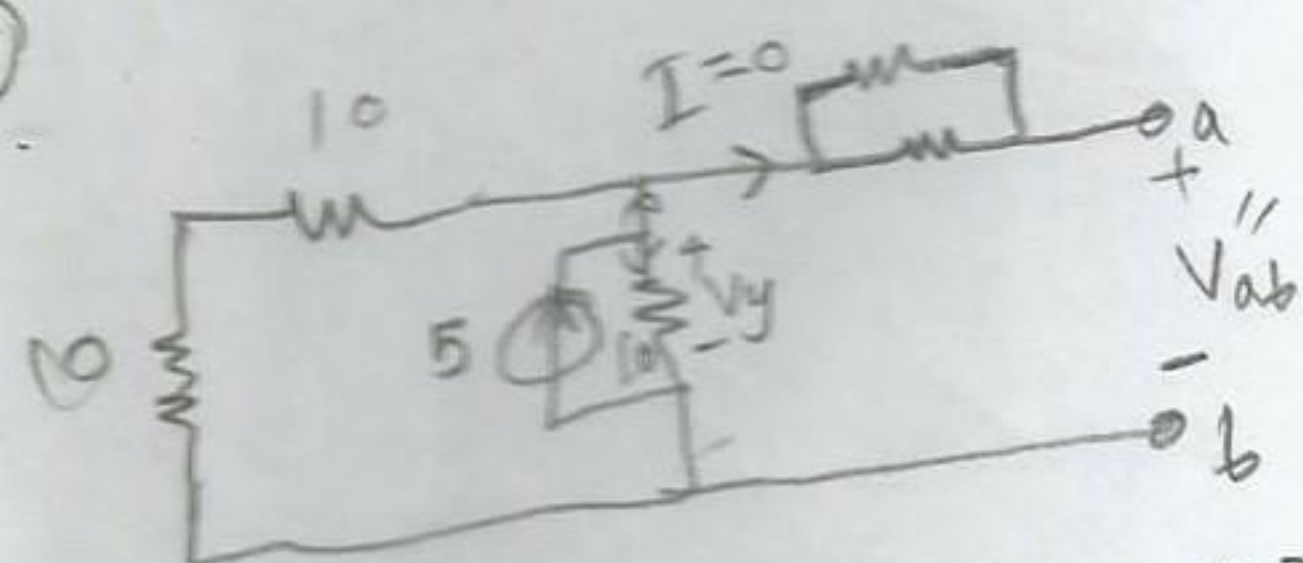

$$I_y = 5 \times \frac{20}{20+10} = \frac{100}{30} = 3.33A$$


$$V_{ab} = V_y = 3.33 \times 10 = 33.3V$$

(III)

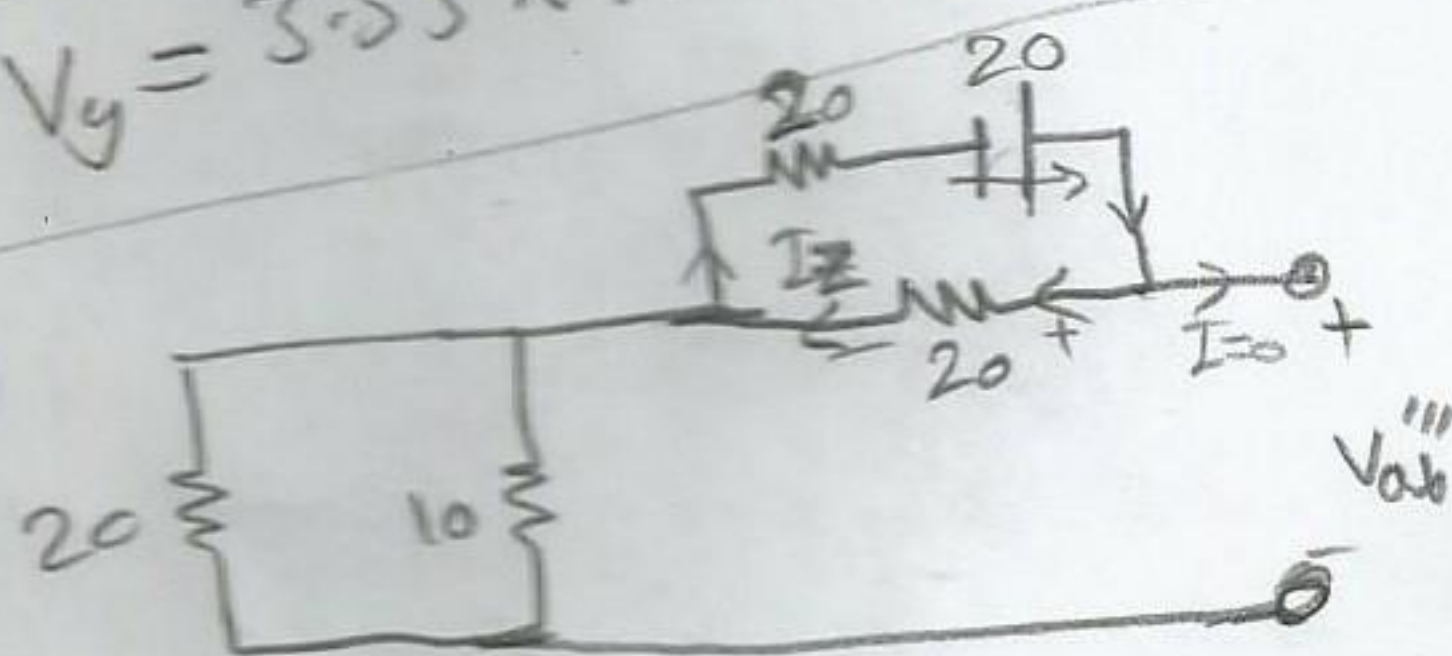

$$I_z = \frac{1}{2}A = \frac{20}{40}$$

or

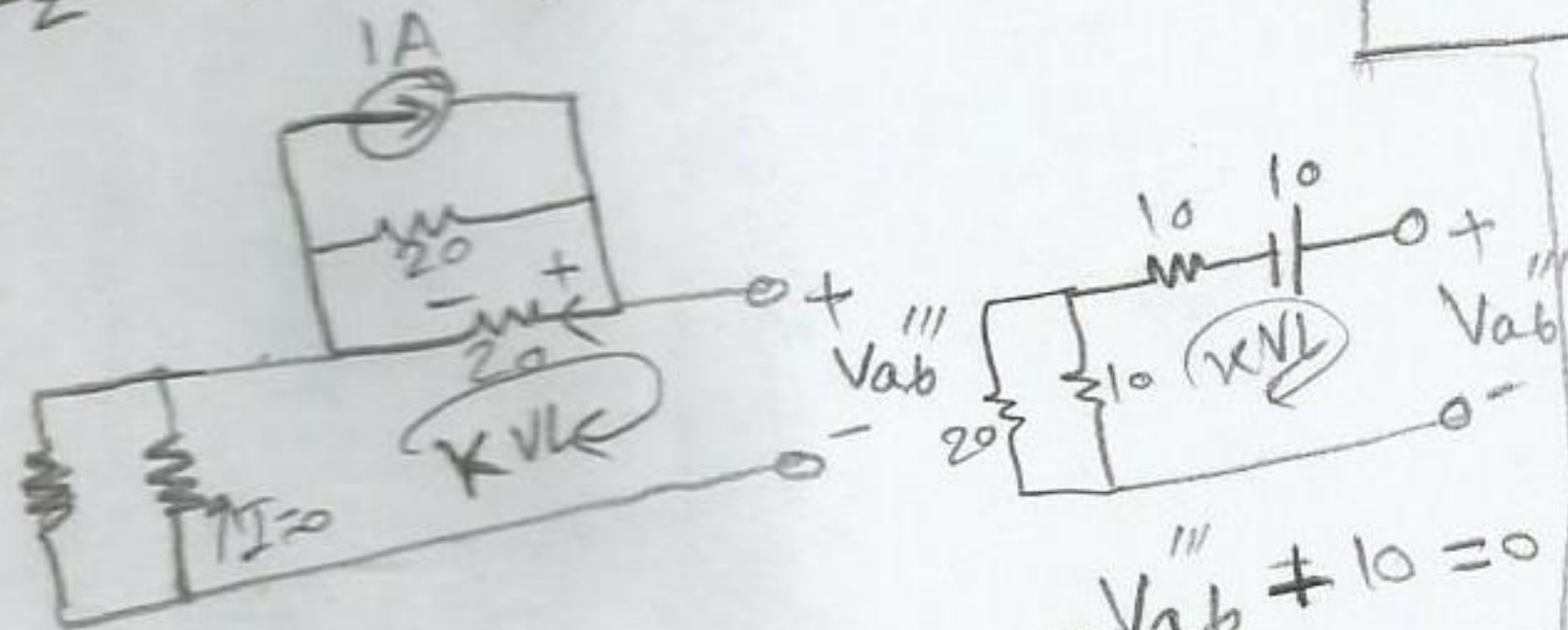

$$-V_{ab} + 10 = 0$$

$$\therefore V_{ab} = 10V$$

by KVL

$$-V_{ab} + 20\left(\frac{1}{2}\right) - (0)(10) = 0$$

$$\therefore V_{ab} = 10V$$


$$\therefore V_{ab} = 10 + 33.3 + 10 = 53.3V$$

(b)

Norton equivalent: I_N and R_N



$$\text{since } E_{Th} = 53.3V$$

$$\therefore R_{Th}$$

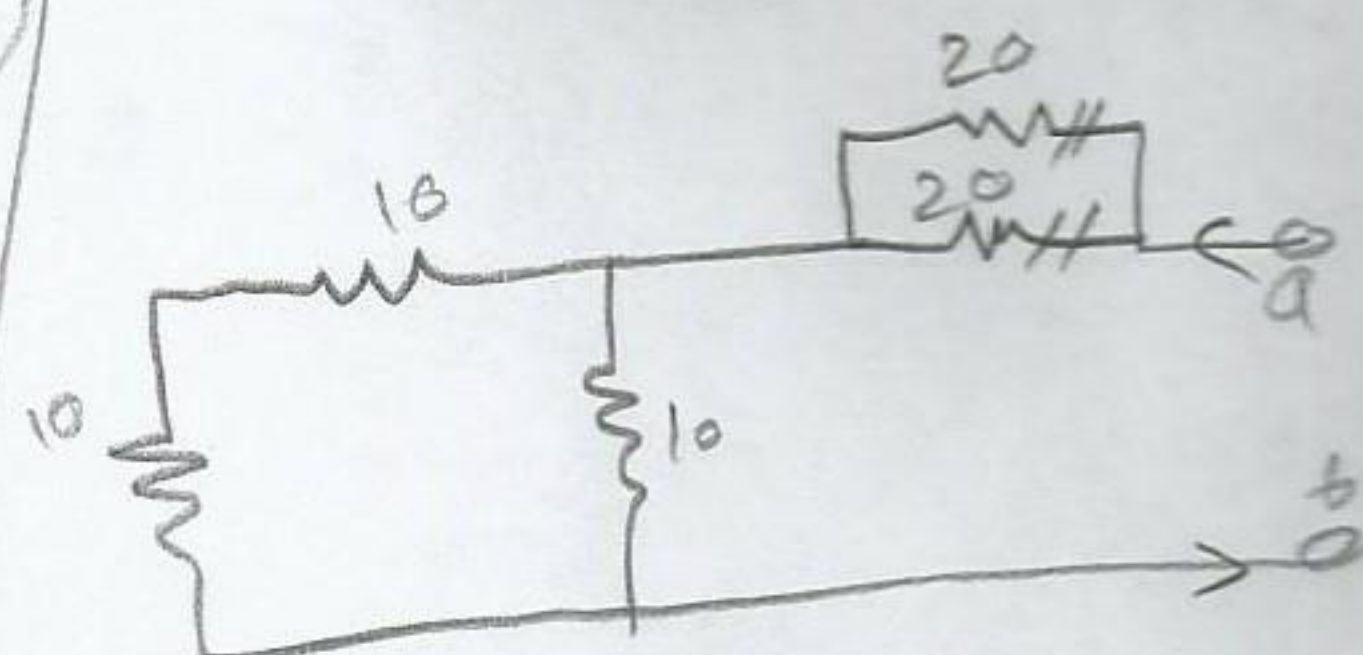

$$R_{Th} = R_N$$
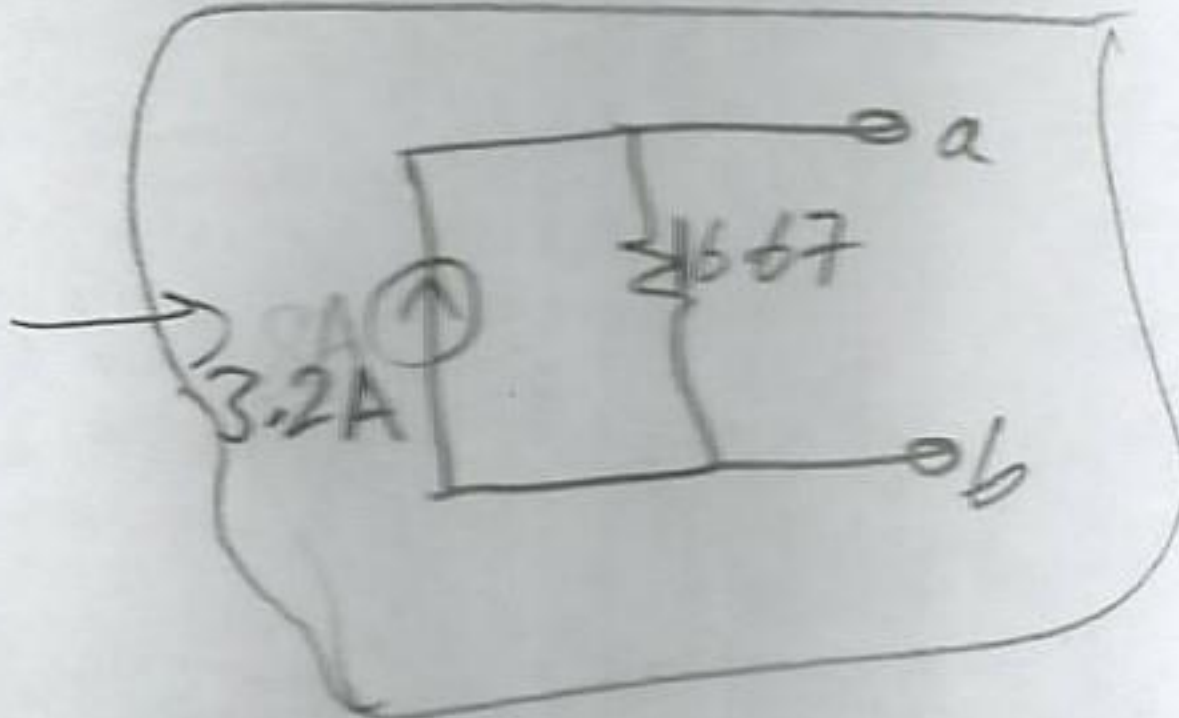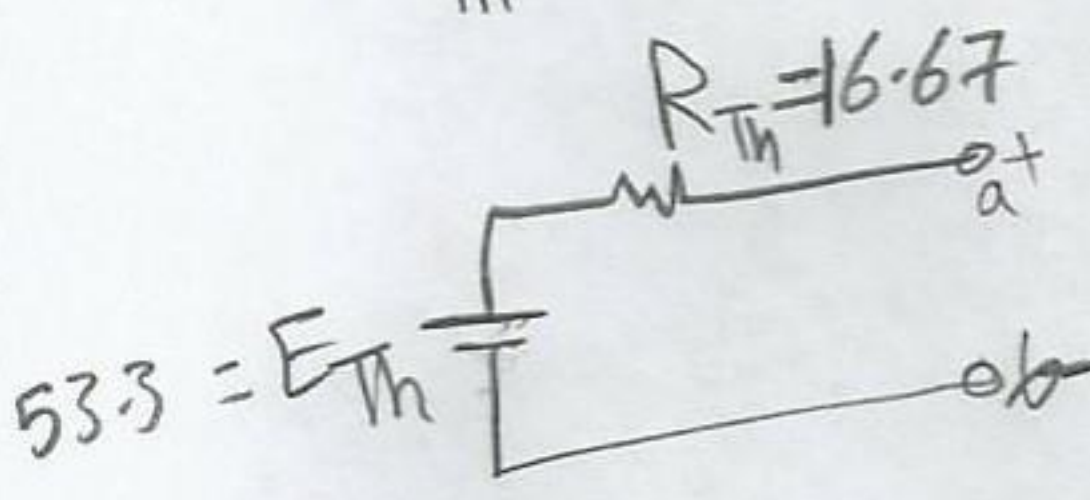
$$\therefore R_{Th} = R_N = 10 + (10 \parallel 20) = 16.67\Omega$$



(c)



to get P_{Lmax} $\therefore R_L = R_N = 16.67$

$$P_{bmax} = \frac{1}{4} \frac{E_{Th}^2}{R_{Th}} = \frac{1}{4} I_N^2 R_N$$

$$= 42.67W$$