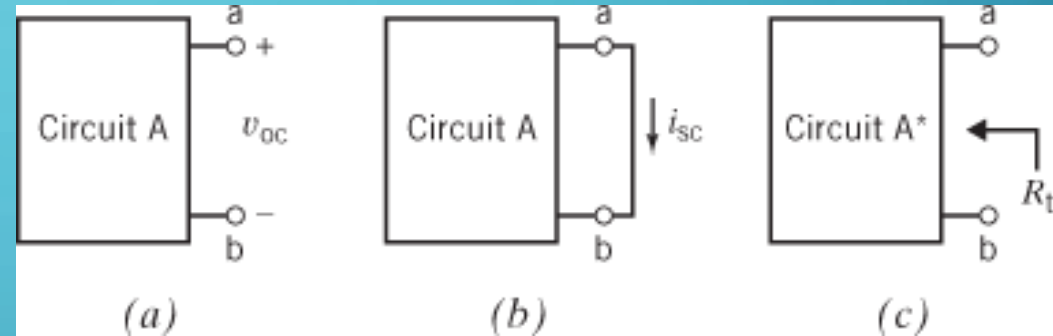


How to find Thevenin/Norton with DS ?


1. Compute V_{oc}

2. Compute I_{sc}


$$\rightarrow R_t = V_{oc}/I_{sc}$$



Thevenin

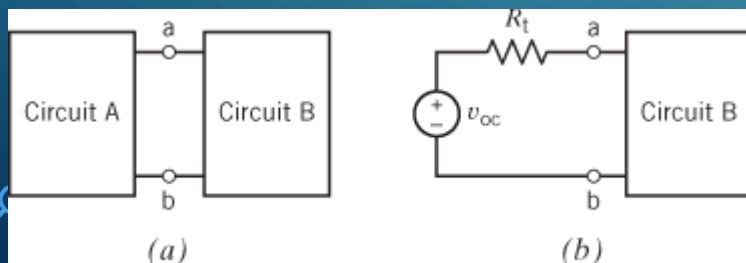

Norton

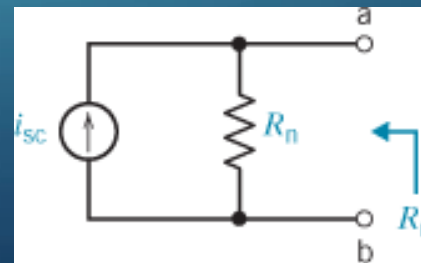

EXAMPLE 5.4-3


Find the Thévenin equivalent circuit for the circuit shown which includes a dependent source.

$v_{oc} = v_{ab}$. Writing KVL


$$\rightarrow -20 + 6i - 2i + 6i = 0$$

$i = 2\text{ A}$
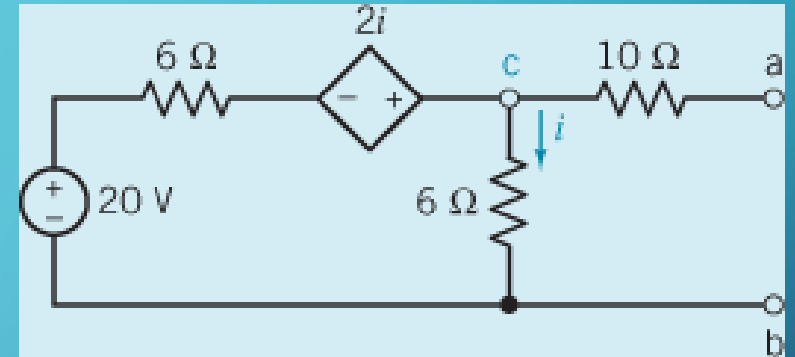
$$\text{Hence, } v_{oc} = 6i = 12\text{ V}$$



Next Find i_{sc}

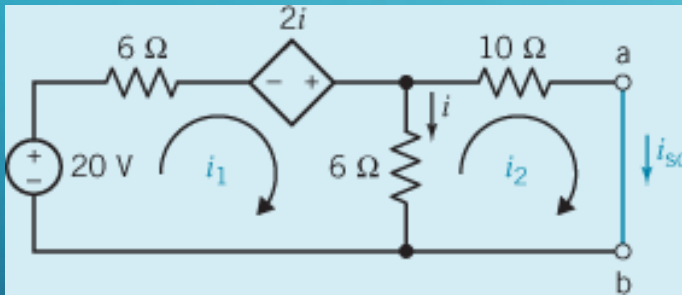

$$-20 + 6i_1 - 2i + 6(i_1 - i_2) = 0$$

and

$$6(i_2 - i_1) + 10i_2 = 0$$

Substitute $i = i_1 - i_2$ and rearrange the two equations to obtain

$$10i_1 - 4i_2 = 20$$

$$i_2 = i_{sc} = 120 / 136\text{ A}$$

$$\rightarrow R_t = \frac{v_{oc}}{i_{sc}} = \frac{12}{120 / 136} = 13.6\Omega$$

** See Ex 5.5-3

Super Position With DS...

$$V_o = \sum a_i V_i$$

- Acceptable inputs are Independent sources only.
- You solve regularly while never changing the DS (like a Resistor).

EX 5.3-2) FIND THE CURRENT i FOR THE FOLLOWING CIRCUIT

- Step 1: Apply Kirchhoff's voltage law to the loop in Figure-b to get

$$-24 + (3 + 2)i_1 + 3i_1 + 0 \Rightarrow i_1 = 3 \text{ A}$$

- Step 2: First, express the controlling current of the dependent source in terms of the node voltage, v_a , using Ohm's law:

$$i_2 = -\frac{v_a}{3} \Rightarrow v_a = -3i_2$$

Next, apply Kirchhoff's current law at node a to get

$$i_2 + 7 = \frac{v_a - 3i_2}{2} \Rightarrow i_2 + 7 = \frac{-3i_2 - 3i_2}{2} \Rightarrow i_2 = -\frac{7}{4} \text{ A}$$

- Step 3: The current, i , caused by the two independent sources acting together is equal to the sum of the currents, i_1 and i_2 , caused by each source acting separately:

$$i = i_1 + i_2 = 3 - \frac{7}{4} = \frac{5}{4} \text{ A}$$

