



College of Computer and Information Sciences
Department of Computer Science

CSC 220: Computer Organization

Unit 11

Basic Computer Organization and Design



- For the rest of the semester, we'll focus on **computer architecture**: how to assemble the combinational and sequential components we've studied so far into a complete computer.
- Today, we'll start with the **datapath**, the part of the central processing unit (CPU) that does the actual computations.

An overview of CPU design

- We can divide the design of our CPU into three parts:
 - The **datapath** does all of the actual data processing.
 - An **instruction set** is the programmer's interface to CPU.
 - A **control unit** uses the programmer's instructions to tell the datapath what to do.
- Today we'll look in detail at a processor's datapath.
- An ALU does computations, as we've seen before.
 - A limited set of registers serves as fast temporary storage.
 - A larger, but slower, random-access memory is also available.


What's in a CPU?



- A processor is just one big sequential circuit.
 - Some registers are used to store values, which form the state.
 - An ALU performs various operations on the data stored in the registers.

Micro-Ops Transfer Bus

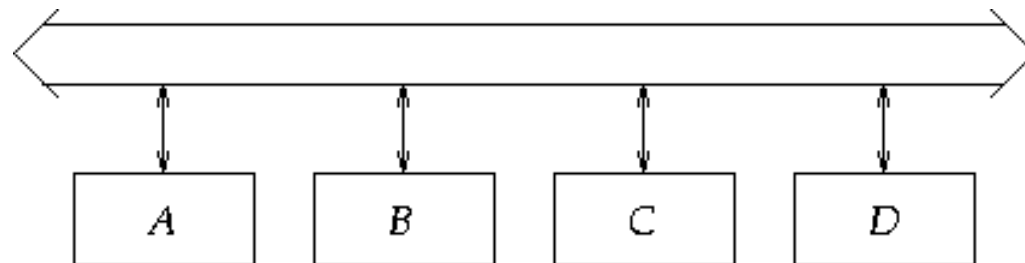- ◆ A bus consists of a set of parallel data lines
- ◆ To transfer data using a bus: connect the output of the source register to the bus; connect the input of the target register to the bus; when the clock pulse arrives, the transfer occurs



Bus and Memory transfers

Figure 4-3 Bus system for four registers.

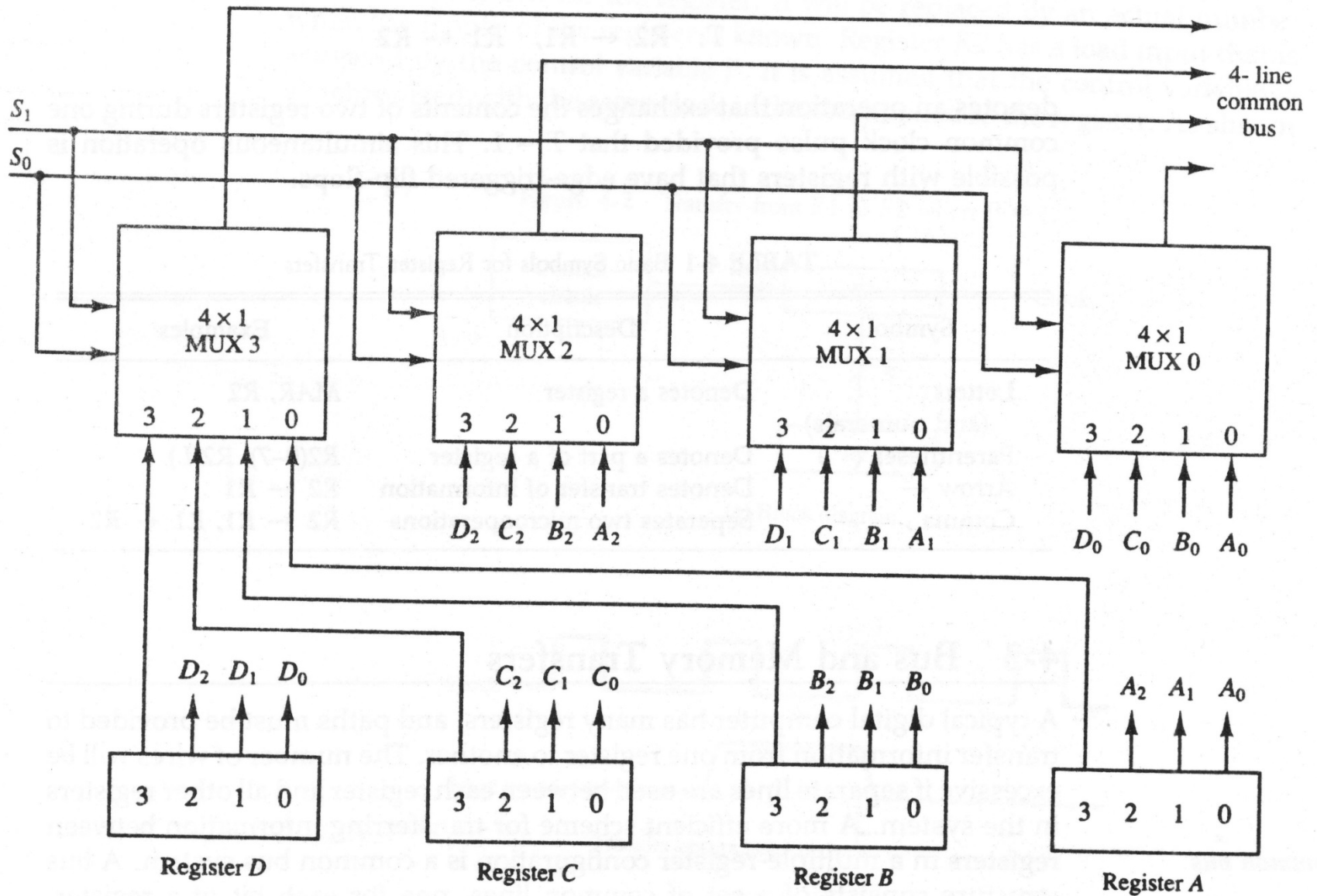


TABLE 4-2 Function Table for Bus of Fig. 4-3

S_1	S_0	Register selected
0	0	A
0	1	B
1	0	C
1	1	D

$BUS \leftarrow C, \quad A \leftarrow BUS$

$A \leftarrow C$

The content of register C is placed on the bus, and the content of the bus is loaded into register A by activating its load control input.


Question

A digital computer has a common bus system for 16 registers of 32 bit each. The bus is constructed with multiplexers.

- How many selection inputs are there in each multiplexer?
- What size of multiplexers is needed?
- How many multiplexers are there in the bus?


Register files

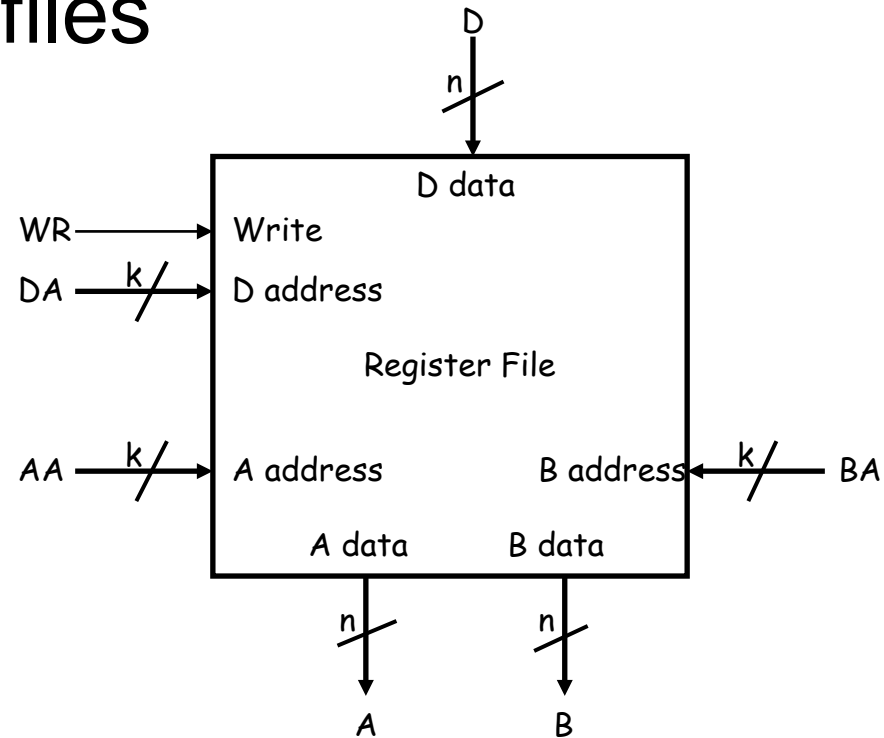- Modern processors contain a number of registers grouped together in a **register file**.
- Much like words stored in a RAM, individual registers are identified by an address.
- Here is a block symbol for a $2^k \times n$ register file.
 - There are 2^k registers, so register addresses are k bits long.
 - Each register holds an n -bit word, so the data inputs and outputs are n bits wide.




Accessing the register file

- You can read *two* registers at once by supplying the **AA** and **BA** inputs. The data appears on the **A** and **B** outputs.
- You can write to a register by using the **DA** and **D** inputs, and setting **WR = 1**.
- These are registers so there must be a clock signal, even though we usually don't show it in diagrams.
 - We can read from the register file at any time.
 - Data is written only on the positive edge of the clock.

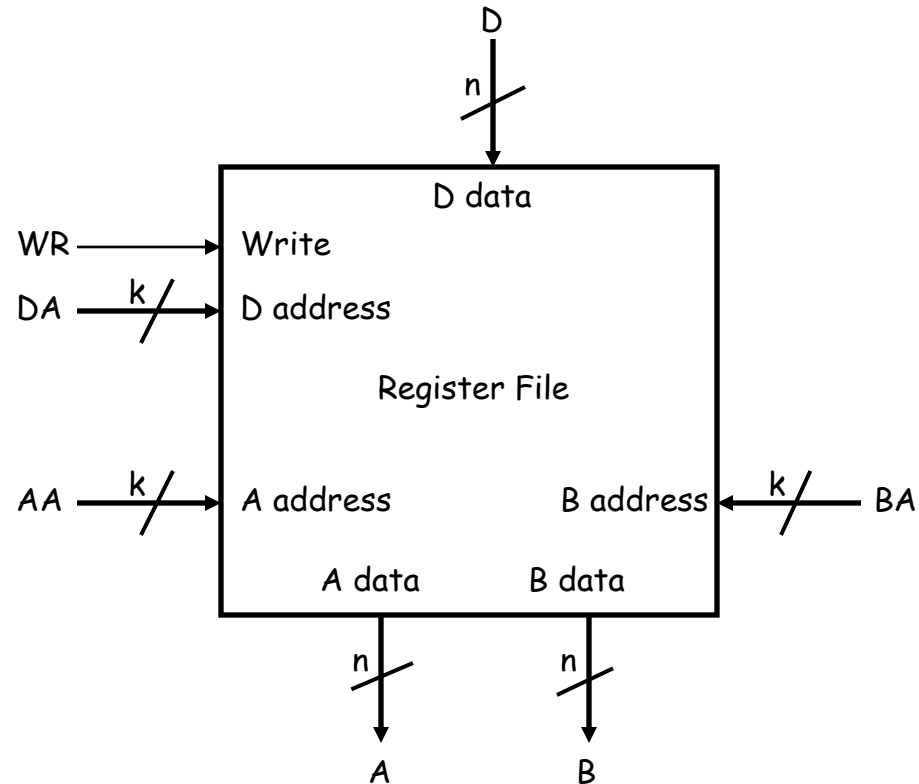


What's inside the register file

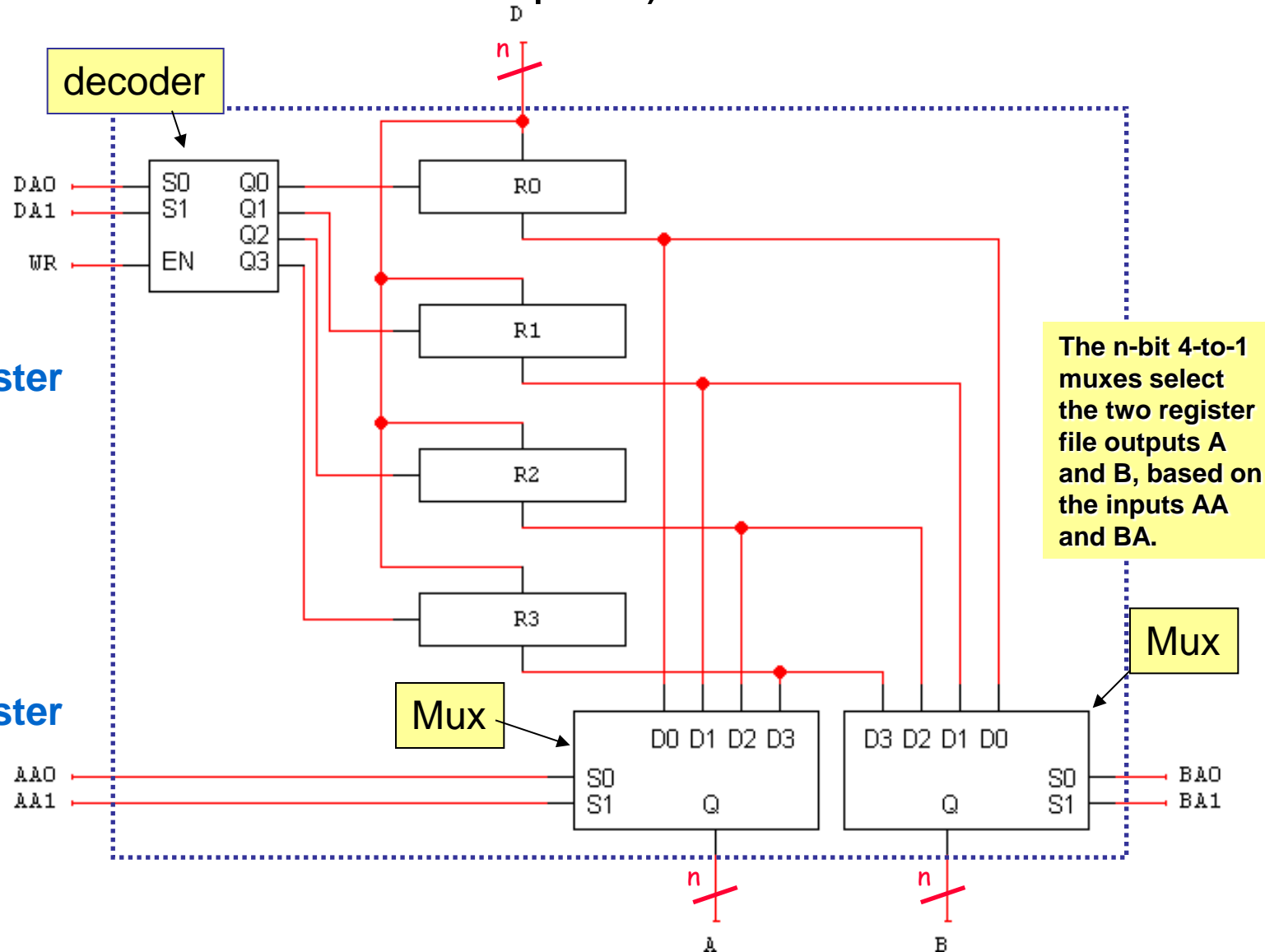- Here's a $4 \times n$ register file. (We'll assume a $2^k \times n = 4 \times n$ register file for all our examples.)




Explaining the register file

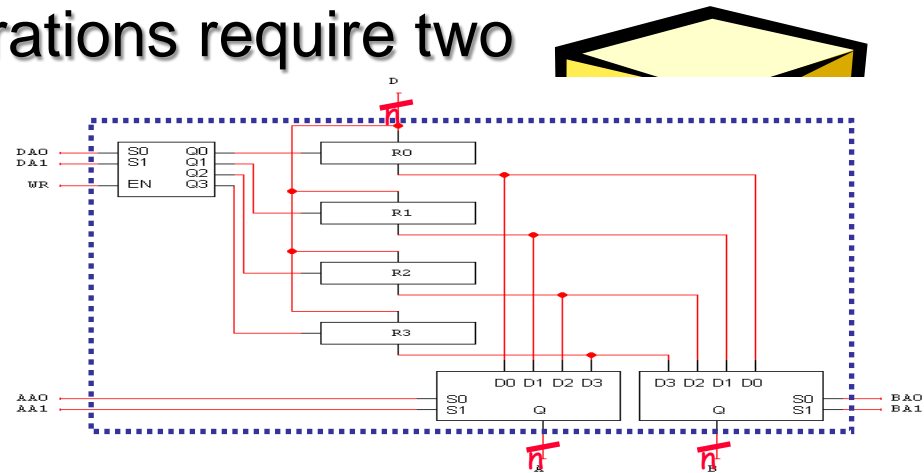- The 2-to-4 decoder selects one of the four registers for writing. If $WR = 1$, the decoder will be enabled and one of the Load signals will be active.
- The n-bit 4-to-1 muxes select the two register file outputs A and B, based on the inputs AA and BA.
- We need to be able to read two registers at once because most arithmetic operations require two operands.



The all-important ALU

- The main job of a central processing unit is to “process,” or to perform computations....remember the ALU from way back when?
- We'll use the following general block symbol for the ALU.
 - **A** and **B** are two n-bit numeric inputs.
 - **FS** is an m-bit function select code, which picks one of 2^m functions.
 - The n-bit result is called **F**.
 - Several **status bits** provide more information about the output F:
 - **V = 1** in case of signed overflow.
 - **C** is the carry out.
 - **N = 1** if the result is negative.
 - **Z = 1** if the result is 0.

 


ALU functions

- For concrete examples, we'll use the ALU as it's presented in chapter 4.
- The function select code FS is 4 bits long, but there are only 15 different functions here.
- We use an alternative notation for AND and OR to avoid confusion with arithmetic operations.

FS	Operation
0000	$F = A$
0001	$F = A + 1$
0010	$F = A + B$
0011	$F = A + B + 1$
0100	$F = A + B'$
0101	$F = A + B' + 1$
0110	$F = A - 1$
0111	$F = A$
1000	$F = A \wedge B$ (AND)
1001	$F = A \vee B$ (OR)
1010	$F = A \oplus B$ (XOR)
1011	$F = A'$
1100	$F = B$
1101	$F = sr B$ (shift right)
1110	$F = sl B$ (shift left)

My first datapath

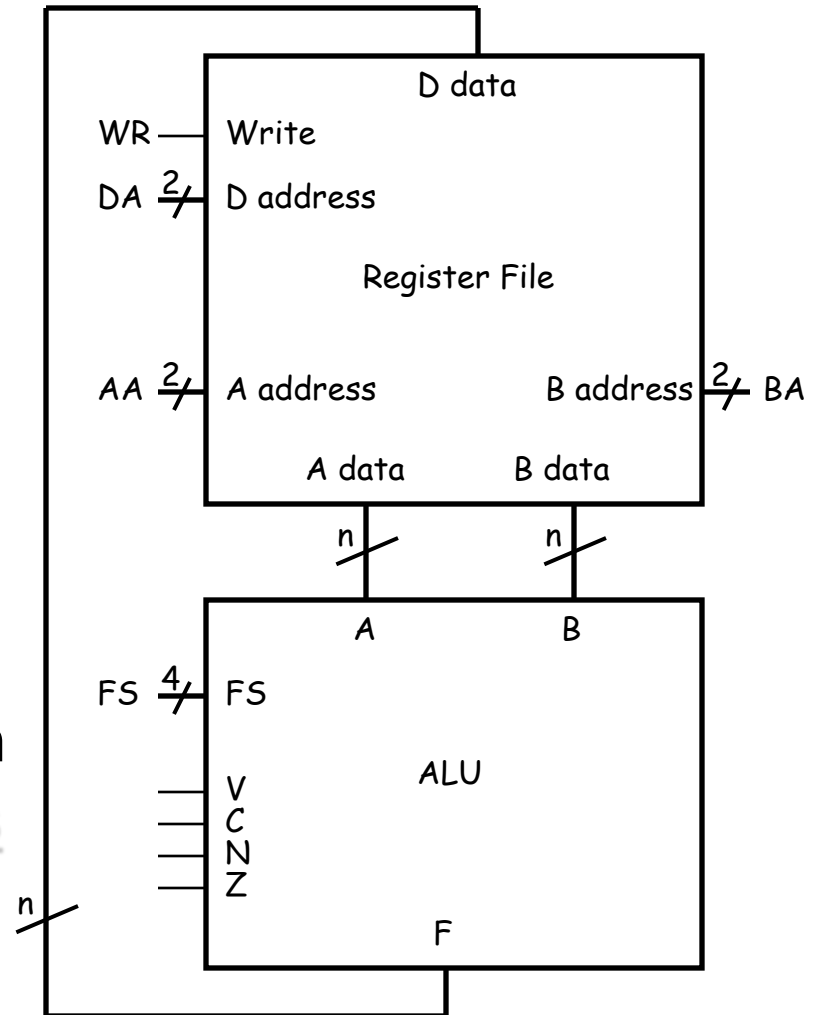- Here is the most basic datapath.
 - The ALU's two data inputs come from the register file.
 - The ALU computes a result, which is saved back to the registers.
- **WR**, **DA**, **AA**, **BA** and **FS** are **control signals**. Their values determine the exact actions taken by the datapath— which registers are used and for what operation.




An example computation

- Let's look at the proper control signals for the operation below:


$$R0 \leftarrow R1 + R3$$

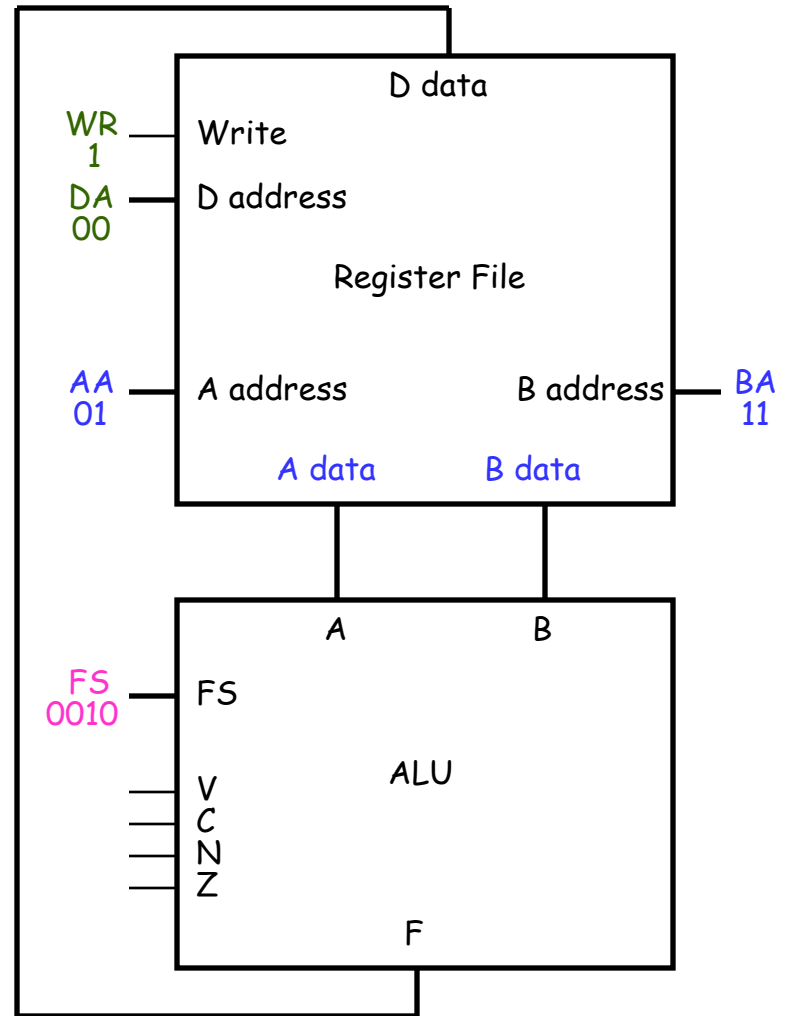- Set $AA = 01$ and $BA = 11$. This causes the contents of R1 to appear at **A data**, and the contents of R3 to appear at **B data**.
- Set the ALU's function select input $FS = 0010$ ($A + B$).
- Set $DA = 00$ and $WR = 1$. On the next positive clock edge, the ALU result ($R1 + R3$) will be stored in R0.




Two questions

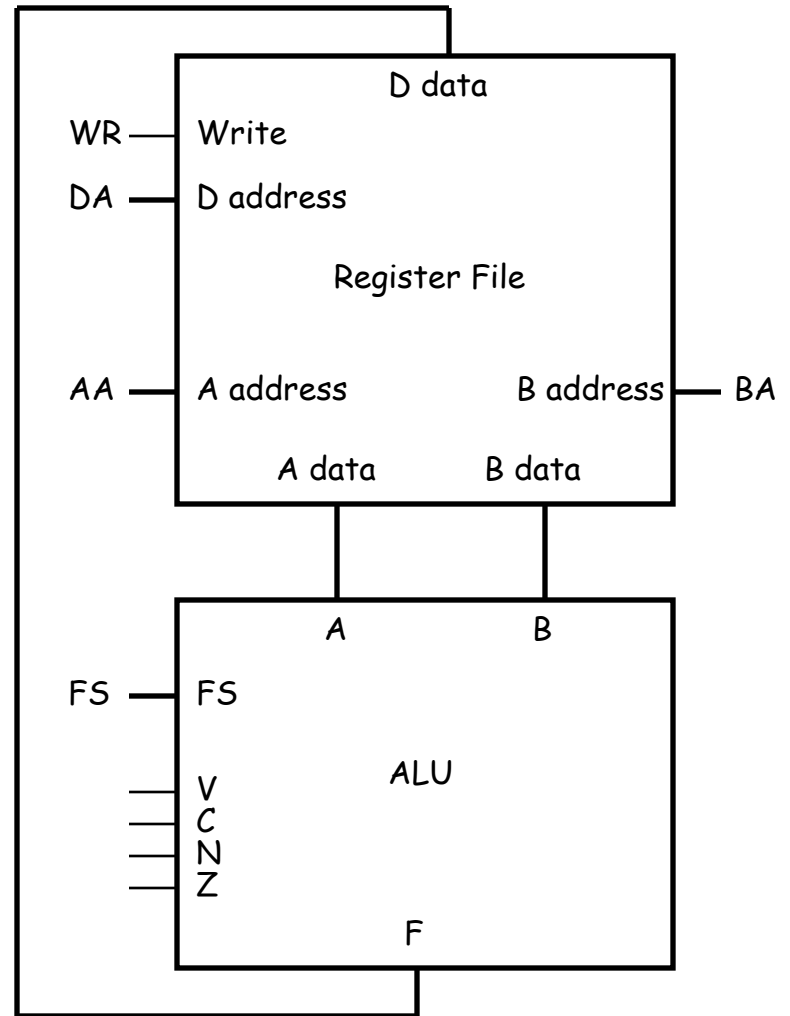- Four registers isn't a lot. What if we need more storage?
- Who exactly decides which registers are read and written and which ALU function is executed?




We can access RAM also

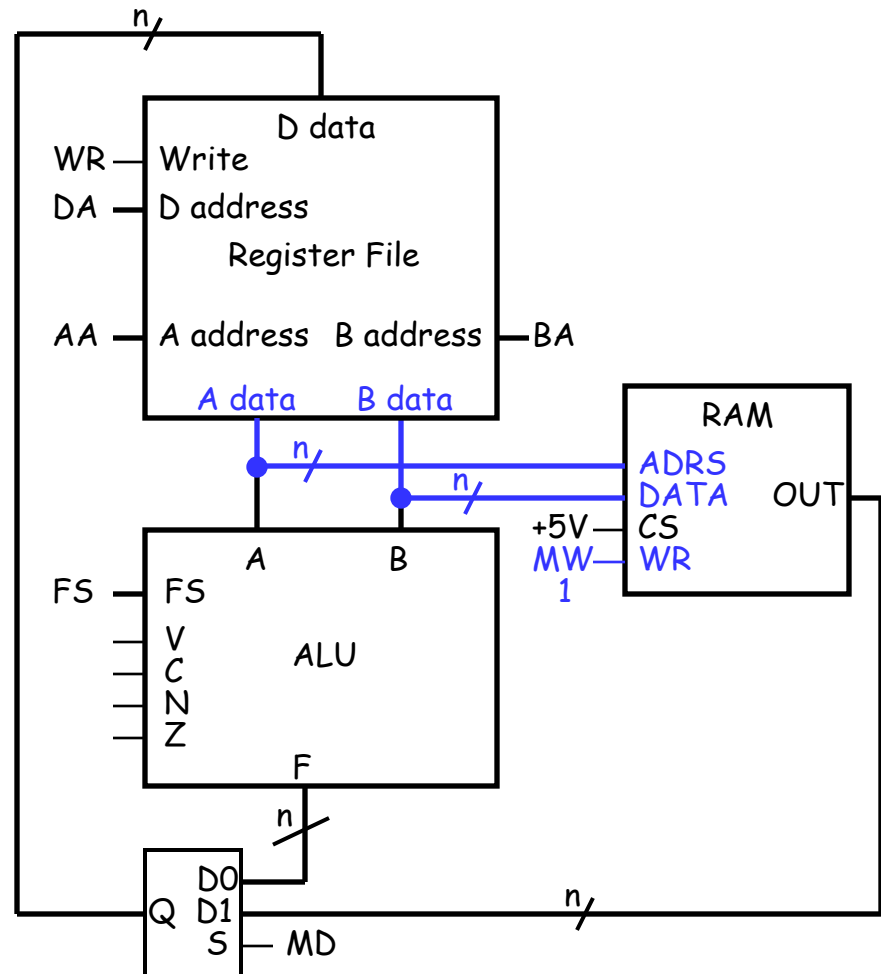- Here's a way to connect RAM into our existing datapath.
- To *write* to RAM, we must give an address and a data value.
- These will come from the registers. We connect **A data** to the memory's **ADRS** input, and **B data** to the memory's **DATA** input.
- Set **MW = 1** to write to the RAM. (It's called MW to distinguish it from the WR write signal on the register file.)




Reading from RAM

- To *read* from RAM, **A data** must supply the address.
- Set **MW = 0** for reading.
- The incoming data will be sent to the register file for storage.
- This means that the register file's **D data** input could come from *either* the ALU output or the RAM.
- A mux **MD** selects the source for the register file.
 - When **MD = 0**, the ALU output can be stored in the register file.
 - When **MD = 1**, the RAM output is sent to the register file instead.

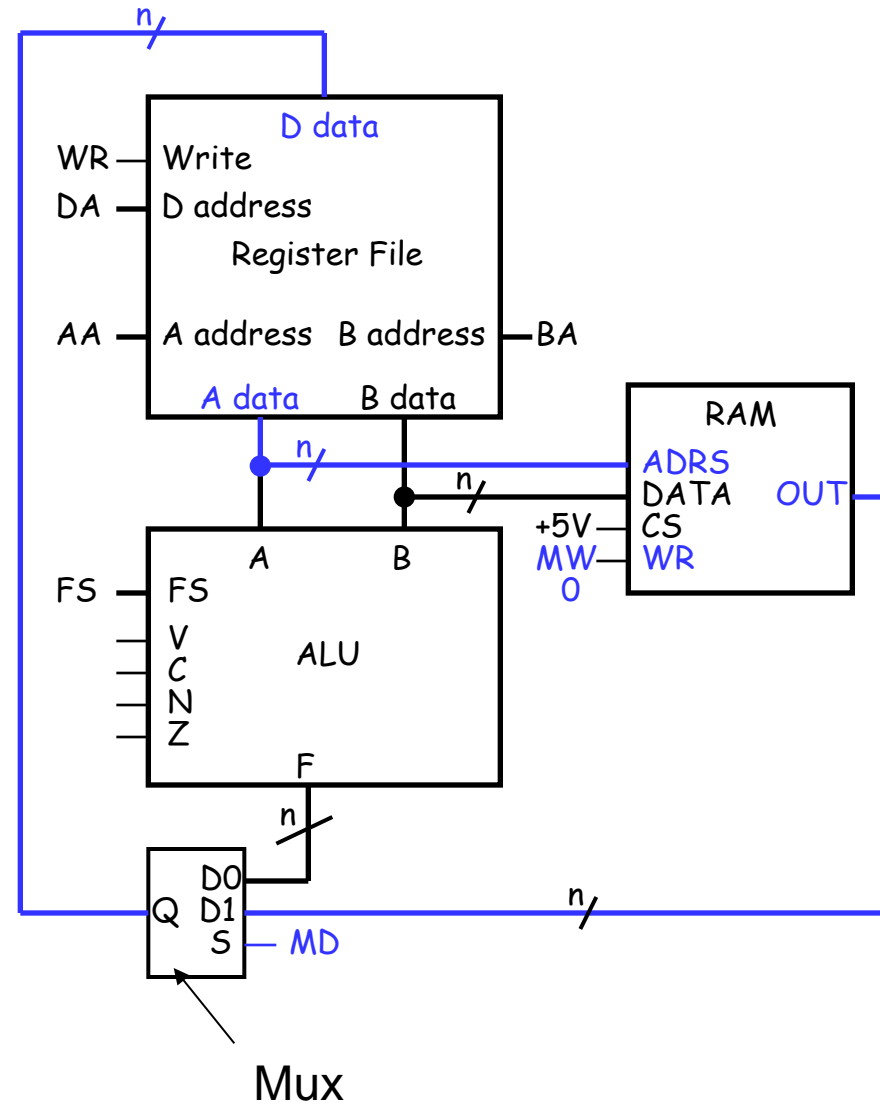


Notes about this setup

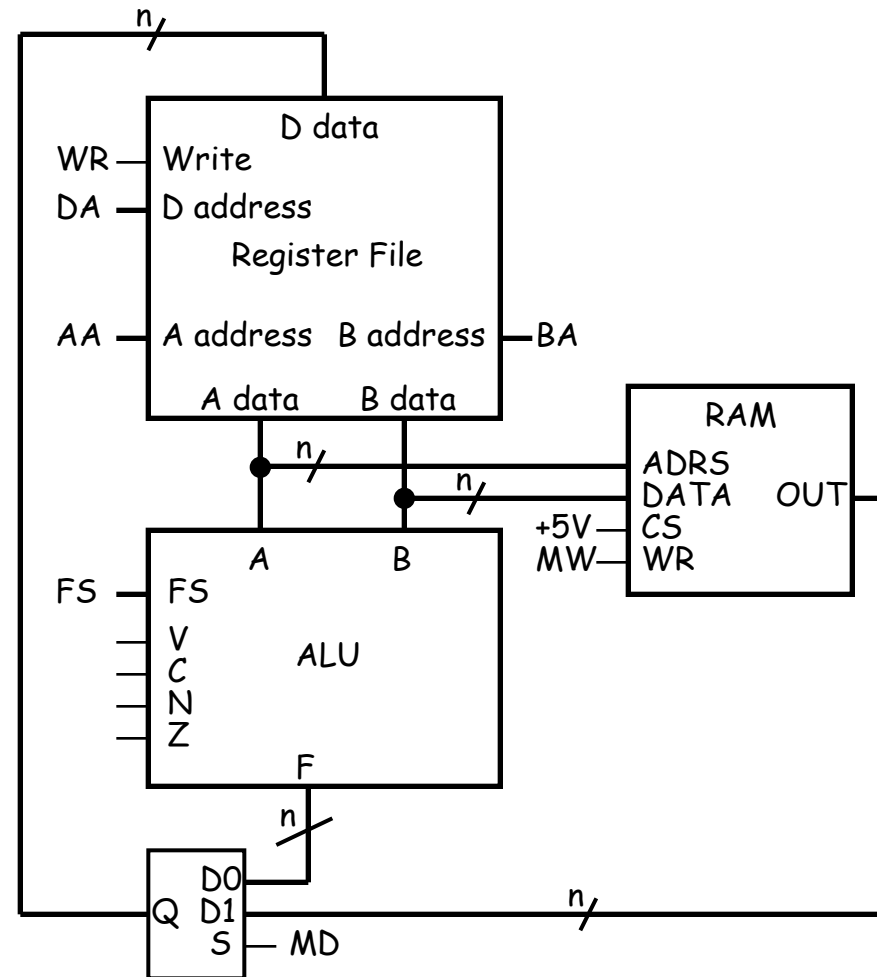- We now have a way to copy data between our register file and the RAM.
- Notice that there's no way for the ALU to directly access the memory—RAM contents *must* go through the register file first.
- Here the size of the memory is limited by the size of the registers; with n -bit registers, we can only use a $2^n \times n$ RAM.



Memory transfer notation

 - In our transfer language, the contents at random access memory address X are denoted $M[X]$. For example:
 - The first word in RAM is $M[0]$.
 - If register $R1$ contains an address, then $M[R1]$ are the contents of that address.
- The $M[]$ notation is like a pointer dereference operation in C or C++.



Example sequence of operations

- Here is a simple series of register transfer instructions:

$M[R0] \leftarrow M[R0] + 1 =$

$R3 \leftarrow M[R0]$


$R3 \leftarrow R3 + 1$

$M[R0] \leftarrow R3$

- This just increments the contents at address R0 in RAM.
 - Again, our ALU only operates on registers, so the RAM contents must first be loaded into a register, and then saved back to RAM.
 - R0 is the first register in our register file. We'll assume it contains a valid memory address.
- How would these instructions execute in our datapath?


$$R3 \leftarrow R3 + 1$$

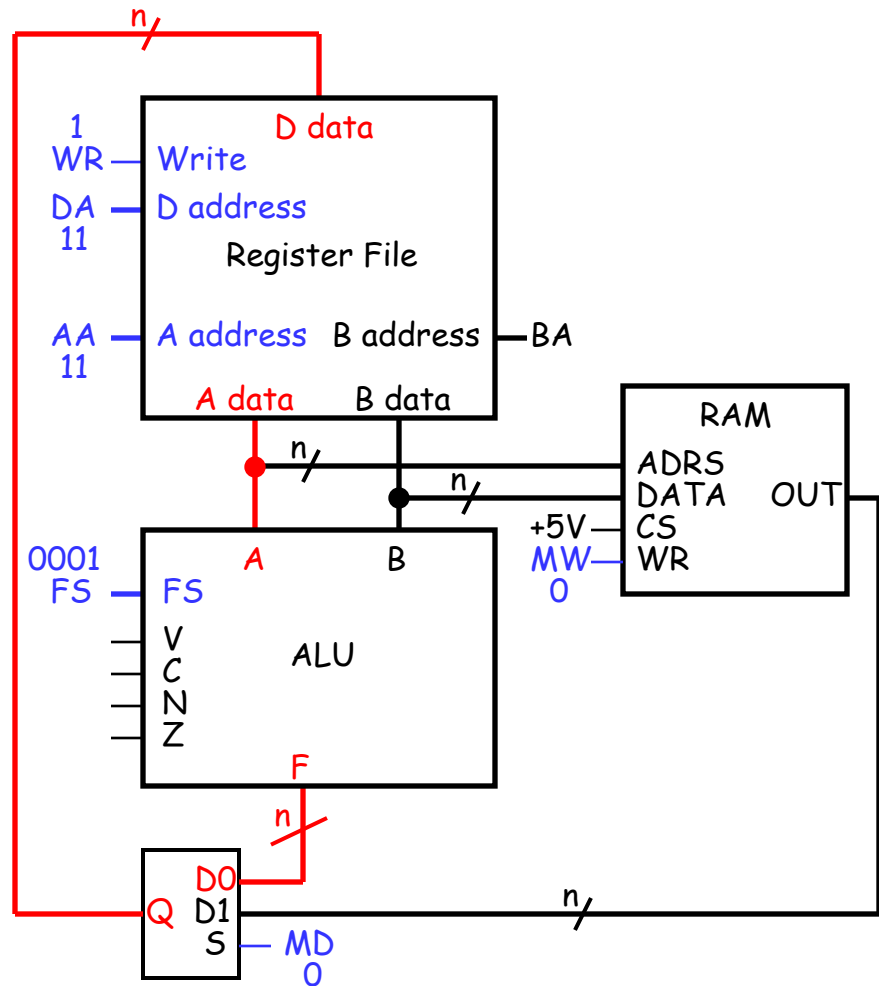- $AA = 11$, so R3 is read from the register file and sent to the ALU's A input.
- FS needs to be 0001 for the operation $A + 1$. Then, $R3 + 1$ appears as the ALU output F .
- If MD is set to 0, this output will go back to the register file.
- To write to R3, we need to make $DA = 11$ and $WR = 1$.
- Again, MW should be 0 so the RAM isn't inadvertently changed.
- We didn't use BA.



M[R0] ← R3


- Finally, we want to store the contents of R3 into RAM address R0.
- Remember the RAM address comes from “A data,” and the contents come from “B data.”
- So we have to set **AA = 00** and **BA = 11**. This sends R0 to ADRS, and R3 to DATA.
- **MW** must be 1 to write to memory.
- No register updates are needed, so **WR** should be 0, and MD and DA are unused.
- We also didn't use the ALU, so FS was ignored.

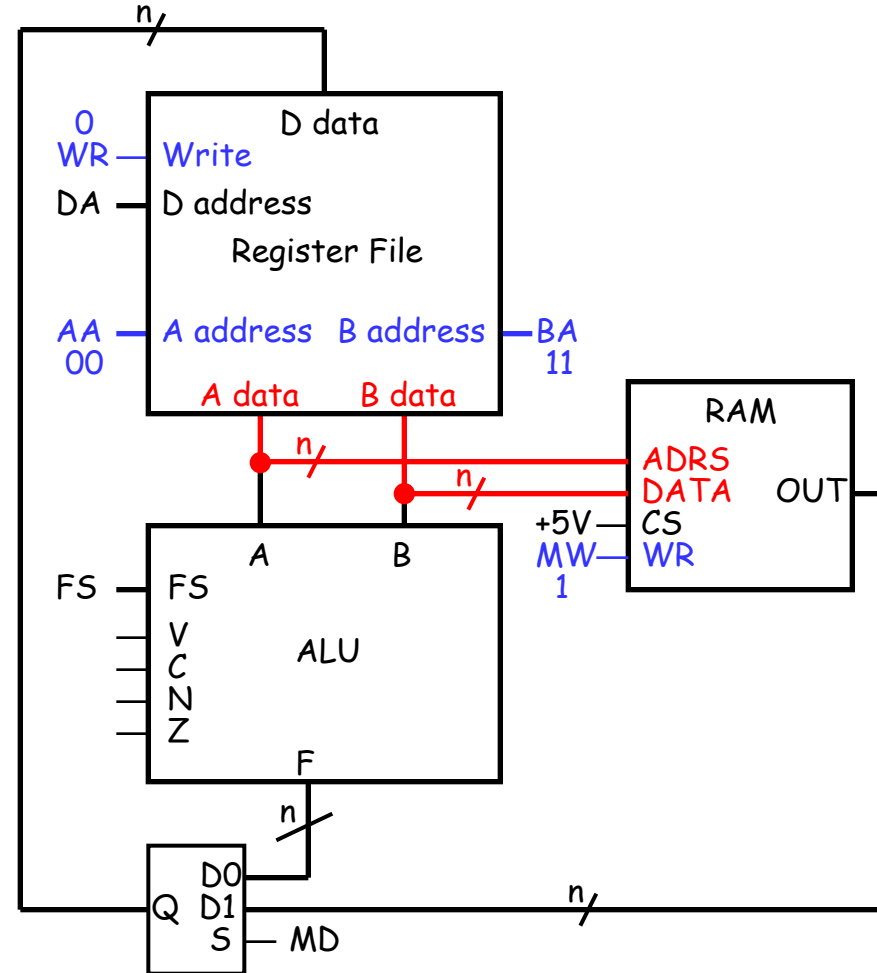

Constant in

- One last refinement is the addition of a **Constant** input.
- The modified datapath is shown on the right, with one extra control signal **MB**.
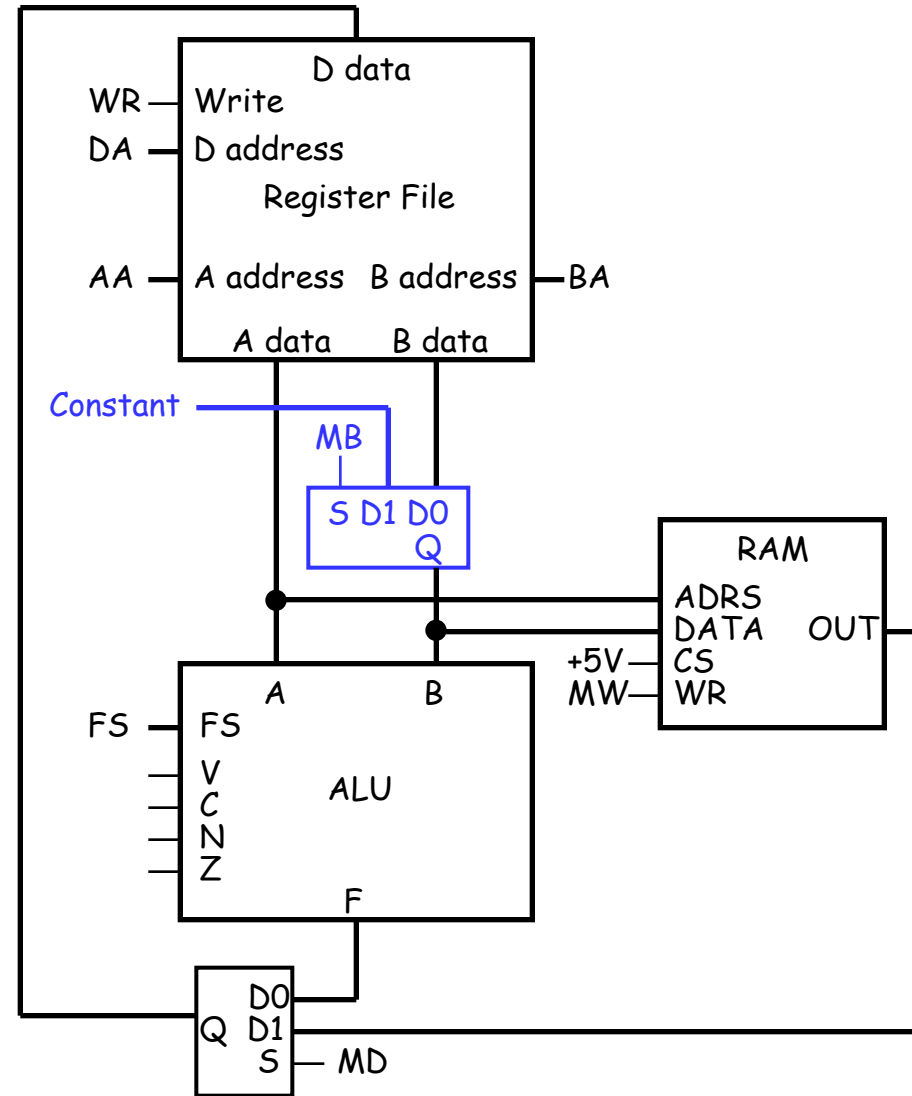
```
NOT R0, R1    R0 ← R1'  
ADD R3, R3, #1  R3 ← R3 + 1  
SUB R1, R2, #5  R1 ← R2 - 5
```



Summary

- The datapath is the part of a processor where computation is done.
 - The basic components are an ALU, a register file and some RAM.
 - The ALU does all of the computations, while the register file and RAM provide storage for the ALU's operands and results.
- Various control signals in the datapath govern its behavior.
- Next week, we'll see how programmers can give commands to the processor, and how those commands are translated in control signals for the datapath.