



College of Computer and Information Sciences  
Department of Computer Science

**CSC 220: Computer Organization**

# **Unit 3**

## **Logic Functions**



# Logic Functions

---

- ▶ Number of functions
  - ▶ With  $N$  logical variables, we can define  $2^N$  combination of inputs
  - ▶ A function relates outputs to inputs
  - ▶ Some of them are useful
    - ▶ AND, NAND, NOR, XOR, ...
  - ▶ Some are not useful:
    - ▶ Output is always 1
    - ▶ Output is always 0



# Logic Functions

---

- ▶ Logical functions can be expressed in several ways:
  - ▶ Truth table
  - ▶ Logical expressions
  - ▶ Graphical form
- ▶ **Example:**
  - ▶ Majority function
    - ▶ Output is one whenever majority of inputs is 1
    - ▶ We use 3-input majority function




# Logic Functions (cont.)

3-input majority function

<b>A</b>	<b>B</b>	<b>C</b>	<b>F</b>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

▶ Logical expression form


$$F = A B + B C + A C$$

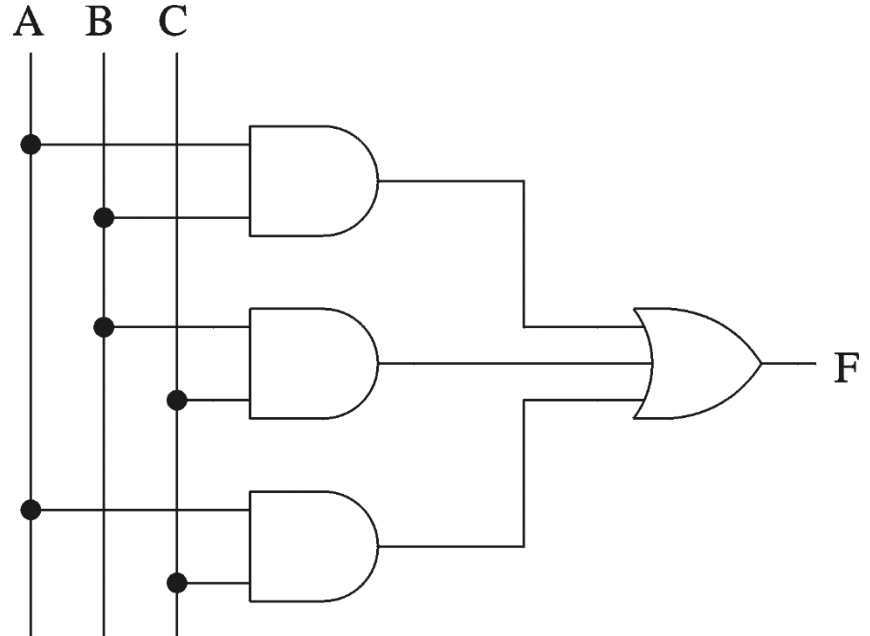

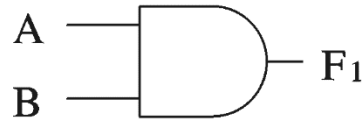
# Logical Equivalence

---


- ▶ All three circuits implement  $F = A B$  function



(a)

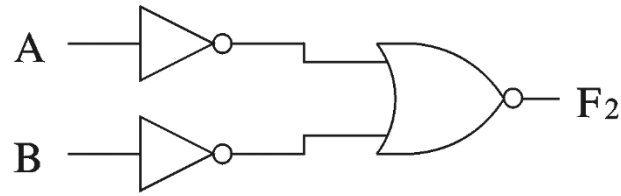


(b)

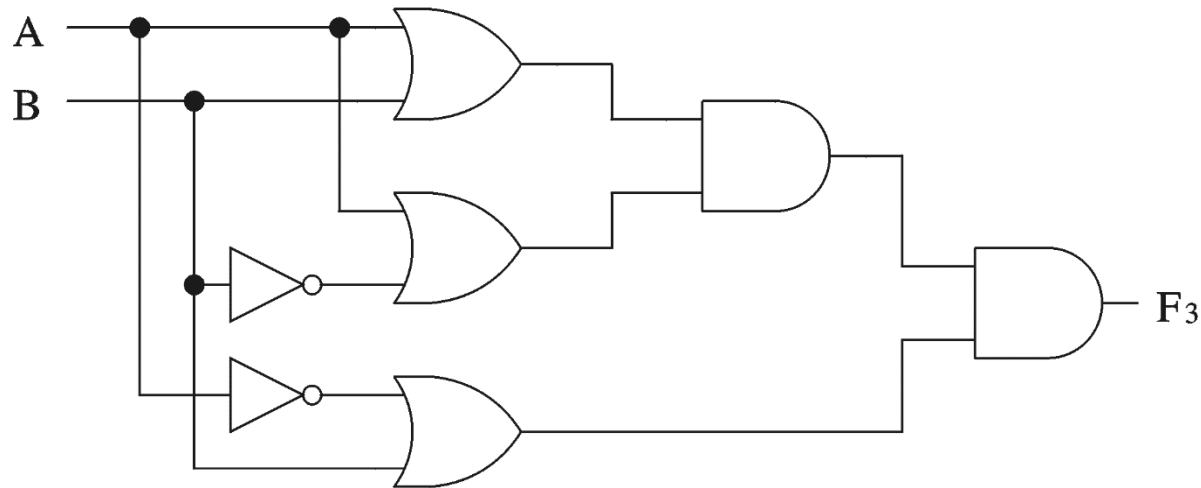

(c)
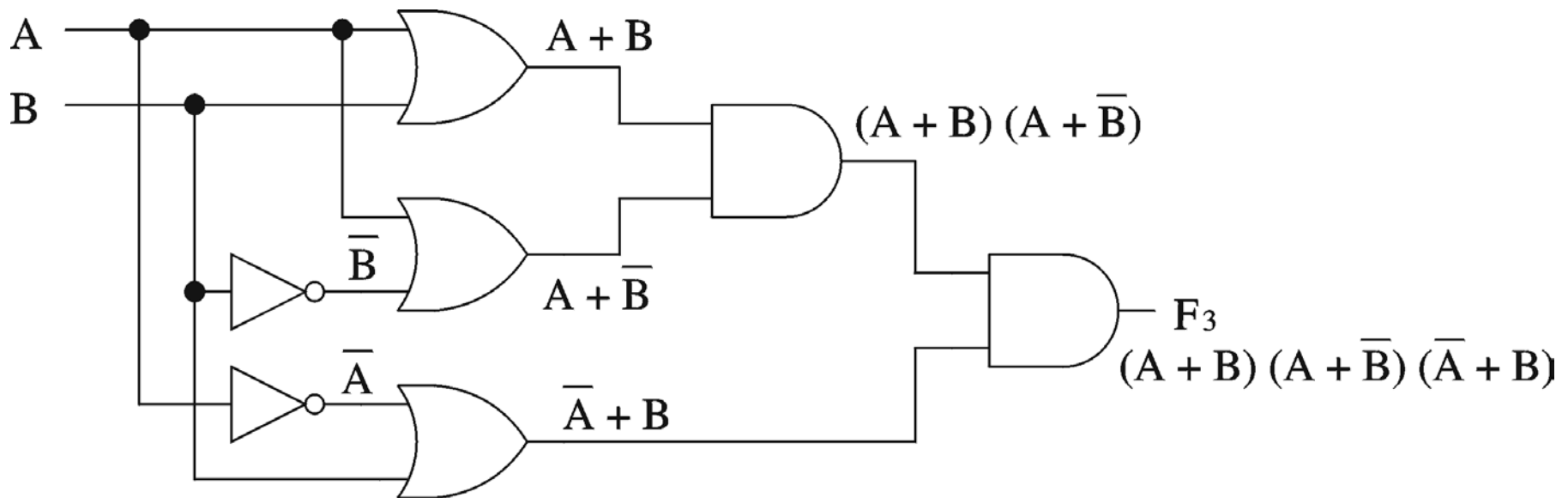
# Logical Equivalence

- ▶ Derivation of logical expression from a circuit
  - ▶ Trace from the input to output
  - ▶ Write down intermediate logical expressions along the path



# Logical Equivalence (cont.)

---

- ▶ Proving logical equivalence: Truth table method

<b>A</b>	<b>B</b>	<b>F1 = A B</b>	<b>F3 = (A + B) (<math>\bar{A}</math> + B) (A + <math>\bar{B}</math>)</b>
<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>
<b>0</b>	<b>1</b>	<b>0</b>	<b>0</b>
<b>1</b>	<b>0</b>	<b>0</b>	<b>0</b>
<b>1</b>	<b>1</b>	<b>1</b>	<b>1</b>



- 
- ▶ **Digital logic function :**
    - ▶ **SOP and POS forms**





# Standard Forms for Boolean Expressions

---

- Sum-of-Products (SOP)
  - Derived from the Truth table for a function by considering those rows for which  $F = 1$ .
  - The logical sum (OR) of product (AND) terms.
  - Realized using an AND-OR circuit.
- Product-of-Sums (POS)
  - Derived from the Truth table for a function by considering those rows for which  $F = 0$ .
  - The logical product (AND) of sum (OR) terms.
  - Realized using an OR-AND circuit.



# Sum-of-Products (SOP)




# 1 Sum of products expressions

- There are many equivalent ways to write a function, but some forms turn out to be more useful than others.
- A **sum of products** or **SOP** expression consists of:
  - One or more terms *summed* (OR'ed) together.
  - Each of those terms is a *product of literals*.

$$f(x, y, z) = y' + x'yz' + xz$$

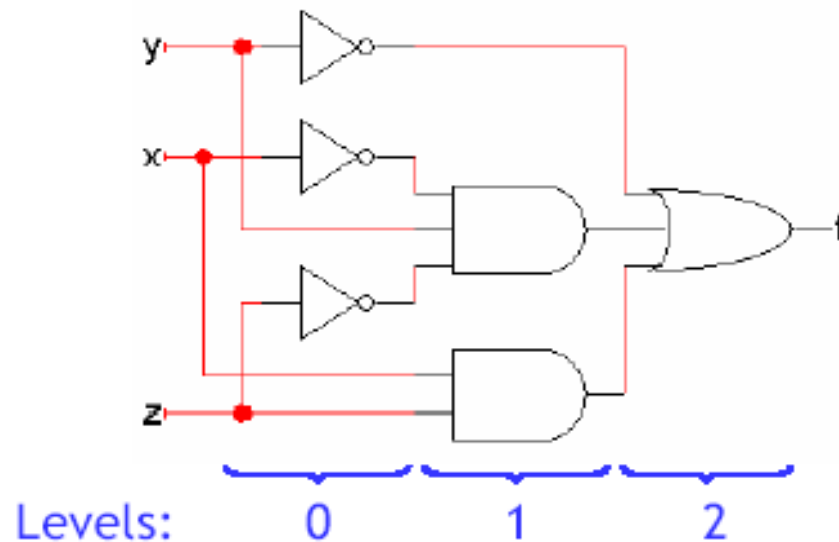- Sum of products expressions can be implemented with **two-level circuits**.




# Minterms

- A **minterm** is a special product of literals, in which each input variable appears exactly once.
- A function with  $n$  input variables has  $2^n$  possible minterms.
- For instance, a three-variable function  $f(x,y,z)$  has 8 possible minterms:

$$\begin{array}{cccc} x'y'z' & x'y'z & x'y z' & x'y z \\ x y'z' & x y'z & x y z' & x y z \end{array}$$

- Each minterm is true for exactly one combination of inputs.

Minterm	True when	Shorthand
$x'y'z'$	$xyz = 000$	$m_0$
$x'y'z$	$xyz = 001$	$m_1$
$x'y z'$	$xyz = 010$	$m_2$
$x'y z$	$xyz = 011$	$m_3$
$x y'z'$	$xyz = 100$	$m_4$
$x y'z$	$xyz = 101$	$m_5$
$x y z'$	$xyz = 110$	$m_6$
$x y z$	$xyz = 111$	$m_7$

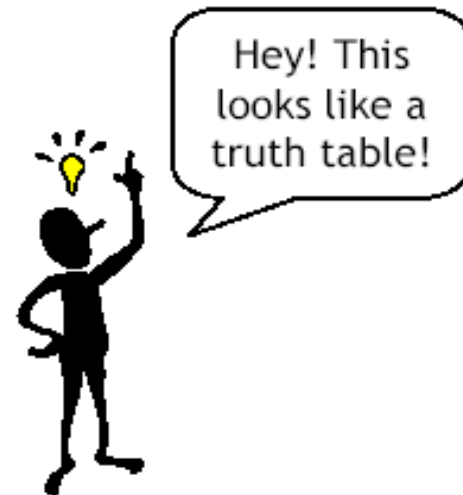

# Minterms

Row number	$x_1$	$x_2$	$x_3$	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1\bar{x}_2\bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1\bar{x}_2x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1x_2\bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1x_2x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1\bar{x}_2\bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1\bar{x}_2x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1x_2\bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1x_2x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$



---

# Sum-of-Products

- Any function  $F$  can be represented by a sum of minterms, where each minterm is ANDed with the corresponding value of the output for  $F$ .

- $F = \sum (m_i \cdot f_i)$

- where  $m_i$  is a minterm

- and  $f_i$  is the corresponding functional output

Denotes the logical  
sum operation

- Only the minterms for which  $f_i = 1$  appear in the expression for function  $F$ .

shorthand notation

- $F = \sum (m_i) = \sum m(i)$



# Sum of minterms expressions

- A **sum of minterms** is a special kind of sum of products.
- Every function can be written as a *unique* sum of minterms expression.
- A truth table for a function can be rewritten as a sum of minterms just by finding the table rows where the function output is 1.

x	y	z	C(x,y,z)	C'(x,y,z)
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$$\begin{aligned}C &= x'yz + xy'z + xyz' + xyz \\ &= m_3 + m_5 + m_6 + m_7 \\ &= \Sigma m(3,5,6,7)\end{aligned}$$

$$\begin{aligned}C' &= x'y'z' + x'y'z + x'yz' + xy'z' \\ &= m_0 + m_1 + m_2 + m_4 \\ &= \Sigma m(0,1,2,4)\end{aligned}$$

C' contains all the minterms *not* in C, and vice versa.

---

# Sum-of-Products

- Sum of minterms are a.k.a. Canonical Sum-of-Products
- Synthesis process
  - Determine the Canonical Sum-of-Products
  - Use Boolean Algebra (and K-maps) to find an optimal, functionally equivalent, expression.





# Product-of-Sums (POS)




## 2 Product of sums expressions

- As you might expect, we can work with the duals of these ideas too.
- A **product of sums** or **POS** consists of:
  - One or more terms *multiplied* (AND'ed) together.
  - Each of those terms is a *sum of literals*.

$$g(x, y, z) = y'(x' + y + z')(x + z)$$

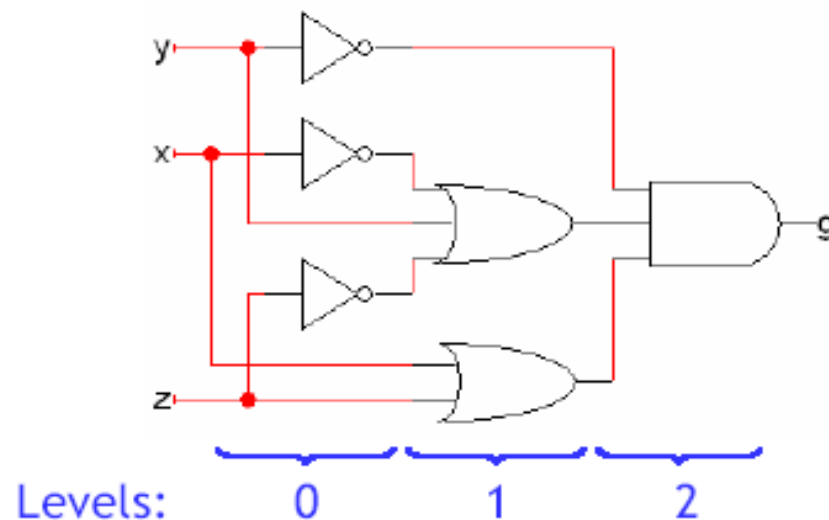- Products of sums can also be implemented with **two-level circuits**.



# Maxterms

- A **maxterm** is a *sum* of literals where each input variable appears once.
- A function with  $n$  input variables has  $2^n$  possible maxterms.
- For instance, a function with three variables  $x$ ,  $y$  and  $z$  has 8 possible maxterms:

$$\begin{array}{cccc} x + y + z & x + y + z' & x + y' + z & x + y' + z' \\ x' + y + z & x' + y + z' & x' + y' + z & x' + y' + z' \end{array}$$

- Each maxterm is *false* for exactly one combination of inputs.

Maxterm	False when	Shorthand
$x + y + z$	$xyz = 000$	$M_0$
$x + y + z'$	$xyz = 001$	$M_1$
$x + y' + z$	$xyz = 010$	$M_2$
$x + y' + z'$	$xyz = 011$	$M_3$
$x' + y + z$	$xyz = 100$	$M_4$
$x' + y + z'$	$xyz = 101$	$M_5$
$x' + y' + z$	$xyz = 110$	$M_6$
$x' + y' + z'$	$xyz = 111$	$M_7$



# Maxterms

Row number	$x_1$	$x_2$	$x_3$	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1\bar{x}_2\bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1\bar{x}_2x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1x_2\bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1x_2x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1\bar{x}_2\bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1\bar{x}_2x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1x_2\bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1x_2x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$



---

## Product-of-Sums

- Any function  $F$  can be represented by a product of Maxterms, where each Maxterm is ANDed with the *complement* of the corresponding value of the output for  $F$ .

- $F = \Pi (M_i \cdot f'_i)$

- where  $M_i$  is a Maxterm
- and  $f'_i$  is the complement of the corresponding functional output

Denotes the logical product operation

- Only the Maxterms for which  $f_i = 0$  appear in the expression for function  $F$ .

- $F = \Pi (M_i) = \Pi M(i)$

← shorthand notation



---

# Product-of-Sums

- The Canonical Product-of-Sums for function  $F$  is the Product-of-Sums expression in which each sum term is a Maxterm.
- Synthesis process
  - Determine the Canonical Product-of-Sums
  - Use Boolean Algebra (and K-maps) to find an optimal, functionally equivalent, expression.



# Product of maxterms expressions

- Every function can also be written as a unique **product of maxterms**.
- A truth table for a function can be rewritten as a product of maxterms just by finding the table rows where the function output is **0**.

x	y	z	C(x,y,z)	C'(x,y,z)
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$$\begin{aligned}
 C &= (x + y + z)(x + y + z') \\
 &\quad (x + y' + z)(x' + y + z) \\
 &= M_0 M_1 M_2 M_4 \\
 &= \prod M(0,1,2,4) \quad \text{When the o/p is Zero} \\
 &= \sum m(3,5,6,7) \quad \text{When the o/p is 1} \\
 C' &= (x + y' + z')(x' + y + z') \\
 &\quad (x' + y' + z)(x' + y' + z') \\
 &= M_3 M_5 M_6 M_7 \\
 &= \prod M(3,5,6,7)
 \end{aligned}$$

C' contains all the maxterms *not* in C, and vice versa.