



College of Computer and Information Sciences
Department of Computer Science


CSC 220: Computer Organization

Unit 5

COMBINATIONAL CIRCUITS-1

(Adder, Subtractor)


Combinational circuits

 

- So far we've only worked with **combinational circuits**, where applying the same inputs always produces the same outputs.
 - This corresponds to a mathematical function, where every input has a single, unique output.
 - In programming terminology, combinational circuits are similar to “functional programs” that do not contain variables and assignments.
- Such circuits are comparatively easy to design and analyze.

Binary addition by hand

 - You can add two binary numbers one column at a time starting from the right, just like you add two decimal numbers.
- But remember it's binary. For example, $1 + 1 = 10$ and you have to carry!



Adder

- Design an Adder for 1-bit numbers?
- **1. Specification:**
 - 2 inputs (X,Y)
 - 2 outputs (C,S)

Adder

- Design an Adder for 1-bit numbers?
- **1. Specification:**
2 inputs (X,Y)
2 outputs (C,S)
- **2. Formulation:**

| X | Y | C | S |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Adder

- Design an Adder for 1-bit numbers?

- **1. Specification:**


2 inputs (X,Y)

2 outputs (C,S)

- **2. Formulation:**

| X | Y | C | S |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |


- **3. Optimization/Circuit**

 

Half Adder

- This adder is called a Half Adder
- **Q: Why?**

| X | Y | C | S |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

 

Full Adder

- A combinational circuit that adds 3 input bits to generate a Sum bit and a Carry bit
- A truth table and sum of minterm equations for C and S are shown below.

| | X | Y | Z | C | S |
|--------------------|---|---|---|---|---|
| | 0 | 0 | 0 | 0 | 0 |
| | 0 | 0 | 1 | 0 | 1 |
| | 0 | 1 | 0 | 0 | 1 |
| $0 + 1 + 1 = 10$ → | 0 | 1 | 1 | 1 | 0 |
| | 1 | 0 | 0 | 0 | 1 |
| | 1 | 0 | 1 | 1 | 0 |
| | 1 | 1 | 0 | 1 | 0 |
| $1 + 1 + 1 = 11$ → | 1 | 1 | 1 | 1 | 1 |

$$C(X,Y,Z) = \Sigma m(3,5,6,7)$$

$$S(X,Y,Z) = \Sigma m(1,2,4,7)$$

Full Adder

- A combinational circuit that adds 3 input bits to generate a Sum bit and a Carry bit

| X | Y | Z | C | S |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

Sum

| | | YZ | | | |
|---|----|----|----|----|--|
| X | | | | | |
| | 00 | 01 | 11 | 10 | |
| 0 | 0 | 1 | 0 | 1 | |
| 1 | 1 | 0 | 1 | 0 | |

$$\begin{aligned}
 S &= X'Y'Z + X'YZ' \\
 &+ XY'Z' + XYZ \\
 &= X \oplus Y \oplus Z
 \end{aligned}$$

Carry

| | | YZ | | | |
|---|----|----|----|----|--|
| X | | | | | |
| | 00 | 01 | 11 | 10 | |
| 0 | 0 | 0 | 1 | 0 | |
| 1 | 0 | 1 | 1 | 1 | |

$$C = XY + YZ + XZ$$

Full Adder = 2 Half Adders

Manipulating the Equations:

$$S = X \oplus Y \oplus Z$$

$$C = XY + XZ + YZ$$

Full Adder = 2 Half Adders

Manipulating the Equations:

$$S = (X \oplus Y) \oplus Z$$

$$C = XY + XZ + YZ$$

$$= XY + XYZ + XY'Z + X'YZ + \cancel{XYZ}$$

$$= XY(1 + Z) + Z(XY' + X'Y)$$


$$= XY + Z(X \oplus Y)$$

Full Adder = 2 Half Adders

Manipulating the Equations:

$$S = (X \oplus Y) \oplus Z$$
 
$$C = XY + XZ + YZ = XY + Z(X \oplus Y)$$



Src: Mano's Book

Bigger Adders

- How to build an adder for n-bit numbers?
 - Example: 4-Bit Adder
 - Inputs ?
 - Outputs ?
 - What is the size of the truth table?
 - How many functions to optimize?

Bigger Adders

- How to build an adder for n-bit numbers?
 - Example: 4-Bit Adder
 - Inputs ? 9 inputs
 - Outputs ? 5 outputs
 - What is the size of the truth table? 512 rows!
 - How many functions to optimize? 5 functions


Binary Parallel Adder

- To add n-bit numbers:
- Use n Full-Adders in parallel
- The carries propagates as in addition by hand
- Use Z in the circuit as a C_{in}

- $$\begin{array}{r} 1\ 0\ 0\ 0 \\ 0\ 1\ 0\ 1 \\ 0\ 1\ 1\ 0 \\ \hline 1\ 0\ 1\ 1 \end{array}$$

Binary Parallel Adder

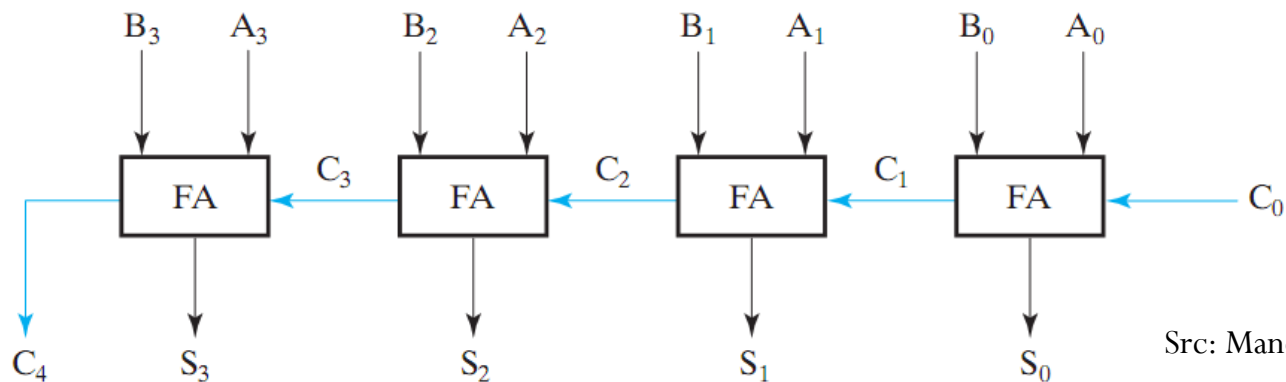- To add n-bit numbers:
- Use n Full-Adders in parallel
- The carries propagate as in addition by hand



Src: Mano's Book


This adder is called *ripple carry adder*

Subtraction (2's Complement)

- How to build a subtractor using 2's complement?

Subtraction (2's Complement)

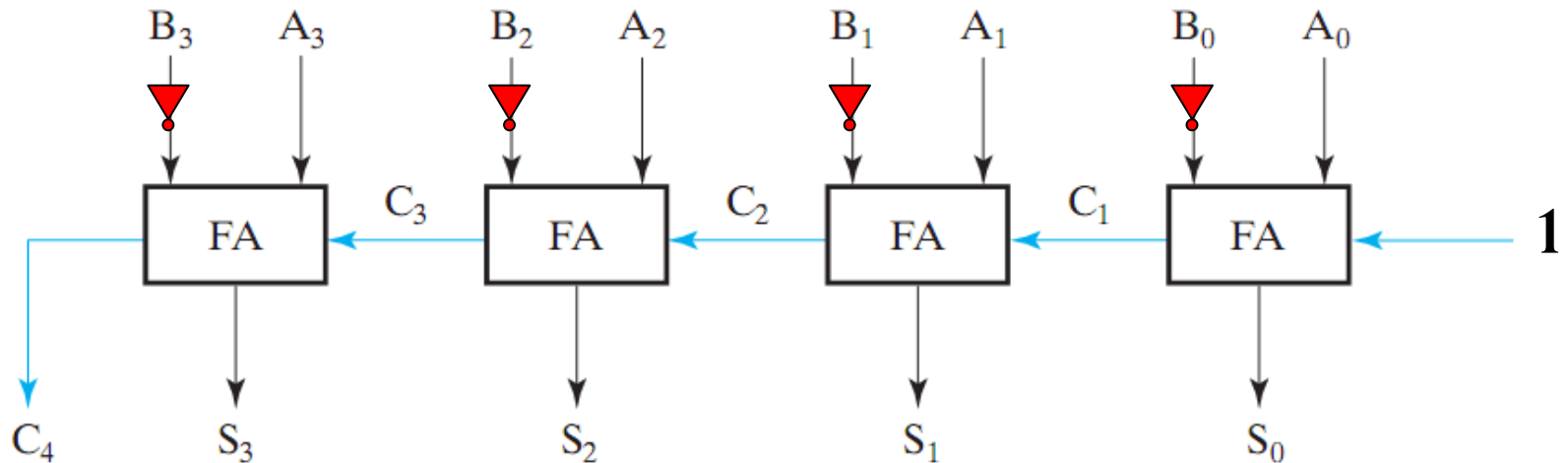- How to build a subtractor using 2's complement?




Src: Mano's Book

$$S = A + (-B)$$

Adder/Subtractor

- How to build a circuit that performs both addition and subtraction?

Adder/Subtractor

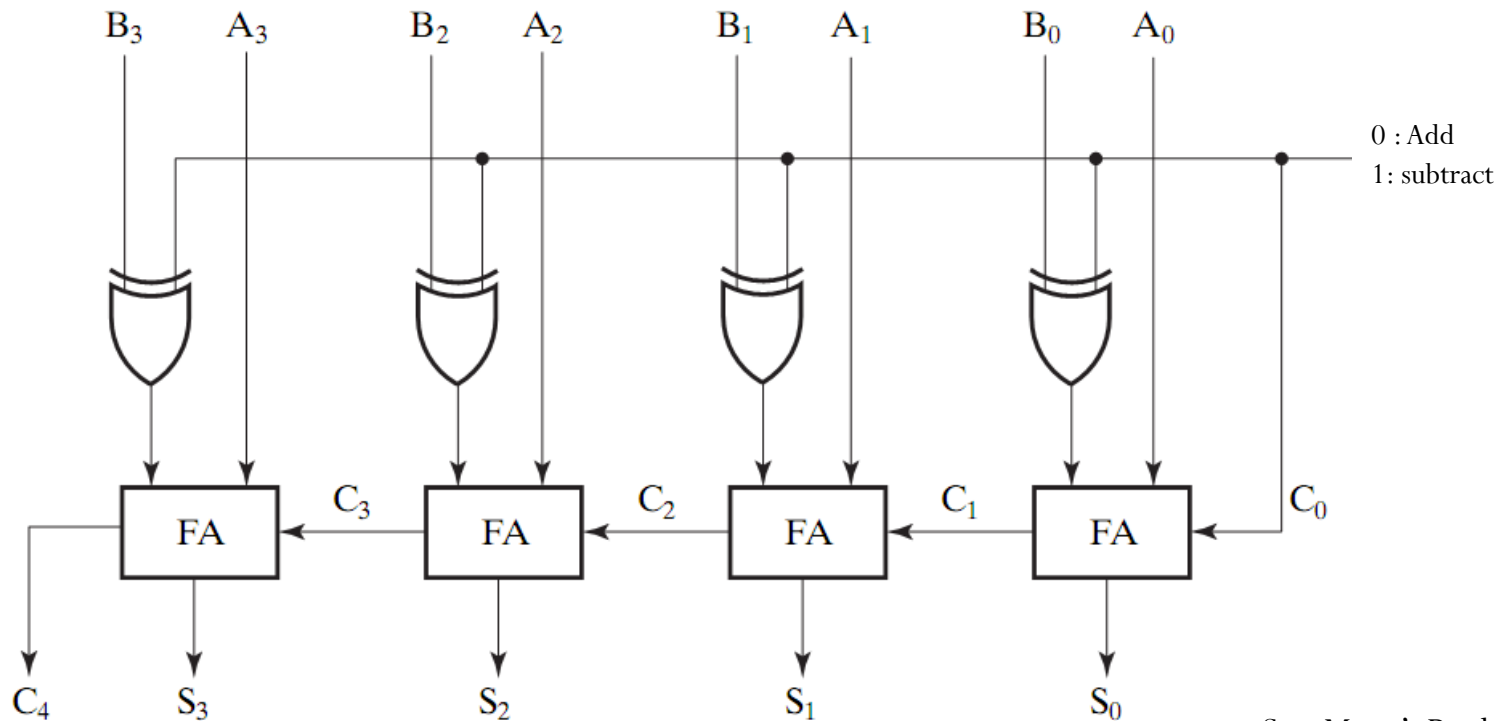


Src: Mano's Book

Using full adders and XOR we can build an Adder/Subtractor!

Binary Parallel Adder (Again)

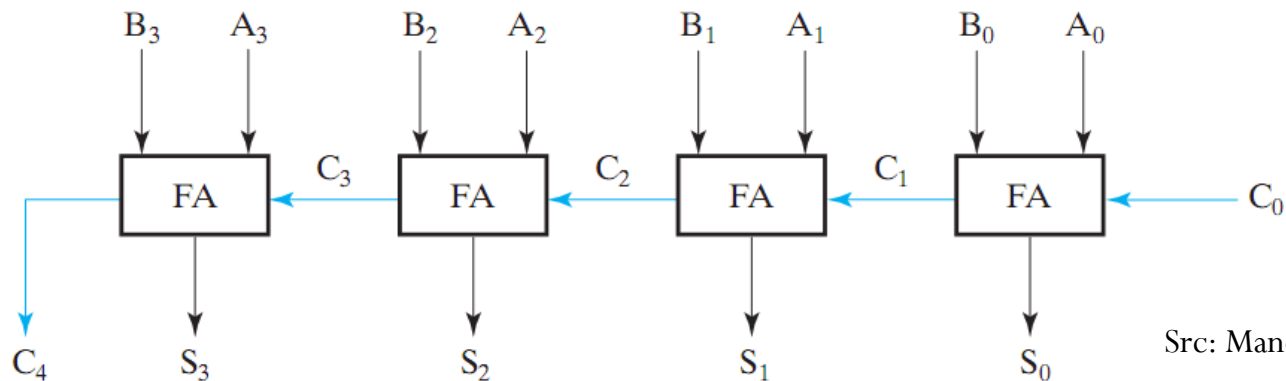- To add n-bit numbers:
- Use n Full-Adders in parallel
- The carries propagate as in addition by hand



Src: Mano's Book

This adder is called *ripple carry adder*

Carry Look Ahead Addder

- How to reduce propagation delay of ripple carry adders?
- **Carry look ahead adder:** All carries are computed as a function of C_0 (independent of n !)
- It works on the following standard principles:
 - A carry bit is generated when both input bits A_i and B_i are 1, or
 - When one of input bits is 1, and a carry in bit exists

