



College of Computer and Information Sciences  
Department of Computer Science

**CSC 220: Computer Organization**

# Unit 6

## **COMBINATIONAL CIRCUITS-2**


# Objectives

- Multiplexers
- DeMultiplexers
- Decoders
- Encoders
 
## A 2-to-1 multiplexer

---

- Here is the circuit analog of that printer switch.



- This is a **2-to-1 multiplexer**, or **mux**.
  - There are two **data inputs** **D0** and **D1**, and a **select input** called **S**.
  - There is one **output** named **Q**.
- The multiplexer routes one of its data inputs (D0 or D1) to the output Q, based on the value of S.
  - If  $S=0$ , the output will be D0.
  - If  $S=1$ , the output will be D1.

## Building a multiplexer

- Here is a truth table for the multiplexer, based on our description from the previous page:

The multiplexer routes one of its data inputs (D0 or D1) to the output Q, based on the value of S.


- If  $S=0$ , the output will be D0.
- If  $S=1$ , the output will be D1.

S	D1	D0	Q
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

- You can then find an MSP for the mux output Q.




 - Note that this corresponds closely to our English specification above—sometimes you can derive an expression without first making a truth table.


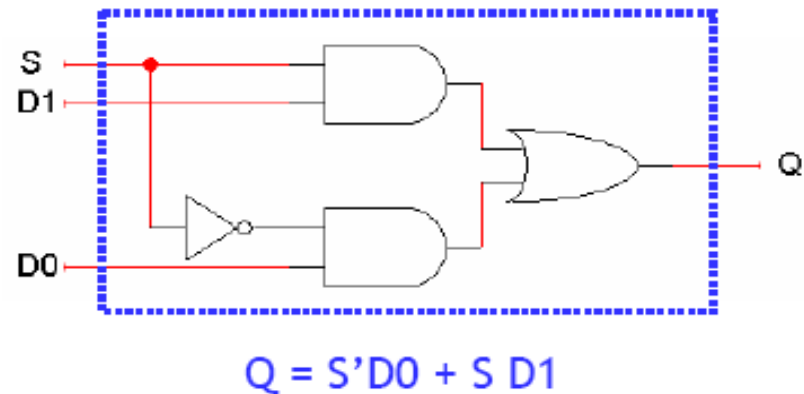
## Multiplexer circuit diagram

- Here is an implementation of a 2-to-1 multiplexer.



- Remember that a minimal sum of products expression leads to a minimal two-level circuit.

## Blocks, abstraction and modularity


---

- Multiplexers are common enough that we often want to treat them as abstract units or black boxes, as symbolized by our block diagrams.
  - Block symbols make circuit diagrams simpler, by hiding the internal implementation details. You can use a device without knowing how it's designed, as long as you know what it does.
  - Different multiplexer implementations should be interchangeable.
  - Circuit blocks also aid hardware re-use, since you don't have to keep building a multiplexer from scratch every time you need one.
- These blocks are similar to functions in programming languages!


 
## Enable inputs

- Many devices have an additional **enable input**, which “activates” or “deactivates” the device.
- We could design a 2-to-1 multiplexer with an enable input that’s used as follows.
  - EN=0 disables the multiplexer, which forces the output to be 0. (It does *not* turn off the multiplexer.)
  - EN=1 enables the multiplexer, and it works as specified earlier.
- Enable inputs are especially useful in combining smaller muxes together to make larger ones, as we’ll see later today.



EN	S	D1	D0	Q
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

## Truth table abbreviations

EN	S	D1	D0	Q
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1



- Notice that when EN=0, then Q is always 0, regardless of what S, D1 and D0 are set to.
- We can shorten the truth table by including Xs in the input variable columns, as shown on the bottom right.

EN	S	D1	D0	Q
0	x	x	x	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1



## Another abbr. 4 U

- Also, when EN=1 notice that if S=0 then Q=D0, but if S=1 then Q=D1.
- Another way to abbreviate a truth table is to list input variables in the output columns, as shown on the right.

EN	S	D1	D0	Q
0	x	x	x	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1




EN	S	Q
0	x	0
1	0	D0
1	1	D1

- This final version of the 2-to-1 multiplexer truth table is much clearer, and matches the equation  $Q = S'D0 + S D1$  very closely.
 
## A 4-to-1 multiplexer

- Here is a block diagram and abbreviated truth table for a 4-to-1 mux, which directs one of four different inputs to the single output line.
  - There are four data inputs, so we need *two* bits, **S1** and **S0**, for the mux selection input.
  - LogicWorks multiplexers have **active-low** enable inputs, so the mux always outputs 1 when  $EN' = 1$ . This is denoted on the block symbol with a bubble in front of EN.




EN'	S1	S0	Q
0	0	0	D0
0	0	1	D1
0	1	0	D2
0	1	1	D3
1	x	x	1

$$Q = S1'S0'D0 + S1'S0 D1 + S1 S0'D2 + S1 S0 D3$$
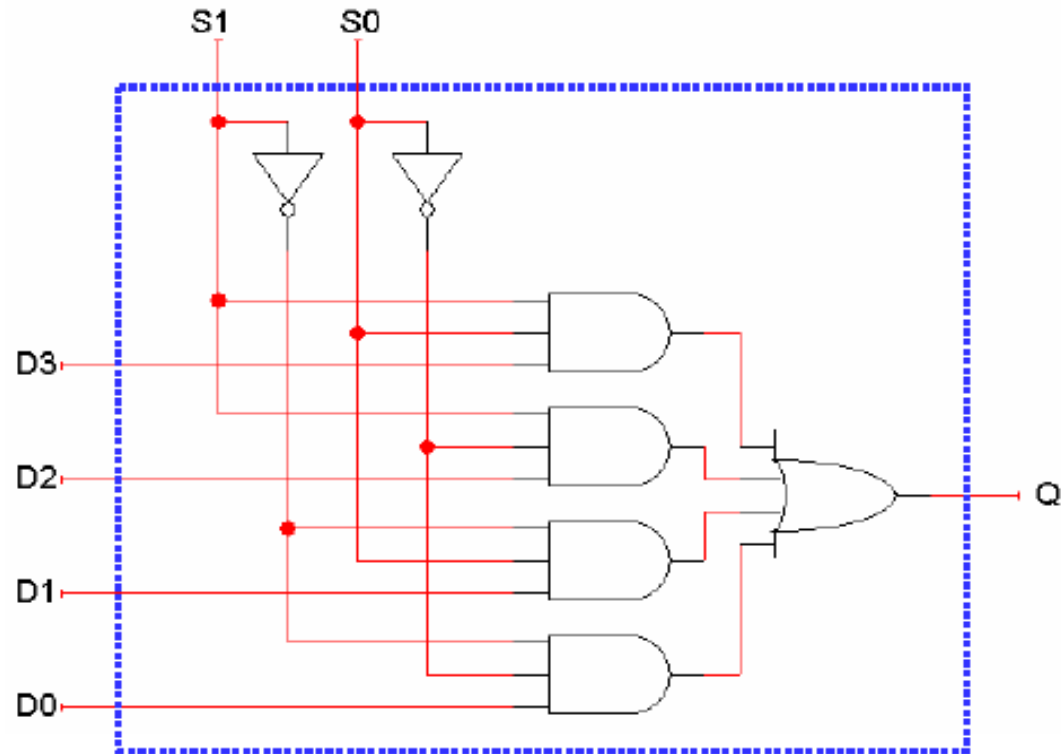
## A 4-to-1 multiplexer implementation


- Again we have a minimal sum of products expression, which leads to a minimal two-level circuit implementation.



$$Q = S1'S0'D0 + S1'S0 D1 + S1 S0'D2 + S1 S0 D3$$
 
## $2^n$ -to-1 multiplexers

- You can make even larger multiplexers, following the same pattern.
- A  $2^n$ -to-1 multiplexer routes one of  $2^n$  input lines to the output line.
  - There are  $2^n$  data inputs, so there must also be  $n$  select inputs.
  - The output is a single bit.
- Here is an 8-to-1 multiplexer, probably the biggest we'll see in this class.



# Implementing Functions with Multiplexers

## Example: addition

- Multiplexers can sometimes make circuit design easier.
- As an example, let's make a circuit to add three 1-bit inputs  $X$ ,  $Y$  and  $Z$ .
- We'll need two bits to represent the total.
  - The bits will be called  $C$  and  $S$ , standing for "carry" and "sum."
  - These are two separate functions of the inputs  $X$ ,  $Y$  and  $Z$ .
- A truth table and sum of minterm equations for  $C$  and  $S$  are shown below.

	X	Y	Z	C	S
	0	0	0	0	0
	0	0	1	0	1
	0	1	0	0	1
$0 + 1 + 1 = 10$ →	0	1	1	1	0
	1	0	0	0	1
	1	0	1	1	0
	1	1	0	1	0
$1 + 1 + 1 = 11$ →	1	1	1	1	1

$$C(X,Y,Z) = \sum m(3,5,6,7)$$


$$S(X,Y,Z) = \sum m(1,2,4,7)$$

	X	Y	Z	C	S
	0	0	0	0	0
	0	0	1	0	1
	0	1	0	0	1
$0 + 1 + 1 = 10$ →	0	1	1	1	0
	1	0	0	0	1
	1	0	1	1	0
	1	1	0	1	0
$1 + 1 + 1 = 11$ →	1	1	1	1	1

$$C(X,Y,Z) = \sum m(3,5,6,7)$$


$$S(X,Y,Z) = \sum m(1,2,4,7)$$

X	Y	Z	C
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 
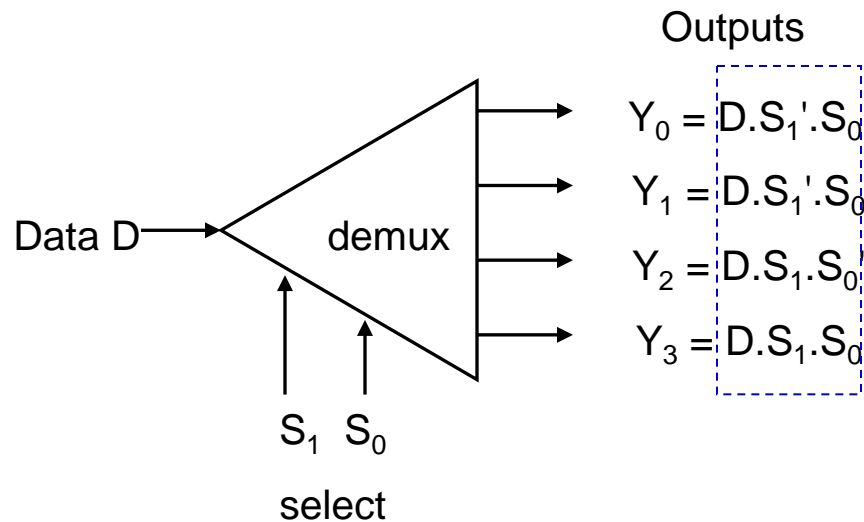
# Demultiplexer

- Given an input line and a set of selection lines, the demultiplexer will direct data from input to a selected output line.
- An example of a 1-to-4 demultiplexer:



$S_1$	$S_0$	$Y_0$	$Y_1$	$Y_2$	$Y_3$
0	0	D	0	0	0
0	1	0	D	0	0
1	0	0	0	D	0
1	1	0	0	0	D

# Demultiplexer

- Takes one input
- Out to one of  $2^n$  possible outputs

 



Fig. 3-24 1-to-4-Line Demultiplexer



# Decoder
 
## What a decoder does

- A  **$n$ -to- $2^n$  decoder** uses its  $n$ -bit input to determine which of  $2^n$  outputs will be uniquely activated.



S1	S0	Q0	Q1	Q2	Q3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

- Here is a block diagram and truth table for a **2-to-4 decoder**.
  - The two-bit input is called **S1S0**, and the four outputs are **Q0-Q3**.
  - If the input is the binary number  $i$ , then output  $Q_i$  alone will be true.
- This circuit “decodes” a binary number into a “one-of-four” code.

## Building a decoder

---

- We can use the truth table to derive minimal sum of products equations for each of the four outputs (Q0-Q3), based on the two inputs (S0-S1).

S1	S0	Q0	Q1	Q2	Q3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

- In this case there's not much to be simplified. Here are the equations:

$$Q0 = S1'S0'$$


$$Q1 = S1'S0$$

$$Q2 = S1 S0'$$


$$Q3 = S1 S0$$
 
# Decoder circuit diagram

- Here is an implementation of a 2-to-4 decoder.




S1	S0	Q0	Q1	Q2	Q3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

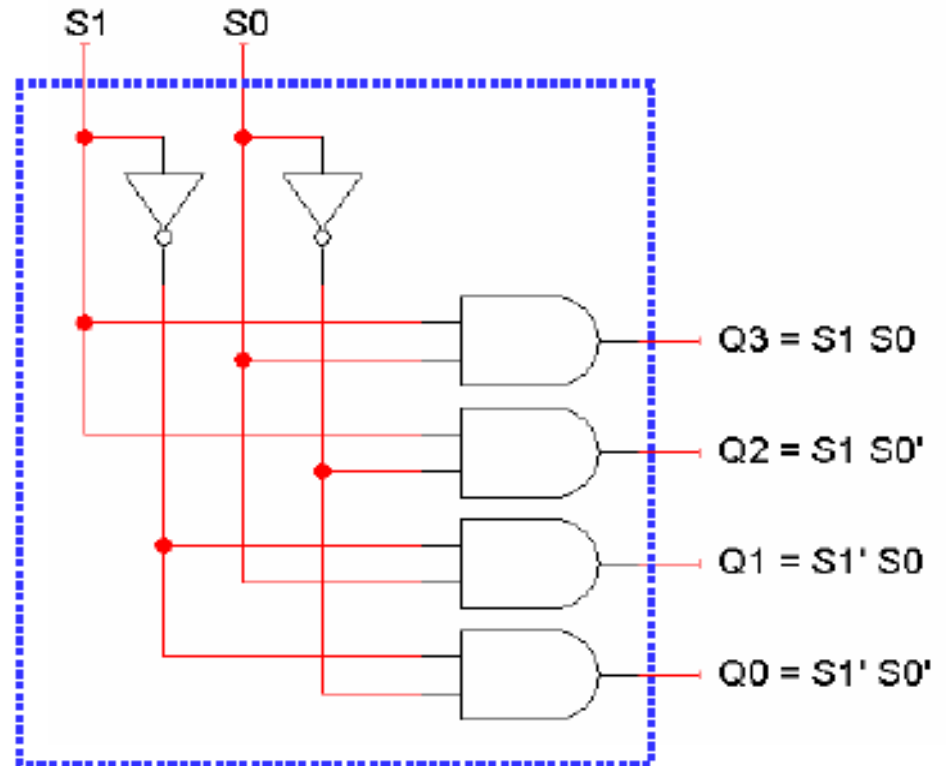
 
## Enable inputs

- Just as with multiplexers, decoders can include **enable inputs**.
  - **EN=0** disables the decoder, which by convention means that all of the decoder's outputs are 0.
  - **EN=1** enables the decoder so that it behaves as specified earlier, with exactly one of the outputs being 1.




EN	S1	S0	Q0	Q1	Q2	Q3
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

# Decoders with Enable (1/2)

- Decoders often come with an enable signal, so that the device is only activated when the enable,  $E=1$ .
- Truth table:


<b>E</b>	<b>X</b>	<b>Y</b>	<b>F<sub>0</sub></b>	<b>F<sub>1</sub></b>	<b>F<sub>2</sub></b>	<b>F<sub>3</sub></b>
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	X	X	0	0	0	0

- Circuit:

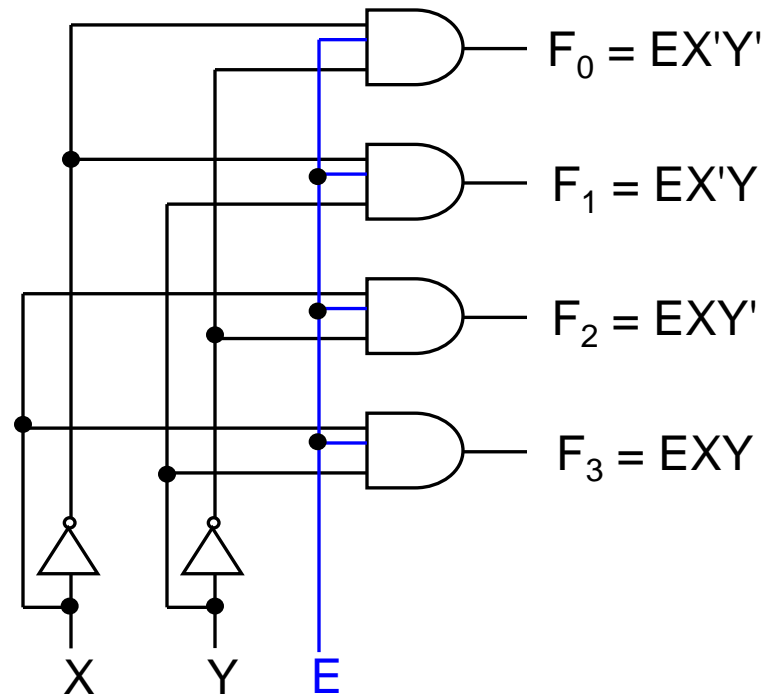

 
# Demultiplexer Vs Decoder

- The demultiplexer is actually identical to a decoder with enable, as illustrated below:



Exercise: Provide the truth table for above demultiplexer.
 
# A Demux Using NAND Gates: A Decoder with an Enable




(a) Logic diagram

$\bar{E}$	$A_1$	$A_0$	$\bar{D}_0$	$\bar{D}_1$	$\bar{D}_2$	$\bar{D}_3$
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	X	X	1	1	1	1
 
## A 3-to-8 decoder

- Larger decoders are similar. Here is a 3-to-8 decoder.
  - There are three selection inputs  $S_2S_1S_0$ , which activate one of eight outputs,  $Q_0-Q_7$ .
  - Again, only one output will be true for any input combination.
- A truth table and output equations for a 3-to-8 decoder (without EN) are given below.



$S_2$	$S_1$	$S_0$	$Q_0$	$Q_1$	$Q_2$	$Q_3$	$Q_4$	$Q_5$	$Q_6$	$Q_7$
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1


$$\begin{aligned}
 Q_0 &= S_2' S_1' S_0' \\
 Q_1 &= S_2' S_1' S_0 \\
 Q_2 &= S_2' S_1 S_0' \\
 Q_3 &= S_2' S_1 S_0 \\
 Q_4 &= S_2 S_1' S_0' \\
 Q_5 &= S_2 S_1' S_0 \\
 Q_6 &= S_2 S_1 S_0' \\
 Q_7 &= S_2 S_1 S_0
 \end{aligned}$$




 
# Decoder expansion


- Here's a 3-to-8 decoder built from two smaller 2-to-4 decoders.
- When  $S_2=0$ , the bottom 2-to-4 decoder is enabled and generates a 1 for one of outputs  $Q_0$ ,  $Q_1$ ,  $Q_2$  or  $Q_3$ .
- When  $S_2=1$ , the top 2-to-4 decoder is enabled instead, and a 1 will be output for either  $Q_4$ ,  $Q_5$ ,  $Q_6$  or  $Q_7$ .





S2	S1	S0	Q0	Q1	Q2	Q3	Q4	Q5	Q6	Q7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1
 
# Modularity



- You could verify that this circuit is a 3-to-8 decoder, by using equations for the 2-to-4 decoders to derive equations for the 3-to-8.
- Be careful not to confuse the “inner” inputs and outputs of the 2-to-4 decoders with the “outer” inputs and outputs of the 3-to-8 decoder.
- This is similar to having several functions in a program which all use a formal parameter “x”.





# Larger Decoders (2/6)

 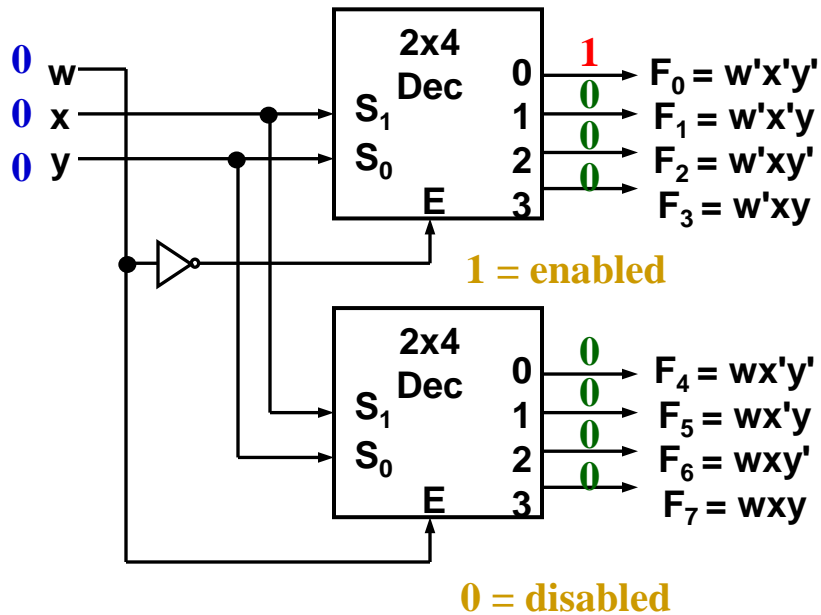

# Larger Decoders (3/6)

 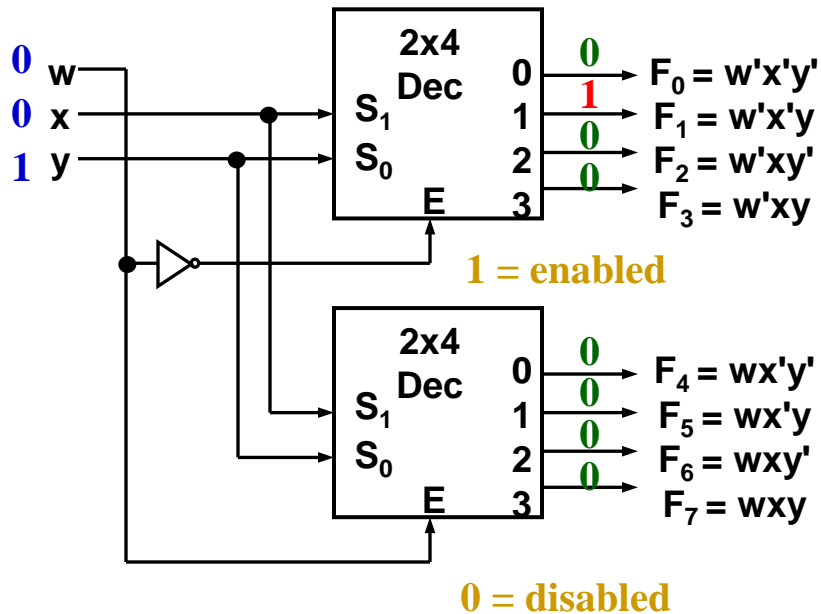



# Larger Decoders (4/6)

 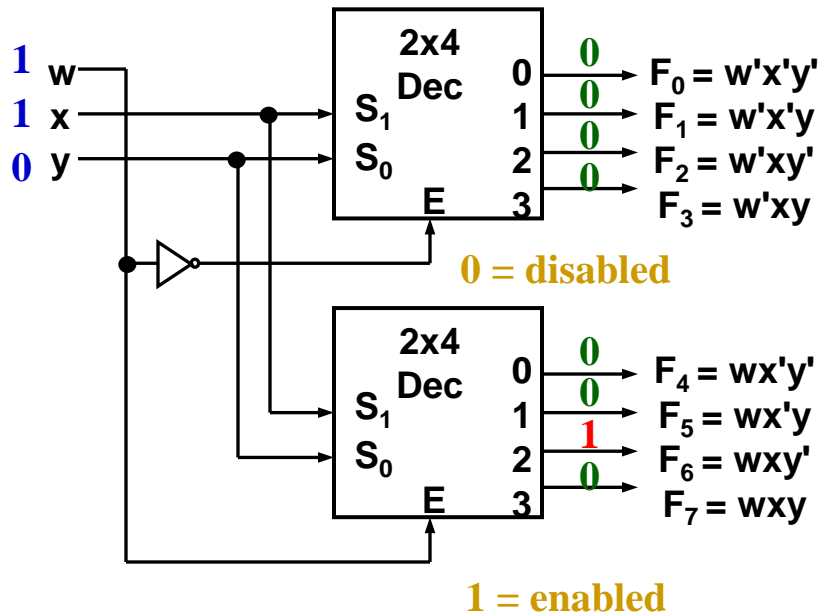
  
# Larger Decoders (5/6)

■ Question:

Construct a 4x16 decoder from two 3x8 decoders with 1-enable.



## So what good is a decoder?

---

- Do the truth table and equations look familiar?

S1	S0	Q0	Q1	Q2	Q3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

$$Q0 = S1'S0'$$

$$Q1 = S1'S0$$

$$Q2 = S1 S0'$$

$$Q3 = S1 S0$$

- Decoders are sometimes called **minterm generators**.
  - For each input combination, exactly one output is true.
  - Each output equation contains all of the input variables.
- This means that you can easily use a decoder, or a minterm generator, to implement any sum of minterms expression.



# Implementing Functions with Decoder

## Example: addition

- Yesterday we presented a simple circuit which added three 1-bit inputs  $X$ ,  $Y$  and  $Z$  to produce a two-bit output,  $C$  ("carry") and  $S$  ("sum").
- A truth table and sum of minterm equations for  $C$  and  $S$  are shown below.

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$C(X,Y,Z) = \Sigma m(3,5,6,7)$$

$$S(X,Y,Z) = \Sigma m(1,2,4,7)$$

- Today we'll implement these two functions using 3-to-8 decoders.

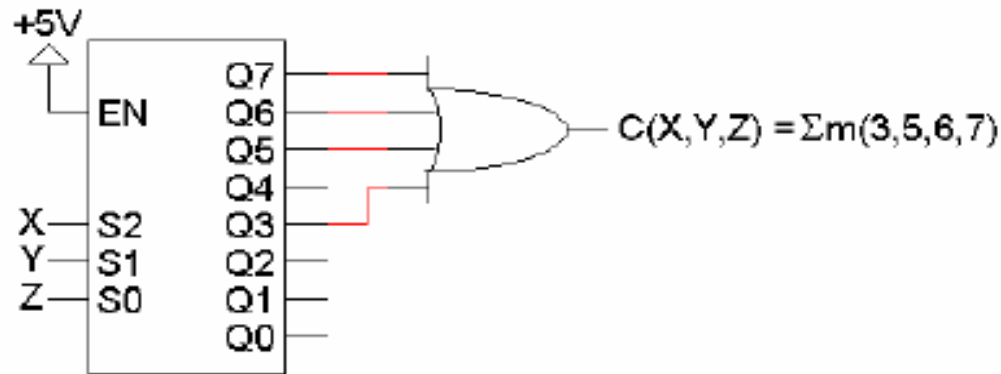
# Implementing functions with decoders

- Here, a 3-to-8 decoder implements  $C$  as a sum of minterms.



- If XYZ is 011, 101, 110 or 111, then one of the decoder outputs Q3, Q5, Q6 or Q7 will be true, and the output  $C(X,Y,Z)$  will also be true.
- The "+5V" symbol ("5 volts") represents a 1 or true in LogicWorks.


## Decoder-based sum

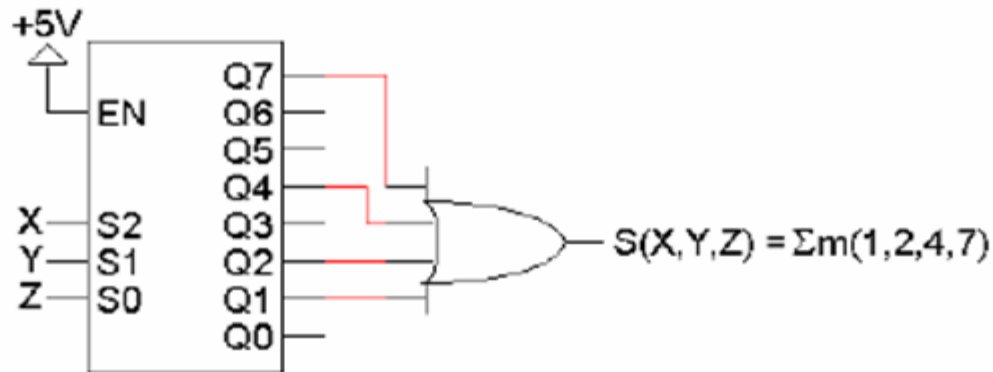

- If XYZ is 001, 010, 100 or 111, then one of decoder outputs Q1, Q2, Q4 or Q7 will be true, and  $S(X, Y, Z)$  will be true as well.
 
## Using just one decoder


- Since the two functions  $C$  and  $S$  both have the same inputs, we could use just one decoder instead of two.




- Decoder output  $Q_0$  is unused, while  $Q_7$  is used multiple times. In general, you can always use circuit outputs as many or as few times as you need.

# Decoders: Implementing Functions

## Example: Full adder

 

# Decoders: Implementing Functions

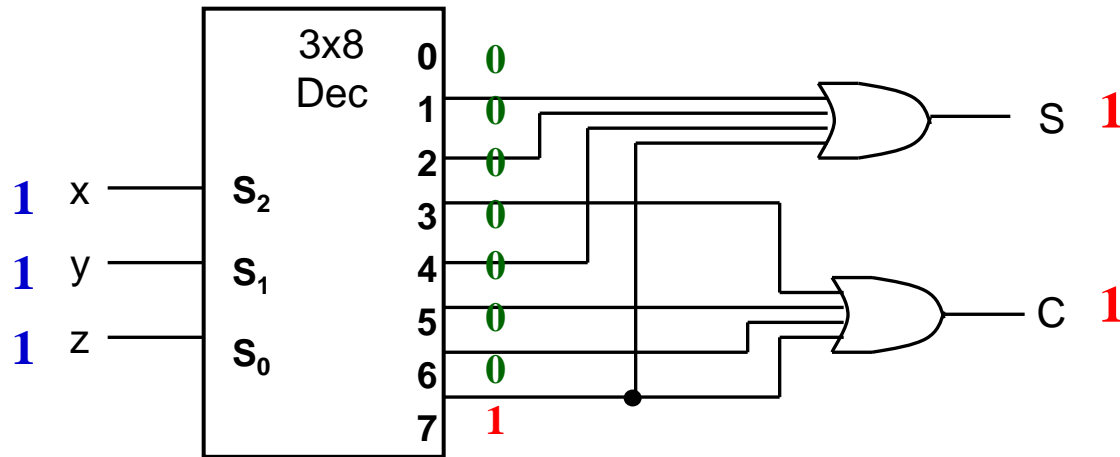


$x$	$y$	$z$	$C$	$S$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 - Example:

$$F(a,b,c) = \sum m(4,6,7)$$

- Using a 3×8 decoder (assuming 1-enable and active-high outputs).



# Encoder

- Encoder is the opposite of decoder
- $2^n$  inputs
  - or less – 10 inputs in “Decimal to BCD” encoder:  $I_0, I_1, I_2, I_3, \dots, I_9$
- n outputs
  - 4 output lines “Decimal to BCD”encoder



# Truth Table: 8-to-3 Binary Encoder

Inputs								Outputs		
$D_7$	$D_6$	$D_5$	$D_4$	$D_3$	$D_2$	$D_1$	$D_0$	$A_2$	$A_1$	$A_0$
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

# Inputs are Minterms

- Can OR the minterms appropriately to get each of the outputs

$A_0, A_1, A_2$

- Example:  $A_0 = D_1 + D_3 + D_5 + D_7$

Inputs								Outputs		
$D_7$	$D_6$	$D_5$	$D_4$	$D_3$	$D_2$	$D_1$	$D_0$	$A_2$	$A_1$	$A_0$
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

# Generating Outputs using OR of Minterms

- $A_0 = D_1 + D_3 + D_5 + D_7$
- $A_1 = D_2 + D_3 + D_6 + D_7$
- $A_2 = D_4 + D_5 + D_6 + D_7$

Inputs								Outputs		
$D_7$	$D_6$	$D_5$	$D_4$	$D_3$	$D_2$	$D_1$	$D_0$	$A_2$	$A_1$	$A_0$
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1