



College of Computer and Information Sciences  
Department of Computer Science

**CSC 220: Computer Organization**



# Unit 8

# Counters, RAM



# Asynchronous (Ripple) Counters

 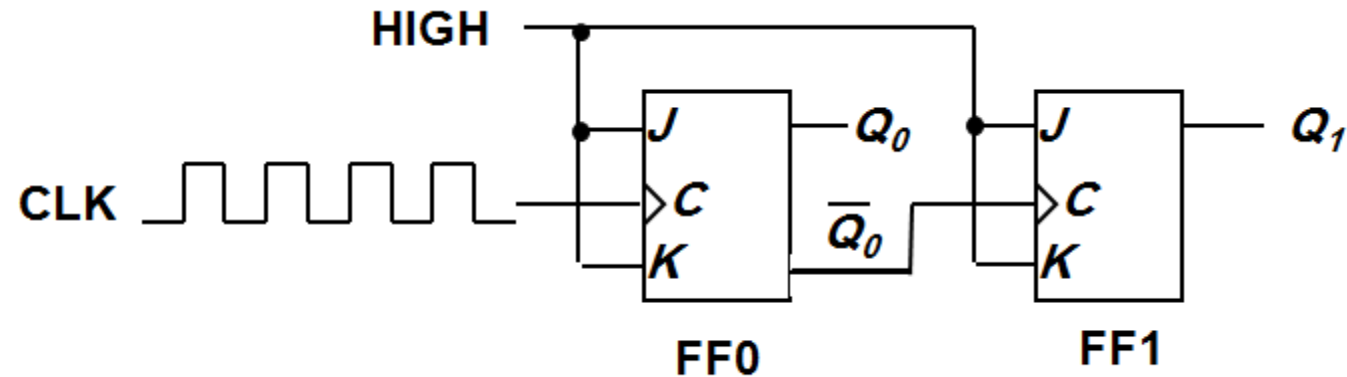- Example: 2-bit ripple binary counter.
- Output of one flip-flop is connected to the clock input of the next more-significant flip-flop.





Timing diagram

00 → 01 → 10 → 11 → 00 ...


# Asynchronous (Ripple) Counters

- Example: 3-bit ripple binary counter.

 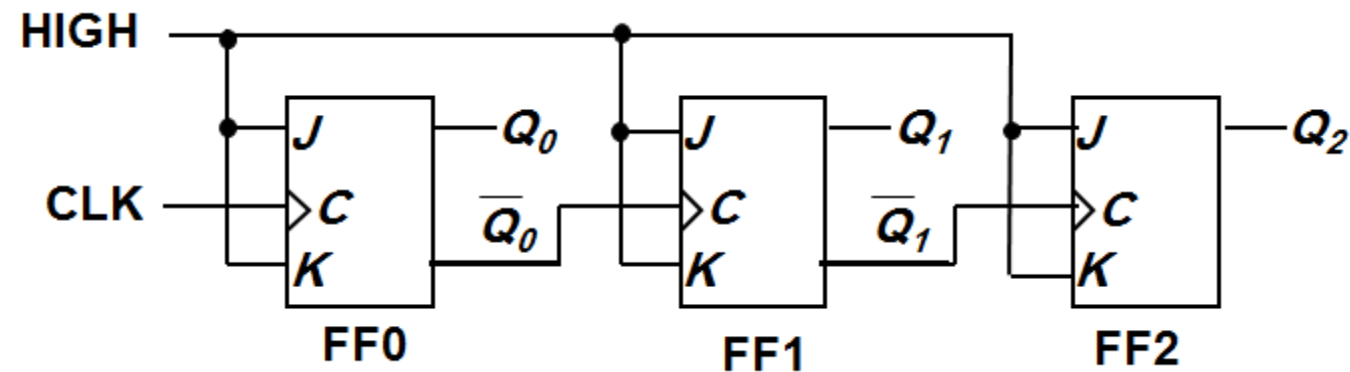


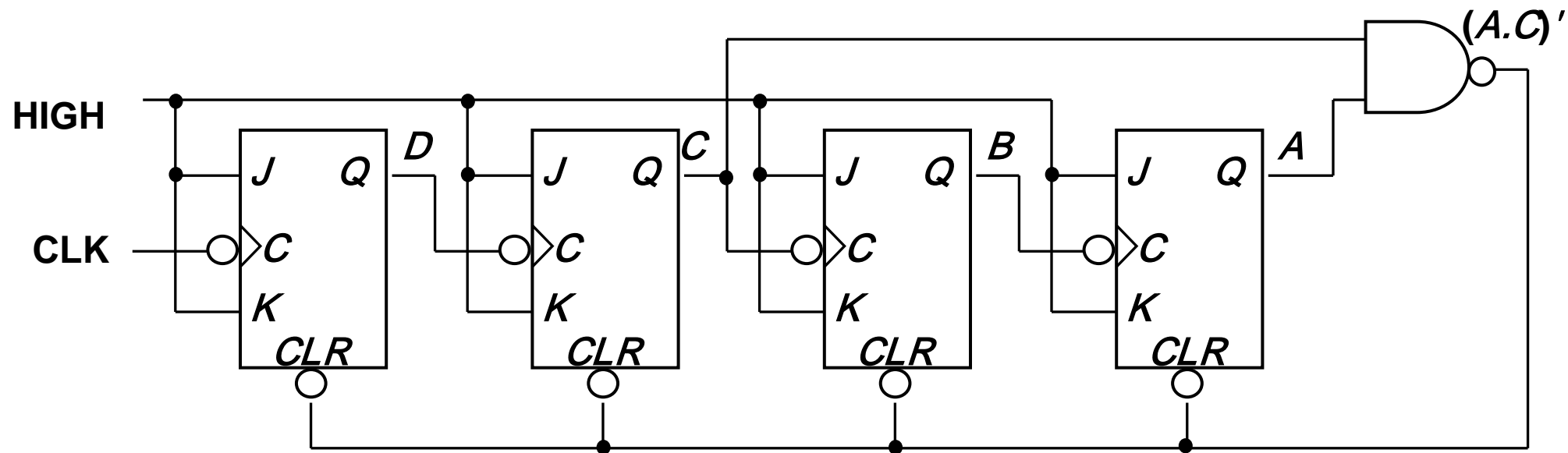
# Asyn. Counters with MOD no. $< 2^n$

- Decade counters (or BCD counters) are counters with 10 states (modulus-10) in their sequence. They are commonly used in daily life (e.g.: utility meters, odometers, etc.).
- Design an asynchronous decade counter.



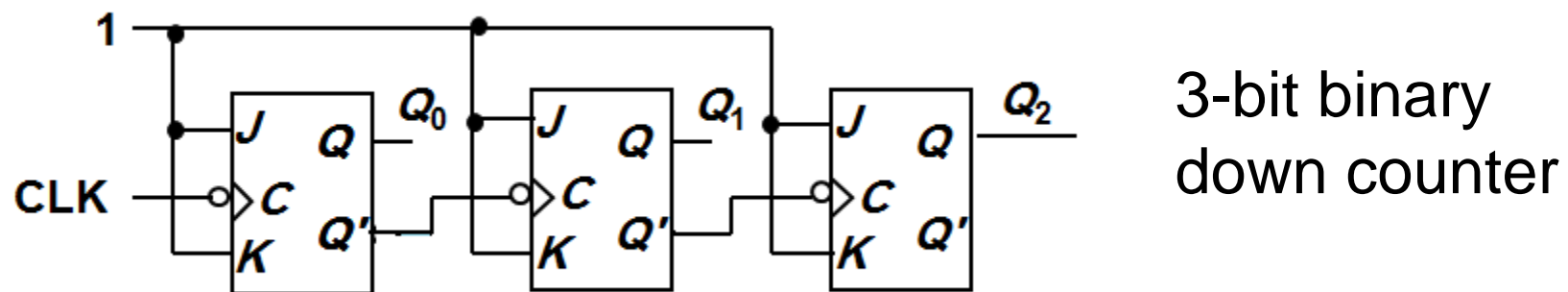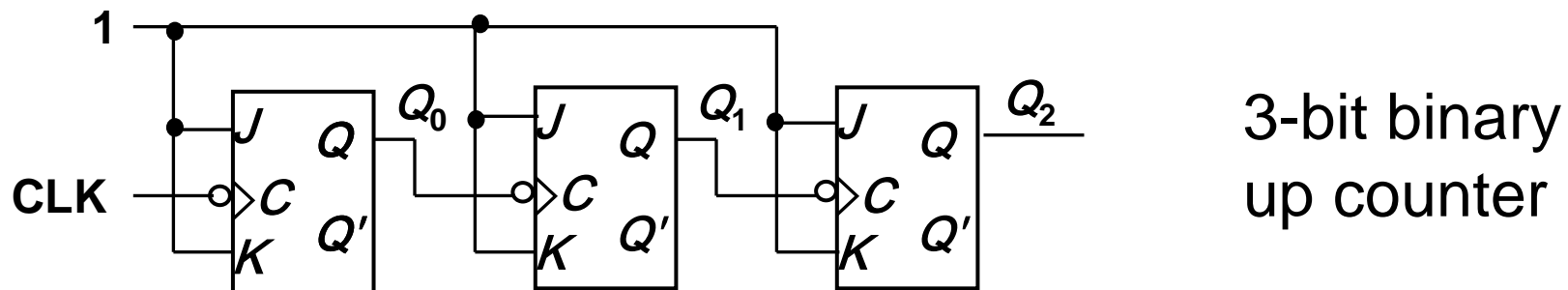
# Asynchronous Down Counters

- So far we are dealing with *up counters*. *Down counters*, on the other hand, count downward from a maximum value to zero, and repeat.
- Example: A 3-bit binary (MOD- $2^3$ ) down counter.




# Asyn. Counters with MOD no. $< 2^n$

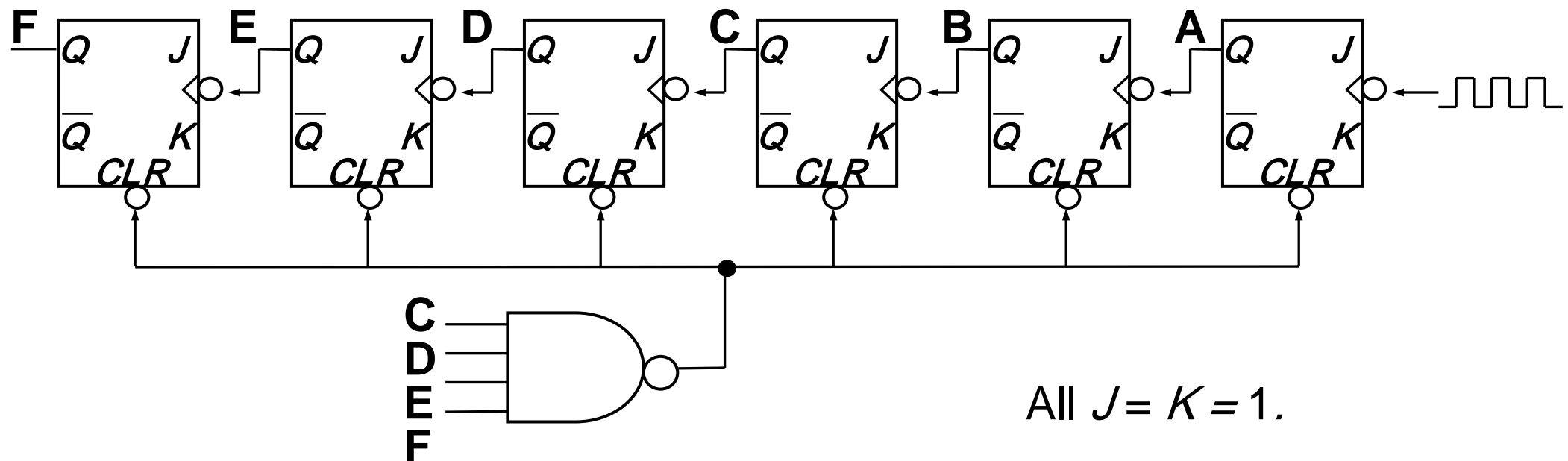- *Exercise:* How to construct an asynchronous MOD-5 counter? MOD-7 counter? MOD-12 counter?
- *Question:* The following is a MOD-? counter?



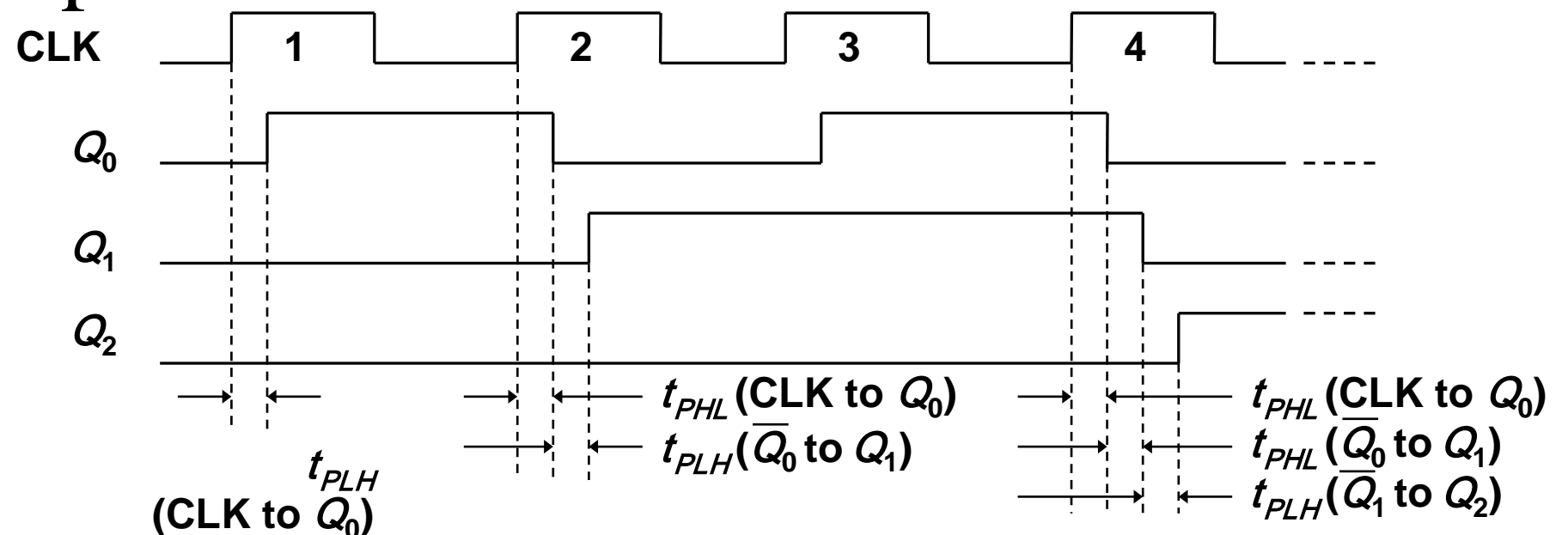
# Asynchronous (Ripple) Counters

- Propagation delays in an asynchronous (ripple-clocked) binary counter.
- If the accumulated delay is greater than the clock pulse, some counter states may be misrepresented!


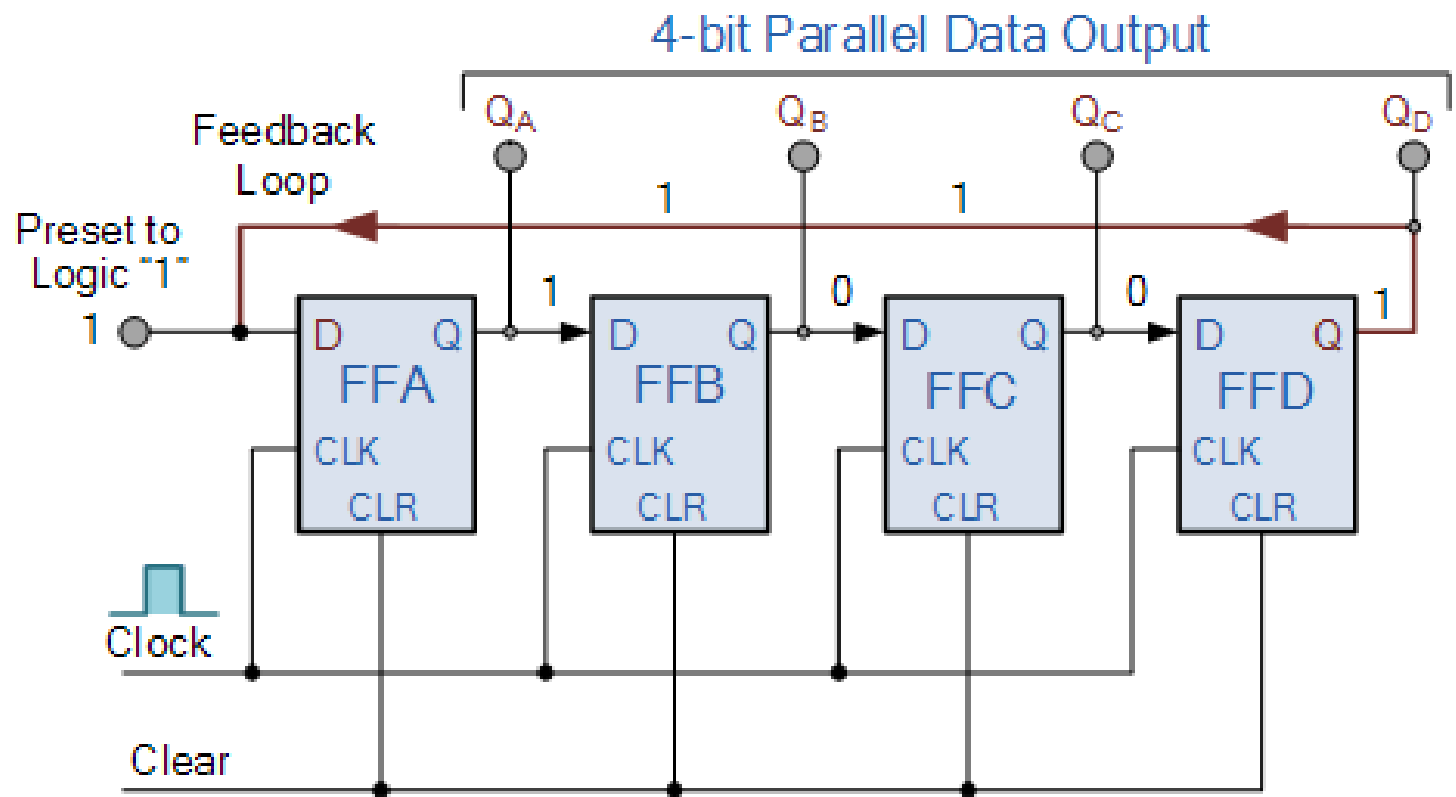
# 4-bit Ring Counter

A “CLEAR” signal is firstly applied to all the flip-flops together in order to “RESET” their outputs to a logic “0” level and then a “PRESET” pulse is applied to the input of the first flip-flop ( FFA ) before the clock pulses are applied. This then places a single logic “1” value into the circuit of the ring counter.




So on each successive clock pulse, the counter circulates the same data bit between the four flip-flops over and over again around the “ring” every fourth clock cycle. But in order to cycle the data correctly around the counter we must first “load” the counter with a suitable data pattern as all logic “0’s” or all logic “1’s” outputted at each clock cycle would make the ring counter invalid.



# Johnson Ring Counter


The **Johnson Ring Counter** or “Twisted Ring Counter”, is another shift register with feedback exactly the same as the standard *Ring Counter* above, except that this time the inverted output  $Q$  of the last flip-flop is now connected back to the input  $D$  of the first flip-flop as shown below.

## 4-bit Johnson Ring Counter

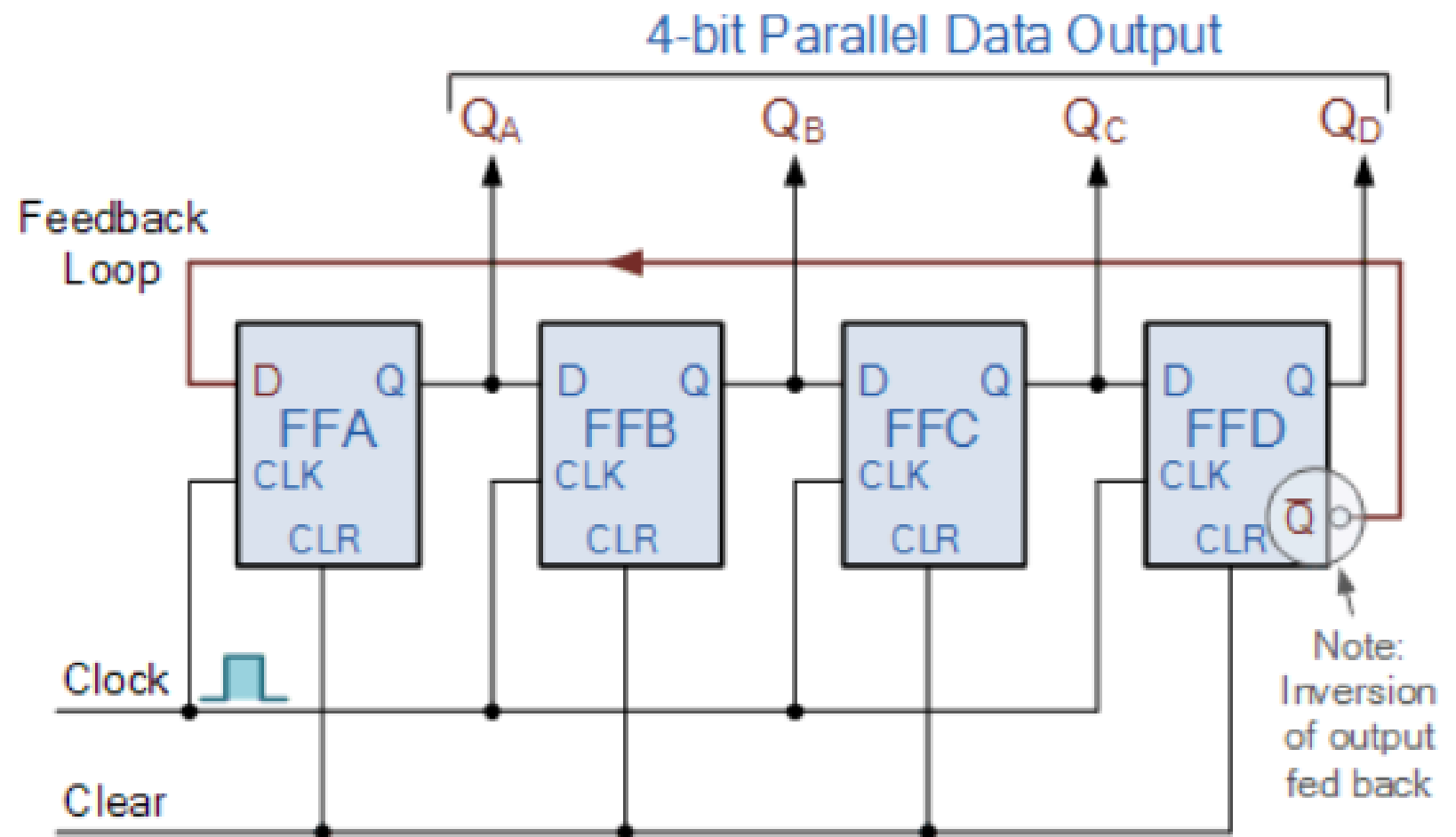

 
# More complex counters

- More complex counters are also possible. The full-featured LogicWorks **Counter-4** device below has several functions.
  - It can count up or down, depending on whether the **UP** input is 1 or 0.
  - You can clear the counter to 0000 asynchronously by setting **CLR = 1**.
  - You can perform a parallel load of **D3-D0** when **LD = 0**.
  - The active-low **EN** input enables or disables the counter.
  - The “counter out” **CO** is normally 1, but becomes 0 when the counter reaches its maximum value of 1111 (if UP = 1) or 0000 (if UP = 0).



 
# A restricted 4-bit counter

- We can also make a counter that “starts” at some value besides 0000.
- In the diagram below, when  $CO = 0$  the LD signal forces the next state to be loaded from D3-D0.
- The result is this counter wraps from 1111 to 0110 (instead of 0000).


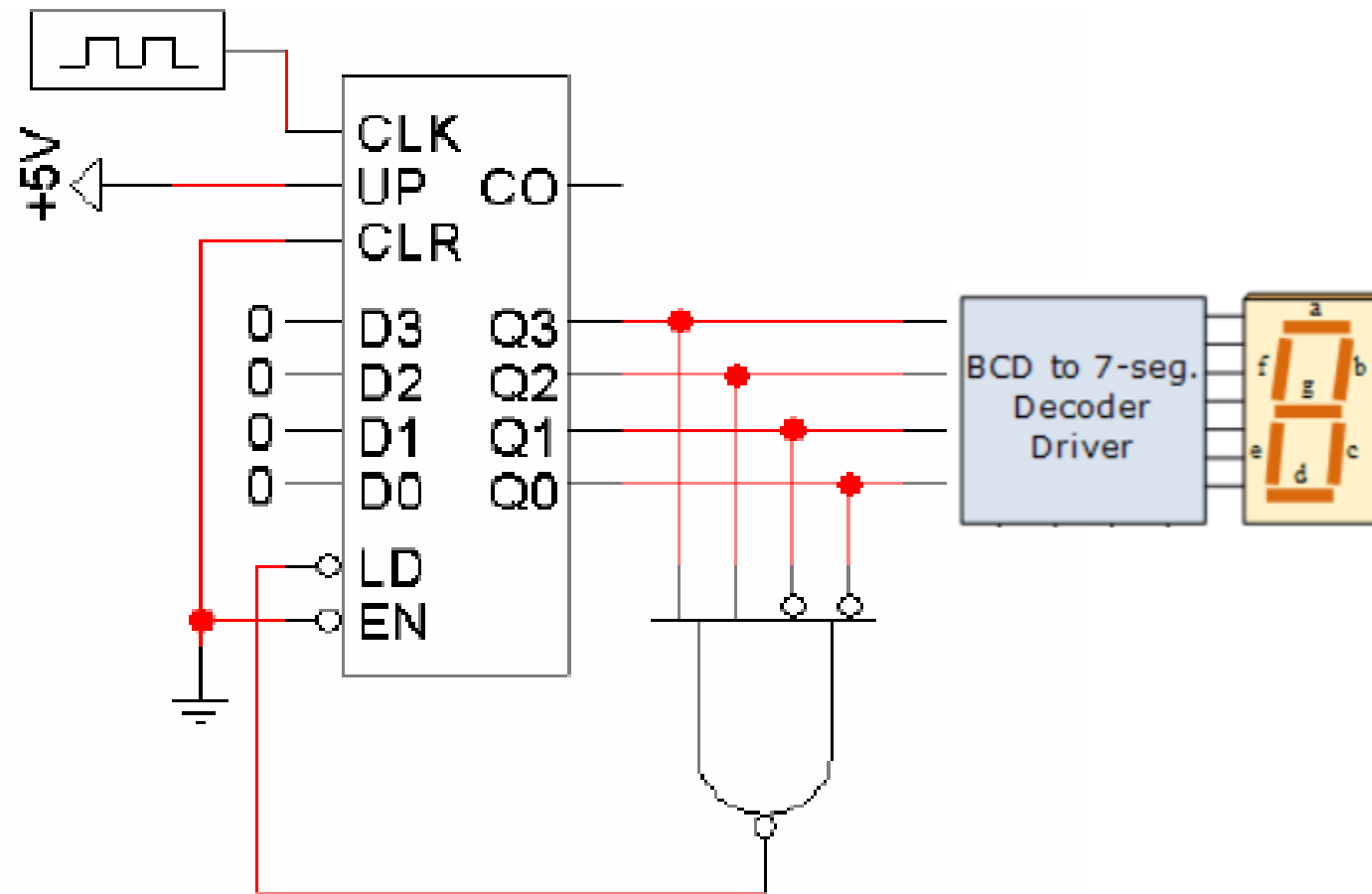
# Another restricted counter

- We can also make a circuit that counts up to only 1100, instead of 1111.
- Here, when the counter output reaches 1100, the NAND gate forces the counter to load, so the next state becomes 0000.




## Here is an 8-bit counter made from two 4-bit

- The bottom device represents the least significant four bits, while the top counter represents the most significant four bits.
- When the bottom counter reaches 1111 (i.e., when CO = 0), it enables the top counter for one cycle.

The two four-bit counters share clock and clear inputs. Sharing the clock is important to ensure that the two counters are synchronized with respect to each other.

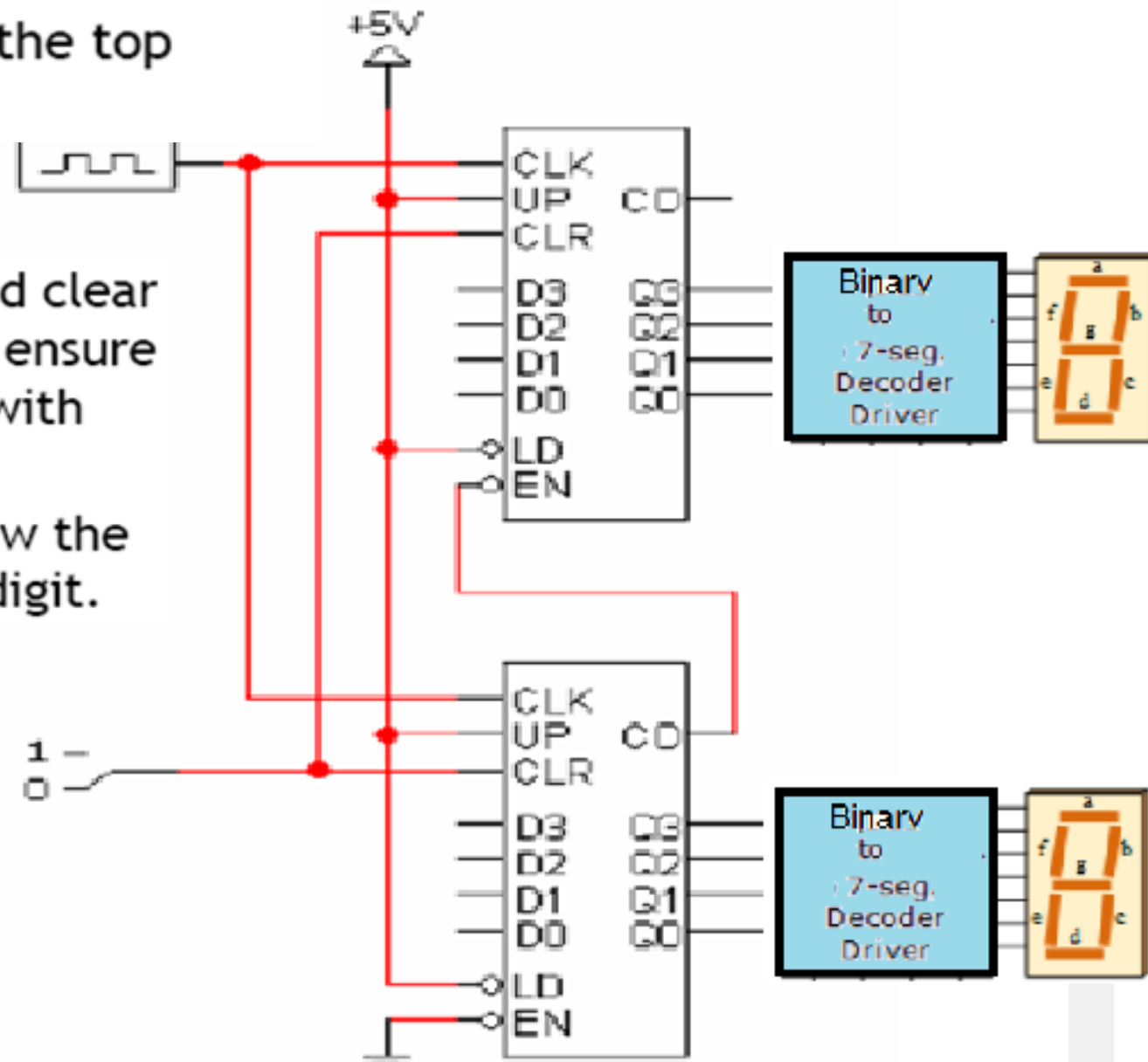We've used [Hex Display](#) units here to view the four-bit output as a single hexadecimal digit.



# Introduction to RAM

- **Random-access memory**, or **RAM**, provides large quantities of temporary storage in a computer system.
- Remember the basic capabilities of a memory.
  - It should be able to store a value.
  - You should be able to read the value that was saved.
  - You should be able to change the stored value.
- A RAM is similar, except that it can store *many* values.
  - An **address** will specify which memory value we're interested in.
  - Each value can be a multiple-bit **word** (e.g., 32 bits).
- We'll refine the memory properties as follows.

A RAM should be able to:


1. Store many words, one per address
2. Read the word that was saved at a particular address
3. Change the word that's saved at a particular address

# Picture of memory

- You can think of computer memory as being one big array of data.
  - The address serves as an array index.
  - Each address refers to one word of data.
- You can read or modify the data at any given memory address, just like you can read or modify the contents of an array at any given index.
- If you've worked with pointers in C or C++, then you've already worked with memory addresses.

Address	Data
00000000	
00000001	
00000010	
.	
.	
.	
.	
.	
.	
.	
.	
.	
.	
FFFFFFFFD	
FFFFFFFE	
FFFFFFF	

# Block diagram of RAM

 


- This block diagram introduces the main interface to RAM.
  - A Chip Select, **CS**, enables or disables the RAM.
  - **ADRS** specifies the address or location to read from or write to.
  - **WR** selects between reading from or writing to the memory.
    - To read from memory, **WR** should be set to 0.  
**OUT** will be the  $n$ -bit value stored at **ADRS**.
    - To write to memory, we set **WR** = 1.  
**DATA** is the  $n$ -bit value to save in memory.
- This interface makes it easy to combine RAMs together, as we'll see.


 
# Memory sizes

- We refer to this as a  $2^k \times n$  memory.
  - There are  $k$  **address lines**, which can specify one of  $2^k$  addresses.
  - Each address contains an  $n$ -bit word.



- For example, a  $2^{24} \times 16$  RAM contains  $2^{24} = 16\text{M}$  words, each 16 bits long.
  - The RAM would need 24 address lines.
  - The total **storage capacity** is  $2^{24} \times 16 = 2^{28}$  bits.



# Size matters!

- Memory sizes are usually specified in numbers of **bytes** (8 bits).
- The  $2^{28}$ -bit memory on the previous page has a capacity of  $2^{25}$  bytes.

$$2^{28} \text{ bits} / 8 \text{ bits per byte} = 2^{25} \text{ bytes}$$


- With the abbreviations below, this is equivalent to 32 megabytes.

$$2^{25} \text{ bytes} = 2^5 \times 2^{20} \text{ bytes} = 32 \text{ MB}$$

	Prefix	Base 2	Base 10
K	Kilo	$2^{10} = 1,024$	$10^3 = 1,000$
M	Mega	$2^{20} = 1,048,576$	$10^6 = 1,000,000$
G	Giga	$2^{30} = 1,073,741,824$	$10^9 = 1,000,000,000$
 
# Reading RAM

- To *read* from a RAM, the controlling circuit must take several steps.
  1. Enable the chip by ensuring  $CS = 1$ .
  2. Select the read operation, by setting  $WR = 0$ .
  3. Send the desired address to the ADRS input.
  4. The contents of that address appear on OUT after a little while.
- Notice that the DATA input is unused for read operations.



# Writing RAM

- To *write* to this RAM, you need to do the following tasks.
  1. Enable the chip by setting  $CS = 1$ .
  2. Select the write operation, by setting  $WR = 1$ .
  3. Send the desired address to the ADRS input.
  4. Send the word to store to the DATA input.
- The output OUT is not needed for memory write operations.

