
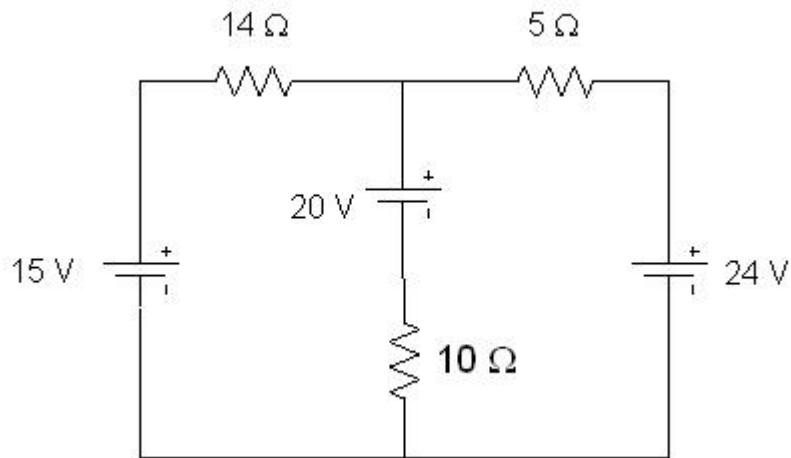


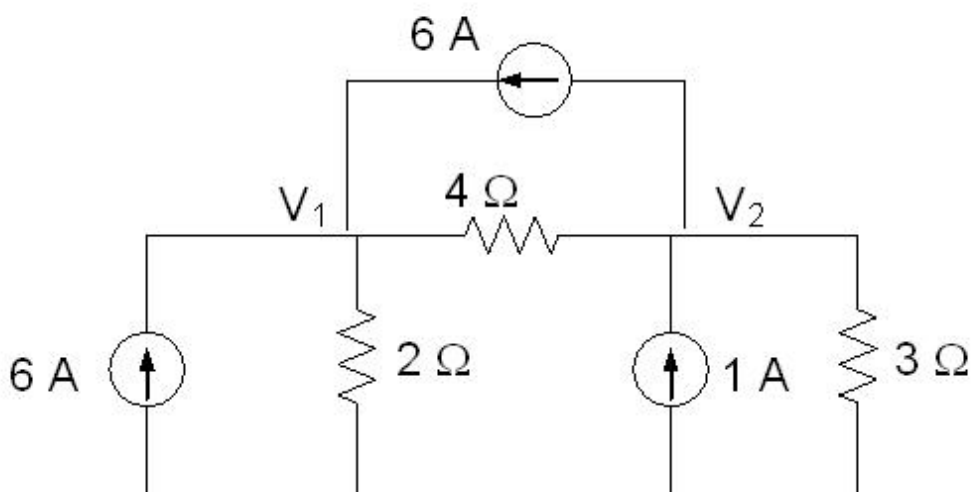**Q (1)** Using Mesh analysis, find the current passing through the  $10\ \Omega$  resistor



**Q (2)** Using Nodal analysis, find **V1** and **V2**.




**Q (3)** A load whose impedance is  $Z = 8 + j6\ \Omega$  is supplied by a source whose

voltage is  $V = \sqrt{2} 30 \cos(\omega t - 30^\circ)\text{ V}$ . it is required to find out:

- the apparent power (S).
- the effective power (P).
- the reactive power (Q).

Also, draw the power triangle.

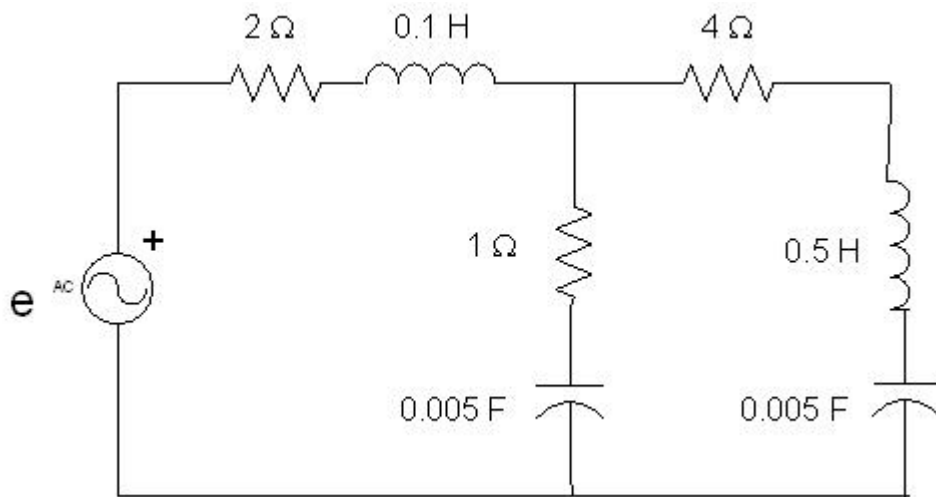**Q (4)** In the circuit shown,  $e = \sqrt{2} 100 \sin 20t$  volts. Find out the total current in the time domain. Also, calculate the total power absorbed in the circuit. [[Hint: use series/parallel method].



**Q (5)** In the circuit shown, find out:

(a) the value of  $Z_L$  to receive maximum power ( $PL_{max}$ ) from the source

$$e = \sqrt{2} 20 \sin \omega t$$

(b) the value of  $PL_{max}$

