



Logic Gates

Objectives:

The main purpose for this lesson is to introduce the following:

- define some important concepts of logic gates.
- Basic types of gates and drawings.


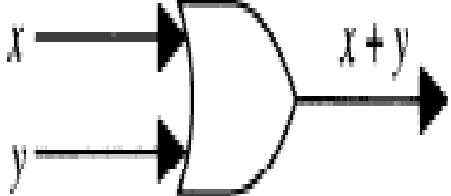
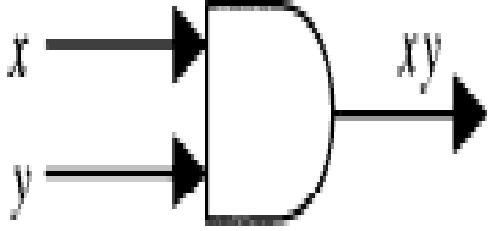
Introduction

- Boolean algebra is used to model the circuitry of electronic devices.
- Each input and each output of such a device can be thought of as a member of the set $\{0,1\}$.

The basic elements of circuits are called *gates*.

- Each type of gate implements a Boolean operation.
- The circuits that we will study in this chapter give output that depends only on the input, and not on the current state of the circuit. Such circuits are called *combinational circuits* or *gating networks*.

Basic Types of Gates

Gate	Input	Output	Figure
<i>Inverter</i>	A value of <u>one</u> Boolean variable	The <u>complement</u> of the value	
<i>The OR gate</i>	The values of <u>two or more</u> Boolean variables	The Boolean <u>sum</u> of their values	
<i>The AND gate</i>	the values of <u>two or more</u> Boolean variables	the Boolean <u>product</u> of their values	

Basic Types of Gates


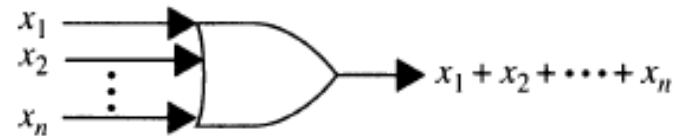
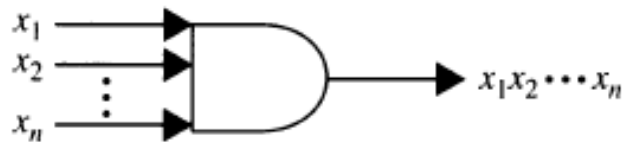
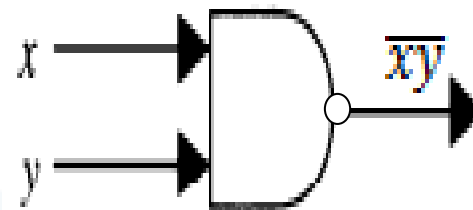


FIGURE 2 Gates with n Inputs.

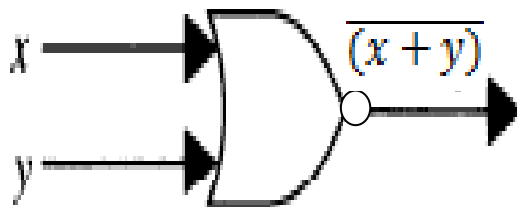

Combinations of Gates

- Combinational circuits can be constructed using a combination of *inverters, OR gates,* and *AND gates.*
- output from a gate may be used as input by one or more other elements
- Both drawings in Figure 3 depict the circuit that produces the output $xy + \bar{x}y$

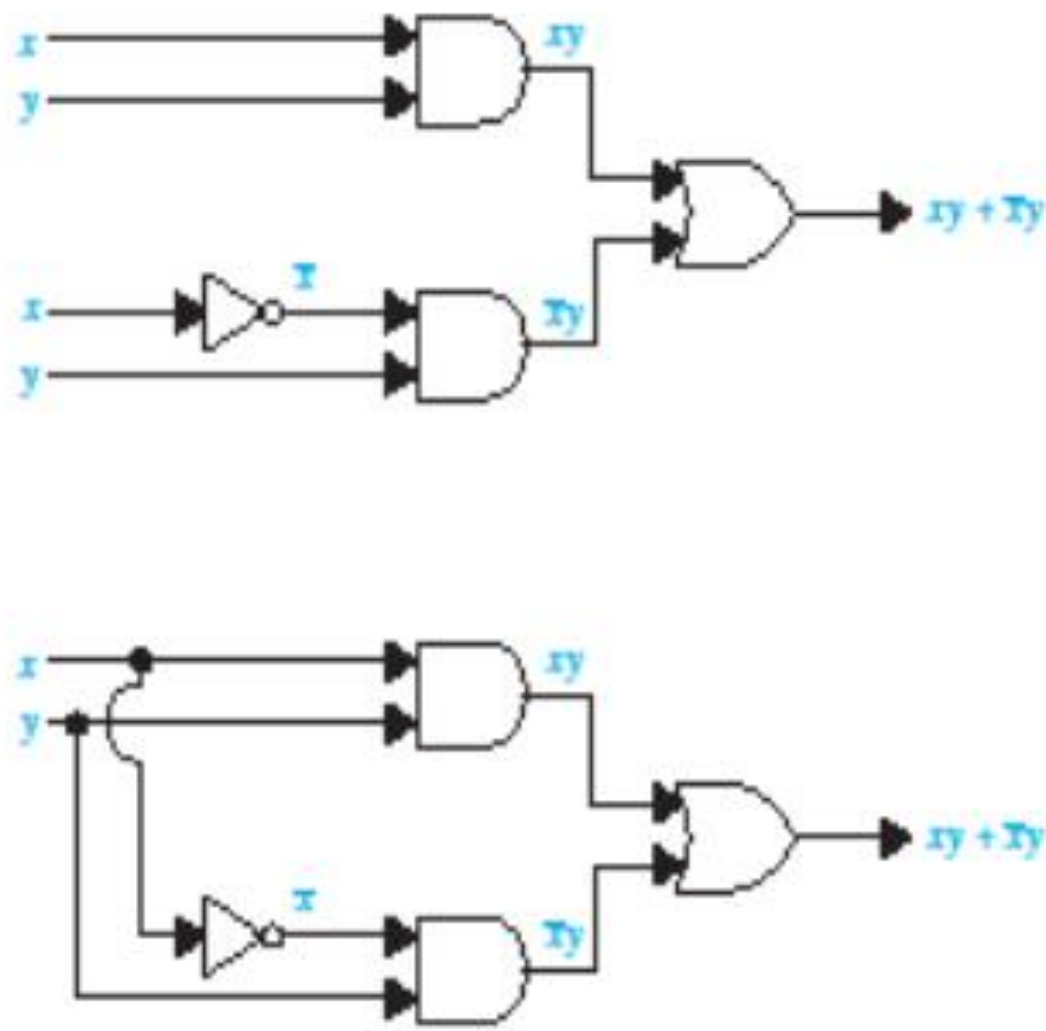


FIGURE 3 Two Ways to Draw the Same Circuit.

EXAMPLE 1

Construct circuits that produce the following outputs:


$$(a) (x + y)\bar{x}$$

$$(b) \bar{x}(y + \bar{z})$$

$$(c) (x + y + z)(\bar{x}\bar{y}\bar{z})$$


Solution

(a) $(x + y)\bar{x}$

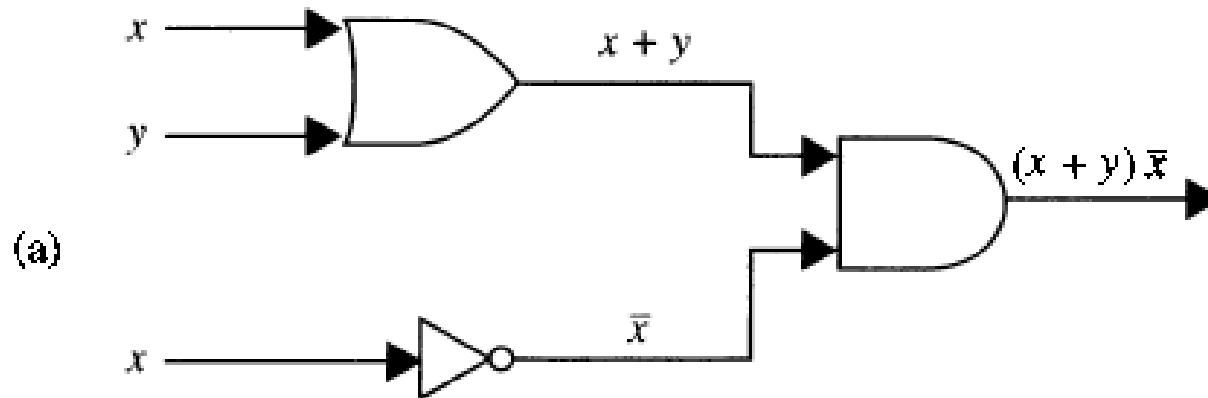


Solution

$$(b) \overline{x}(y + \overline{z})$$

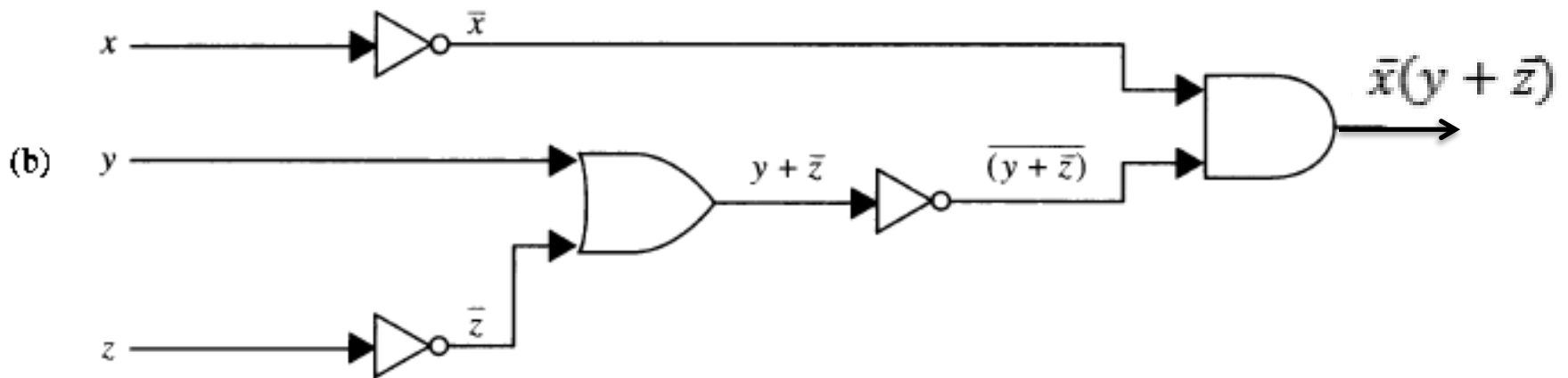

Solution
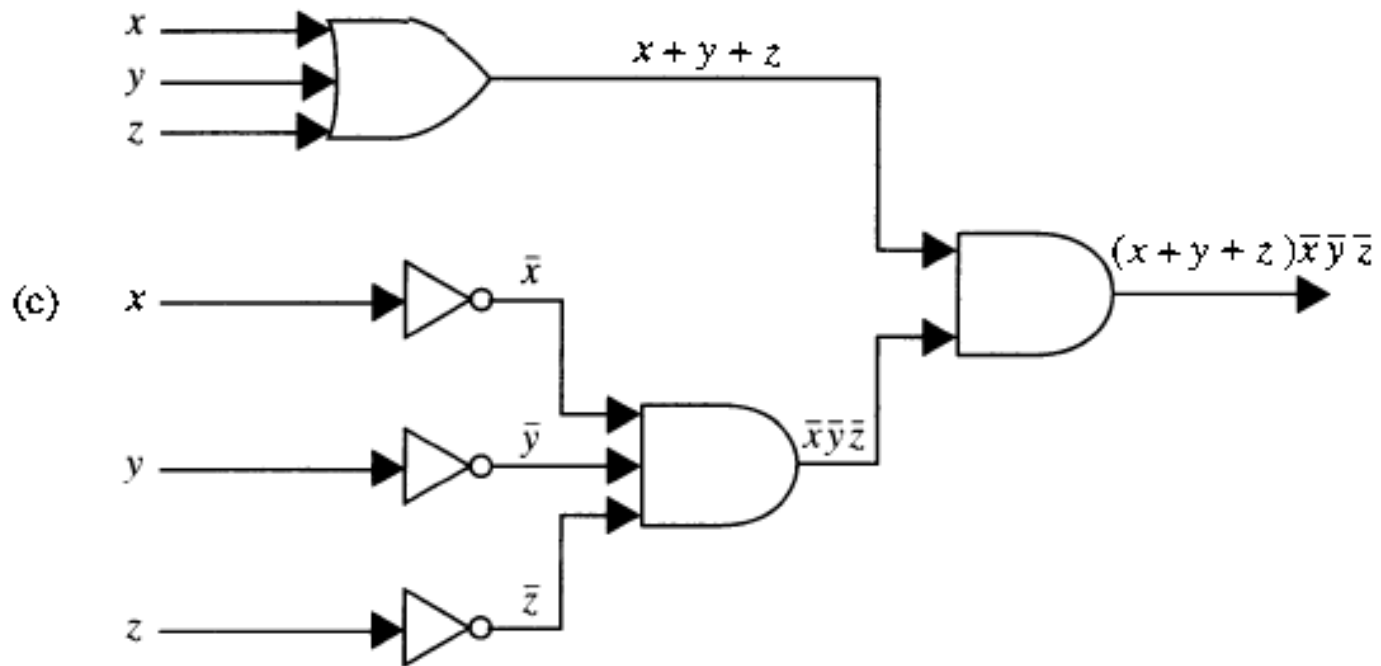
$$(c) (x + y + z)(\bar{x}\bar{y}\bar{z})$$



Homework

Page 827/828

- 1
- 3
- 5