

19. An inductor ( $L = 400 \text{ mH}$ ), a capacitor ( $C = 4.43 \text{ } \mu\text{F}$ ), and a resistor ( $R = 500 \text{ } \Omega$ ) are connected in series. A  $50.0\text{-Hz}$  AC source produces a peak current of  $250 \text{ mA}$  in the circuit. (a) Calculate the required peak voltage  $\Delta V_{\text{max}}$ . (b) Determine the phase angle by which the current leads or lags the applied voltage.
20. At what frequency does the inductive reactance of a  $57.0\text{-}\mu\text{H}$  inductor equal the capacitive reactance of a  $57.0\text{-}\mu\text{F}$  capacitor?
21. A series AC circuit contains the following components:  $R = 150 \text{ } \Omega$ ,  $L = 250 \text{ mH}$ ,  $C = 2.00 \text{ } \mu\text{F}$  and a source with  $\Delta V_{\text{max}} = 210 \text{ V}$  operating at  $50.0 \text{ Hz}$ . Calculate the (a) inductive reactance, (b) capacitive reactance, (c) impedance, (d) maximum current, and (e) phase angle between current and source voltage.
22. A sinusoidal voltage  $\Delta v(t) = (40.0 \text{ V}) \sin(100t)$  is applied to a series  $RLC$  circuit with  $L = 160 \text{ mH}$ ,  $C = 99.0 \text{ } \mu\text{F}$ , and  $R = 68.0 \text{ } \Omega$ . (a) What is the impedance of the circuit? (b) What is the maximum current? (c) Determine the numerical values for  $I_{\text{max}}$ ,  $\omega$ , and  $\phi$  in the equation  $i(t) = I_{\text{max}} \sin(\omega t - \phi)$ .
23. An  $RLC$  circuit consists of a  $150\text{-}\Omega$  resistor, a  $21.0\text{-}\mu\text{F}$  capacitor, and a  $460\text{-mH}$  inductor, connected in series with a  $120\text{-V}$ ,  $60.0\text{-Hz}$  power supply. (a) What is the phase angle between the current and the applied voltage? (b) Which reaches its maximum earlier, the current or the voltage?

## P33.19

$$(a) \quad X_L = \omega L = 2\pi(50.0)(400 \times 10^{-3}) = 126 \, \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi(50.0)(4.43 \times 10^{-6})} = 719 \, \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{500^2 + (126 - 719)^2} = 776 \, \Omega$$

$$\Delta V_{m \text{ ax}} = I_{m \text{ ax}} Z = (250 \times 10^{-3})(776) = \boxed{194 \text{ V}}$$

$$(b) \quad \phi = \tan^{-1}\left(\frac{X_L - X_C}{R}\right) = \tan^{-1}\left(\frac{126 - 719}{500}\right) = \boxed{-49.9^\circ}. \text{ Thus, the}$$

Current leads the voltage.

$$\text{P33.20} \quad \omega L = \frac{1}{\omega C} \rightarrow \omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(57.0 \times 10^{-6})(57.0 \times 10^{-6})}} = 1.75 \times 10^4 \text{ rad/s}$$

$$f = \frac{\omega}{2\pi} = \boxed{2.79 \text{ kHz}}$$

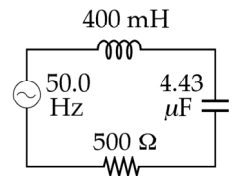


FIG. P33.19

**P33.21**

(a)  $X_L = \omega L = 2\pi(50.0 \text{ s}^{-1})(250 \times 10^{-3} \text{ H}) = \boxed{78.5 \Omega}$

(b)  $X_C = \frac{1}{\omega C} = \left[ 2\pi(50.0 \text{ s}^{-1})(2.00 \times 10^{-6} \text{ F}) \right]^{-1} = \boxed{1.59 \text{ k}\Omega}$

(c)  $Z = \sqrt{R^2 + (X_L - X_C)^2} = \boxed{1.52 \text{ k}\Omega}$

(d)  $I_{\text{max}} = \frac{\Delta V_{\text{max}}}{Z} = \frac{210 \text{ V}}{1.52 \times 10^3 \Omega} = \boxed{138 \text{ mA}}$

(e)  $\phi = \tan^{-1} \left[ \frac{X_L - X_C}{R} \right] = \tan^{-1}(-10.1) = \boxed{-84.3^\circ}$

**P33.22**

(a)  $Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{68.0^2 + (16.0 - 101)^2} = \boxed{109 \Omega}$   
 $X_L = \omega L = (100)(0.160) = 16.0 \Omega$   
 $X_C = \frac{1}{\omega C} = \frac{1}{(100)(99.0 \times 10^{-6})} = 101 \Omega$

(b)  $I_{\text{max}} = \frac{\Delta V_{\text{max}}}{Z} = \frac{40.0 \text{ V}}{109 \Omega} = \boxed{0.367 \text{ A}}$

(c)  $\tan \phi = \frac{X_L - X_C}{R} = \frac{16.0 - 101}{68.0} = -1.25$   
 $\phi = -0.896 \text{ rad} = -51.3^\circ$   
 $\boxed{I_{\text{max}} = 0.367 \text{ A}} \quad \boxed{\omega = 100 \text{ rad/s}} \quad \boxed{\phi = -0.896 \text{ rad} = -51.3^\circ}$

**P33.23**

$X_L = 2\pi fL = 2\pi(60.0)(0.460) = 173 \Omega$   
 $X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(60.0)(21.0 \times 10^{-6})} = 126 \Omega$

(a)  $\tan \phi = \frac{X_L - X_C}{R} = \frac{173 \Omega - 126 \Omega}{150 \Omega} = 0.314$   
 $\phi = 0.304 \text{ rad} = \boxed{17.4^\circ}$

(b) Since  $X_L > X_C$ ,  $\phi$  is positive; so  $\boxed{\text{voltage leads the current}}$ .