


# Parallel ac Circuits

## 15.7 ADMITTANCE AND SUSCEPTANCE

In dc circuit we used the *conductance*  $G$ ,  $G = \frac{1}{R}$

In ac circuit the *admittance*  $Y$  is defined as the reciprocal of the impedance  $Z$ .

$$Y = \frac{1}{Z} \quad (\text{S}) \text{ Siemens}$$

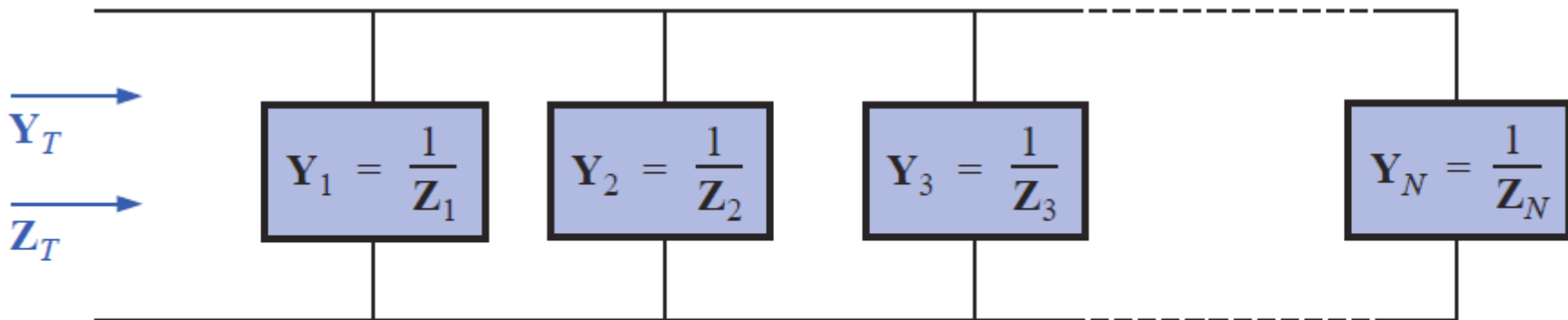

**FIG. 15.54**  
*Parallel ac network.*

$$\mathbf{Y}_T = \mathbf{Y}_1 + \mathbf{Y}_2 + \mathbf{Y}_3 + \dots + \mathbf{Y}_N$$

$$\frac{1}{\mathbf{Z}_T} = \frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_2} + \frac{1}{\mathbf{Z}_3} + \dots + \frac{1}{\mathbf{Z}_N}$$

For two impedances in parallel:

$$\mathbf{Z}_T = \frac{\mathbf{Z}_1 \mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2}$$

$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

For three impedances in parallel:

$$\mathbf{Z}_T = \frac{\mathbf{Z}_1 \mathbf{Z}_2 \mathbf{Z}_3}{\mathbf{Z}_1 \mathbf{Z}_2 + \mathbf{Z}_2 \mathbf{Z}_3 + \mathbf{Z}_1 \mathbf{Z}_3}$$

$$R_T = \frac{R_1 R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

## Resistor:

Reciprocal of resistance R is called conductance G

$$\mathbf{Y}_R = \frac{1}{\mathbf{Z}_R} = \frac{1}{R \angle 0^\circ} = G \angle 0^\circ$$

Reciprocal of reactance ( $1/X$ ) is called *susceptance* symbol

$$\mathbf{B} = 1/X \quad (\text{S})$$

## Inductor:

$$\mathbf{Y}_L = \frac{1}{\mathbf{Z}_L} = \frac{1}{X_L \angle 90^\circ} = \frac{1}{X_L} \angle -90^\circ$$

Defining

$$B_L = \frac{1}{X_L}$$

(siemens, S)

$$\mathbf{Y}_L = B_L \angle -90^\circ$$

Capacitor:

$$\mathbf{Y}_C = \frac{1}{\mathbf{Z}_C} = \frac{1}{X_C \angle -90^\circ} = \frac{1}{X_C} \angle 90^\circ$$

Defining

$$B_C = \frac{1}{X_C} \quad (\text{siemens, S})$$


we have

$$\mathbf{Y}_C = B_C \angle 90^\circ$$

## Admittance Diagram:

*For any configuration (series, parallel, series-parallel, etc.), the angle associated with the total admittance is the angle by which the source current leads the applied voltage.*


- *inductive networks,  $\theta_T$  is negative,*
- *capacitive networks,  $\theta_T$  is positive.*

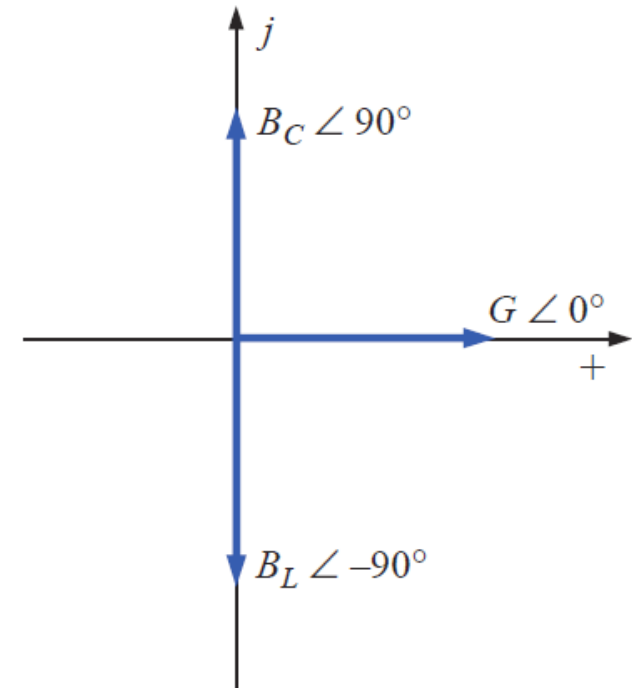

**FIG. 15.55**  
*Admittance diagram.*

**EXAMPLE 15.12** For the network

- Find the admittance of each parallel branch.
- Determine the input admittance.
- Calculate the input impedance.
- Draw the admittance diagram.

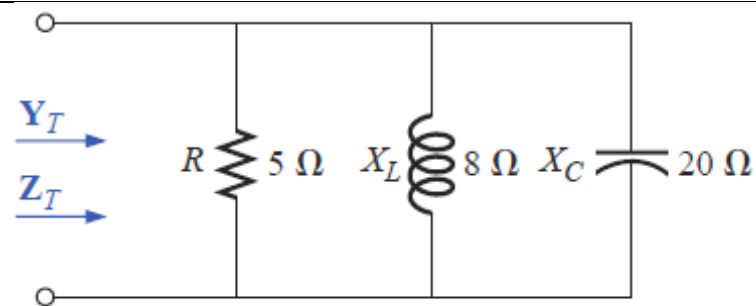


**FIG. 15.58**

*Example 15.13.*

**Solutions:**

$$\begin{aligned} \text{a. } \mathbf{Y}_R &= G \angle 0^\circ = \frac{1}{R} \angle 0^\circ = \frac{1}{5 \Omega} \angle 0^\circ \\ &= \mathbf{0.2 \text{ S} } \angle 0^\circ = \mathbf{0.2 \text{ S} + j 0} \\ \mathbf{Y}_L &= B_L \angle -90^\circ = \frac{1}{X_L} \angle -90^\circ = \frac{1}{8 \Omega} \angle -90^\circ \\ &= \mathbf{0.125 \text{ S} } \angle -90^\circ = \mathbf{0 - j 0.125 \text{ S}} \\ \mathbf{Y}_C &= B_C \angle 90^\circ = \frac{1}{X_C} \angle 90^\circ = \frac{1}{20 \Omega} \angle 90^\circ \\ &= \mathbf{0.050 \text{ S} } \angle +90^\circ = \mathbf{0 + j 0.050 \text{ S}} \end{aligned}$$

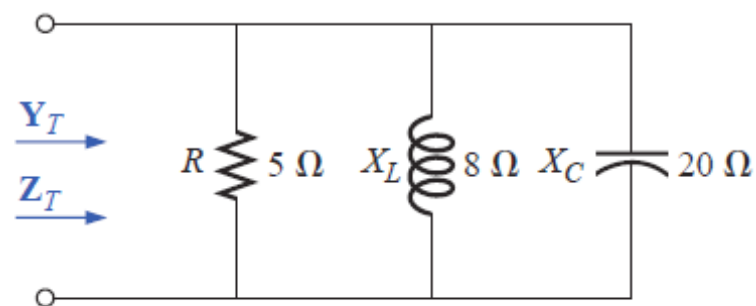

**FIG. 15.58**


*Example 15.13.*

$$\begin{aligned}
 \text{b. } \mathbf{Y}_T &= \mathbf{Y}_R + \mathbf{Y}_L + \mathbf{Y}_C \\
 &= (0.2 \text{ S} + j 0) + (0 - j 0.125 \text{ S}) + (0 + j 0.050 \text{ S}) \\
 &= 0.2 \text{ S} - j 0.075 \text{ S} = \mathbf{0.2136 \text{ S} } \angle -\mathbf{20.56^\circ}
 \end{aligned}$$

$$\text{c. } \mathbf{Z}_T = \frac{1}{0.2136 \text{ S} \angle -20.56^\circ} = \mathbf{4.68 \Omega} \angle \mathbf{20.56^\circ}$$


or

$$\begin{aligned}
 \mathbf{Z}_T &= \frac{\mathbf{Z}_R \mathbf{Z}_L \mathbf{Z}_C}{\mathbf{Z}_R \mathbf{Z}_L + \mathbf{Z}_L \mathbf{Z}_C + \mathbf{Z}_R \mathbf{Z}_C} \\
 &= \frac{(5 \Omega \angle 0^\circ)(8 \Omega \angle 90^\circ)(20 \Omega \angle -90^\circ)}{(5 \Omega \angle 0^\circ)(8 \Omega \angle 90^\circ) + (8 \Omega \angle 90^\circ)(20 \Omega \angle -90^\circ) + (5 \Omega \angle 0^\circ)(20 \Omega \angle -90^\circ)} \\
 &= \frac{800 \Omega \angle 0^\circ}{40 \angle 90^\circ + 160 \angle 0^\circ + 100 \angle -90^\circ} \\
 &= \frac{800 \Omega}{160 + j 40 - j 100} = \frac{800 \Omega}{160 - j 60} \\
 &= \frac{800 \Omega}{170.88 \angle -20.56^\circ} \\
 &= \mathbf{4.68 \Omega} \angle \mathbf{20.56^\circ}
 \end{aligned}$$

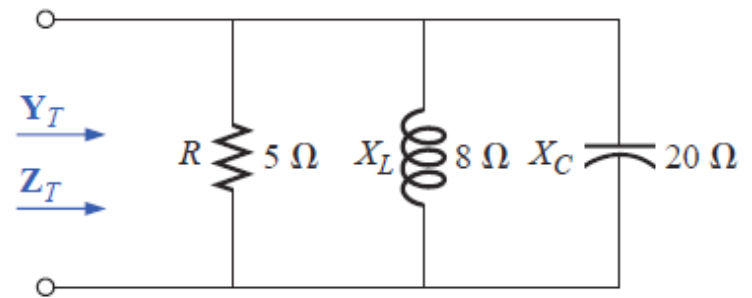

**FIG. 15.58**

*Example 15.13.*

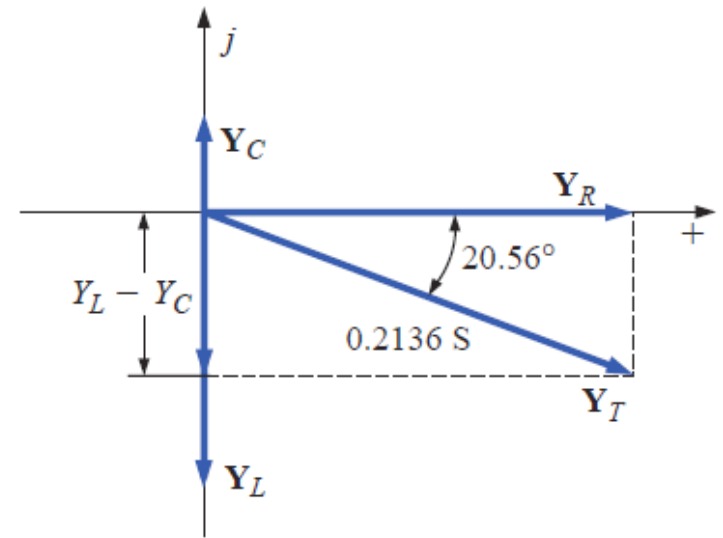

**FIG. 15.59**

*Admittance diagram for the network of Fig. 15.58.*

## 15.8 PARALLEL ac NETWORKS

$$\mathbf{I} = \frac{\mathbf{E}}{\mathbf{Z}_T} = \mathbf{E}\mathbf{Y}_T$$

$$\mathbf{I}_1 = \frac{\mathbf{E}}{\mathbf{Z}_1} = \mathbf{E}\mathbf{Y}_1$$


$$\mathbf{I}_2 = \frac{\mathbf{E}}{\mathbf{Z}_2} = \mathbf{E}\mathbf{Y}_2$$

$$\mathbf{I} - \mathbf{I}_1 - \mathbf{I}_2 = 0$$

$$\mathbf{I} = \mathbf{I}_1 + \mathbf{I}_2$$


The power:

$$P = EI \cos \theta_T$$

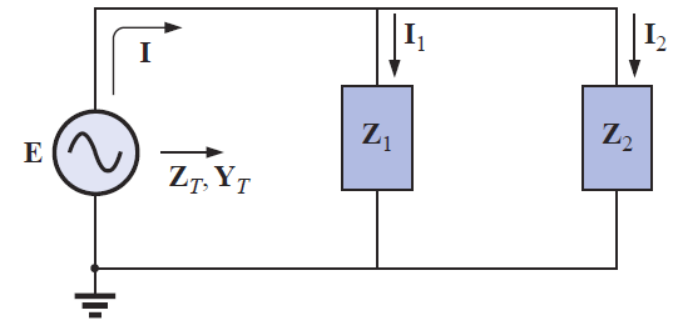


**FIG. 15.61**  
*Parallel ac network.*



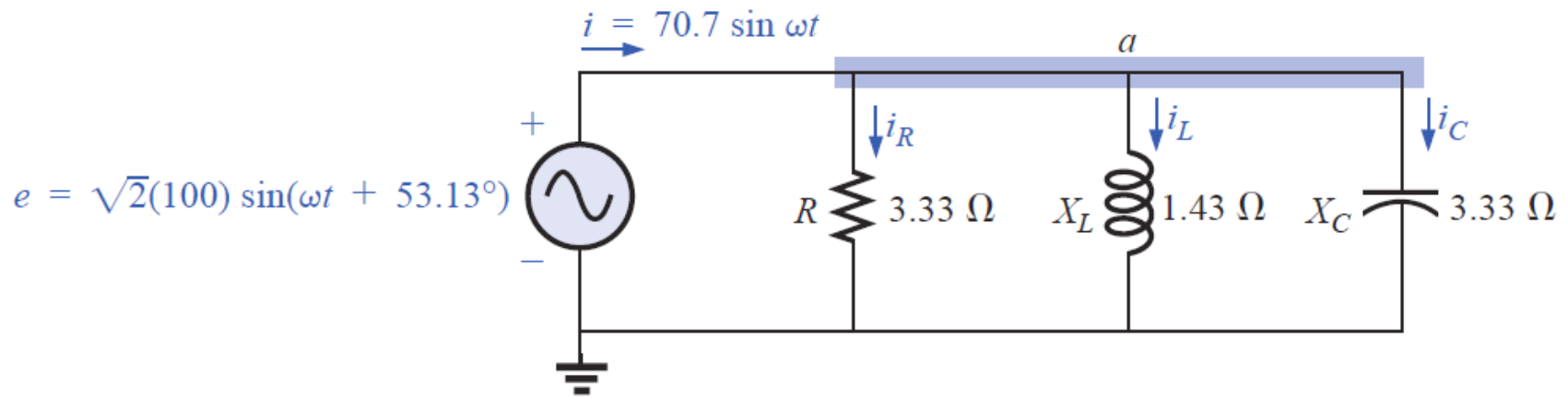

**FIG. 15.71**  
*Parallel R-L-C ac network.*

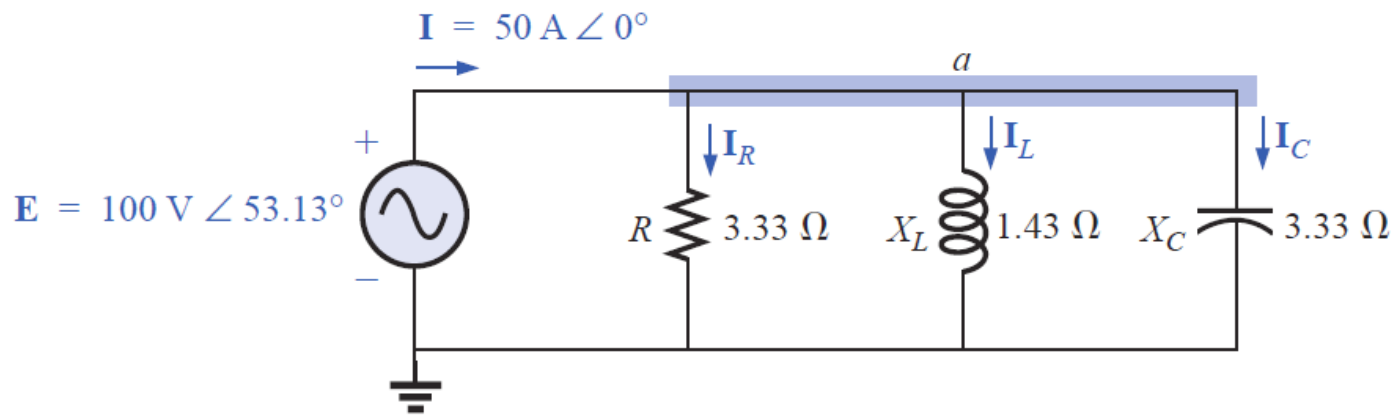


**FIG. 15.72**  
*Applying phasor notation to the network of Fig. 15.71.*

### $Y_T$ and $Z_T$

$$\begin{aligned} Y_T &= Y_R + Y_L + Y_C = G \angle 0^\circ + B_L \angle -90^\circ + B_C \angle 90^\circ \\ &= \frac{1}{3.33 \Omega} \angle 0^\circ + \frac{1}{1.43 \Omega} \angle -90^\circ + \frac{1}{3.33 \Omega} \angle 90^\circ \\ &= 0.3 \text{ S} \angle 0^\circ + 0.7 \text{ S} \angle -90^\circ + 0.3 \text{ S} \angle 90^\circ \\ &= 0.3 \text{ S} - j 0.7 \text{ S} + j 0.3 \text{ S} \\ &= 0.3 \text{ S} - j 0.4 \text{ S} = \mathbf{0.5 \text{ S} \angle -53.13^\circ} \end{aligned}$$

$$Z_T = \frac{1}{Y_T} = \frac{1}{0.5 \text{ S} \angle -53.13^\circ} = \mathbf{2 \Omega \angle 53.13^\circ}$$

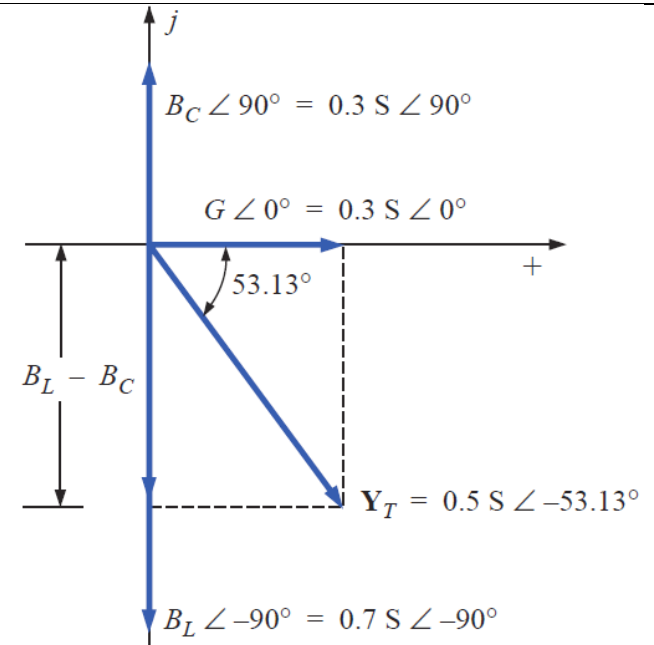

**FIG. 15.73**

*Admittance diagram for the parallel R-L-C network of Fig. 15.71.*

$$\mathbf{I} = \frac{\mathbf{E}}{\mathbf{Z}_T} = \mathbf{E}\mathbf{Y}_T = (100 \text{ V } \angle 53.13^\circ)(0.5 \text{ S } \angle -53.13^\circ) \\ = 50 \text{ A } \angle 0^\circ$$

$\mathbf{I}_R$ ,  $\mathbf{I}_L$ , and  $\mathbf{I}_C$


$$\mathbf{I}_R = (E \angle \theta)(G \angle 0^\circ) \\ = (100 \text{ V } \angle 53.13^\circ)(0.3 \text{ S } \angle 0^\circ) = 30 \text{ A } \angle 53.13^\circ$$

$$\mathbf{I}_L = (E \angle \theta)(B_L \angle -90^\circ) \\ = (100 \text{ V } \angle 53.13^\circ)(0.7 \text{ S } \angle -90^\circ) = 70 \text{ A } \angle -36.87^\circ$$

$$\mathbf{I}_C = (E \angle \theta)(B_C \angle 90^\circ) \\ = (100 \text{ V } \angle 53.13^\circ)(0.3 \text{ S } \angle +90^\circ) = 30 \text{ A } \angle 143.13^\circ$$

*Kirchhoff's current law:* At node  $a$ ,

$$\mathbf{I} - \mathbf{I}_R - \mathbf{I}_L - \mathbf{I}_C = 0 \text{ or } \mathbf{I} = \mathbf{I}_R + \mathbf{I}_L + \mathbf{I}_C$$

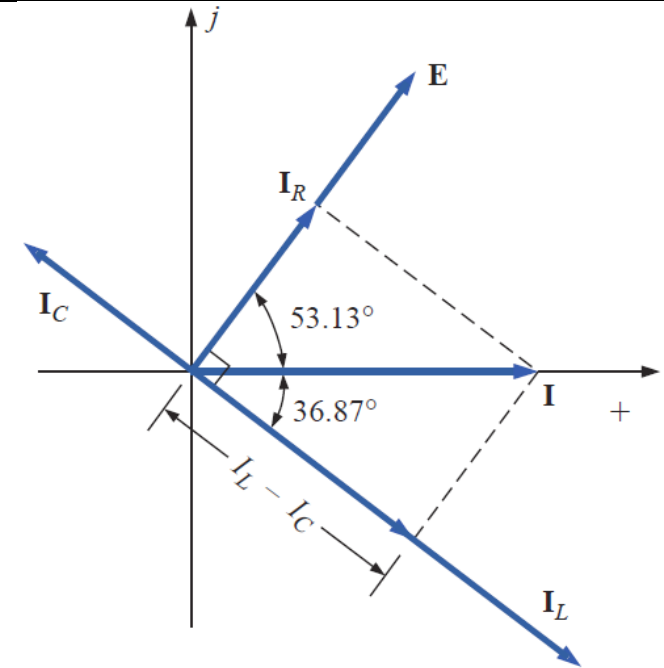

**FIG. 15.74**

*Phasor diagram for the parallel R-L-C network of Fig. 15.71.*


Time domain:

$$i = \sqrt{2}(50) \sin \omega t = 70.70 \sin \omega t$$

$$i_R = \sqrt{2}(30) \sin(\omega t + 53.13^\circ) = 42.42 \sin(\omega t + 53.13^\circ)$$

$$i_L = \sqrt{2}(70) \sin(\omega t - 36.87^\circ) = 98.98 \sin(\omega t - 36.87^\circ)$$

$$i_C = \sqrt{2}(30) \sin(\omega t + 143.13^\circ) = 42.42 \sin(\omega t + 143.13^\circ)$$

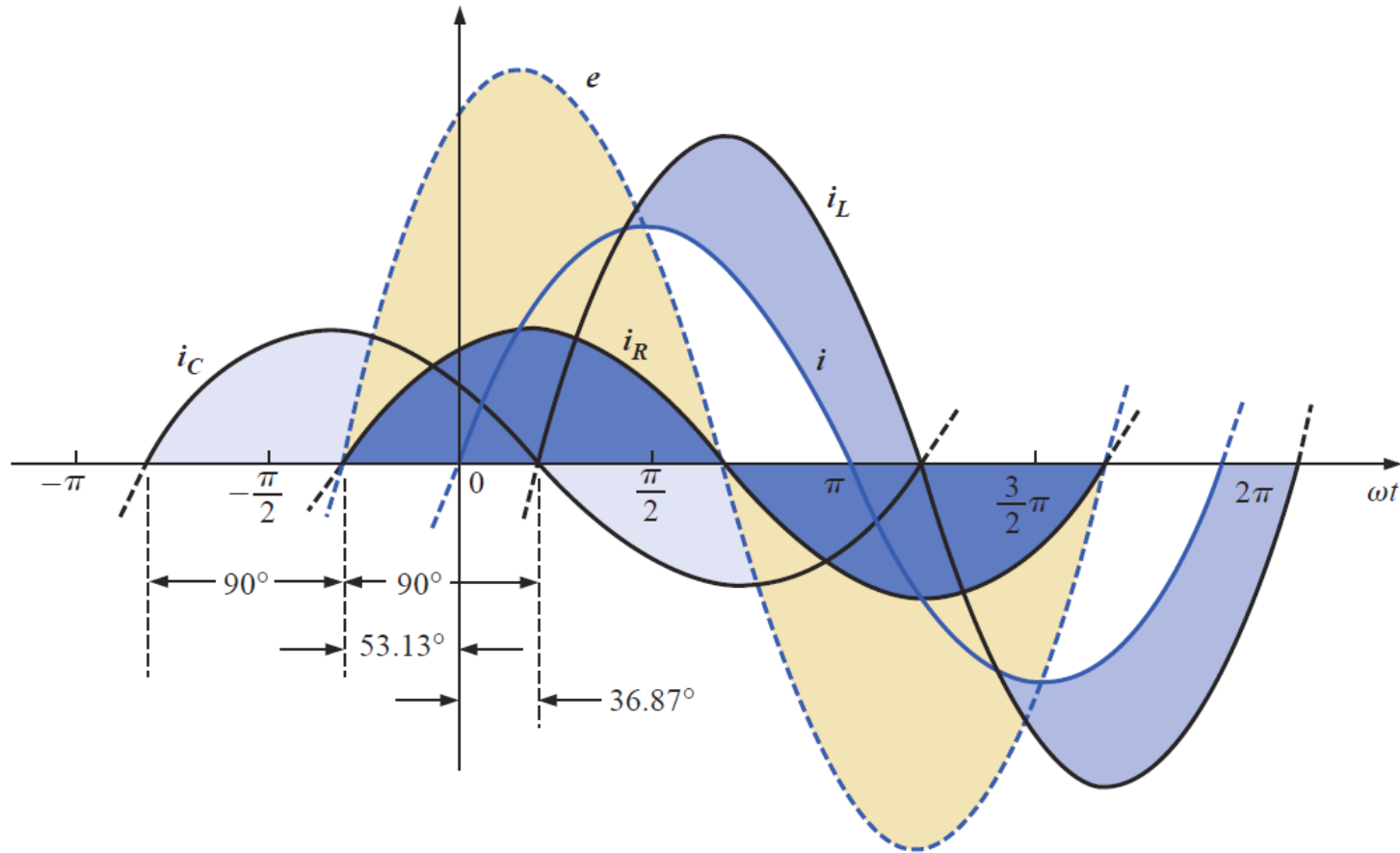

**FIG. 15.75**

Waveforms for the parallel R-L-C network of Fig. 15.71.

*Power:* The total power in watts delivered to the circuit is

$$\begin{aligned} P_T &= EI \cos \theta = (100 \text{ V})(50 \text{ A}) \cos 53.13^\circ = (5000)(0.6) \\ &= \mathbf{3000 \text{ W}} \end{aligned}$$

or 
$$P_T = E^2 G = (100 \text{ V})^2(0.3 \text{ S}) = \mathbf{3000 \text{ W}}$$

or, finally,

$$\begin{aligned} P_T &= P_R + P_L + P_C \\ &= EI_R \cos \theta_R + EI_L \cos \theta_L + EL_C \cos \theta_C \\ &= (100 \text{ V})(30 \text{ A}) \cos 0^\circ + (100 \text{ V})(70 \text{ A}) \cos 90^\circ \\ &\quad + (100 \text{ V})(30 \text{ A}) \cos 90^\circ \\ &= 3000 \text{ W} + 0 + 0 = \mathbf{3000 \text{ W}} \end{aligned}$$

*Power factor:* The power factor of the circuit is


$$F_p = \cos \theta_T = \cos 53.13^\circ = \mathbf{0.6 \text{ lagging}}$$

$$F_p = \cos \theta_T = \frac{G}{Y_T} = \frac{0.3 \text{ S}}{0.5 \text{ S}} = \mathbf{0.6 \text{ lagging}}$$

## 15.9 CURRENT DIVIDER RULE

Just similar to dc current divider rule:


$$\mathbf{I_1 = \frac{Z_2 I_T}{Z_1 + Z_2} \quad \text{or} \quad I_2 = \frac{Z_1 I_T}{Z_1 + Z_2}}$$

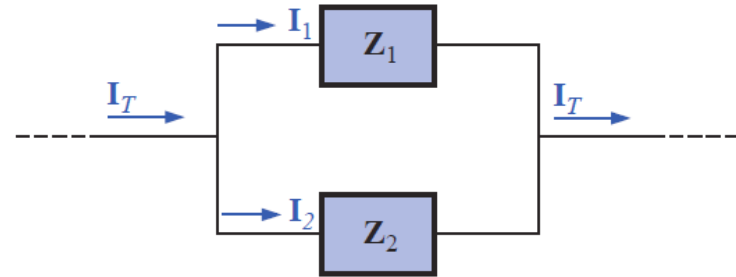

**FIG. 15.76**

*Applying the current divider rule.*

**EXAMPLE 15.16** Using the current divider rule, find the current through each parallel branch of Fig. 15.78.

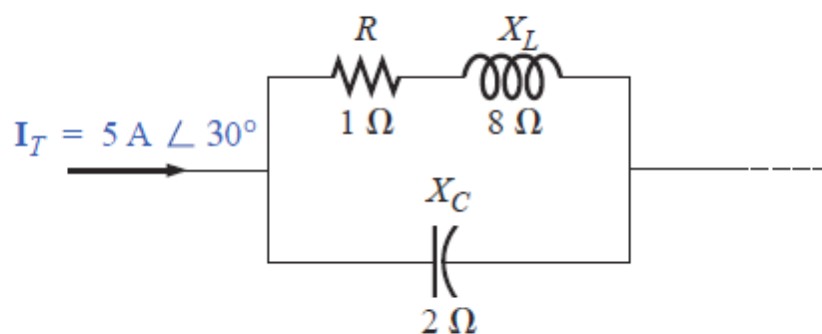

**FIG. 15.78**  
Example 15.16.

**Solution:**

$$\begin{aligned} \mathbf{I}_{R-L} &= \frac{\mathbf{Z}_C \mathbf{I}_T}{\mathbf{Z}_C + \mathbf{Z}_{R-L}} = \frac{(2 \Omega \angle -90^\circ)(5 \text{ A} \angle 30^\circ)}{-j 2 \Omega + 1 \Omega + j 8 \Omega} = \frac{10 \text{ A} \angle -60^\circ}{1 + j 6} \\ &= \frac{10 \text{ A} \angle -60^\circ}{6.083 \angle 80.54^\circ} \cong \mathbf{1.644 \text{ A} \angle -140.54^\circ} \end{aligned}$$

$$\begin{aligned} \mathbf{I}_C &= \frac{\mathbf{Z}_{R-L} \mathbf{I}_T}{\mathbf{Z}_{R-L} + \mathbf{Z}_C} = \frac{(1 \Omega + j 8 \Omega)(5 \text{ A} \angle 30^\circ)}{6.08 \Omega \angle 80.54^\circ} \\ &= \frac{(8.06 \angle 82.87^\circ)(5 \text{ A} \angle 30^\circ)}{6.08 \angle 80.54^\circ} = \frac{40.30 \text{ A} \angle 112.87^\circ}{6.083 \angle 80.54^\circ} \\ &= \mathbf{6.625 \text{ A} \angle 32.33^\circ} \end{aligned}$$

## 15.11 SUMMARY: PARALLEL ac NETWORKS

*For series ac circuits with reactive elements:*

- 1. The total admittance (impedance) will be frequency dependent.*
- 2. The impedance of any one element can be less than the total impedance (recall that for dc the total resistance must always be less than the smallest parallel resistance).*
- 3. The inductive and capacitive susceptances are always in direct opposition on an admittance diagram.*
- 4. Depending on the frequency applied, the same circuit can be either predominantly inductive or predominantly capacitive.*
- 5. At high frequencies the capacitive elements will usually have the most impact on the total impedance, while at lower frequencies the inductive elements will usually have the most impact.*
- 6. The magnitude of the current through any one branch can be greater than the source current.*




7. *The magnitude of the current through an element, compared to the other elements of the circuit, is directly related to the magnitude of its impedance; that is, the smaller the impedance of an element, the larger the magnitude of the current through the element.*
8. *The current through a coil or capacitor are always in direct opposition on a phasor diagram.*
9. *The applied voltage is always in phase with the current through the resistive elements, leads the current through all the inductive elements by  $90^\circ$ , and lags the current through all the capacitive elements by  $90^\circ$ .*
10. *The smaller the resistive element of a circuit compared to the net reactive susceptance, the closer the power factor is to unity.*

## 15.12 EQUIVALENT CIRCUITS


In series or parallel ac circuits:

- The total impedance of two or more elements is equivalent to an impedance that can be achieved with fewer elements of different values.
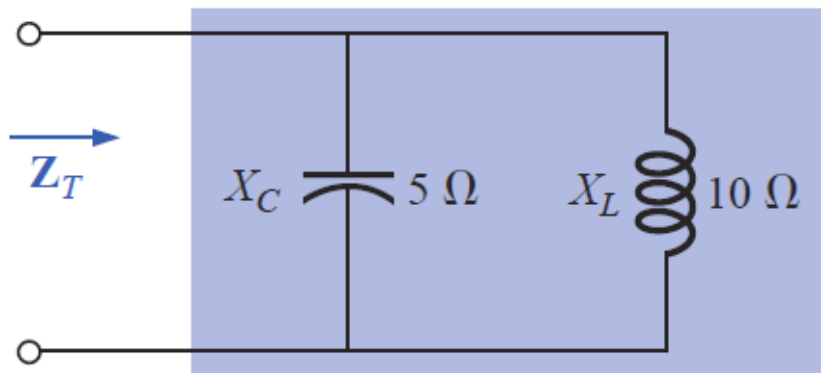
$$\begin{aligned} \mathbf{Z}_T &= \frac{\mathbf{Z}_C \mathbf{Z}_L}{\mathbf{Z}_C + \mathbf{Z}_L} = \frac{(5 \Omega \angle -90^\circ)(10 \Omega \angle 90^\circ)}{5 \Omega \angle -90^\circ + 10 \Omega \angle 90^\circ} = \frac{50 \angle 0^\circ}{5 \angle 90^\circ} \\ &= 10 \Omega \angle -90^\circ \end{aligned}$$




(a)

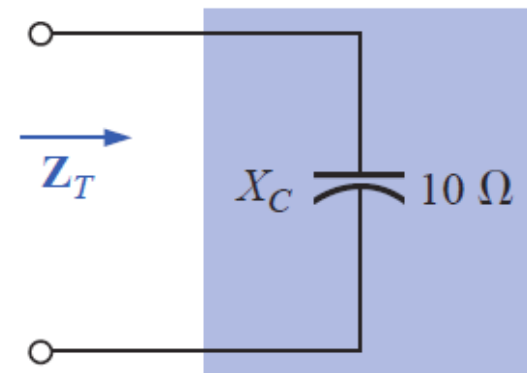

(b)

**FIG. 15.87**

*Defining the equivalence between two networks at a specific frequency.*

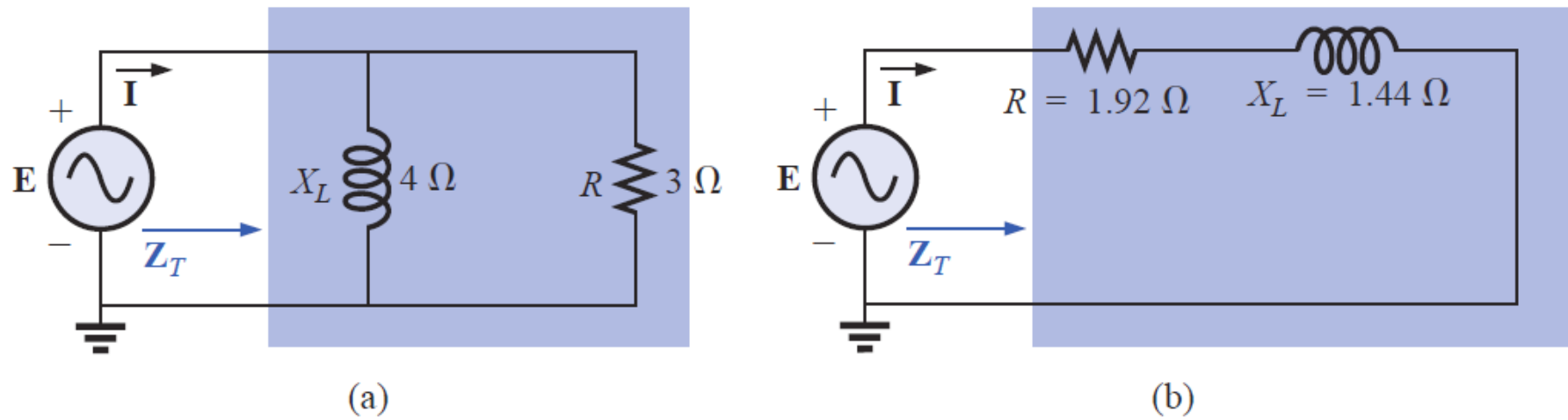


**FIG. 15.88**

*Finding the series equivalent circuit for a parallel R-L network.*

$$\begin{aligned}
 \mathbf{Z}_T &= \frac{\mathbf{Z}_L \mathbf{Z}_R}{\mathbf{Z}_L + \mathbf{Z}_R} = \frac{(4 \Omega \angle 90^\circ)(3 \Omega \angle 0^\circ)}{4 \Omega \angle 90^\circ + 3 \Omega \angle 0^\circ} \\
 &= \frac{12 \angle 90^\circ}{5 \angle 53.13^\circ} = 2.40 \Omega \angle 36.87^\circ \\
 &= 1.920 \Omega + j 1.440 \Omega
 \end{aligned}$$

*the term equivalent refers only to the fact that for the same applied potential, the same impedance and input current will result.*

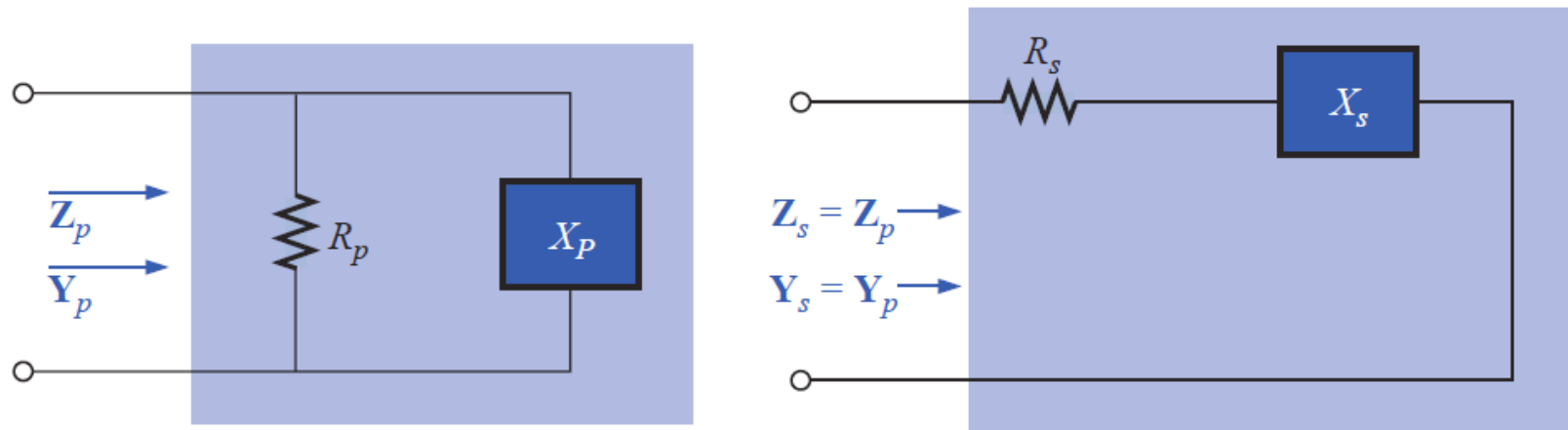

**FIG. 15.89**

*Defining the parameters of equivalent series and parallel networks.*

$$\mathbf{Y}_p = \frac{1}{R_p} + \frac{1}{\pm j X_p} = \frac{1}{R_p} \mp j \frac{1}{X_p}$$

$$\mathbf{Z}_p = \frac{1}{\mathbf{Y}_p} = \frac{1}{(1/R_p) \mp j (1/X_p)} = \frac{1/R_p}{(1/R_p)^2 + (1/X_p)^2} \pm j \frac{1/X_p}{(1/R_p)^2 + (1/X_p)^2}$$

$$\mathbf{Z}_p = \frac{R_p X_p^2}{X_p^2 + R_p^2} \pm j \frac{R_p^2 X_p}{X_p^2 + R_p^2} = R_s \pm j X_s$$

$$R_s = \frac{R_p X_p^2}{X_p^2 + R_p^2}$$

$$X_s = \frac{R_p^2 X_p}{X_p^2 + R_p^2}$$


$$\mathbf{Z}_s = R_s \pm j X_s$$

$$\begin{aligned} \mathbf{Y}_s &= \frac{1}{\mathbf{Z}_s} = \frac{1}{R_s \pm j X_s} = \frac{R_s}{R_s^2 + X_s^2} \mp j \frac{X_s}{R_s^2 + X_s^2} \\ &= G_p \mp j B_p = \frac{1}{R_p} \mp j \frac{1}{X_p} \end{aligned}$$

$$R_p = \frac{R_s^2 + X_s^2}{R_s}$$

$$X_p = \frac{R_s^2 + X_s^2}{X_s}$$

$$i = \sqrt{2} (12) \sin 1000t$$

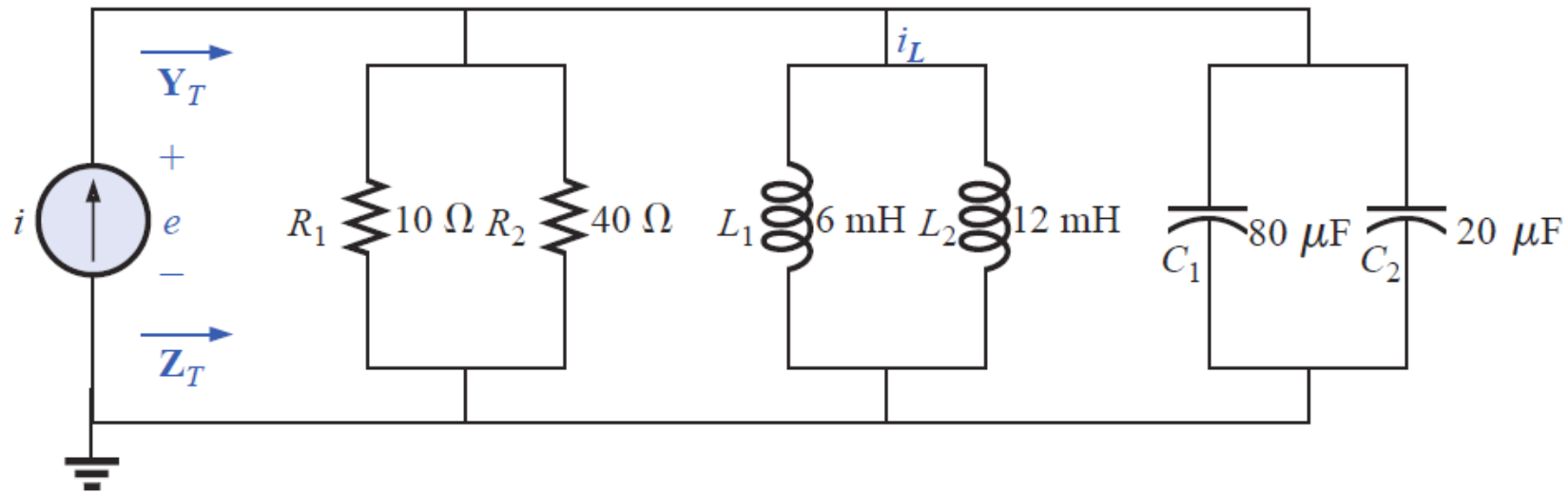


$$R_T = 10 \Omega \parallel 40 \Omega = 8 \Omega$$

$$L_T = 6 \text{ mH} \parallel 12 \text{ mH} = 4 \text{ mH}$$

$$C_T = 80 \mu\text{F} + 20 \mu\text{F} = 100 \mu\text{F}$$

$$\mathbf{I} = 12 \text{ A} \angle 0^\circ$$

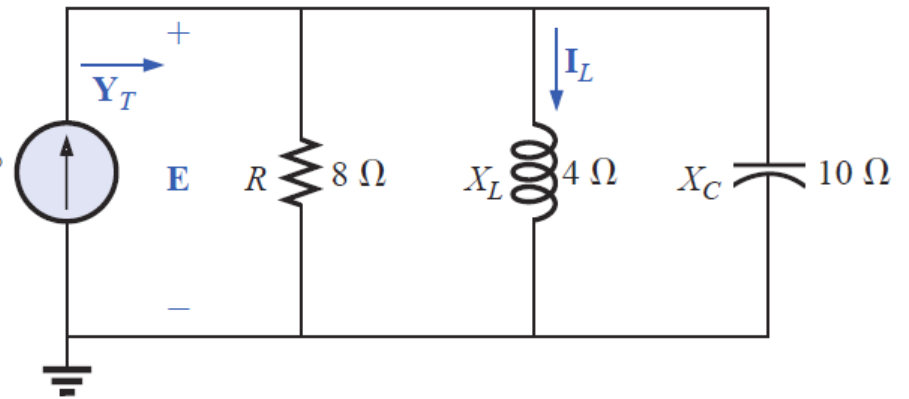

**FIG. 15.93**

Applying phasor notation to the network of Fig. 15.92.