

Power (ac)

19.1 INTRODUCTION

- The discussion about power in the previous chapters only included the *average power* delivered to ac network.
- We will examine the total power equation and introduce two additional types of power: *apparent power* and *reactive power*.

The power at any instant is always defined as:

$$p = v \cdot i$$

When v and i are sinusoidal:

$$v = V_m \sin(\omega t + \theta)$$

$$i = I_m \sin(\omega t)$$

Load purely resistive $\theta = 0^\circ$

Load purely inductive $\theta = 90^\circ$

Load purely capacitive $\theta = -90^\circ$

Load primarily inductive: $\theta > 0^\circ$ (v leads i)

Load primarily capacitive: $\theta < 0^\circ$ (i leads v)

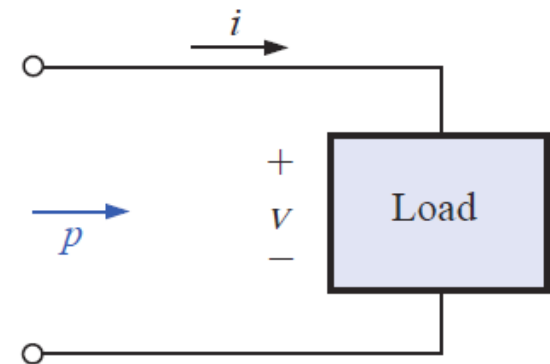


FIG. 19.1

Defining the power delivered to a load.

$$P = V_m I_m \sin(\omega t + \theta) \sin(\omega t)$$

Using the trigonometric identity: $\cos(\alpha \pm \beta) = \cos(\alpha) \cos(\beta) \mp \sin(\alpha) \sin(\beta)$
two times results in:

$$p = VI \cos \theta (1 - \cos 2\omega t) + VI \sin \theta (\sin 2\omega t)$$

Where: V and I are the rms values, $V = V_m/\sqrt{2}$ and $I = I_m/\sqrt{2}$

If Equation (19.1) is expanded to the form

$$p = \underbrace{VI \cos \theta}_{\text{Average}} - \underbrace{VI \cos \theta}_{\text{Peak}} \underbrace{\cos 2\omega t}_{2x} + \underbrace{VI \sin \theta}_{\text{Peak}} \underbrace{\sin 2\omega t}_{2x}$$

Three terms:

- 1- **Average power:** independent of time
- 2- **The other two terms:** vary at a frequency of (2ω)
Peak values having similar format:
($VI \cos \theta$ and $VI \sin \theta$)

19.2 RESISTIVE CIRCUIT

$$\theta = 0^\circ \Rightarrow P_R = VI(1 - \cos 2\omega t)$$

$$p_R = VI - VI \cos 2\omega t$$

- VI is the average term
- $-VI \cos 2\omega t$ is a negative cosine wave with frequency twice the frequency of the voltage and current

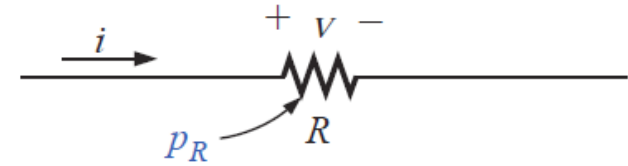


FIG. 19.2

Determining the power delivered to a purely resistive load.

$T_1 =$ period of input quantities

$T_2 =$ period of power curve p_R

The power curve is always positive. \Rightarrow

the total power delivered to a resistor will be dissipated in the form of heat.

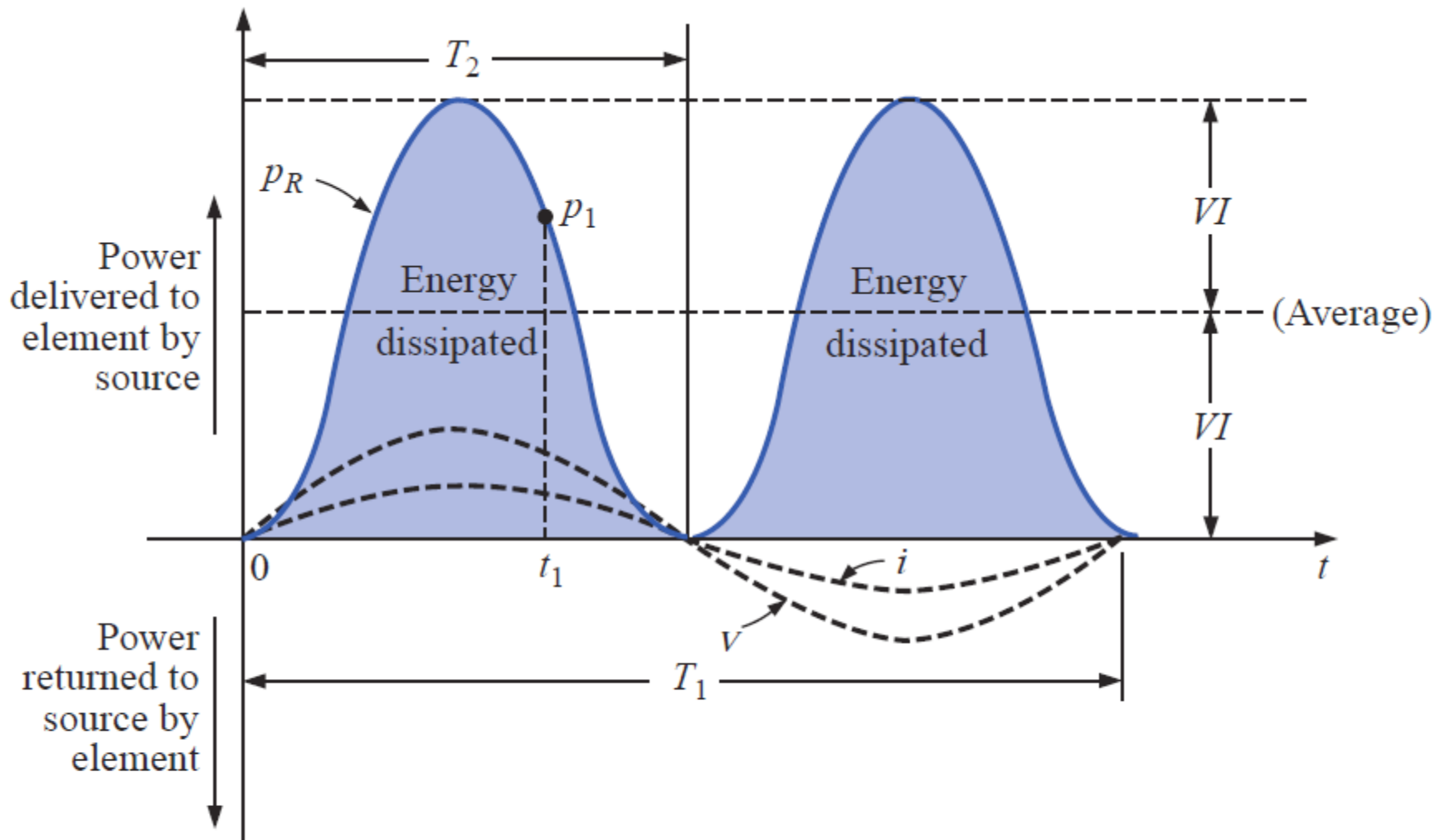


FIG. 19.3

Power versus time for a purely resistive load.

- The power returned to the source is represented by the portion of the curve below the axis, which is zero in this case.
- The power p_I dissipated by the resistor at time t_1 can be found by simply substituting the time t_1 into the equation of the power, as indicated in Fig. 19.3.
- The **average (real) power** is VI :

$$P = VI = \frac{V_m I_m}{2} = I^2 R = \frac{V^2}{R} \quad (\text{watts, W})$$

The energy dissipated by the resistor W_R over any period of time t is:

$$W_R = Pt = VIt \quad (\text{Joule, J})$$

For one cycle $t=T_1$:

$$W_R = VIT_1 = \frac{VI}{f_1} \quad (\text{Joule, J})$$

19.3 APPARENT POWER

From what we have studied it seems *apparent* that the power delivered to the load is simply:

$$P = VI$$

We found: the power factor $\cos \theta$ of the load has a significant effect on the power dissipated.

The product VI is not the power delivered, but it is a useful power rating in the study of ac networks: it is called the *apparent power* and is represented by the symbol S .

It's unit is simply: *Volt-Ampere* (VA)

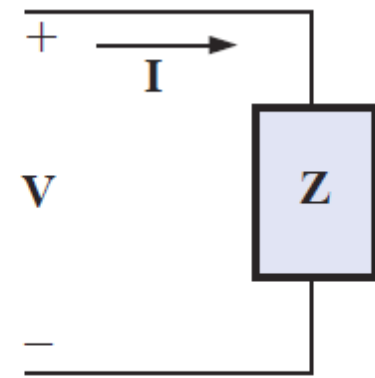


FIG. 19.4

Defining the apparent power to a load.

$$S = VI$$

(volt-amperes, VA)

or, since

$$V = IZ \quad \text{and} \quad I = \frac{V}{Z}$$

$$S = I^2 Z$$

(VA)

$$S = \frac{V^2}{Z}$$

(VA)

The average power to the load of Fig. 19.4 is

$$P = VI \cos \theta$$

However,

$$S = VI$$

Therefore,

$$P = S \cos \theta$$

(W)

and the power factor of a system F_p is

$$F_p = \cos \theta = \frac{P}{S} \quad (\text{unitless})$$

For a purely resistive circuit:

$$P = VI = S$$

$$F_p = \cos \theta = \frac{P}{S} = 1$$

In general: power equipments are rated in: (**VA**) or (**kVA**)

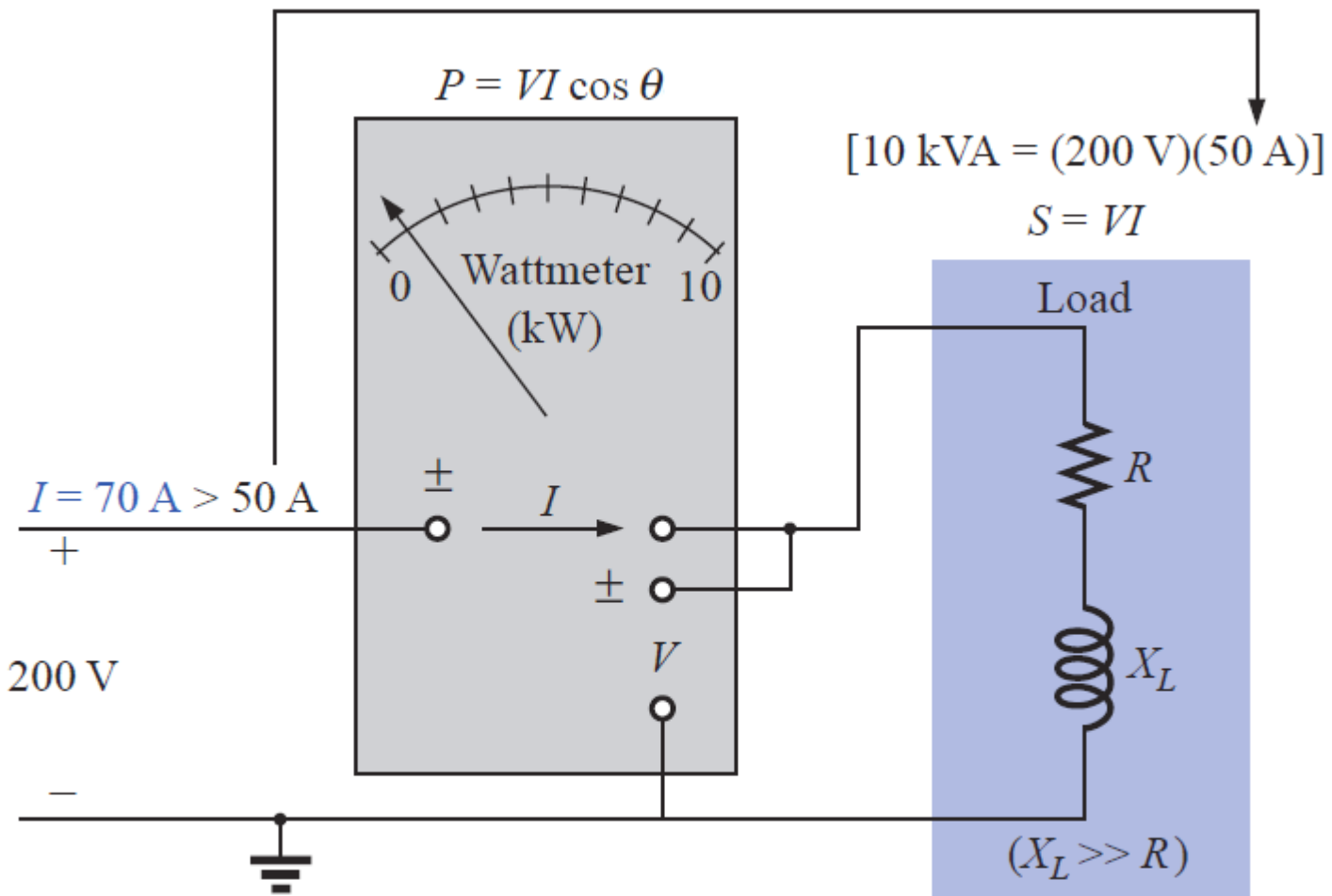


FIG. 19.5

Demonstrating the reason for rating a load in kVA rather than kW.

19.4 INDUCTIVE CIRCUIT AND REACTIVE POWER

v leads i by 90° : $\theta = 90^\circ, \Rightarrow$

$$p_L = VI \cos(90^\circ)(1 - \cos 2\omega t) + VI \sin(90^\circ)(\sin 2\omega t)$$

$$= 0 + VI \sin 2\omega t$$

$$p_L = VI \sin 2\omega t$$

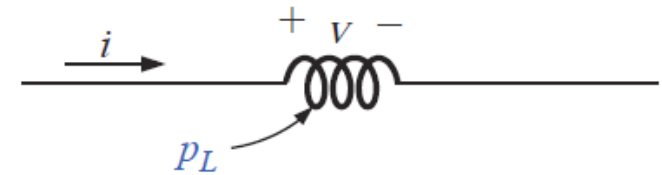


FIG. 19.6

Defining the power level for a purely inductive load

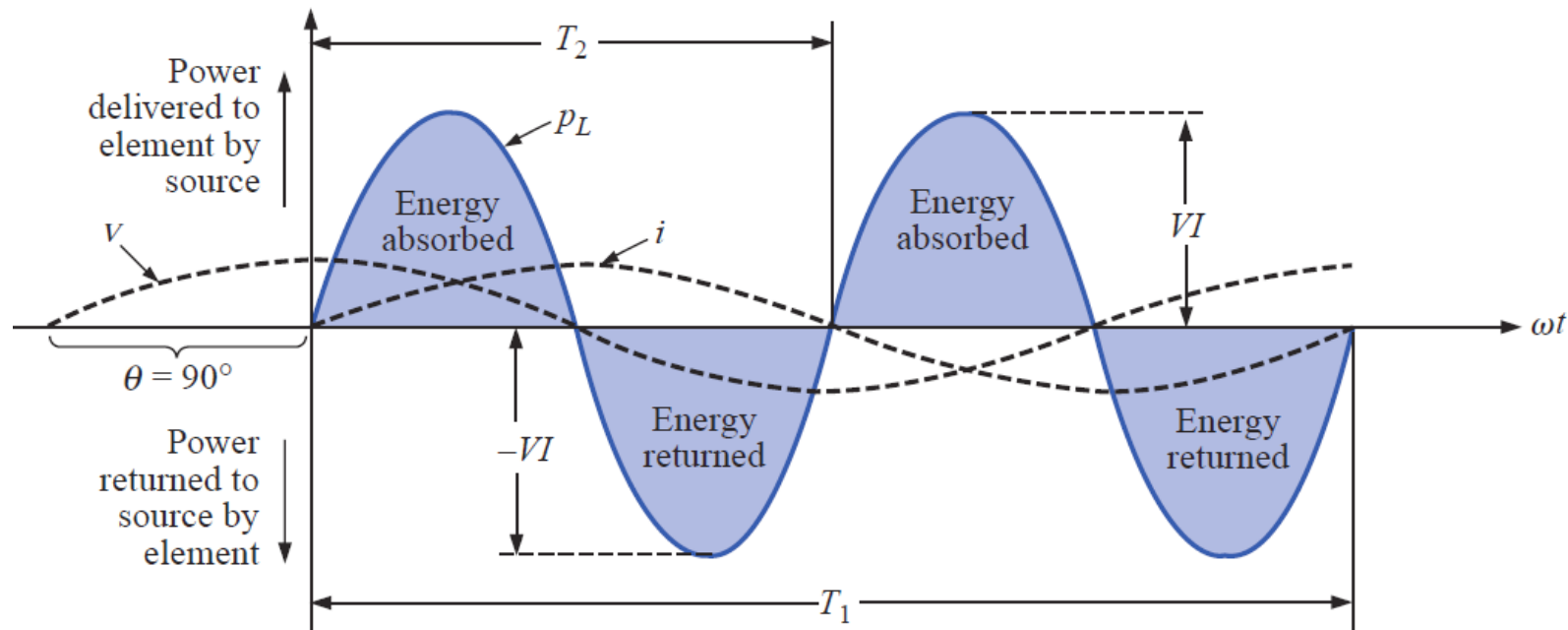


FIG. 19.7

The power curve for a purely inductive load.

- It is a sinewave with frequency twice that of the voltage or current and a peak value equal to VI .
- There is no average value

$T_1 =$ period of either input quantity

$T_2 =$ period of p_L curve

Over one cycle: area above the horizontal axis = The area below the axis
 power delivered to inductor = power returned by inductor

The net flow of power to the pure (ideal) inductor is zero over a full cycle, and no energy is lost in the transaction.

The peak value of the power curve ($V \cdot I$) is defined as the *reactive power*.

In general: *reactive power* $\equiv V \cdot I \cdot \sin \theta$

A factor appearing in the general form of the power:

$$P = VI \cos \theta (1 - \cos 2\omega t) + VI \sin \theta (\sin 2\omega t)$$

The symbol of reactive power is Q unit *Volt-Ampere Reactive* (VAR)

$$Q = VI \sin \theta$$

(volt-ampere reactive, VAR)

Inductor: $\theta = 90^\circ \Rightarrow$

$$Q_L = VI \quad (\text{VAR})$$

or, since $V = IX_L$ or $I = V/X_L$,

$$Q_L = I^2 X_L \quad (\text{VAR})$$

or

$$Q_L = \frac{V^2}{X_L} \quad (\text{VAR})$$

Apparent power: $S = VI$

Average power: $P = VI \cos \theta = 0$

Then:

$$F_p = \cos \theta = \frac{P}{S} = \frac{0}{VI} = 0$$

The energy stored by the inductor during half-cycle is:

$$W_L = \left(\frac{2VI}{\pi}\right) \times \left(\frac{T_2}{2}\right) \quad \boxed{W_L = \frac{VIT_2}{\pi}} \quad \boxed{W_L = \frac{VI}{\pi f_2}} \quad (\text{J})$$

$$W_L = \frac{VI}{\pi(2f_1)} = \frac{VI}{\omega_1}$$

However,

$$V = IX_L = I\omega_1 L$$

so that

$$W_L = \frac{(I\omega_1 L)I}{\omega_1}$$

and

$$\boxed{W_L = LI^2} \quad (\text{J})$$

The energy stored or released by the inductor during half-cycle.

19.5 CAPACITIVE CIRCUIT

i leads v by 90° : $\theta = -90^\circ$, \Rightarrow

$$p_C = VI \cos(-90^\circ)(1 - \cos 2\omega t) + VI \sin(-90^\circ)(\sin 2\omega t)$$

$$= 0 - VI \sin 2\omega t$$

$$p_C = -VI \sin 2\omega t$$


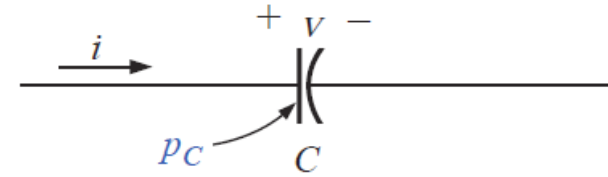


FIG. 19.8

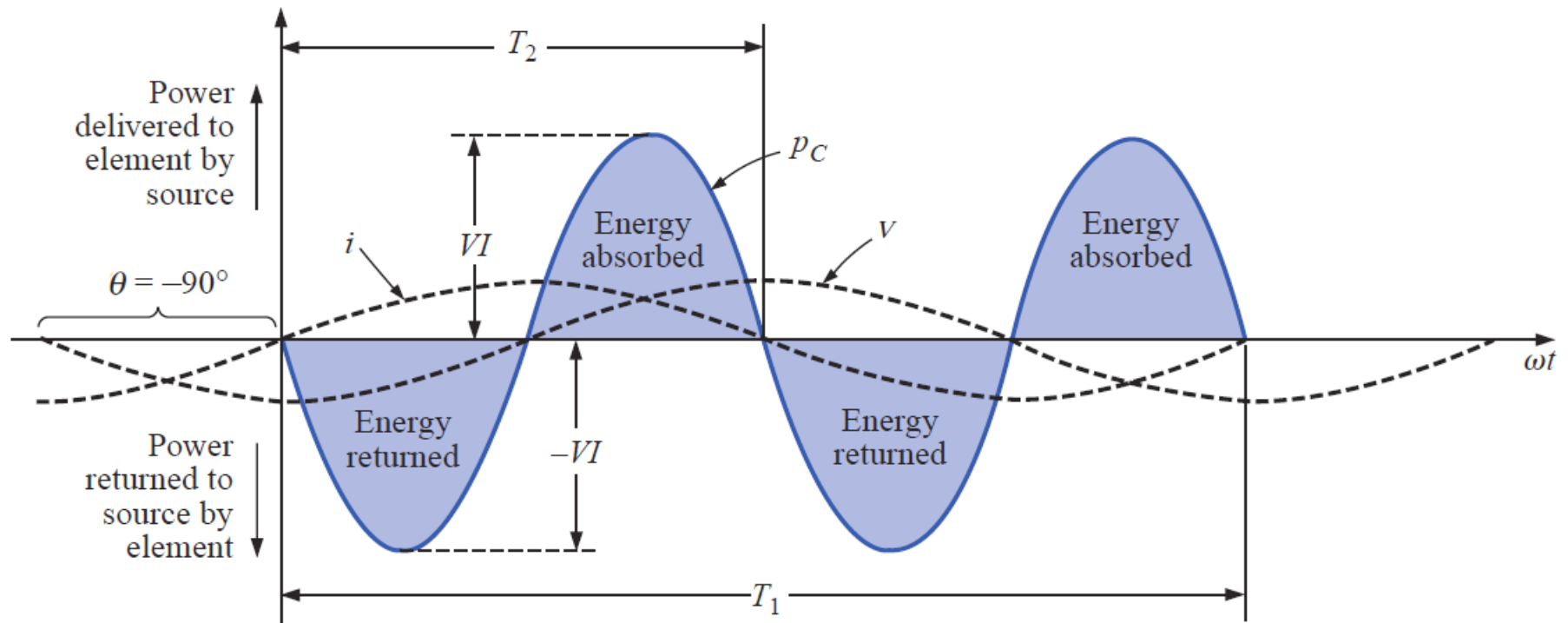Defining the power level for a purely capacitive load.



- It is a negative sinewave with frequency twice that of the voltage or current and a peak value equal to VI .
- There is no average value

$$T_1 = \text{period of either input quantity}$$

$$T_2 = \text{period of } p_L \text{ curve}$$

Over one cycle: area above the horizontal axis = The area below the axis
 power delivered to Capacitor = power returned by Capacitor

The net flow of power to the pure (ideal) capacitor is zero over a full cycle, and no energy is lost in the transaction.

The reactive power associated with the capacitor is again the peak value of P_C curve

$$Q_C = VI \quad (\text{VAR})$$

since $V = IX_C$ and $I = V/X_C$, the reactive power

$$Q_C = I^2 X_C \quad Q_C = \frac{V^2}{X_C} \quad (\text{VAR})$$

Apparent power: $S = VI$

Average power: $P = VI \cos \theta = 0$

Then:

$$F_p = \cos \theta = \frac{P}{S} = \frac{0}{VI} = 0$$

The energy stored by the capacitor during the positive half-cycle is:

$$W_C = CV^2 \quad (\text{J})$$

19.6 THE POWER TRIANGLE

The three quantities *average power*, *apparent power*, and *reactive power* can be related in the vector domain by:

$$\mathbf{S} = \mathbf{P} + \mathbf{Q}$$

with

$$\mathbf{P} = P \angle 0^\circ \quad \mathbf{Q}_L = Q_L \angle 90^\circ \quad \mathbf{Q}_C = Q_C \angle -90^\circ$$

\mathbf{S} is called the *phasor power*,

Inductive Load:

$$\mathbf{S} = P + jQ_L$$

The 90° shift in Q_L from P give another name for the reactive power: *quadrature power*.

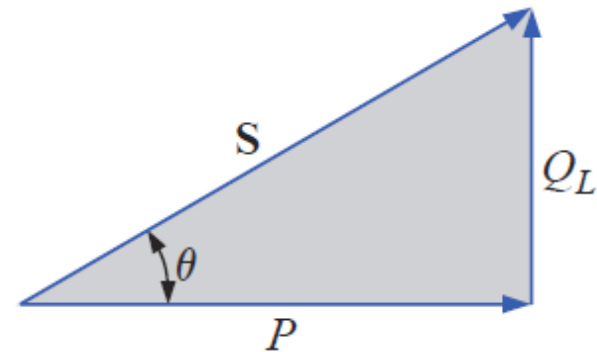


FIG. 19.10

Power diagram for inductive loads.

Capacitive Load:

$$S = P - jQ_c$$

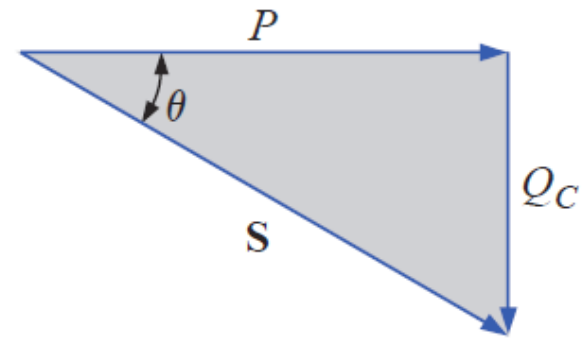


FIG. 19.11

Power diagram for capacitive loads.

If Load has both Capacitive and inductive elements:

The reactive component of the power triangle is the difference between Q_L and Q_C :

1. $Q_L > Q_C$ Power triangle similar to the case of *inductive load*
2. $Q_C > Q_L$ Power triangle similar to the case of *capacitive load*

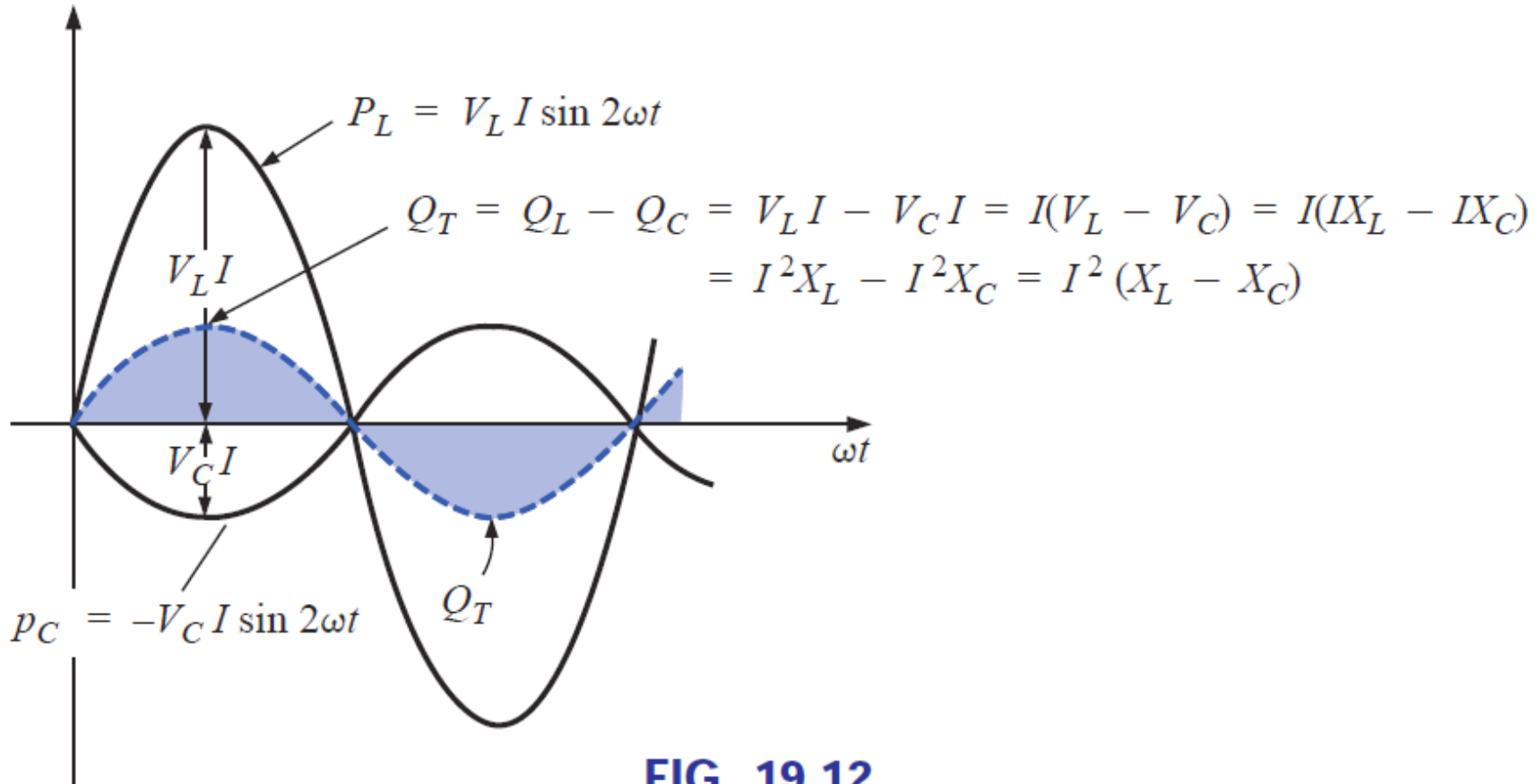


FIG. 19.12

Demonstrating why the net reactive power is the difference between that delivered to inductive and capacitive elements.

Series R-L-C Load:

If we multiply each vector in the impedance diagram by I^2 :

We obtain the power triangle:

$$S^2 = P^2 + Q^2$$

It is particularly interesting that the equation

$$\mathbf{S} = \mathbf{VI}^*$$

Provides the vector form of the apparent power.

\mathbf{V} is the phasor voltage across the system

\mathbf{I}^* is the complex conjugate of the phasor current

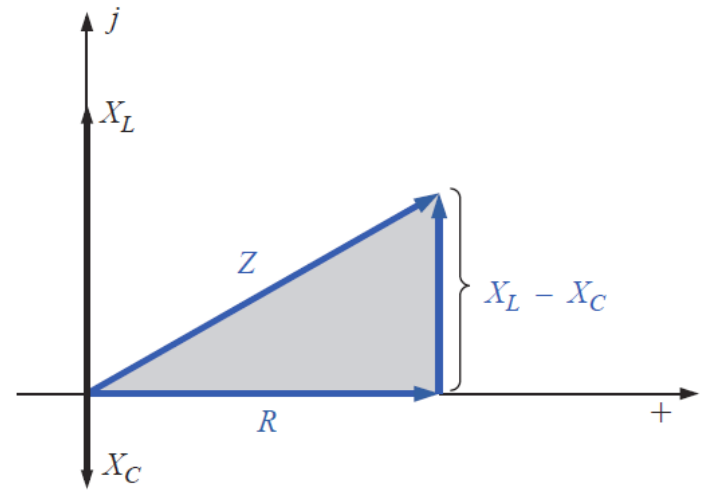


FIG. 19.13

Impedance diagram for a series R-L-C circuit.

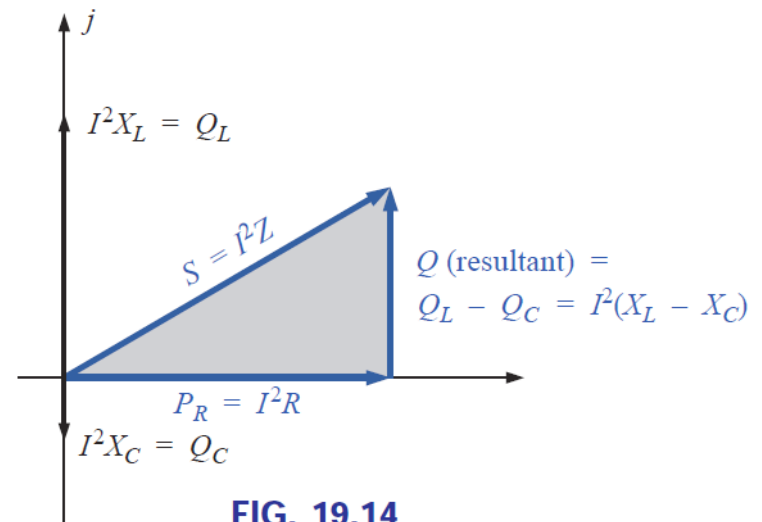


FIG. 19.14

The result of multiplying each vector of Fig. 19.13 by I^2 for a series R-L-C circuit.

$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}_T} = \frac{10 \text{ V } \angle 0^\circ}{3 \Omega + j4 \Omega} = \frac{10 \text{ V } \angle 0^\circ}{5 \Omega \angle 53.13^\circ} = 2 \text{ A } \angle -53.13^\circ$$

The real power $P = I^2 R = (2 \text{ A})^2 (3 \Omega) = 12 \text{ W}$

the reactive power is $Q_L = I^2 X_L = (2 \text{ A})^2 (4 \Omega) = 16 \text{ VAR (L)}$

$$\mathbf{S} = P + jQ_L = 12 \text{ W} + j16 \text{ VAR (L)} = 20 \text{ VA } \angle 53.13^\circ$$

$$\mathbf{S} = \mathbf{V}\mathbf{I}^* = (10 \text{ V } \angle 0^\circ)(2 \text{ A } \angle +53.13^\circ) = 20 \text{ VA } \angle 53.13^\circ$$

$$P = VI \cos \theta \quad P = S \cos \theta$$

$$F_p = \cos \theta = \frac{P}{S}$$


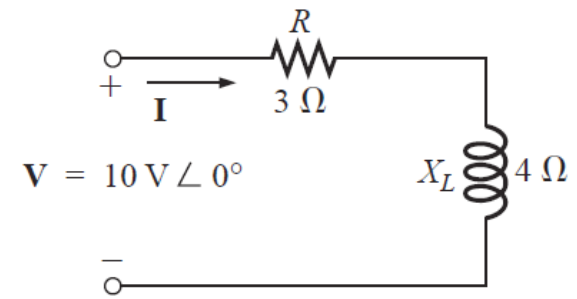


FIG. 19.15

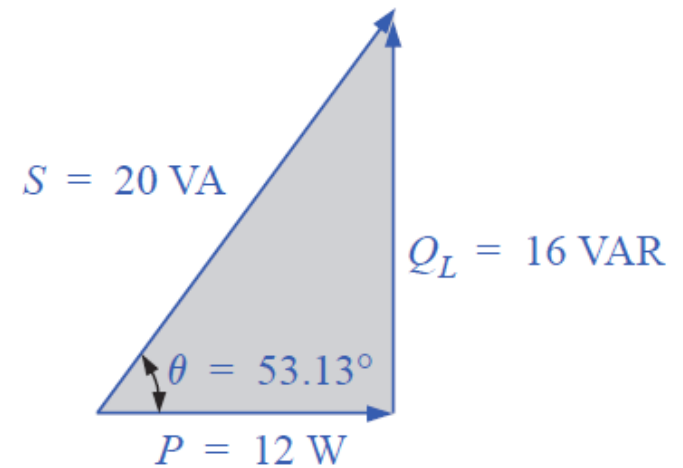Demonstrating the validity of Eq. (19.29).




19.7 THE TOTAL P , Q , AND S

The total **number of watts**, **volt-amperes reactive**, and **volt-amperes**, and the **power factor** of any system can be found using the following procedure:

1. Find the **real power** and **reactive power** for each branch of the circuit.
2. The **total real power** of the system (P_T) is then the sum of the average power delivered to each branch.
3. The **total reactive power** (Q_T) is the **difference** between the **reactive power** of the **inductive loads** and that of the **capacitive loads**.
4. The **total apparent power** is $S_T = \sqrt{P_T^2 + Q_T^2}$.
5. The **total power factor** is P_T/S_T .

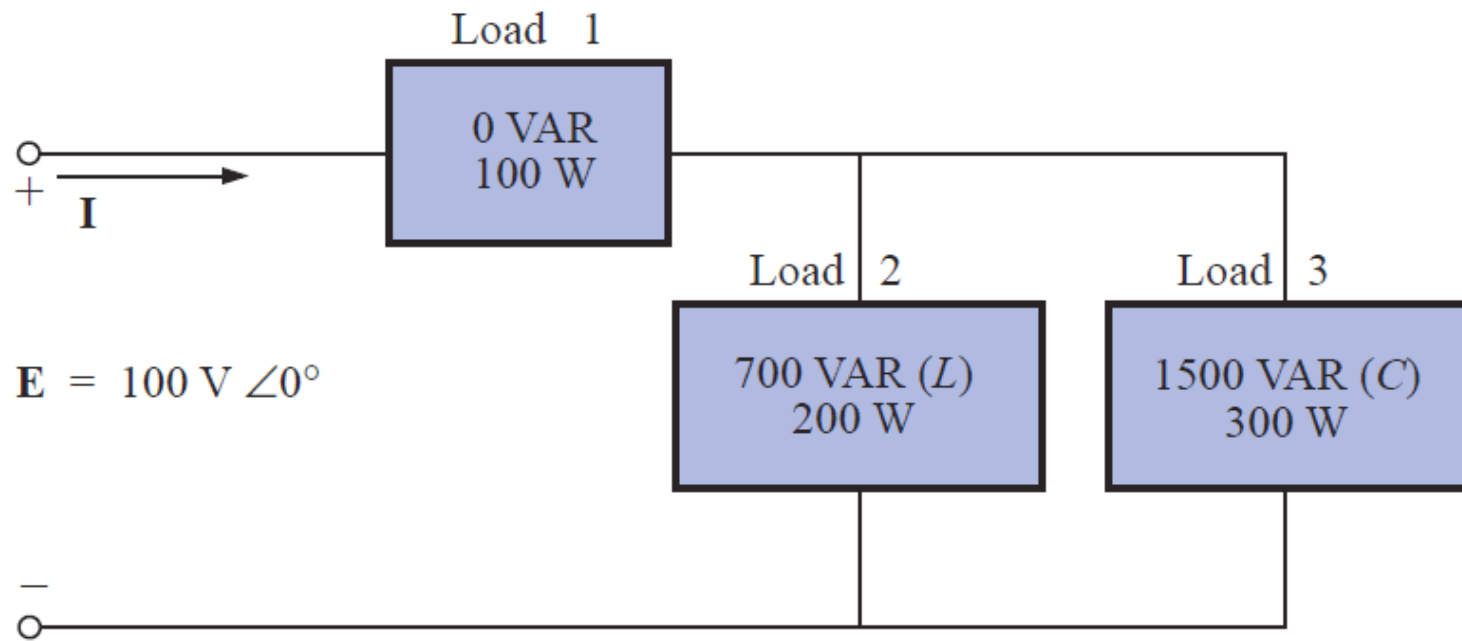EXAMPLE 19.1 Find the total number of watts, volt-amperes reactive, and volt-amperes, and the power factor F_p of the network in Fig. 19.17. Draw the power triangle and find the current in phasor form.



Solution: Construct a table such as shown in Table 19.1.

TABLE 19.1

Load	W	VAR	VA
1	100	0	100
2	200	700 (L)	$\sqrt{(200)^2 + (700)^2} = 728.0$
3	300	1500 (C)	$\sqrt{(300)^2 + (1500)^2} = 1529.71$
	$P_T = 600$	$Q_T = 800 (C)$	$S_T = \sqrt{(600)^2 + (800)^2} = 1000$
	Total power dissipated	Resultant reactive power of network	(Note that $S_T \neq$ sum of each branch: $1000 \neq 100 + 728 + 1529.71$)

Thus,

$$F_p = \frac{P_T}{S_T} = \frac{600 \text{ W}}{1000 \text{ VA}} = \mathbf{0.6 \text{ leading (C)}}$$

The power triangle is shown in Fig. 19.18.

Since $S_T = VI = 1000 \text{ VA}$, $I = 1000 \text{ VA}/100 \text{ V} = 10 \text{ A}$; and since θ of $\cos \theta = F_p$ is the angle between the input voltage and current:

$$\mathbf{I = 10 \text{ A} \angle +53.13^\circ}$$

The plus sign is associated with the phase angle since the circuit is predominantly capacitive.

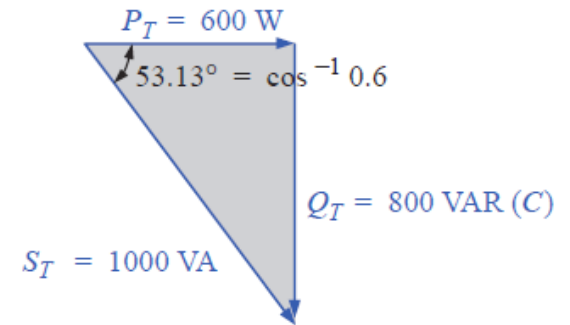


FIG. 19.18

Power triangle for Example 19.1.

EXAMPLE 19.2

- a. Find the total number of watts, volt-amperes reactive, and volt-amperes, and the power factor F_p for the network of Fig. 19.19.

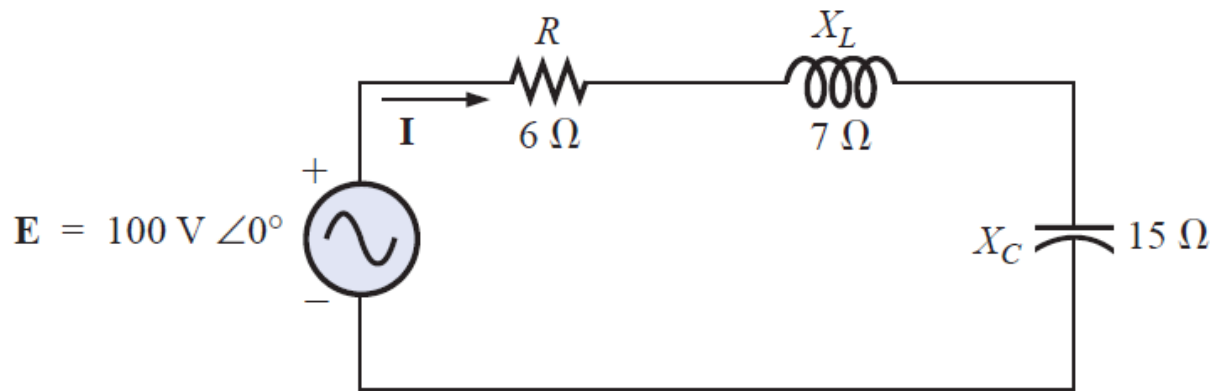


FIG. 19.19

Example 19.2.

- b. Sketch the power triangle.
- c. Find the energy dissipated by the resistor over one full cycle of the input voltage if the frequency of the input quantities is 60 Hz.
- d. Find the energy stored in, or returned by, the capacitor or inductor over one half-cycle of the power curve for each if the frequency of the input quantities is 60 Hz.

Solutions:

$$\text{a. } \mathbf{I} = \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{100 \text{ V } \angle 0^\circ}{6 \Omega + j7 \Omega - j15 \Omega} = \frac{100 \text{ V } \angle 0^\circ}{10 \Omega \angle -53.13^\circ} \\ = 10 \text{ A } \angle 53.13^\circ$$

$$\mathbf{V}_R = (10 \text{ A } \angle 53.13^\circ)(6 \Omega \angle 0^\circ) = 60 \text{ V } \angle 53.13^\circ$$

$$\mathbf{V}_L = (10 \text{ A } \angle 53.13^\circ)(7 \Omega \angle 90^\circ) = 70 \text{ V } \angle 143.13^\circ$$

$$\mathbf{V}_C = (10 \text{ A } \angle 53.13^\circ)(15 \Omega \angle -90^\circ) = 150 \text{ V } \angle -36.87^\circ$$

$$P_T = EI \cos \theta = (100 \text{ V})(10 \text{ A}) \cos 53.13^\circ = \mathbf{600 \text{ W}}$$

$$= I^2 R = (10 \text{ A})^2 (6 \Omega) = \mathbf{600 \text{ W}}$$

$$= \frac{V_R^2}{R} = \frac{(60 \text{ V})^2}{6} = \mathbf{600 \text{ W}}$$

$$S_T = EI = (100 \text{ V})(10 \text{ A}) = \mathbf{1000 \text{ VA}}$$

$$= I^2 Z_T = (10 \text{ A})^2 (10 \Omega) = \mathbf{1000 \text{ VA}}$$

$$= \frac{E^2}{Z_T} = \frac{(100 \text{ V})^2}{10 \Omega} = \mathbf{1000 \text{ VA}}$$

$$Q_T = EI \sin \theta = (100 \text{ V})(10 \text{ A}) \sin 53.13^\circ = \mathbf{800 \text{ VAR}}$$

$$= Q_C - Q_L$$

$$= I^2 (X_C - X_L) = (10 \text{ A})^2 (15 \Omega - 7 \Omega) = \mathbf{800 \text{ VAR}}$$

$$Q_T = \frac{V_C^2}{X_C} - \frac{V_L^2}{X_L} = \frac{(150 \text{ V})^2}{15 \Omega} - \frac{(70 \text{ V})^2}{7 \Omega}$$

$$= 1500 \text{ VAR} - 700 \text{ VAR} = \mathbf{800 \text{ VAR}}$$

$$F_p = \frac{P_T}{S_T} = \frac{600 \text{ W}}{1000 \text{ VA}} = \mathbf{0.6 \text{ leading (C)}}$$

b. The power triangle is as shown in Fig. 19.20.

$$\text{c. } W_R = \frac{V_R I}{f_1} = \frac{(60 \text{ V})(10 \text{ A})}{60 \text{ Hz}} = \mathbf{10 \text{ J}}$$

$$\text{d. } W_L = \frac{V_L I}{\omega_1} = \frac{(70 \text{ V})(10 \text{ A})}{(2\pi)(60 \text{ Hz})} = \frac{700 \text{ J}}{377} = \mathbf{1.86 \text{ J}}$$

$$W_C = \frac{V_C I}{\omega_1} = \frac{(150 \text{ V})(10 \text{ A})}{377 \text{ rad/s}} = \frac{1500 \text{ J}}{377} = \mathbf{3.98 \text{ J}}$$

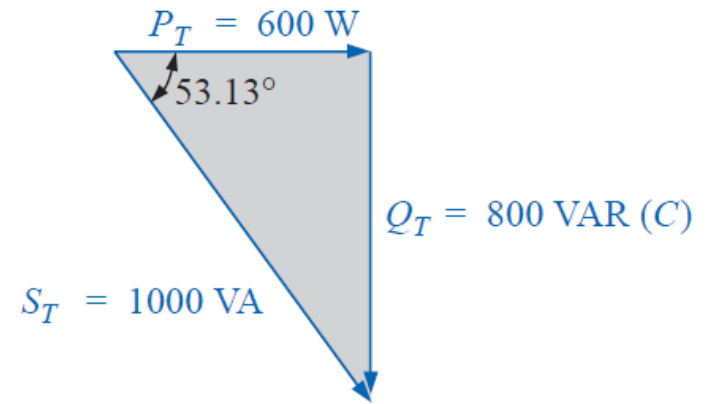


FIG. 19.20

Power triangle for Example 19.2.

EXAMPLE 19.3 For the system of Fig. 19.21,

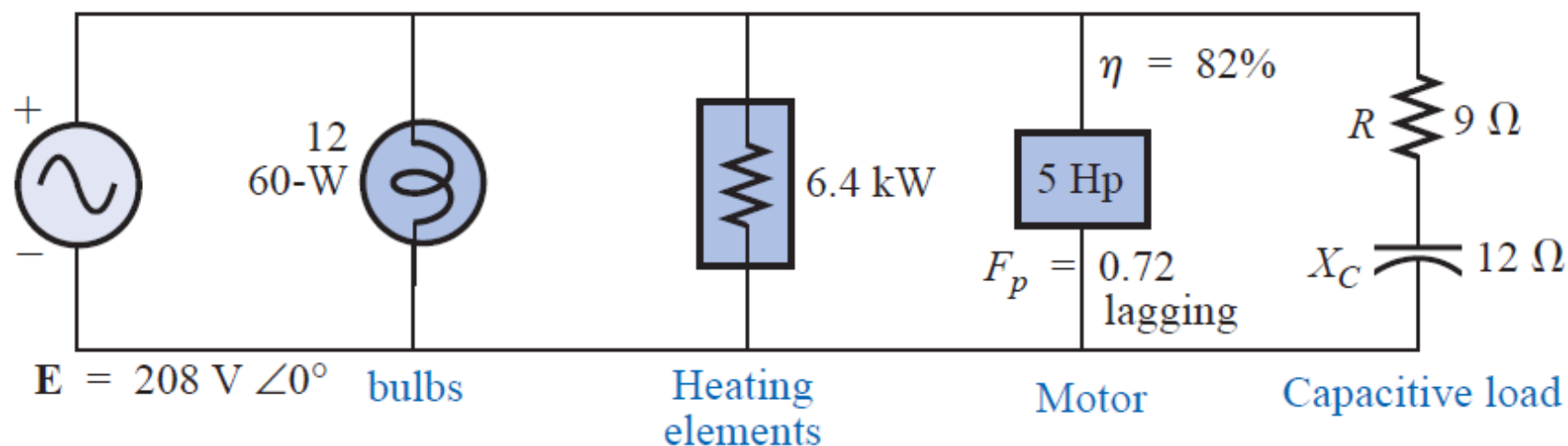


FIG. 19.21

Example 19.3.

- Find the average power, apparent power, reactive power, and F_p for each branch.
- Find the total number of watts, volt-amperes reactive, and volt-amperes, and the power factor of the system. Sketch the power triangle.
- Find the source current I .

Solutions:

a. *Bulbs:*

Total dissipation of applied power

$$P_1 = 12(60 \text{ W}) = \mathbf{720 \text{ W}}$$

$$Q_1 = \mathbf{0 \text{ VAR}}$$

$$S_1 = P_1 = \mathbf{720 \text{ VA}}$$

$$F_{p_1} = \mathbf{1}$$

Heating elements:

Total dissipation of applied power

$$P_2 = \mathbf{6.4 \text{ kW}}$$

$$Q_2 = \mathbf{0 \text{ VAR}}$$

$$S_2 = P_2 = \mathbf{6.4 \text{ kVA}}$$

$$F_{p_2} = \mathbf{1}$$

Motor:

$$\eta = \frac{P_o}{P_i} \longrightarrow P_i = \frac{P_o}{\eta} = \frac{5(746 \text{ W})}{0.82} = \mathbf{4548.78 \text{ W}} = P_3$$

$$F_p = \mathbf{0.72 \text{ lagging}}$$

$$P_3 = S_3 \cos \theta \longrightarrow S_3 = \frac{P_3}{\cos \theta} = \frac{4548.78 \text{ W}}{0.72} = \mathbf{6317.75 \text{ VA}}$$

Also, $\theta = \cos^{-1} 0.72 = 43.95^\circ$, so that

$$\begin{aligned} Q_3 &= S_3 \sin \theta = (6317.75 \text{ VA})(\sin 43.95^\circ) \\ &= (6317.75 \text{ VA})(0.694) = \mathbf{4384.71 \text{ VAR (L)}} \end{aligned}$$

Capacitive load:

$$\mathbf{I} = \frac{\mathbf{E}}{\mathbf{Z}} = \frac{208 \text{ V} \angle 0^\circ}{9 \Omega - j 12 \Omega} = \frac{208 \text{ V} \angle 0^\circ}{15 \Omega \angle -53.13^\circ} = 13.87 \text{ A} \angle 53.13^\circ$$

$$P_4 = I^2 R = (13.87 \text{ A})^2 \cdot 9 \Omega = \mathbf{1731.39 \text{ W}}$$

$$Q_4 = I^2 X_C = (13.87 \text{ A})^2 \cdot 12 \Omega = \mathbf{2308.52 \text{ VAR (C)}}$$

$$\begin{aligned} S_4 &= \sqrt{P_4^2 + Q_4^2} = \sqrt{(1731.39 \text{ W})^2 + (2308.52 \text{ VAR})^2} \\ &= \mathbf{2885.65 \text{ VA}} \end{aligned}$$

$$F_p = \frac{P_4}{S_4} = \frac{1731.39 \text{ W}}{2885.65 \text{ VA}} = \mathbf{0.6 \text{ leading}}$$

$$\begin{aligned}
 \text{b. } P_T &= P_1 + P_2 + P_3 + P_4 \\
 &= 720 \text{ W} + 6400 \text{ W} + 4548.78 \text{ W} + 1731.39 \text{ W} \\
 &= \mathbf{13,400.17 \text{ W}} \\
 Q_T &= \pm Q_1 \pm Q_2 \pm Q_3 \pm Q_4 \\
 &= 0 + 0 + 4384.71 \text{ VAR (L)} - 2308.52 \text{ VAR (C)} \\
 &= \mathbf{2076.19 \text{ VAR (L)}} \\
 S_T &= \sqrt{P_T^2 + Q_T^2} = \sqrt{(13,400.17 \text{ W})^2 + (2076.19 \text{ VAR})^2} \\
 &= 13,560.06 \text{ VA} \\
 F_p &= \frac{P_T}{S_T} = \frac{13.4 \text{ kW}}{13,560.06 \text{ VA}} = \mathbf{0.988 \text{ lagging}} \\
 \theta &= \cos^{-1} 0.988 = 8.89^\circ
 \end{aligned}$$

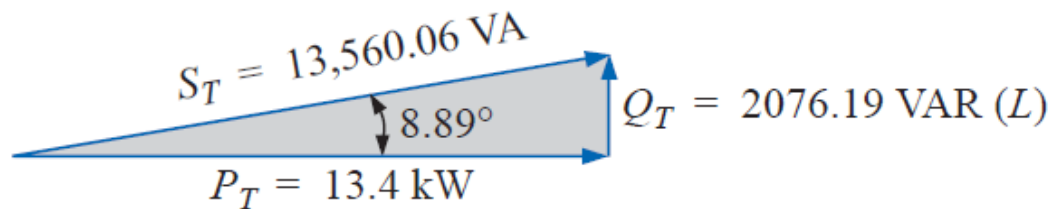


FIG. 19.22

Power triangle for Example 19.3.

$$\text{c. } S_T = EI \longrightarrow I = \frac{S_T}{E} = \frac{13,559.89 \text{ VA}}{208 \text{ V}} = 65.19 \text{ A}$$

Lagging power factor: **E** leads **I** by 8.89° , and

$$\mathbf{I} = 65.19 \text{ A} \angle -8.89^\circ$$

19.8 POWER FACTOR CORRECTION

In power transmission system we need to minimize the magnitude of the current:

- Minimize power losses in the lines ($P = I^2 R$)
- Large current require large conductors \implies more copper

Since the line voltage of a system is fixed \implies the apparent power is related to the current level

Smaller apparent power \implies smaller current drawn from the supply

➡ Minimum current is drawn when: $S = P$ and $Q_T = 0$

Note the effect of decreasing levels of Q_T on the length (magnitude) of S . For the same real power.

The power factor angle: $\theta \rightarrow 0$

The power factor: $F_P \rightarrow 1$

The network becoming more and more resistive at the input terminal.

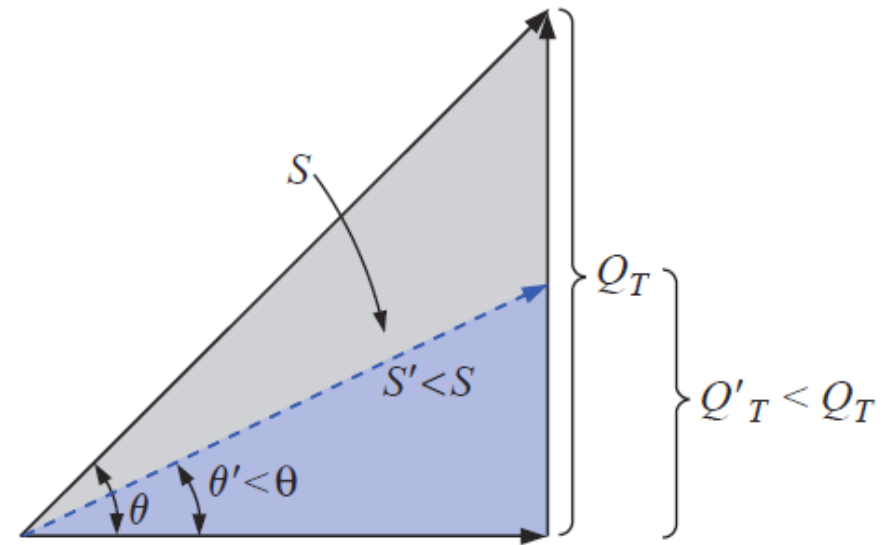


FIG. 19.24

Demonstrating the impact of power-factor correction on the power triangle of a network.

The process of introducing reactive element to bring the power factor closer to unity is called ***power-factor correction***.

Most loads are inductive \Rightarrow the process involve introducing capacitive elements.

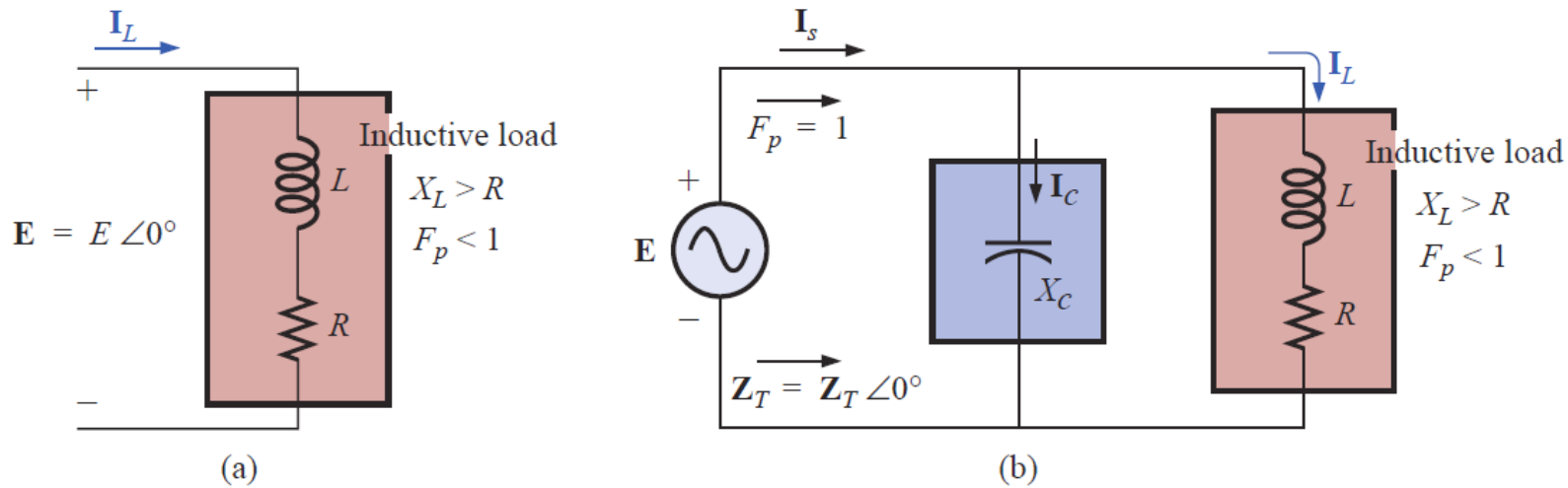


FIG. 19.25

Demonstrating the impact of a capacitive element on the power factor of a network.

In the two circuits the Inductive load receive the same current in both cases: there is no difference for the load.

Solving for the source current in Fig. 19.25(b):

$$\begin{aligned}
 \mathbf{I}_s &= \mathbf{I}_C + \mathbf{I}_L \\
 &= j I_C(I_{\text{mag}}) + I_L(R_e) + j I_L(I_{\text{mag}}) \\
 &= I_L(R_e) + j [I_L(I_{\text{mag}}) + I_C(I_{\text{mag}})]
 \end{aligned}$$

If X_C is chosen such that $|I_C(I_{\text{mag}})| = |I_L(I_{\text{mag}})|$ Then:

$$\mathbf{I}_s = I_L(R_e) + j (0) = I_L(R_e) \angle 0^\circ$$

EXAMPLE 19.5 A 5-hp motor with a 0.6 lagging power factor and an efficiency of 92% is connected to a 208-V, 60-Hz supply.

- Establish the power triangle for the load.
- Determine the power-factor capacitor that must be placed in parallel with the load to raise the power factor to unity.
- Determine the change in supply current from the uncompensated to the compensated system.
- Find the network equivalent of the above, and verify the conclusions.

Solutions:

- Since 1 hp = 746 W,

$$P_o = 5 \text{ hp} = 5(746 \text{ W}) = 3730 \text{ W}$$

$$\text{and } P_i \text{ (drawn from the line)} = \frac{P_o}{\eta} = \frac{3730 \text{ W}}{0.92} = 4054.35 \text{ W}$$

Also,

$$F_p = \cos \theta = 0.6$$

and

$$\theta = \cos^{-1} 0.6 = 53.13^\circ$$

$$\text{Applying } \tan \theta = \frac{Q_L}{P_i}$$

$$\begin{aligned} \text{we obtain } Q_L &= P_i \tan \theta = (4054.35 \text{ W}) \tan 53.13^\circ \\ &= 5405.8 \text{ VAR (L)} \end{aligned}$$

and

$$\begin{aligned} S &= \sqrt{P_i^2 + Q_L^2} = \sqrt{(4054.35 \text{ W})^2 + (5405.8 \text{ VAR})^2} \\ &= 6757.25 \text{ VA} \end{aligned}$$

The power triangle appears in Fig. 19.26.

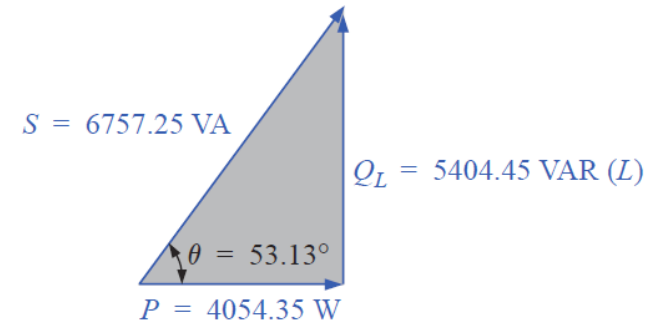


FIG. 19.26

Initial power triangle for the load of Example 19.5.

b. A net unity power-factor level is established by introducing a capacitive reactive power level of 5405.8 VAR to balance Q_L . Since

$$Q_C = \frac{V^2}{X_C}$$

then
$$X_C = \frac{V^2}{Q_C} = \frac{(208 \text{ V})^2}{5405.8 \text{ VAR (C)}} = 8 \Omega$$

and
$$C = \frac{1}{2\pi f X_C} = \frac{1}{(2\pi)(60 \text{ Hz})(8 \Omega)} = 331.6 \mu\text{F}$$

c. At $0.6F_p$,

$$S = VI = 6757.25 \text{ VA}$$

and
$$I = \frac{S}{V} = \frac{6757.25 \text{ VA}}{208 \text{ V}} = 32.49 \text{ A}$$

At unity F_p ,

$$S = VI = 4054.35 \text{ VA}$$

and
$$I = \frac{S}{V} = \frac{4054.35 \text{ VA}}{208 \text{ V}} = 19.49 \text{ A}$$

producing a 40% reduction in supply current.

d. For the motor, the angle by which the applied voltage leads the current is

$$\theta = \cos^{-1} 0.6 = 53.13^\circ$$

and $P = EI_m \cos \theta = 4054.35 \text{ W}$, from above, so that

$$I_m = \frac{P}{E \cos \theta} = \frac{4054.35 \text{ W}}{(208 \text{ V})(0.6)} = \mathbf{32.49 \text{ A}} \quad (\text{as above})$$

resulting in $\mathbf{I_m = 32.49 \text{ A} \angle -53.13^\circ}$

Therefore,

$$\begin{aligned} \mathbf{Z_m} &= \frac{\mathbf{E}}{\mathbf{I_m}} = \frac{208 \text{ V} \angle 0^\circ}{32.49 \text{ A} \angle -53.13^\circ} = 6.4 \Omega \angle 53.13^\circ \\ &= 3.84 \Omega + j 5.12 \Omega \end{aligned}$$

as shown in Fig. 19.27(a).

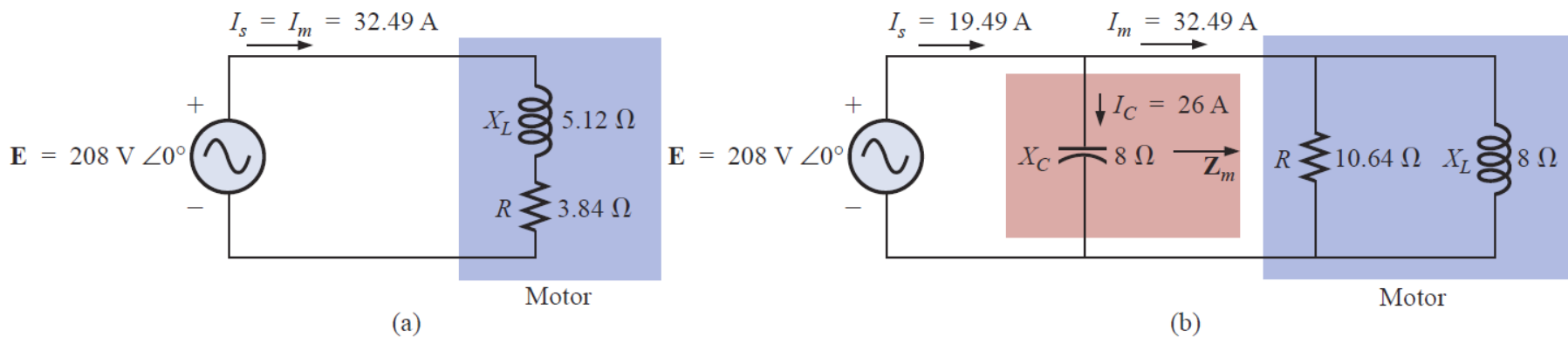


FIG. 19.27

Demonstrating the impact of power-factor corrections on the source current.

The equivalent parallel load is determined from

$$\begin{aligned}\mathbf{Y} &= \frac{1}{\mathbf{Z}} = \frac{1}{6.4 \Omega \angle 53.13^\circ} \\ &= 0.156 \text{ S} \angle -53.13^\circ = 0.094 \text{ S} - j 0.125 \text{ S} \\ &= \frac{1}{10.64 \Omega} + \frac{1}{j 8 \Omega}\end{aligned}$$

as shown in Fig. 19.27(b).

It is now clear that the effect of the 8- Ω inductive reactance can be compensated for by a parallel capacitive reactance of 8 Ω using a power-factor correction capacitor of 332 μF .

Since

$$\mathbf{Y}_T = \frac{1}{-j X_C} + \frac{1}{R} + \frac{1}{+j X_L} = \frac{1}{R}$$

$$I_s = E Y_T = E \left(\frac{1}{R} \right) = (208 \text{ V}) \left(\frac{1}{10.64 \Omega} \right) = \mathbf{19.54 \text{ A}} \quad \text{as above}$$

In addition, the magnitude of the capacitive current can be determined as follows:

$$I_C = \frac{E}{X_C} = \frac{208 \text{ V}}{8 \Omega} = \mathbf{26 \text{ A}}$$

EXAMPLE 19.6

- a. A small industrial plant has a 10-kW heating load and a 20-kVA inductive load due to a bank of induction motors. The heating elements are considered purely resistive ($F_p = 1$), and the induction motors have a lagging power factor of 0.7. If the supply is 1000 V at 60 Hz, determine the capacitive element required to raise the power factor to 0.95.
- b. Compare the levels of current drawn from the supply.

Solutions:

- a. For the induction motors,

$$S = VI = 20 \text{ kVA}$$

$$P = S \cos \theta = (20 \times 10^3 \text{ VA})(0.7) = 14 \times 10^3 \text{ W}$$

$$\theta = \cos^{-1} 0.7 \cong 45.6^\circ$$

and

$$Q_L = VI \sin \theta = (20 \times 10^3 \text{ VA})(0.714) = 14.28 \times 10^3 \text{ VAR (L)}$$


The power triangle for the total system appears in Fig. 19.28.

Note the addition of real powers and the resulting S_T :

$$S_T = \sqrt{(24 \text{ kW})^2 + (14.28 \text{ kVAR})^2} = 27.93 \text{ kVA}$$

with
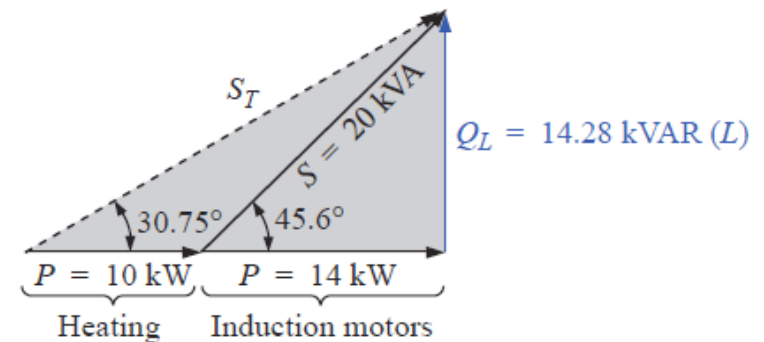
$$I_T = \frac{S_T}{E} = \frac{27.93 \text{ kVA}}{1000 \text{ V}} = \mathbf{27.93 \text{ A}}$$



The desired power factor of 0.95 results in an angle between S and P of

$$\theta = \cos^{-1} 0.95 = 18.19^\circ$$

changing the power triangle to that of Fig. 19.29:

$$\begin{aligned} \text{with } \tan \theta &= \frac{Q'_L}{P_T} \rightarrow Q'_L = P_T \tan \theta = (24 \times 10^3 \text{ W})(\tan 18.19^\circ) \\ &= (24 \times 10^3 \text{ W})(0.329) = 7.9 \text{ kVAR (L)} \end{aligned}$$

The inductive reactive power must therefore be reduced by

$$Q_L - Q'_L = 14.28 \text{ kVAR (L)} - 7.9 \text{ kVAR (L)} = 6.38 \text{ kVAR (L)}$$

Therefore, $Q_C = 6.38 \text{ kVAR}$, and using $Q_C = \frac{E^2}{X_C}$

$$\text{we obtain } X_C = \frac{E^2}{Q_C} = \frac{(10^3 \text{ V})^2}{6.38 \times 10^3 \text{ VAR}} = 156.74 \Omega$$

$$\text{and } C = \frac{1}{2\pi f X_C} = \frac{1}{(2\pi)(60 \text{ Hz})(156.74 \Omega)} = \mathbf{16.93 \mu\text{F}}$$

$$\begin{aligned} \text{b. } S_T &= \sqrt{(24 \text{ kW})^2 + [7.9 \text{ kVAR (L)}]^2} \\ &= 25.27 \text{ kVA} \end{aligned}$$

$$I_T = \frac{S_T}{E} = \frac{25.27 \text{ kVA}}{1000 \text{ V}} = \mathbf{25.27 \text{ A}}$$

The new I_T is $I_T = 25.27 \text{ A} \angle 27.93^\circ$ (original)

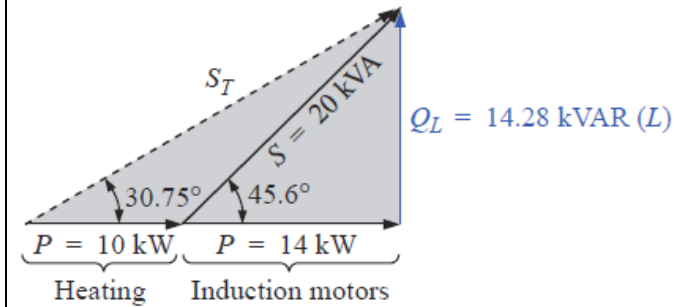


FIG. 19.28

Initial power triangle for the load of Example 19.6.

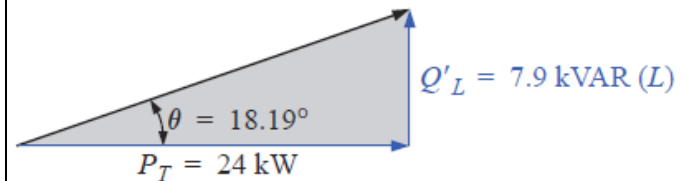


FIG. 19.29

Power triangle for the load of Example 19.6 after raising the power factor to 0.95.